



Corso Luigi Einaudi, 55 - Torino

Appunti universitari

Tesi di laurea

Cartoleria e cancelleria

Stampa file e fotocopie

Print on demand

Rilegature

NUMERO : 13

DATA : 26/01/2011

# A P P U N T I

STUDENTE : CAUSA Bruno

MATERIA : Electronics For Embedded System

Prof. Del Corso - Gregoretti


Il presente lavoro nasce dall'impegno dell'autore ed è distribuito in accordo con il Centro Appunti.

Tutti i diritti sono riservati. È vietata qualsiasi riproduzione, copia totale o parziale, dei contenuti inseriti nel presente volume, ivi inclusa la memorizzazione, rielaborazione, diffusione o distribuzione dei contenuti stessi mediante qualunque supporto magnetico o cartaceo, piattaforma tecnologica o rete telematica, senza previa autorizzazione scritta dell'autore.


**ATTENZIONE: QUESTI APPUNTI SONO FATTI DA STUDENTIE NON SONO STATI VISIONATI DAL DOCENTE.  
IL NOME DEL PROFESSORE, SERVE SOLO PER IDENTIFICARE IL CORSO.**

## Operational Amplifiers

### • Amplifier

 

### • Operational Amplifier

 

Usually the power supply is differential (+5V, -5V for example)


Ideal assumptions

$$A_d \rightarrow +\infty$$

$$i_{i+} = i_{i-} = 0$$

In order to have  $v_o \neq +\infty, 0$  we have to feedback the op. amp; so  $v_d = 0$ .


The equivalent circuit is

 

## Real Amplifiers

The study of real operational amplifiers comes from the elimination of the two assumptions  $A_d \rightarrow \infty$  and  $v_o = v_i = 0$  initially, we can study the effect of each of the two eliminations without considering the other, that means that the amplifier is considered ideal except from:

- differential gain:  $A_d$  finite

 

$$v_e = \frac{R_2}{R_1 + R_2} v_o = \beta v_o$$

$$v_i = v_d + v_e = v_d + \beta v_o$$

In the ideal case  $v_d = 0$  and so

$$v_o = \frac{1}{\beta} v_i = \frac{R_1 + R_2}{R_2} v_i, \text{ as seen before.}$$

In the real case instead we have  $v_d = \frac{v_o}{A_d}$

$$v_o = \frac{1}{\frac{1}{A_d} + \beta} v_i = \frac{1}{\beta} \frac{1}{1 + \frac{1}{A_d \beta}} v_i$$



So, the higher is the product  $A_d \beta = T$ , less is the error that we commit assuming  $A_d \rightarrow \infty$

$$A_{v, \text{real}} = \frac{1}{1 + \frac{1}{A_d \beta}} \cdot A_{v, \text{ideal}} \approx A_{v, \text{ideal}} \left( 1 - \frac{1}{T} \dots \right)$$

From the last formula we can evaluate the error made using the ideal formula, it is called gain error and is


$$E_{\text{gain}} = A_{v, \text{ideal}} \cdot \frac{1}{T}$$

  - **Saturation:**  $-V_s < v_o < V_s \quad \forall v_d$




Saturation can cause distortion to the signal shapes, it is important that also  $|v_d| < V_s$

 The power supply can also be a single supply with the other pin connected to ground;



because in this case the excursion is lower, so it is easier to have saturation, particular amplifiers are built and they are called RAIL TO RAIL op. amps.

- **frequency response:**  $|A_d|_{dB} = f(\omega)$

 

for  $\omega < \omega_c$   $A_{v,real} \approx \frac{1}{\beta}$

for  $\omega \approx \omega_c$   $A_d$  is a low value


so  $A_{v,real} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{A_d \beta}} \approx$

$\approx \frac{1}{\beta} \frac{1}{\frac{1}{A_d \beta}} \rightarrow A_d$

GBF (Gain x Bandwidth product) is the same for all the points in the slope segment.




If I need more bandwidth, I have to change my operational amplifier.

# Subtractor

 

$$V_0 = -V_1 \frac{R_f}{R_1} + \left(1 + \frac{R_f}{R_1}\right) V_A$$

   But maybe we want  $V_0 = k(V_1 - V_2)$ ; differential signals are often used because they reject common mode noise.



$$V_A = \frac{R_4}{R_2 + R_4} V_2$$

$$V_0 = -V_1 \frac{R_f}{R_1} + \left(1 + \frac{R_f}{R_1}\right) \frac{R_4}{R_2 + R_4} V_2$$


In order to have a perfect differential signal, it must be:

$$\frac{R_f}{R_1} = \left(1 + \frac{R_f}{R_1}\right) \frac{R_4}{R_2 + R_4}$$

$$\frac{R_2 + R_4}{R_4} \frac{R_f}{R_1} = \frac{R_f}{R_1} \left(1 + \frac{R_f}{R_1}\right)$$

$$\frac{R_2 + R_4}{R_4} = \frac{R_f + R_1}{R_f}$$

 
$$\Rightarrow \begin{cases} R_f = R_4 \\ R_2 = R_1 \end{cases}$$



Explanation of the hysteresis curve: let's assume that the initial value of the output is low - 0. It won't change until  $v_i = v_{s1}$ ; when  $v_i = v_{s1}$  the output will switch to logic 1; if the input is still increasing, the output will continue to be 1; if the output instead is decreasing, it has to reach the value  $v_i = v_{s2}$  in order to switch to the logic 0.



This comparator is also called SCHMITT TRIGGER: the feedback (positive!) allows the output to change value in just few nanoseconds (while the normal comparator needs  $\mu s$ ).

### ③ Switched capacitor SC

 

They are actually the most used, are made of a capacitor and a switch, easily implemented with a transistor.

  Let's have a look at a simple 1<sup>st</sup> order filter with a resistance and a capacitor. We would like to replace the resistance with a switched capacitor.



Ⓐ Charge of the capacitor:  $Q = V_A C_1$

Ⓑ Discharge of the capacitor:  $Q = V_B C_1$


$$\Delta Q = C_1 (V_A - V_B)$$

Assuming  $f$  as the switching frequency

$$I = \Delta Q f = C_1 f (V_A - V_B)$$

$$\underline{R_{eq}} = \frac{V_A - V_B}{I} = \underline{\frac{1}{C_1 f}}$$

 So now we can use the switched capacitor instead of the resistance,




The time constant of the circuit is

$$\tau = R_{eq} C_2 = \frac{1}{f} \frac{C_2}{C_1}$$


The ratio of the capacitors is easily precise: this is the main advantage!



 In the frequency domain the sampling cause a repetition of the spectrum, so.



 The sine wave of the previous page (1<sup>st</sup> picture) -  $f = 5 \text{ kHz}$ , with a  $f_s = 16 \text{ kHz}$ , would have this spectrum:



Working on the frequency domain, in order to reconstruct the original signal after a sampling, we need a pass-band filter that includes only the original spectrum. So it is necessary that the repetition of the spectrum doesn't affect the original one. This is the Shannon theorem:


$$f_s \geq 2 \text{ BW}$$

where BW is the bandwidth of the signal.


This ideal situation has two problems:

1) the filter is supposed to be ideal, while in the real case the filter cannot be instantaneously 0.

 
2) a finite-frequency spectrum means an infinite time signal; in the real case instead the time signal is limited and so the spectrum is unlimited, that means that there is always a little quantity of aliasing.



 In order to reduce this second effect usually a




 Quantization can be seen as a noise that is added to the sampled signal



We can define the SNR<sub>q</sub> due to the quantization error:

$$SNR_q = \frac{P_s}{P_{E_q}}$$

 

The power of noise that is a random variable, is  $P_{E_q} = \sigma_{E_q}^2 = \int_{-\infty}^{+\infty} p(E_q) E_q^2 dE_q$

In the picture is shown the Probability Density Function (PDF) of a triangular wave, like  $E_q(A)$  is, assuming  $H = \Delta/2$  we have:

$$\begin{aligned}
 P_{E_q} = \sigma_{E_q}^2 &= \int_{-\infty}^{+\infty} p(E_q) E_q^2 dE_q = \int_{-\frac{\Delta}{2}}^{\frac{\Delta}{2}} \frac{1}{\Delta} E_q^2 dE_q = \\
 &= \frac{1}{\Delta} \left[ \frac{E_q^3}{3} \right]_{-\frac{\Delta}{2}}^{\frac{\Delta}{2}} = \frac{1}{3\Delta} \left( \frac{\Delta^3}{8} + \frac{\Delta^3}{8} \right) = \\
 &= \frac{1}{3\Delta} \frac{\Delta^3}{4} = \frac{\Delta^2}{12}
 \end{aligned}$$

Errors due to: amplifier, filter, S&H, A/D; the total error is the sum of these errors,  $SNR_T$

Convention (due to sine wave):

$$SNR_q = N \cdot 6 \text{ dB} + 1.76 \text{ dB}$$


$$N = \frac{SNR_q - 1.76}{6}$$

If we substitute  $SNR_q$  with  $SNR_T$  we obtain the ENOB, equivalent number of useful bits:


$$ENOB = \frac{SNR_T - 1.76}{6}$$

### D/A converters

The chain for a D/A conversion is:

 

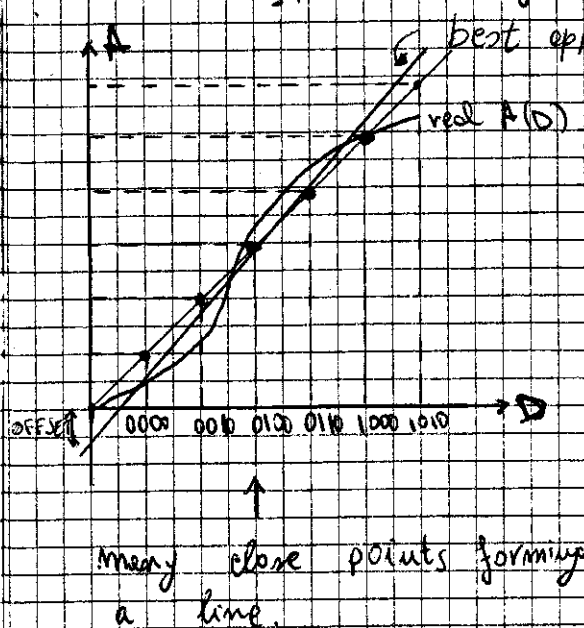Let's concentrate on the first block - D/A: we will see initially the other errors that occur in a DAC; they are linear errors, gain and offset, integral and differential nonlinearity, and dynamic parameters.



$A(D)$  is a sequence of dots  
 $N \rightarrow \infty$  becomes a line

$E_0 \rightarrow$  OFFSET, compensated adding a constant


$E_g \rightarrow$  GAIN ERROR, difference among ideal and best approximation slopes, compensated by a gain correction



This phenomenon is called GLITCH.


DAC

error summary:

 


- linear { gain  $E_g$   
offset  $E_o$
- non-linear { integral  $E_{ine}$   
differential  $E_{dne}$
- dynamic { settling time  $T_s$   
glitches

 Let's see now how to build a DAC: it can be seen as the sum of elementary quantities controlled by  $D$




 The elementary quantities can be all 1, and it is called UNIFORM CONVERSION, or powers of 2, and it is called WEIGHTED CONVERSION




Assuming a current analog output, these are the electrical circuit of the two converters; the first one is the uniform converter: its problem is that if the digital value is  $N$ -bits, the uniform converter needs  $2^N$  resistances, so it becomes very big! the second is the weighted converter: for an  $N$ -bits digital value, it needs  $N$  weighted branches, that means  $N$  different values of resistors that must be precise!

 The circuits we draw have a switch that can switch between  $V_R$  and  $GND$ ; this is called voltage switch; another approach



 
① The first error is a GAIN error that can occur when the value of  $V_A$  is not exactly the ideal value but has some percentage of error.



② OFFSET error is due to the offset of an eventual op. amp, but mostly the cause is the Leakage current of switches, that means that  $I_{switch} \neq 0$  even if it is OFF. This current depends mostly on temperature.

Both GAIN and OFFSET don't depend on  $D$  value, so they can easily be corrected, once they've been detected.

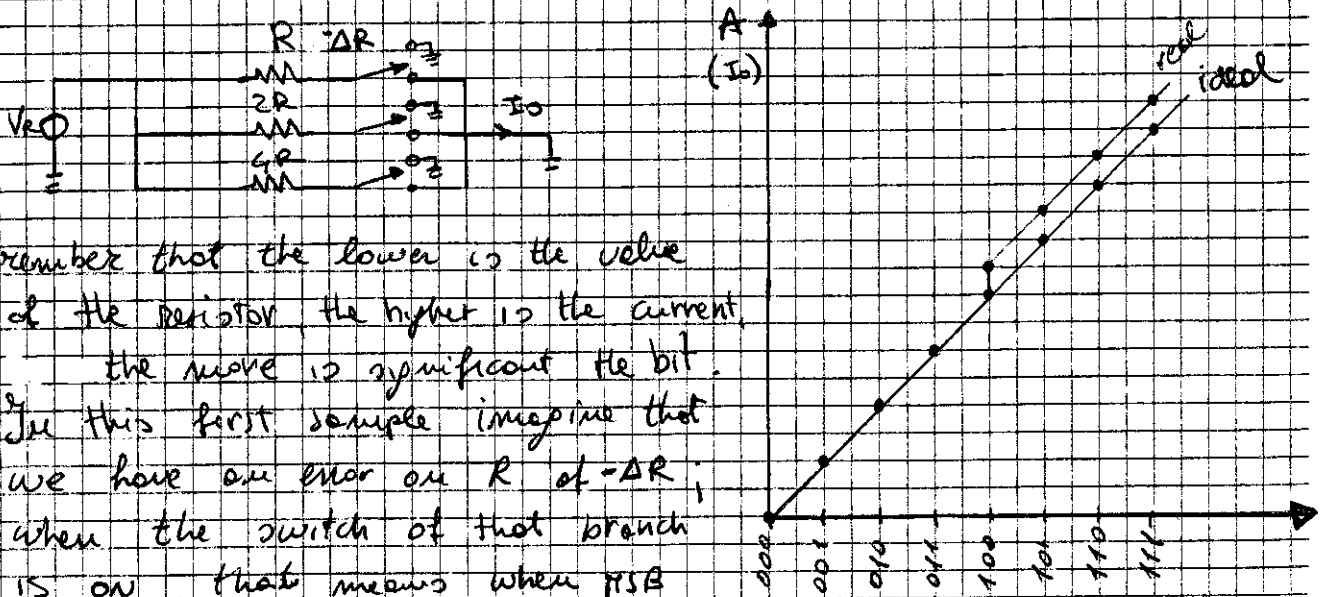③ Consider a weighted converter (current switches) - 3 bits:




remember that the lower is the value of the resistor, the higher is the current, the more is significant the bit.

In this first sample imagine that we have an error on  $R$  of  $-\Delta R$ ; when the switch of that branch is ON, that means when MSB is 1, the output will be higher.


Let's see what happens if the error is in the second or

 ⑦ Consider now a uniform converter; imagine to have  $N$  resistors



and that each resistor has an error because they are same resistors in the same circuit it is very likely that the error will be  $\pm \Delta R$  for all of them. Imagine the first  $N/2$  resistors have  $\Delta R > 0$ , the others  $\Delta R < 0$


 
For the first half, the higher resistances will allow less current to pass, so lower values; in the second half the lower values will equilibrate. We can so find the  $E_{int}$ .



As the operation in an uniform DAC is always an adding of current (D mapping) it is impossible to have non-monotonicity.

- So:
- WEIGHTED:  $N$  bits  $\rightarrow$   $N$  branches
  - NON MONOTONICITY (HIGH PRECISION NEEDED)
  - UNIFORM:  $N$  bits  $\rightarrow$   $2^N - 1$  branches
  - Always MONOTONE

We can mix the two solutions:

  


The two latches are needed in order to synchronize all the bits and avoid GLITCHES. The MSB decoder converts the value of the 5 bit in a 31-bit code for the switches of the uniform DAC.

→  $E_{DNL}$  DIFFERENTIAL NONLINEARITY

In the ideal case each step is  $\Delta$  long, in the real case we have  $\Delta_{i+1} \neq \Delta_i$ , so the differential nonlinearity error is really  $E_{DNL} = \Delta_i - \Delta_{i+1}$

 
As is shown in the picture, if  $E_{DNL} > 1 \text{ LSB}$  one code (011) will be lost. This error is called MISSING CODE ERROR and is the corresponding of the non-monotonicity error of the DAC.



In general the integral nonlinearity  $E_{INL}$  is how much the real function deviates from the ideal function, and is a unique value; the differential nonlinearity  $E_{DNL}$  instead is the difference point-to-point between the ideal behaviour and the real one, so is specific of each interval (but it has a max). The relation is:

$$E_{INL} = \sum E_{DNL}$$

 
As regards the dynamic parameters, just remember the CONVERSION TIME, that is the time from when the input is applied, to when the output is correct,  $T_c$ ; the conversion frequency is obviously  $F_c = 1/T_c$ .




An ADC cannot be both simple and fast! To have a fast ADC is necessary a complex design, and if we want a simple ADC, it will be slower.

The complexity of an ADC is due to the number of voltage comparators; this is directly connected to the area and to the cost of the circuit. Remember that the cost of

## Signal conditioning

 


 Here we have the conversion chain from analog to digital; in respect to the previous representations there is one more block that is the PROTECTION CIRCUIT; we will look first at this protection circuit and then to the part made of filters and amplifiers.




Here there is an example of protection called DOUBLE ANODE ZENER; the resistor is needed to limit input current (otherwise it would destroy also the diodes); remembering that a zener diode has a voltage of  $0.7$  if it is conducting in normal mode, and a voltage of  $-V_z$  if an inverse current flow in it, when  $v_i$  is high  $z_1$  is ON and  $z_2$  is in break down, vice versa if  $v_i$  is low.

 The operation range depends always on the power supply; so with power off no signals can be input (or we will damage the circuit)





 
Let's talk now about the FILTERS: the analog signal must be filtered for two reasons: elimination of the noise at different frequencies, and limited band to avoid ALIASING (it is called anti-aliasing filter).






Another way is the RAMP CONVERTER; instead of the DAC there is an integrator, so while  $EN=1$   $A'$  increases as a ramp.

   The integrator can be usually made as an operation amplifier with a resistance and a capacitor



### TRACKING ADC

 

The UP/DOWN - DOWN/UP counter allows to follow signal changing. Counter doesn't need to start from ZERO again. However in the worst

case, that is at the beginning with the higher value, the time needed is  $2^N$  cycle for N bits at most.



If the signal changes too quickly,  $A'$  cannot change so quickly and there is an OVERLOAD.


So all the FEEDBACK, the RAMP and the TRACKING AD converters have just one voltage comparator, so a complexity of 1, but a conversion time of  $2^N$  for N bits. We will see a better converter that has just one converter

$$SNR_{Tot} = \frac{P_s}{P_n} = \frac{P_s}{P_a + P_q} = \frac{1}{\frac{P_a}{P_s} + \frac{P_q}{P_s}} = \frac{1}{\frac{1}{SNR_a} + \frac{1}{SNR_q}} =$$

$$\approx \frac{1}{\frac{1}{4000} + \frac{1}{700}} = 595,7 = 55 \text{ dB}$$

$$ENOB = \frac{SNR_{Tot, dB} - 1,76}{6} = \frac{55 - 1,76}{6} = 8,87 \rightarrow 9 \text{ bits are enough!}$$

 We didn't consider the amplifier in the chain:




$$V_0 = -\frac{R_3}{R_1} V_1 + \frac{R_4}{R_2 + R_4} \left( 1 + \frac{R_3}{R_1} \right) V_2 \Rightarrow \frac{R_3}{R_1} (V_2 - V_1)$$

assuming that  $R_1 = R_2$  and  $R_3 = R_4$  that are the conditions to minimize the bias error because the equivalent resistances from the two inputs of the op.amps are equal.

$$V_0 = A_d (V_1 - V_2) + A_{cm} \frac{V_1 + V_2}{2}$$

In our ideal circuit  $A_d = -\frac{R_3}{R_1}$ ,  $A_{cm} = 0$

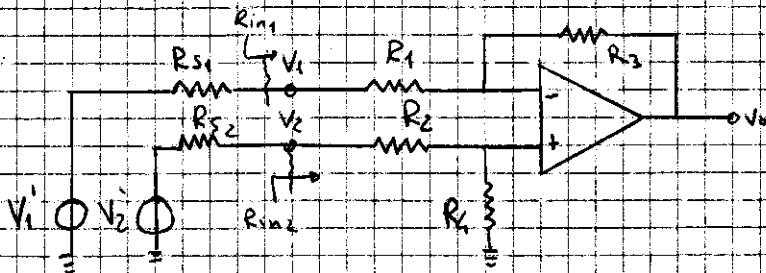
In the real circuit each voltage input has a series resistance:



$$R_{in1} = R_1$$


$$R_{in2} = R_2 + R_4$$

## RESIDUE ADC

 

Each residue is multiplied by two and compared with  $S/2$ ; for each bit one comparator is needed, one 1-bit DAC to build the approximation, one analog adder to evaluate the residue, and one amplifier with gain 2.

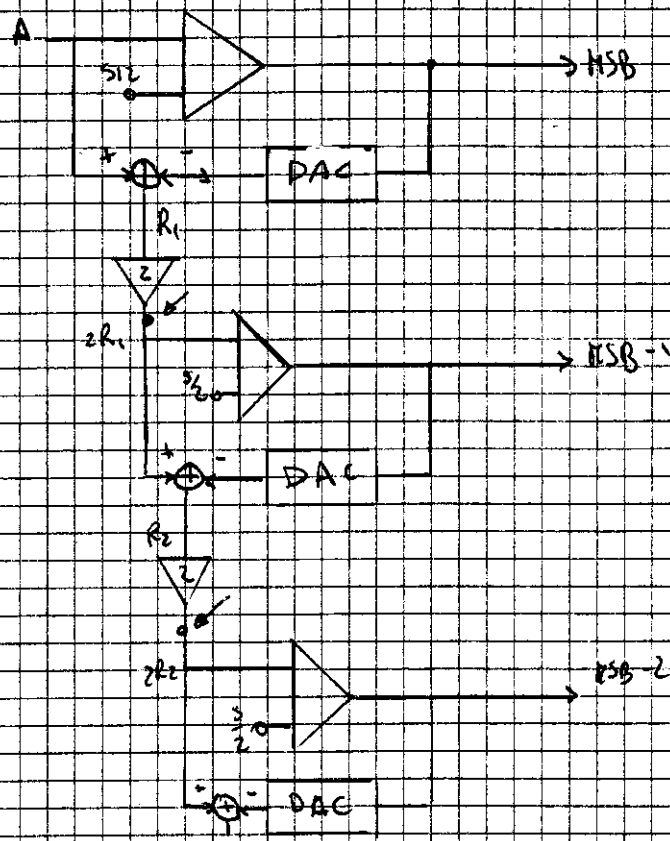So it needs  $N$  comparators and has a conversion time of  $N$ ; no benefits in comparison with the successive approximation ADC.





This is the way how to build a RESIDUE ADC. Really, it is useful only as starting structure for pipeline ADC.

The idea of the pipeline is those that while a digital output is computed at step 2 (MSB-1), the previous circuit is free and you can send it the second analog value; so it operates on different samples at the same time.
  
## PIPELINE SUBRANGING ADC

The only difference with the residue ADC, from a structural point of view, is that some S/H are placed after the amplifiers (→). It uses  $N$  comparators and the con.



$v_o = A_d v_d$  gain

$v_o = A_1 \cdot A_2 v_d = A_d v_d$

$v_{on2} = v_{in2} \cdot A_d$  offset error ( $v_{in2}$ )


$v_{on2} = v_{in2} A_2$

$v_{on1} = v_{in1} \cdot A_d$  noise error

$v_{on1} = v_{in1} \cdot A_d$

As we can see, Offset error is less in the second choice because of the divided gain.

### MULTIPLEXER

 



A multiplexer is useful to use S/H and ADC for several channels; it selects one of the  $N$  inputs and stops the others; so it is made of  $N$  switches; a switch is a MOS transistor that has an equivalent series resistance  $R_{on}$ , and a leakage current  $I_{off}$ .

### SAMPLE & HOLD


The sample & hold unit has two functions: it samples the analog signal at  $t = k T_s$ ,  $k = 1, 2, \dots$ , and keep the sample value at the output as long as required for A/D conversion.

In order to have a small pedestal error  $C_H$  should be high but it would become slower. The smaller is  $C_H$ , the faster it is, the bigger is this error.

  The switch has a leakage current  $I_{off}$  that causes an HOLD error:




 $C_H$  should discharge only through  $R_1$ , but actually it discharges also through  $I_{off}$




$C_H$  needs some time to charge and this cause the acquisition delay. In order to have a small acquisition time,  $C_H$  should be very small, but this would cause a worse hold error.

 In order to solve these problems we can put two followers:



Coming back to converters, we will talk now about DIFFERENTIAL CONVERTERS; consider the tracking ADC; it is possible to obtain the output starting just from

 
Also, the variation of the signal cannot be too fast, otherwise the digital output cannot follow the input, and there is an overload.



While for a standard converter is  $E_q < V < \frac{S}{2}$ ; the delta converter does not require high precision devices, but has a limited range depending on the frequency.

 EXAMPLE

In order to study the advantages of OVERSAMPLING consider this practical case: we need a 8-bit A/D system for voice signal, limited to 3 kHz



The bit rate is  $8 \text{ bit} \times 8 \frac{\text{ksample}}{\text{s}} = 64 \frac{\text{kbit}}{\text{s}}$ ; the  $SNR_q$  is

$SNR_q = 6 \cdot N = 6 \cdot 8 = 48 \text{ dB}$ ; the range of variation in a NYQUIST converter is  $\frac{E_q}{2} < V < \frac{S}{2}$ ; the ratio is  $\frac{S}{E_q}$ ;

$$E_q = \frac{S}{2^{N+1}} \rightarrow \frac{S}{E_q} = 2^{N+1} = 2^9 = 512.$$

If we want the same variation in a  $\Delta$  converter (also called OVERSAMPLING converter), we have


$$\frac{\frac{S}{\omega T_{ck}}}{\frac{S}{2}} = \frac{2}{\omega T_{ck}} = 2^9 \rightarrow T_{ck} = \frac{1}{\omega \cdot 2^8}$$

$$\omega = 2\pi \cdot f_s = 2\pi \cdot 3 \text{ k} \rightarrow f_{ck} = 2\pi \cdot 3 \text{ k} \cdot 2^8 = 4.8 \frac{\text{Mbit}}{\text{s}}$$


So the bit rate is much higher in a  $\Delta$  converter

derivative. So this scheme starts from the STANDARD CHAIN and adds an integrator at the input (with the goal of decreasing amplitude when frequency goes up - in fact if  $A = V \sin(\omega t)$ , then  $A_i = \frac{V}{\omega} \cos(\omega t)$ ) and also a derivative at the output.

 However this diagram can be improved: the decoder is made of an integrator and a derivative, that have an inverse function; so they can be substituted with a wire. At the input there is the sum between two values integrated; it is the same if we integrate the difference of the two signals. So:



 
Let's study it in the frequency domain, taking into account the quantization noise.



$A=0 \rightarrow$

$$D = I + \epsilon_p = -\frac{D}{s} + \epsilon_p$$

 
$$D \left( 1 + \frac{1}{s} \right) = \epsilon_p \rightarrow \frac{D}{\epsilon_p} = \frac{s}{s+1}$$



The circuit behaves as a high-pass filter for the noise, that means that noise is present only at higher frequencies, so it is easier to be reduced with the reconstruction filter.

12 poles are needed to more  $SNR_a = 72 \text{ dB} @ 100 \text{ kHz}$

 Consider now a sine wave input of  $50 \text{ kHz}$ ; we want to evaluate the  $SNR_j$  (jittering) due to the limited variation of the ADC; assume  $T_j = 1,2 \text{ ns}$



$$\Delta V_j = SR_{max} \cdot T_j$$


$$SR_{max} = \omega V = \frac{S}{2} \cdot 2\pi \cdot 50 \text{ K}$$

$$\Delta V_j = \frac{S}{2} \cdot 2\pi \cdot 50 \text{ K} \cdot 1,2 \cdot 10^{-9} = 5 \cdot 188 \cdot 10^{-6}$$



$$SNR_j = \frac{P_s}{P_{N_j}} = \frac{P_s}{\frac{\Delta V_j^2}{12}} = \frac{P_s}{\frac{5^2 \cdot 188^2 \cdot 10^{-12}}{12}} = \frac{\left(\frac{S}{2}\right)^2 \cdot \frac{1}{2}}{\frac{5^2 \cdot 188^2 \cdot 10^{-12}}{12}} = 76 \text{ dB}$$



 for current and voltage shown in the circuit symbol, breakdown voltage is positive; imagine to use it in a simple circuit with a voltage generation and a resistor, even if the voltage in the generator changes, the one of the zener diode remains always the same.




  Diodes are used in rectifier circuits; the circuit on the right offers to the load only the positive half of the input sine voltage; the first output is shown using the ideal model of short for the diode, the second using the model with 0.7V and the resistance.




With 4 diodes it is possible to obtain a full wave rectifier. We can also put a capacitor in parallel with the load to have less variations in output voltage.

 
To limit voltage instead we can use a couple of zener diodes.



### BJT

 

 
The BJT is used as an amplifier in the active region; instead is used as a switch in saturation (ON) and cut-off (OFF).




substance higher currents and voltages. However this kind of transistor can be built in single pieces, so it is used only in small numbers for power applications.

Triode and cut-off regions are used to implement switches.

 Mosfet are majority carriers, so they have a higher switching speed.




 In the way vertical MOSFET are built, there is a diode between bulk and drain; so the model, if we want to use the MOSFET as a switch is:




Current can flow from S to D, so this is a unidirectional switch; in order to have a complete switch we have to put two transistors back to back.

### THYRISTOR

 

 Gate is the control input of this device; actually, it is the name of connecting two BJT as in figure:



giving a small current to  $g$ ,  $T_2$  turns on and his  $I_{C2}$  becomes base current for  $T_1$ ,  $I_{B1}$ ; so both device conduct until current goes to 0



HEAT SINK

Usually we have a structure useful to dissipate heat better; it is called heat sink. Its thermal resistance  $\theta_{rea}$  depends on air velocity (that's why we use fans in the pcs)


EXAMPLE

$P_d = 5W$

$T_a = 50^\circ C$

$T_j = ?$


 
From the BJT data sheet we have  $\theta_{rjc} = 3,125 \frac{^\circ C}{W}$  while the heat sink has  $\theta_{rca} = 3 \frac{^\circ C}{W}$ .



$$T_j = T_a + \Delta T = T_a + (\theta_{rjc} + \theta_{rca}) \cdot P_d = 50^\circ C + 6,125 \frac{^\circ C}{W} \cdot 5W \approx 80^\circ C$$


Power Circuits

  An amplifier produces "power amplification", power amplifiers must handle large amounts of power (> 1W)




CLASS A

$I_c$  circulates all the time

 

CLASS B

Each transistor conducts for half period, if  $|V_i| < 0,7V$  then the circuit is off, no current to the load.

 


two following parameters.

→ load regulation

$$R_o = \frac{\Delta V_o}{\Delta I_o} \quad (\text{output resistance})$$

→ line regulation

$$S_r = \frac{\Delta V_o}{\Delta V_i}$$

 


Another parameter is the behaviour in load changings: if it has a LIMITER CIRCUIT, increasing R too much the voltage will decrease but the current will be the same. Or, it can have a FOLDBACK that switches off the circuit if  $I_o$  is too high.

A circuit is also characterised by Input inrush current, that is the current needed when it is switched on; and also, the hold-up time, that is how long output voltage is sustained after a power failure. During this time the system is put in a safe condition, saving data in memories and moving mechanical parts to a safe position etc.




 The first step is a switch with a FUSE: the fuse is a wire that blows when current is too high - it is a thermal behaviour on the energy of the input: a FAST FUSE doesn't accept spikes even for a very short time, while a SLOW FUSE doesn't accept spikes only if they are present for a longer time.



We also have to evaluate the peak current of the diode in order to choose the right components; we can evaluate it remembering that the charge that goes into C must be equal to the one that goes out.

 
It is difficult to evaluate it with the strange shape of  $I_D$ , so we can approximate, in 3 different ways:



 1. RECTANGULAR

$$\tilde{I}_D T_1 = I_L \frac{T_1}{2}$$

$$\tilde{I}_D = \frac{I_L \cdot T_1}{T_1}$$



2. TRIANGULAR

$$\frac{\tilde{I}_D}{2} T_1 = I_L \frac{T_1}{2}$$

$$\tilde{I}_D = \frac{I_L \cdot T_1}{T_1}$$




3. PARABOLIC

$$\tilde{I}_D = 1,5 \frac{I_L \cdot T_1}{T_1}$$

In order to be safe I choose a diode that can support the higher current (worst condition) → triangular approximation.

EXAMPLE

 


We have 12 V<sub>rms</sub> at the output of the transformer; we want to evaluate the output DC V. Knowing that  $I_L = 200 \text{ mA}$ ,  $C = 4000 \mu\text{F}$  and  $V_D = 1,5 \text{ V}$


$$V_R = \frac{I_L \cdot T_1}{C} = 0,5 \text{ V}$$

$$V_{DC} = V_P - 2V_D - V_R/2 = \sqrt{2} V_{in} - 2V_D - \frac{V_R}{2} =$$
 
$$= (12 \cdot \sqrt{2} - 3 - 0,5) \text{ V} = 13,7 \text{ V}$$





 Voltage reference  $V_{20}$  in series with a resistance  $R_z$ ; remember that current must be higher than  $I_{2min}$  to have a proper working.



  EXAMPLE

$V_{20} = 5V$      $R_z = 10 \Omega$      $I_{2min} = 5mA$



$$I_{min} = \frac{10V - 5V}{110 \Omega} = 45 \mu A$$

$$I_{max} = \frac{20V - 5V}{110 \Omega} = 130 \mu A$$


$$\left. \begin{aligned} V_{0,dc, min} &= I_{min} \cdot R_z + V_{20} = 5,45V \\ V_{0,dc, max} &= I_{max} \cdot R_z + V_{20} = 6,3V \end{aligned} \right\} \Delta V_0 = 0,85V$$

$$P_{max, Dz} = V_{0, max} \cdot I_{max} = 6,3V \cdot 130 \mu A = 0,819W$$

$$S_i = \frac{\Delta V_0}{\Delta V_i} = \frac{0,85}{10} = 0,085$$


If  $\Delta V_i = 2V \rightarrow \Delta V_0 = \Delta V_i \cdot S_i = 2 \cdot 0,085V = 0,17V$

Series regulator instead needs a controlled variable resistor, and a feedback loop with a voltage reference and an Op Amp. These regulators have a voltage drop so  $V_0 < V_i$ . They are however better than shunt regulators, so are widely used. One of the fields in which SHUNT regulator is needed is the credit card circuit (credit card is the load) because in series regulator the current is the same on card and device, and reading this current it is possible to obtain the secret code of the card; instead in shunt regulators the current divider load/diode doesn't allow this reading.

 

exist and they are called

 
A voltage regulator has a DROPOUT in it; this reduces the available  $V_o$ ; some regulators with low  $V_{drop}$  exist and they are called LOW DROP REGULATOR



Using a PNP transistor in a CE configuration, it is an amplifier (no more a voltage follower); pins of the Op Amps must be inverted to keep negative the loop.


Manufacturers specify both type and value of output capacitor; in

 this way the equivalent resistance and inductance are kept at the desired values.



Good design rules for LDO regulators are the use of a capacitance  $C_1$  to compensate wire inductance

 
and a diode to allow current flows and  $V_o = 0V$  when  $V_i = 0V$ , because otherwise  $V_o > V_i$  could damage the voltage regulator.



Wires or lines in PCB have a resistance that cause voltage drops, so that  $V_{on}$  (coming out from the VR) is different from  $V_{or}$  in the load. To solve this problem


some regulators have two more pins just to connect wires for voltage; no current flows in those wires so they can be also thinner; these wires are called remote sense wires.

 A quiescent current flows out from the pin down in the picture (next page); if this current is very low (LT1317) we can use this device to build a variable voltage regulator.




This circuit can work for the OFF state, but not for the ON state because the current is too low.

 The equivalent circuit for the ON state is a voltage generator of  $V_{CEsat}$ , instead for the OFF state it is an open circuit, because of the leakage current  $I_{CBO}$  from collector to base it is necessary that the base is connected through a resistance to ground so that in the OFF state  $I_{CBO}$  can flow to ground and not through the BST.



 
### HIGH SIDE SWITCH

It is not possible to drive an npn BST used as high side switch, because the ON state would need a voltage at the base higher than  $V_{CC}$ , so we can use a pnp as




high side switch and it is possible to drive it with an npn, as shown in the picture. When  $T_1$  is ON, base of  $T_2$  is at 0V so it is also ON; when  $T_1$  is OFF, base of  $T_2$  is near 12V and so  $T_2$  is ON.


### MOS

 

 MOS transistor is OFF till  $V_{GS} < V_T$ ; when  $V_{GS} > V_T$  it is ON and we have  $I_D = V_{DS} / R_d$



 where  $R_d$  is the internal resistance that depends on temperature,  $V_{GS}$  and  $V_{DS}$ .  $I_D$  is always limited by  $R_d$  because in any case  $I_D \leq \frac{V_{DS}}{R_d}$




low side switch

An N-MOS is used as low side switch, if we used a p-mos we wouldn't have known source voltage



### H-BRIDGE

 


This bridge allows to change the sense of the current in the load, if  $M_1$  and  $M_4$  are on, current flows in one direction, if  $M_2$  and  $M_3$  are on, it flows in the other direction; pay attention in order to don't have both the transistor of one side on at the same time.

there would be a short between  $V_S$  and  $GND$ , and everything would be destroyed.
 
### FLOATING SWITCH


An example of floating switch is the switch of a SRK unit; this circuit allows to drive a floating switch



$$I = 0 \rightarrow V_{GS} = 0 \rightarrow \text{OFF}$$


$$I = I_c \rightarrow V_{GS} = R I_c \rightarrow \text{ON}$$

### OVERVOLTAGE PROTECTION

 


Consider an inductive load; when switch goes OFF the current in the inductance cannot go to 0 immediately. A path for current to flow out is needed. So a diode is used in this way.

 Finally, we didn't discuss yet the need of a galvanic isolation between power section and control section. It can be provided with a transformer or an optocoupler.



### BUCK

 

ON:  $V_L = V_i - V_o$

$$\Delta I_L = \frac{V_L \cdot T_{on}}{L} = \frac{(V_i - V_o) T_{on}}{L}$$

OFF:  $V_L = -V_o$

$$\Delta I_L = - \frac{V_o \cdot t_{off}}{L}$$

$$\Delta I_{on} = - \Delta I_{off}$$

$$V_i T_{on} - V_o T_{on} = V_o T_{off}$$


$$V_i T_{on} = V_o T_s$$

$$\frac{V_o}{V_i} = \frac{T_{on}}{T_s} = D$$

$$\frac{V_o}{V_i} = D$$

We can even replace the diode with a switch driven in the reverse way.

### BOOST

 

ON:  $V_L = V_i$

$$\Delta I_L = \frac{V_i \cdot T_{on}}{L}$$

OFF:  $V_L = V_i - V_o$

$$\Delta I_L = \frac{(V_i - V_o) \cdot T_{off}}{L}$$

$$\Delta I_{on} = - \Delta I_{off}$$

$$V_i T_{on} = -V_i T_{off} + V_o T_{off}$$

$$V_i T_s = V_o T_{off}$$

$$\frac{V_o}{V_i} = \frac{T_s}{T_{off}} = \frac{1}{1-D}$$

$$\frac{V_o}{V_i} = \frac{1}{1-D}$$


## Semiconductor Memories

In all fields where a programmable processor is needed (embedded systems for example), a memory from which processor takes the instructions is needed.

Let's first introduce taxonomy by consider these parameters:

- size (total number of bits)
- organization (size of a word)
- external access (serial or parallel)
- Read / write capability
- Volatility

 From the point of view of external access, a parallel access is faster, but requires more wires, than a serial one.




From the point of view of read / write capabilities instead we can distinguish:

- read only memories ROM
- read and write at the same speed READ WRITE M.
- read faster than writing PROGRAMMABLE M.

And, from the point of view of volatility:

 - data stored forever
- data stored until  $V_{DD}$
- data stored for a limited time.



## ROM

Read Only Memory - Non-volatile; it is programmed before being inserted in the embedded system; they are used to store programs for general purpose processors, to store constant data needed by system or implement COMBINATIONAL CIRCUIT (just by putting in the right row - referred to a certain input - the output values).

Costs overview: the cost to produce one ROM (or any other device) can be divided in RECURRENT and NON-RECURRENT. The first one is the real cost of fabrication, and it is constant; the second one instead depends on the number of pieces produced; non-recurrent costs are the cost of the mask and the cost of the farm i.e.; so the total cost of one piece is

$$\text{TOTAL COST} = \text{RECURRENT COST} + \frac{\text{NON-RECURRENT COSTS}}{N \# \text{ PIECES}}$$

The producer must keep this cost as low as possible, to earn more money. In this context non-recurrent costs have to be kept as low as possible.


Instead of a fuse, an ANTIFUSE can be used; it performs the opposite operation of a fuse: it is a dielectric that can become a short circuit.

NRC are much fewer in this case; OTP-RDT must be small: they cannot be tested at production time, because to be tested they must be programmed, so it is very important that they work all (nearly all) properly, that means a very high yield; since yield decreases with dimension, one must be small.

• EPROM

Erasable Programmable ROM.

 
First of all an introduction to some different devices.



For our purpose an nMOS can be seen just as a switch;

$V_{GS} > V_T \rightarrow ON \rightarrow$  short  
 $V_{GS} < V_T \rightarrow OFF \rightarrow$  open

 The idea to SET the state of the transistor (to store the bit) is to modify  $V_T$ , a very low  $V_T$  makes the MOS always on, while a very high  $V_T$  makes it always off.




$V_T$  can be controlled by putting positive or negative charges in the oxide: if I put negative charges, the channel is created with more difficulties, so  $V_T$  increases; if I put positive charges, the channel is easily created so  $V_T$  decreases. This method is used for SONOS transistors (Silicon - Oxide - Nitride - Oxide - Silicon).

However this device is much bigger than a normal MOS, so they are used in environment with ionizing radiation only (military space nuclear plants).

rays: because  $E = hf$ , this energy (high because  $f$  is high) is transmitted to the electron that can return to channel. So an EPROM package has a quartz window through which UV light can pass.

 
## 2nd - FOWLER NORDHEIM EFFECT

Fowler Nordheim Effect requires a very thin oxide; this allow electrons to pass through the barrier by tunnelling; the oxide in the thin zone is



 8-10 nm wide; one problem is that this process is not self-repeating, the cell is programmed giving a high voltage

at the gate and putting source and drain to GND; to erase it instead I have to put gate to ground and give a high voltage at source.



But, imagine I want to programme transistor 1; I give high voltage at gate and put source to ground, in order not to programme also MOS 2, I have to give  $V_D$  also at 2nd bit line; then, not to erase MOS 1, I'll put  $V_D$  to ground, but so MOS 2 is erased.

Everytime I programme one cell, I lose another one!!!

The solution is to put another transistor that controls the drain of our MOS;

only if the programming line is on ( $V_p$ ) then the MOS is programmed or erased; this cause a doubled space, or, with the same area, half memory, but we can have electrically erasing instead of lightings one.

## ◦ EEPROM (E<sup>2</sup> PROM)

They use the desolated FOWLER NORDHEIM EFFECT: their advantage


we have  $t = RC \ln \frac{3}{3} = 0,09 \cdot R_c$ , i.e. it is 7 times faster.

Moreover, because of noise, a differential signal is always used, taking a line from  $V_{DD}$  and comparing it with the output using a sense amplifier.


## RAM

Rams are volatile memories that can be written and read at the same speed. Information can be stored in a capacitor or in an inverter. In the first case we have dynamic RAM, while in the second we have Static RAM.

### SRAM - Static RAM

 


 A couple of inverters can store the data (either 1 or 0) in the stable points SP, while MSP is a metastable point, like in a mechanical equivalent; the point is how can we modify the state.




behaves as an inverter, instead if I put 0 I reset the cell.

 If we use a NAND instead of an inverter we have another input that we can use to set the value; if I put 1 as input the NAND behaves as an inverter, instead if I put 0 I reset the cell.




Another method is to use a couple of inverters with two switches that works in reverse (when one is open the other is closed); we close "1" to set the state I, then we close "2" to keep the fixed value so an enable line is needed to close

## • MULTIPORT RAMS

 

 In some applications, and usually with multi-processor, it is useful to have multiple access to memory; of course there are some restrictions: for example it is forbidden to write the same cell at the same time from two different processors; the implementation is shown below.




## • ASSOCIATIVE RAMS

An associative RAM allows me to perform three operations: read, write and MATCH. Match operation finds the address of a word that I give to the memory (if it is already in memory); another line called "match line" is needed. Let's see how it works for each bit:

imagine first we have  $H=0$  and we are looking for bit  $D=1$ ; we give  $D$  to the bit line, and put the word line at low state  $M_i$ .



(left) is on because  $F=1$ , while  $H_i$  is off, so gate of  $M_n$  (match) is at high value, so also  $M_n$  is on and match line is at 0. When instead  $H=1$  we have the conducting so match line goes at 1. When I'm looking for a word all the cells are attached at the same match line,

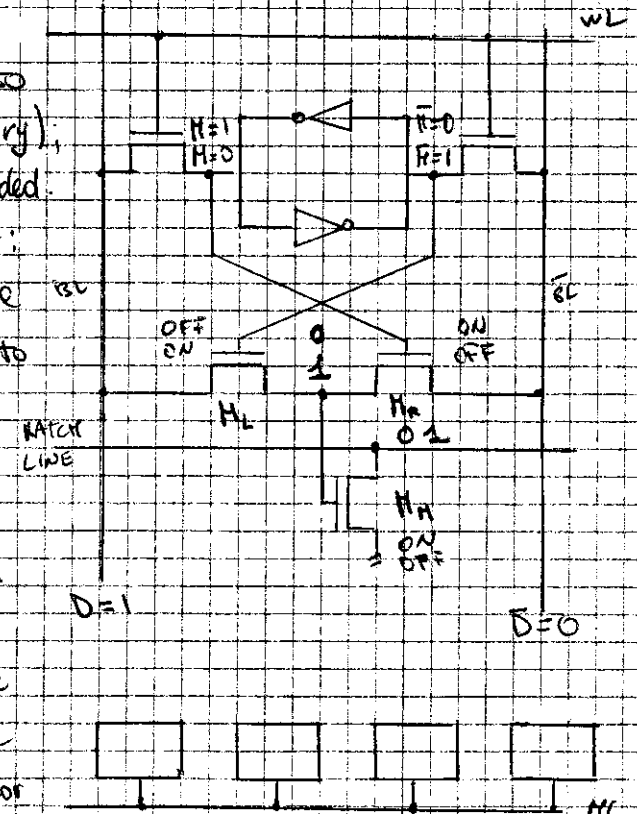and only if all of  $H_{em}$  give 1 as result, the match is 1. Then an encoder is needed, that has the match lines as input and gives the address of the right line as output.






• Multiplexed addressing RAS and CAS

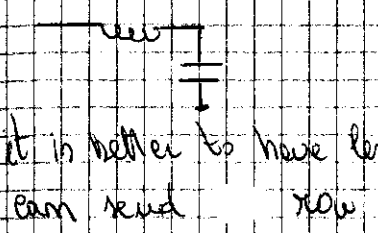
 


Consider the RAM in its package; it has pins to achieve the address to W/R; increasing the number of pins (bigger memory) the cost increases and also the parasitic effects of connections (connection wires have parasitic capacitances and inductances) increases. So

 it is better to have less pins as possible. In order to do this we can send row address and column address to the same pin.



  The memory gets the row address and select the correct row; while all data of the row are read and taken to the multiplexer, column address is get and used to select the right word among those of the selected row. This needs two other controls (pins).





If row address dimension is the same of column address dimension then the number of pins is halved with this method.

There are some RAMS with variations: PSRAM (pseudo-static) have built-in memory refresh controller; NVRAM (non-volatile) holds data after power removed by using a battery; SRAM with EEPROM or FLASH move the content to the non-volatile part before turning off.

Ferroelectric memories

 Using ferroelectric materials, the logic state can be saved as dipoles oriented due to polarisation (with an electric field); so data remain stored even without voltage supply; these memories cannot be as small as DRAM (or, less memory with same dimensions - up to 256 MB), but they are more resistant to radiations than EEPROM and FLASH.



 


Because of these delays, access to memory is slow in comparison with processor work frequency. To reduce this gap two methods can be adopted:

- 1 - SPEED UP ADVANCED RAS
- 2 - CACHE
 
### ① SPEED UP ADVANCED RAS

Addresses that I usually needs are sequentially (both for data and instructions): calling "PAGE" all the words of the same row, after selecting a row, and the needed column, all next columns of same page are read. Data are given at output after a CAS signal and before next CAS signal; introducing a latch before output buffer; time reduction is of 20, 30 %.



Instead of giving different CAS signals it is possible to synchronise the DRAM with the edge of the clock connected both to processor and memory. In this case a counter is needed; the elimination of time to detect RAS/CAS and RD/WR signals makes the RAM faster.

Direct mapping is simple and inexpensive but, on the other hand fixed locations for given blocks cause that if a program accesses 2 blocks that map to the same line repeatedly, cache misses are very high.

Fully associative instead has an expensive searching because all tags have to be compared with the one searched.

Replacement Algorithm: the question is how to choose the block to replace in a cache; this problem doesn't exist for direct mapped caches because each block can go only in one fixed position.

For fully associative and set associative caches we have four algorithms possible:

- Random → the cheapest one
- Least Recently Used (LRU) → a cycles counter is needed (it restarts counting when the block is accessed)
- First In First out (FIFO) → FIFO structure needed
- Least frequently used → a counter is needed (how many accesses to that block) doubt: access in memory, then if another access in memory is needed, the most recent data is cancelled!

Write policy: obviously a cache block cannot be overwritten before memory updating; here are two different policies for memory updating:

- Write through → writes go to cache and memory; this causes a high traffic and slower writes, but memory is always consistent, so access from other CPU's or I/O devices to memory gets always the right data.
- write back → updates are made in cache only initially, then memory is updated only if bits in cache for a block have changed. This causes non consistent memory, so I/O must access memory through cache; but, this reduces a lot traffic and jam-writes (successive updating of the same data).

Cache must have the right dimension; a too small cache causes a high miss rate, while a too big cache causes higher