



Corso Luigi Einaudi, 55 - Torino

Appunti universitari

Tesi di laurea

Cartoleria e cancelleria

Stampa file e fotocopie

Print on demand

Rilegature

NUMERO: 803

DATA: 31/01/2014

A P P U N T I

STUDENTE: Casalino

MATERIA: Fundamentals Of Electrical And Electronic System

Prof. Maio

Il presente lavoro nasce dall'impegno dell'autore ed è distribuito in accordo con il Centro Appunti.

Tutti i diritti sono riservati. È vietata qualsiasi riproduzione, copia totale o parziale, dei contenuti inseriti nel presente volume, ivi inclusa la memorizzazione, rielaborazione, diffusione o distribuzione dei contenuti stessi mediante qualunque supporto magnetico o cartaceo, piattaforma tecnologica o rete telematica, senza previa autorizzazione scritta dell'autore.

ATTENZIONE: QUESTI APPUNTI SONO FATTI DA STUDENTIE NON SONO STATI VISIONATI DAL DOCENTE.
IL NOME DEL PROFESSORE, SERVE SOLO PER IDENTIFICARE IL CORSO.

09/10/2013


CIRCUIT ANALYSIS: GENERALITIES

- ANALYSIS: COMPUTATION OF ALL VOLTAGES AND CURRENTS
 \Rightarrow WRITE CIRCUIT EQUATIONS AND SOLVE
- CIRCUIT EQUATIONS:
 - VOLTAGE & CURRENT EQUATIONS: CIRCUIT TOPOLOGY (LINEAR MEMORYLESS)
 - CONSTITUTIVE RELATIONS: ELEMENT BEHAVIORS (ANY TYPE)
- ANALYSIS METHODS
 - ELEMENTAL: CIRCUIT TRANSFORMATIONS & KNOWN SOLUTIONS FOR SIMPLE TOPOLOGIES
 - GENERAL: VIA EXPEDIENT FORMS OF CIRCUIT EQUATIONS (WORK FOR ANY CIRCUIT)

NODAL ANALYSIS METHOD

CONSTRAINTS

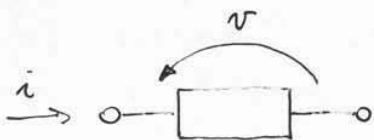
- CONNECTED NETWORK (NO SEPARATE PARTS)
- NATURAL CONDITION: NETWORK ELEMENTS MUST BE VOLTAGE CONTROLLED (NO SHORTS & VOLTAGE SOURCES BETWEEN NODES); IN OTHER WORDS,



2 TERMINAL ELEMENTS: CURRENT i CAN BE EXPRESSED THROUGH VOLTAGE OF THE ELEMENT

$i = F(v) \Leftrightarrow$ VOLTAGE CONTROLLED

RESISTOR

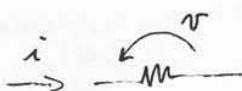


$i = G \cdot v$ WHERE $G = \frac{1}{R}$ CONDUCTANCE

VOLTAGE CONTROLLED

EQUATIONS

NODAL EQUATIONS OF $n-1$ NODES THAT DEFINES THE $n-1$ VOLTAGES
LET'S CONSIDER THIS EXAMPLE

HOW TO WRITE THE NODAL EQUATIONS

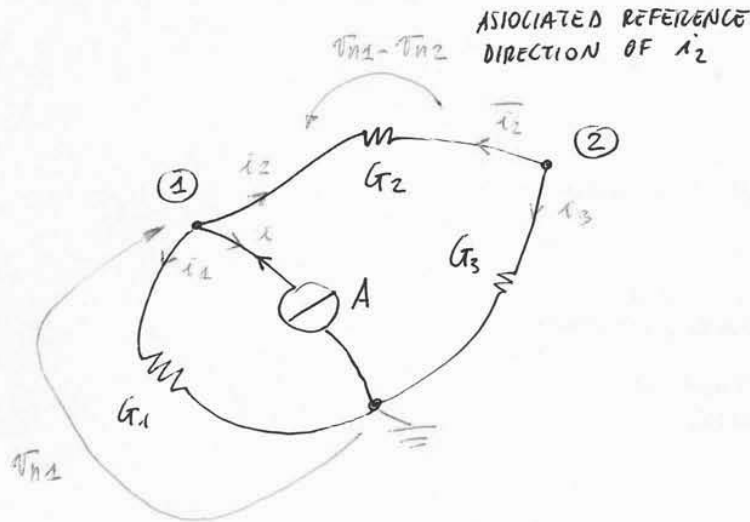

- 1) SELECT THE REFERENCE NODE & LABEL THE OTHER $n-1$ NODES FROM 1
- 2) WRITE NODAL EQUATION FOR EACH OF THE $n-1$ NODES (IN THIS CASE, ① AND ②)

FOR EVERY EQUATION, ASSUME POSITIVE THE CURRENTS EXITING THE NODE; CURRENTS ARE DEFINED AS FLOWING OUT FROM THE NODE

$$\textcircled{1} \quad i_1 + i_2 + i = 0$$

$$\textcircled{2} \quad i_2 + i_3 = 0$$

TO COMPLETE THIS STEP, EXPRESS EACH CURRENT FOR THE NODAL VOLTAGE

$$\textcircled{1} \quad G_1 V_{n1} + G_2 (V_{n1} - V_{n2}) - A = 0$$

$$\textcircled{2} \quad G_2 (V_{n2} - V_{n1}) + G_3 V_{n2} = 0$$

$$V_n = \begin{bmatrix} V_{n1} \\ V_{n2} \end{bmatrix}$$

VECTOR OF UNKNOWNNS

LET'S USE INVERSE OF CONDUCTANCE MATRIX METHOD TO SOLVE ~~THE~~ THE PREVIOUS PROBLEM


$$\begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \frac{1}{(G_1+G_2)(G_2+G_3) - G_2^2} \begin{bmatrix} G_2+G_3 & G_2 \\ G_2 & G_1+G_2 \end{bmatrix} \begin{bmatrix} A \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \frac{1}{\det} \begin{bmatrix} G_2+G_3 \\ G_2 \end{bmatrix} A$$

LET'S CHECK THE RESULT BY USING CRAMER RULE, SUPPOSE ONE IS INTERESTED TO COMPUTE v_{n2}

$$v_{n2} = \frac{\det \begin{bmatrix} G_2+G_3 & A \\ -G_2 & 0 \end{bmatrix}}{\det \begin{bmatrix} G_1+G_2 & -G_2 \\ -G_2 & G_2+G_3 \end{bmatrix}} = \frac{G_2 A}{\det} \quad \text{AS BEFORE !}$$

SAMPLE 2

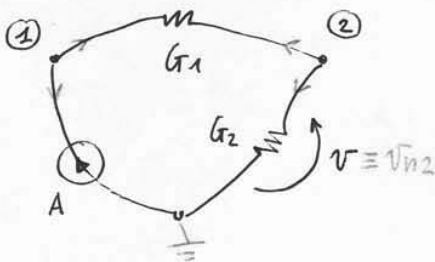

WRITE THE EQUATION FOR NODAL VOLTAGES AND COMPUTE v

$$\textcircled{1} \quad G_1 (v_{n1} - v_{n2}) - A = 0$$

$$\textcircled{2} \quad G_2 v_{n2} + G_1 (v_{n2} - v_{n1}) = 0$$

$$\begin{bmatrix} G_1 & -G_1 \\ -G_1 & G_1+G_2 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \begin{bmatrix} A \\ 0 \end{bmatrix}$$


APPLYING CRAMER RULE

$$v \equiv v_{n2} = \frac{G_1 A}{G_1(G_1+G_2) - G_1^2} = R_2 A$$

THE OBTAINED RESULT IS EASY TO BE CHECKED; THE INTENDED CURRENT (CURRENT SOURCE) IS ALSO THE CURRENT FLOWING THROUGH G_1 & G_2 (1 BRANCH)

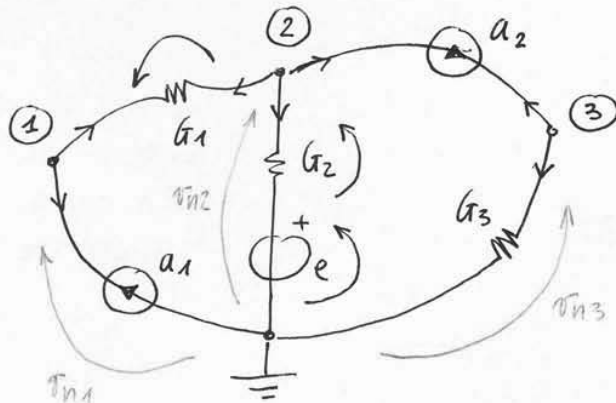PROBLEM 2

COMPUTE NODAL VOLTAGES OBTAINED THROUGH NODAL ANALYSIS METHOD



$$\textcircled{1} -a_1 + G_1(v_{n1} - v_{n2}) = 0$$

$$\textcircled{2} G_1(v_{n2} - v_{n1}) + G_2(v_{n2} - e) + a_2 = 0$$

$$\textcircled{3} -a_2 + G_3 v_{n3} = 0$$

$$\begin{bmatrix} G_1 & -G_1 & 0 \\ -G_1 & G_1 + G_2 & 0 \\ 0 & 0 & G_3 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \end{bmatrix} = \begin{bmatrix} a_1 \\ G_2 e - a_2 \\ +a_2 \end{bmatrix}$$

LOOP EQUATION $v_{n1} - v_{n2} = v_{12}$

REPLACE NUMBERS

$$\begin{matrix} r_1 \\ r_2 \\ r_3 \end{matrix} \begin{bmatrix} 2 & -2 & 0 \\ -2 & 3 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \end{bmatrix} = \begin{bmatrix} 1 \\ e - 1 \\ 1 \end{bmatrix}$$

$$r_2 \rightarrow r_2 + r_1$$


$$\begin{bmatrix} 2 & -2 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \end{bmatrix} = \begin{bmatrix} 1 \\ e \\ 1 \end{bmatrix}$$

$$\Rightarrow \begin{matrix} v_{n3} = 1V \\ v_{n2} = e(t) V \\ v_{n1} = (1 + 2e(t)) \frac{1}{2} V \end{matrix}$$


SAMPLE

1 TERMINAL ELEMENT DOES NOT PLAY ANY ROLE !

COMPUTE i_{sc} BY NODAL ANALYSIS METHOD

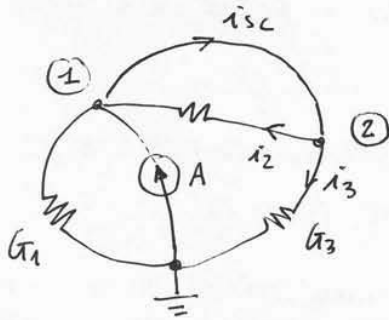

WE ONE CANNOT APPLY NA DIRECTLY

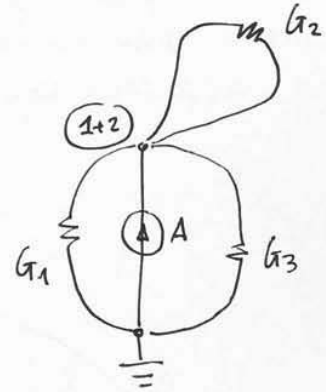

$$G_1 v_{n1} + G_3 v_{n1} = A \Rightarrow v_{n1} = \frac{A}{G_1 + G_3}$$

IN THE SIMPLIFIED CIRCUIT, ONE CAN COMPUTE i_3 AND i_2 , THAT ARE THE SAME FLOWING IN THE ORIGINAL ONE

$$i_3 = G_3 \cdot \frac{1}{G_1 + G_3} A$$

$i_2 = 0$ WHY? BECAUSE IT IS 1 TERMINAL ELEMENT ? NOT ENOUGH TO SAY !

$i_2 = 0$ BECAUSE THE VOLTAGE ACROSS THE RESISTOR 2 IS ZERO BY DEFINITION $\Rightarrow 0$ VOLTAGE = 0 CURRENT !


LET'S COME BACK TO ORIGINAL CIRCUIT

$$i_{sc} = i_3 + i_2 = 0 \Rightarrow \boxed{i_{sc} = i_3}$$

$$\textcircled{1+2} \quad G_1 v_{n1} - A + G_3 (v_{n1} + e) = 0$$

$$(G_1 + G_3) v_{n1} = A - G_3 e$$

APPENDIX

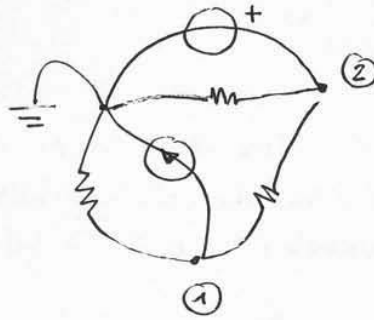


VOLTAGE SOURCE NO LONGER INVOLVED, EQUATIONS ARE SIMPLER



PROBLEM 2

COMPUTE NODAL VOLTAGES DEFINED BY LABELS

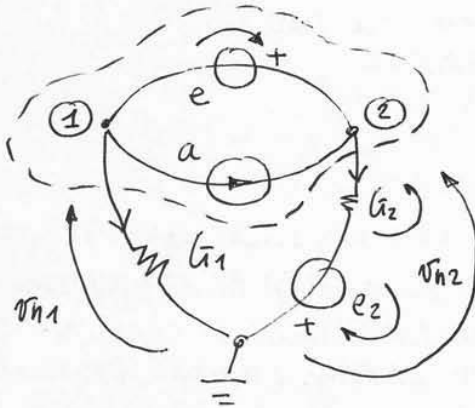

$$v_{n2} = v_{n1} + e$$

$$G_1 v_{n1} + G_2 (v_{n2} + e_2) = 0$$


$$G_1 v_{n1} + G_2 (v_{n1} + e + e_2) = 0$$

$$v_{n1} (G_1 + G_2) = -G_2 (e + e_2)$$

$$v_{n1} = - \frac{G_2}{G_1 + G_2} (e + e_2)$$

$$v_{n2} = - \frac{G_2}{G_1 + G_2} (e_2 + e) + e$$

EXAMPLE

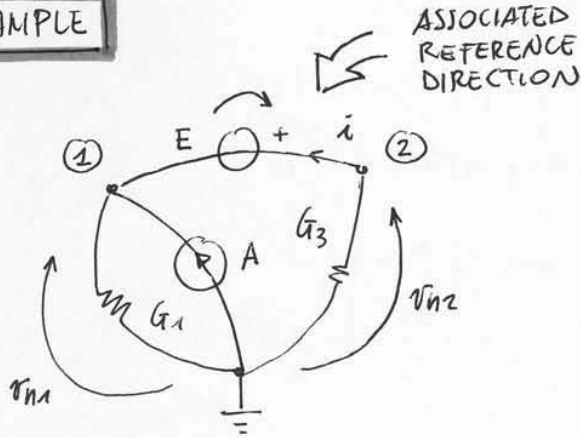

ACCORDING TO MNA RULES
 UNKNOWNNS : $\{v_{n1}, v_{n2}, i\}$

VECTOR OF
 UNKNOWNNS $\begin{bmatrix} v_{n1} \\ v_{n2} \\ i \end{bmatrix}$

① $G_1 v_{n1} - A - i = 0$ WHERE i IS ONE OF THE UNKNOWNNS,
 NO FUNCTION OF NODAL VOLTAGE

② $i + G_3 v_{n2} = 0$

⊖ $v_{n2} - v_{n1} = E$ CHARACTERISTIC OF IDEAL VOLTAGE SOURCE

LET'S MOVE TO MATRIX FORM

$$\begin{bmatrix} G_1 & 0 & -1 \\ 0 & G_3 & +1 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ i \end{bmatrix} = \begin{bmatrix} A \\ 0 \\ E \end{bmatrix}$$


MODIFIED NODAL ANALYSIS IS CONVENIENT

- 1) FOR NUMERICAL SOLUTION
- 2) WHERE REQUESTED
- 3) WHEN ONE WANTS TO PROOVE GENERAL PROPERTIES

IN ALL OTHER CASES, IT IS BETTER TO USE THE OTHER METHOD

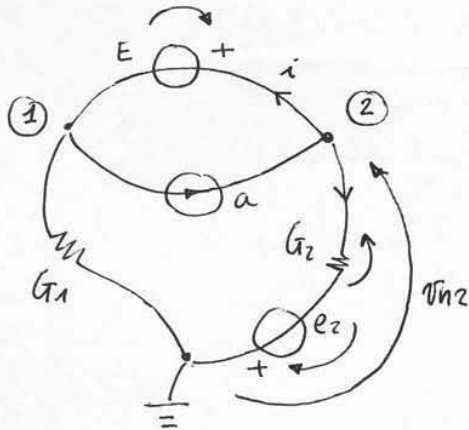PROBLEM 1

WRITE THE MATRIX EQUATION OF THE MNA METHOD



LOOP EQUATION

$$v_{G2} = v_{n2} + e_2$$

$$W^T = [v_{n1}, v_{n2}, i]$$

$$(1) \quad G_1 v_{n1} + a - i = 0$$

$$(2) \quad +i - a + G_2(v_{n2} + e_2) = 0$$

$$(3) \quad v_{n2} - v_{n1} = e \quad \text{---} \bigcirc$$


$$\begin{aligned} G_1 v_{n1} + 0 v_{n2} + (-1) i &= -a \\ 0 v_{n1} + G_2 v_{n2} + 1 i &= a - G_2 e_2 \\ -1 v_{n1} + 1 v_{n2} + 0 i &= E \end{aligned}$$

$$\begin{bmatrix} G_1 & 0 & -1 \\ 0 & G_2 & 1 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ i \end{bmatrix} = \begin{bmatrix} -a \\ a - G_2 e_2 \\ E \end{bmatrix}$$


THEOREM 1

CIRCUITS WITH LOOPS (WT-SETS) COMPOSED OF VOLTAGE (CURRENTS) SOURCES HAVE EITHER NO OR INFINITELY MANY SOLUTIONS

NECESSARY CONDITION

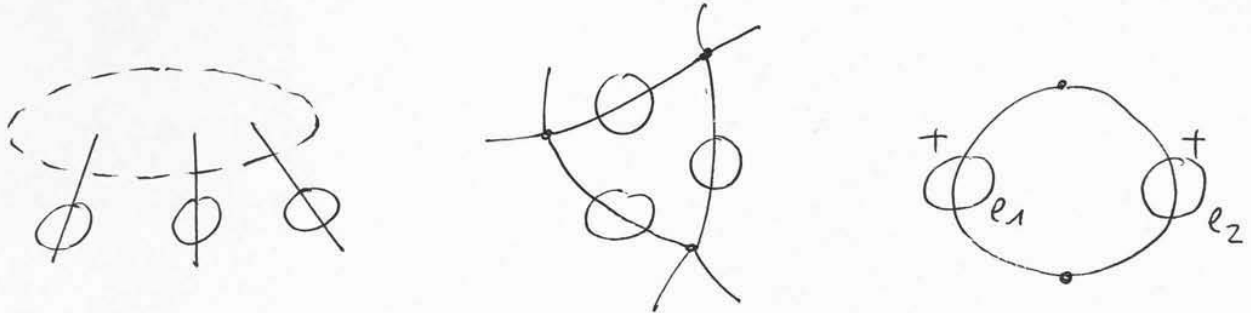

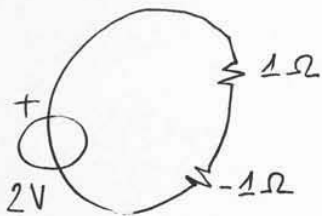NO POSSIBLE INTERPRETATION, MEANINGLESS FOR CIRCUIT POINT OF VIEW
CIRCUIT IS MODEL OF NO PHYSICAL SYSTEM IN THESE CASES



NONE OF THOSE TOPOLOGICAL ERRORS BUT THIS CIRCUIT HAS AGAIN NO SOLUTIONS
⇒ THEOREM 1 JUST NECESSARY CONDITION



THEOREM 2

CIRCUITS COMPOSED OF RESISTORS WITH POSITIVE RESISTANCE AND INDEPENDENT SOURCES WITHOUT LOOPS OF VOLTAGE SOURCES AND CUT-SET OF CURRENT SOURCES HAVE ONE SOLUTION


SUFFICIENT CONDITION

WITHOUT
 / FORBIDDEN TOPOLOGY
 \ NEGATIVE RESISTORS

ONLY NECESSARY & SUFFICIENT CONDITION IS INVOLVING ?


SERIES AND PARALLEL CONNECTIONS

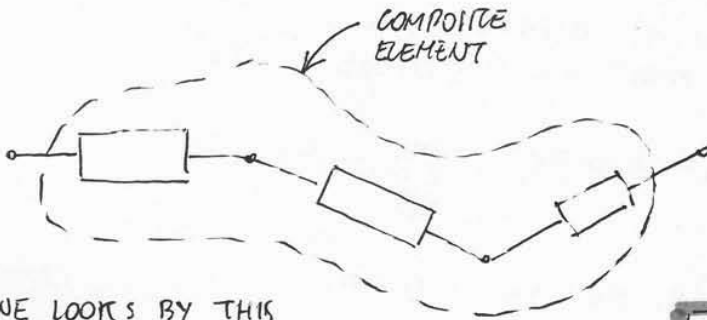2-TERMINAL ELEMENTS ARE CONNECTED IN **SERIES** IFF THEY ONLY FORM A SINGLE PATH SO THAT THE SAME CURRENT FLOWS THRU EACH ELEMENT




TOPOLOGY: TERMINALS OF ELEMENTS MUST BE JOINED, 1 DIMENSIONAL CHAIN; CURRENT FLOW IS THE SAME FOR ALL ELEMENTS OF THE CONNECTION

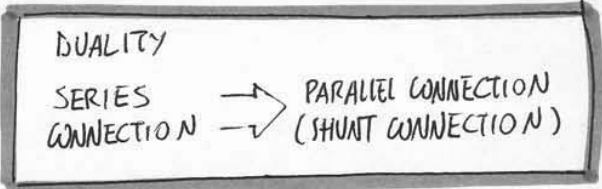IF ONE LOOKS BY THIS CONNECTION, WHAT HE GETS IS A NEW ELEMENT, COMPOSED 2 TERMINAL ELEMENT



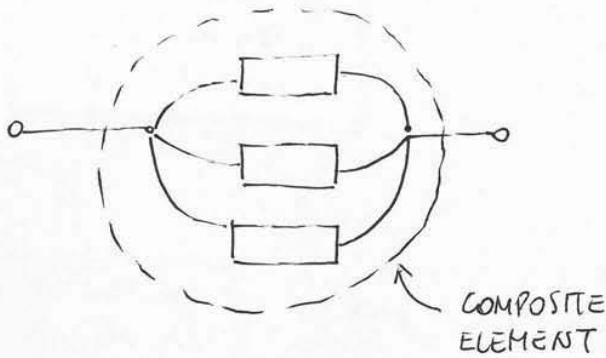2-TERMINAL ELEMENTS ARE CONNECTED IN **PARALLEL** IFF THEIR TERMINALS ARE CONNECTED TO THE SAME TWO NODES SO THAT THE SAME VOLTAGE IS APPLIED TO EACH ELEMENT




EACH ELEMENT HAS THE SAME VOLTAGE ACROSS BECAUSE THE TERMINALS ARE CONNECTED TO THE SAME 2 NODES

RESISTORS IN SERIES

TO DESCRIBE THE BEHAVIOR OF NEW ELEMENTS, ~~WE~~ THE CHARACTERISTIC IS NEEDED; IN THIS CASE, $V = V(i)$

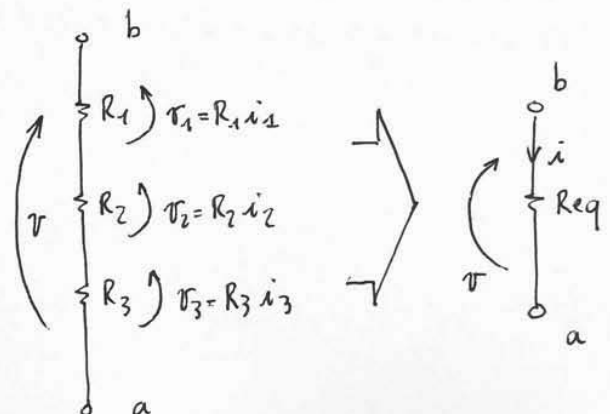~~WE~~ LET'S TRANSFORM THE 3 RESISTORS AS A NEW 2-TERMINAL ELEMENTS



POWERFUL TOOL TO SIMPLIFY CIRCUITS

CURRENT i IS THE SUM OF THE 3 CURRENTS FLOWING THROUGH THE RESISTORS

BY DEFINITION OF PARALLEL CONNECTION, VOLTAGE ACROSS IS THE SAME OF THE COMPOSITE ELEMENT

THE COMPOSITE ELEMENT CAN BE REPLACED BY A SINGLE RESISTOR WHOSE CONDUCTANCE IS THE SUM OF CONDUCTANCES

$$G_{eq} = \sum_k G_k = \sum_k \frac{1}{R_k}$$

KCE

$$\begin{cases} i = i_1 + i_2 + i_3 = G_1 v_1 + G_2 v_2 + G_3 v_3 \\ v = v_1 = v_2 = v_3 \end{cases}$$

$$i = (G_1 + G_2 + G_3) v = G_{eq} v = \frac{1}{R_{eq}} v$$

DUALITY


SERIES CONNECTION RESISTANCE

$$R_{eq} = \sum R_k$$

PARALLEL CONNECTION RESISTANCE

$$G_{eq} = \sum G_k$$

SPECIAL CASE OF 2 RESISTORS

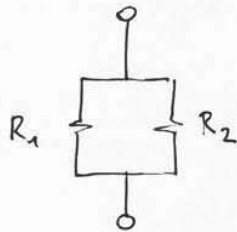

$$G_{eq} = G_1 + G_2 = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

USEFUL PROPERTIES

IF ONE HAS A SERIES CONNECTION OF RESISTORS WHOSE RESISTANCES R_k ARE ALL POSITIVE RESISTANCES, THE EQUIVALENT RESISTANCE IS FOR SURE GREATER THAN THE RESISTANCE OF EACH COMPONENT

SERIES CONNECTION

$$\{R_k\} \quad R_k \geq 0 \quad \forall k \quad R_{eq} \geq R_k \quad \forall k$$

DUALITY

PARALLEL CONNECTION

$$\{G_k\} \quad G_k \geq 0 \quad \forall k \quad G_{eq} \geq G_k \quad \forall k$$


LET'S DEAL WITH PARALLEL CONNECTIONS NOW

$$\frac{1}{R_{eq}} = \frac{1}{G_{eq}} ; \quad \frac{1}{G_{eq}} \leq \frac{1}{G_k} \quad \text{THAT MEANS}$$

$$R_{eq} \leq R_k \quad \forall k$$

PARALLEL CONNECTION

LET'S CONSIDER THIS PROBLEM

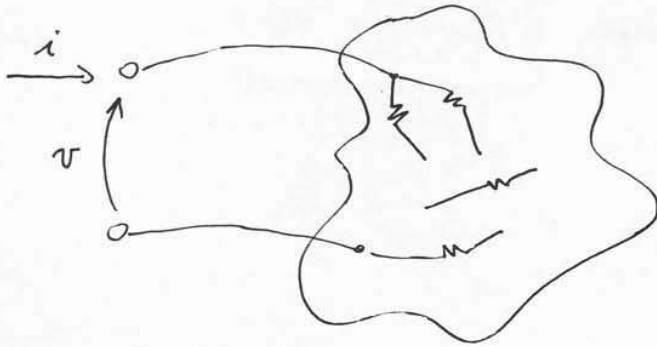


WHAT IS THE RELATION
BETWEEN v AND i ?
FOR WRE $v = R_{EQ} \cdot i$

ANY NETWORK COMPOSED BY RESISTORS BEHAVES LIKE
THE EQUIVALENT RESISTOR



LET'S PROOVE IT BY USING N.A. METHOD

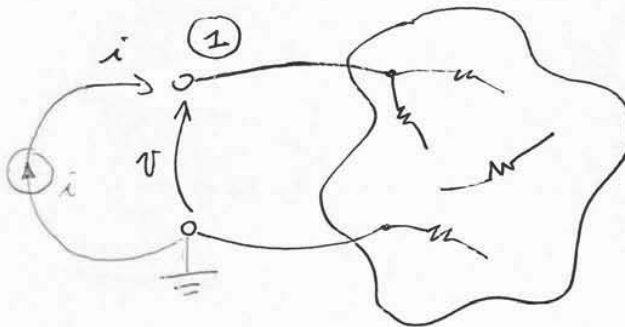

$$P \cdot W = U$$

$$P \begin{bmatrix} v_{n1} \\ \vdots \\ \cdot \end{bmatrix} = \begin{bmatrix} i \\ 0 \\ \vdots \end{bmatrix}$$

$$\begin{bmatrix} v_{n1} \\ \vdots \\ \cdot \end{bmatrix} = P^{-1} \begin{bmatrix} i \\ 0 \\ \vdots \end{bmatrix}$$

ONE IS INTERESTED IN v_{n1}


$$v_{n1} = v = (P^{-1})_{1i} \cdot i \quad \text{WHERE}$$

v : VOLTAGE ACROSS THE ELEMENT

$$(P^{-1})_{1i} = \text{EQUIVALENT RESISTANCE}$$

ANALYSIS OF CIRCUITS WITH 1-SOURCE ONLY

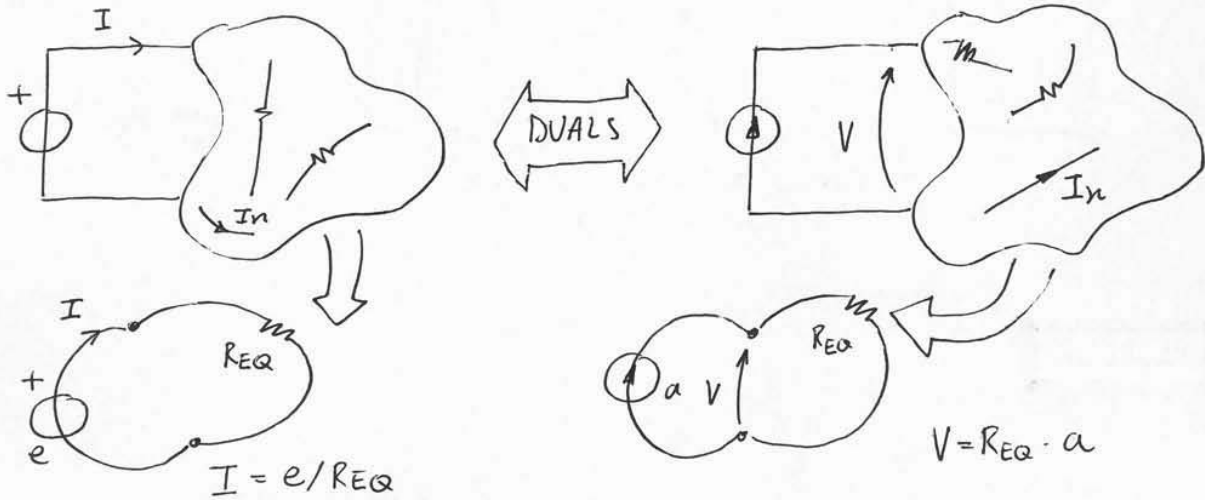
HOW TO COMPUTE THE EXTERNAL (I AND V) OR INTERNAL (I_x) UNKNOWN VARIABLES?



I, V ARE THE ONLY TERMS DEFINED IN BOTH ORIGINAL CIRCUIT AND SIMPLIFIED ONE; IF ONE IS INTERESTED IN INTERNAL QUANTITIES, HE HAS TO STEP BACK TO THE ORIGINAL CIRCUIT



EXAMPLE 1

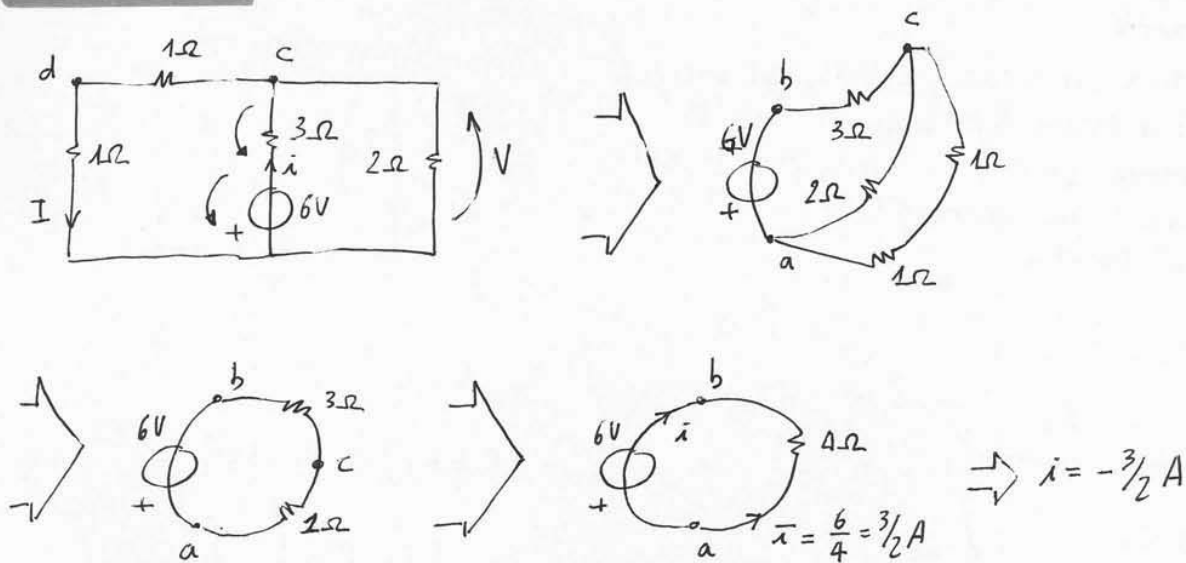


$$V_{3\Omega} = 3\Omega \cdot \left(-\frac{3}{2}A\right) = -\frac{9}{2}V \quad ; \quad V = -6 - \left(-\frac{9}{2}V\right) \quad \text{LOOP EQUATION}$$

$$I = V \cdot \frac{1}{2} \Rightarrow I = \left(-6 + \frac{9}{2}\right)V \cdot \frac{1}{2}S = -\frac{3}{4}A$$

$G_{EQ} = 1/(1+1)$


SAMPLE 1

PAY ATTENTION ON SIGNS

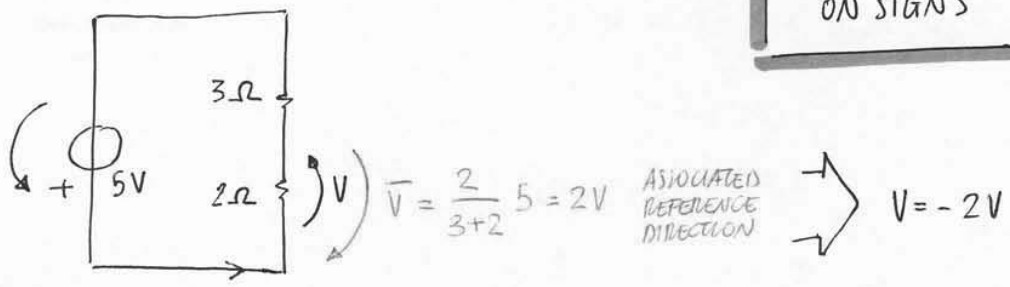

SAMPLE 2


PAY ATTENTION ON TOPOLOGY

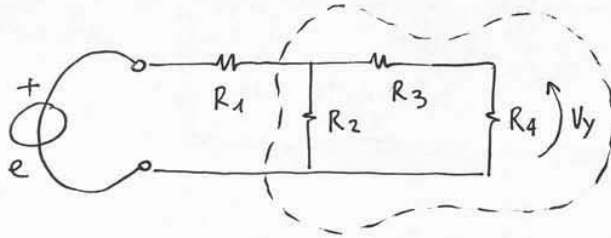

VOLTAGE DIVIDER HOLD ONLY FOR SERIES CONNECTIONS, WE MUST NOT APPLY TO EVERYTHING THAT IS NOT SERIES CONNECTED


R_1 SERIES CONNECTED TO THE COMPOSITE 2-TERMINAL ELEMENTS

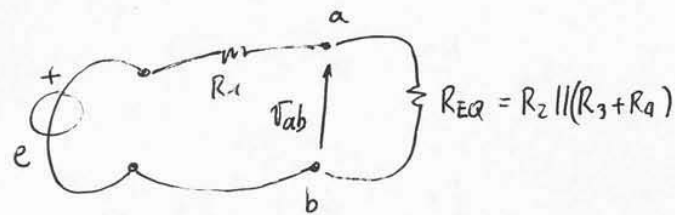CURRENT FLOWING THROUGH $R_1 \neq$ CURRENT FLOWING THROUGH R_2



ACCORDING TO VOLTAGE DIVIDER RULE $V_{ab} = e \frac{R_{EQ}}{R_{EQ} + R_1}$

SINCE THE 2 CIRCUITS ARE EQUIVALENT, THE QUANTITIES COMPUTED HAVE THE SAME VALUE IN BOTH THE CIRCUITS

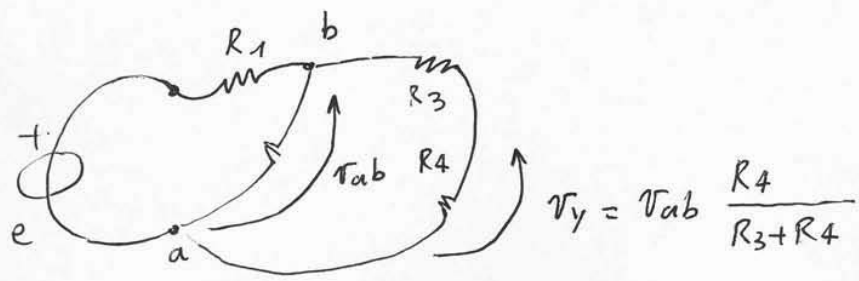

SAMPLE 1


COMPUTE THE CURRENT I and i_x
and THE VOLTAGE v_x

$$i_x = 2A \cdot \frac{1/2}{1/3 + 1/2 + 1/2}$$

PAY ATTENTION
TO THE SIGNS

$$v_x = 2\Omega \cdot i_x$$

$$v_x = -3\Omega \cdot I \Rightarrow I = v_x / -3$$

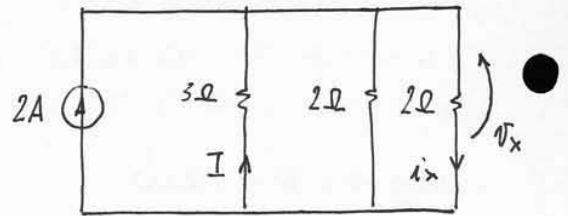

SAMPLE 2



COMPUTE CURRENT i_x and I

LET'S COMPUTE THE EQUIVALENT RESISTANCE
OF THE SERIES CONNECTION BETWEEN
 R_1 AND $R_2 \parallel R_2$; NOW, ONE IS ABLE TO
COMPUTE i_x (ONLY PARALLEL CONNECTIONS)

$$i_x = 5 \cdot \frac{3}{3+2} = 3A$$

PAY ATTENTION
TO THE
TOPOLOGY

$$I = i_x \cdot \frac{1}{2} = \frac{3}{2} A$$

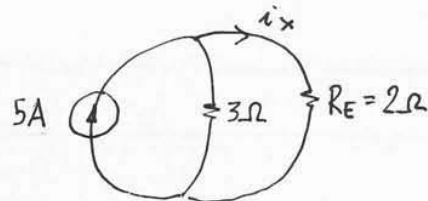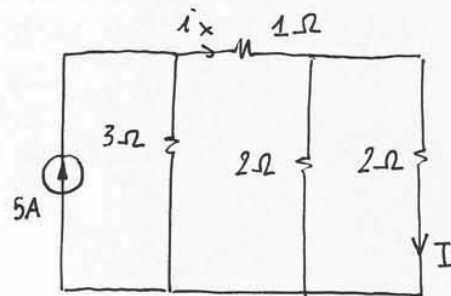

PROBLEM 2


DETERMINE i AND v VIA EITHER CURRENT OR THE VOLTAGE DIVISION RULE

$$R_{EQ} = (1+3+2) \parallel (1+1+2) = 12/5 \Omega$$

$$v_T = \frac{12}{5} \cdot 5 = 12V ; v = -\frac{3 \cdot 12}{1+3+2} = -6V$$

$$i = -5 \cdot \frac{G_1}{G_E} = -5 \cdot \frac{1/4}{5/12} = -3A$$


PAY ATTENTION
TO THE SIGNS

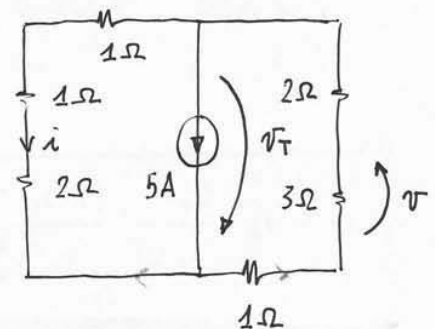

e EFFECT AND a EFFECT CAN BE COMPUTED INDEPENDENTLY BY SETTING ONE OR THE OTHER ONE EQUAL TO ZERO



e-EFFECT $V_{h1}|_{a=0}$

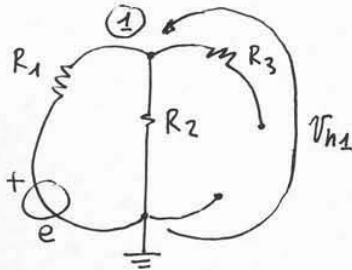


$a=0 \Leftrightarrow$ OPEN CIRCUIT

LET'S APPLY VOLTAGE DIVIDER RULE

$$V_{h1}|_{a=0} = \frac{R_2}{R_1+R_2} e$$

a-EFFECT $V_{h1}|_{e=0}$

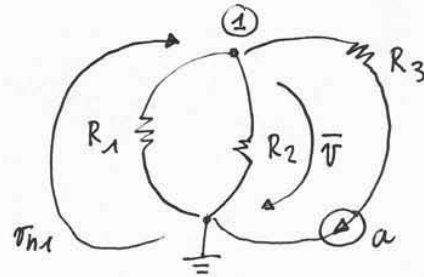

$e=0 \Leftrightarrow$ SHORT CIRCUIT

$$\bar{V} = \frac{R_1 R_2}{R_1 + R_2} a$$

$$V_{h1}|_{e=0} = - \frac{R_1 R_2}{R_1 + R_2} a$$


$$V_{h1} = \frac{R_2}{R_1+R_2} e - \frac{R_1 R_2}{R_1+R_2} a$$

NOT EFFECTIVE METHOD



MILLMAN'S THEOREM, CONT'D

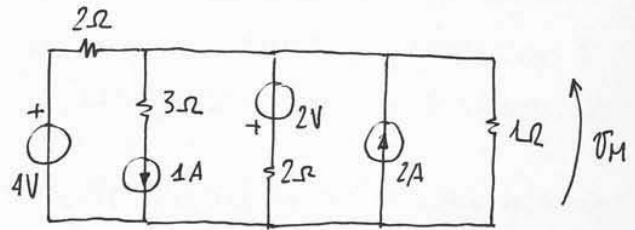
$$V_M = \frac{[A] + [B]}{[C]} = \frac{\left(\frac{4V}{2\Omega} - \frac{2V}{2\Omega}\right) + (2A - 1A)}{\left(\frac{1}{2\Omega} + \frac{1}{2\Omega} + \frac{1}{1\Omega}\right)} = 1V$$



THE ELEMENTS CONNECTED IN SERIES TO A CURRENT SOURCE HAVE NO EFFECTS ON V_M !

SAMPLE 2
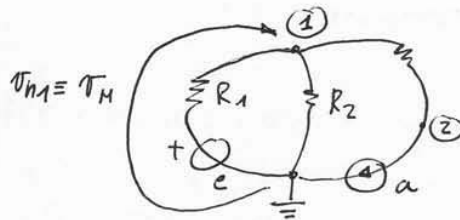
$$V_{M1} = \frac{G_1 e - a}{G_1 + G_2} \quad \text{MILLMAN}$$



IT IS FASTER THAN SUPERPOSITION METHOD AND IT LEADS TO THE SAME RESULT

PROBLEM 1

DETERMINE VOLTAGE V & CURRENT i


$$V_M = \frac{-1/2 \cdot 10 - 1/4 \cdot 4 + 2}{1/2 + 1/4} = -\frac{16}{3} V$$

LOOP EQUATION

$$V_M + V_x + 10 = 0$$


$$\Rightarrow V_x = -10 + \frac{16}{3} = -\frac{14}{3} V$$
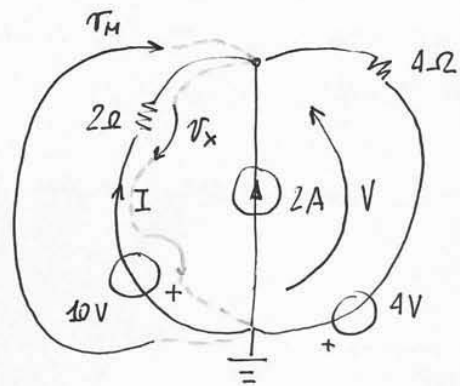
$$\Rightarrow I = \left(-\frac{14}{3}\right) \cdot \frac{1}{2} = -\frac{7}{3} A$$




AFTER COMPUTING THE MILLMAN'S VOLTAGE, THE OTHER UNKNOWN ARE SIMPLY COMPUTED !

THEVENIN'S THEOREM

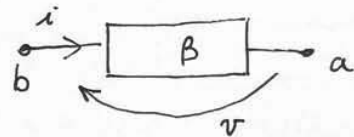

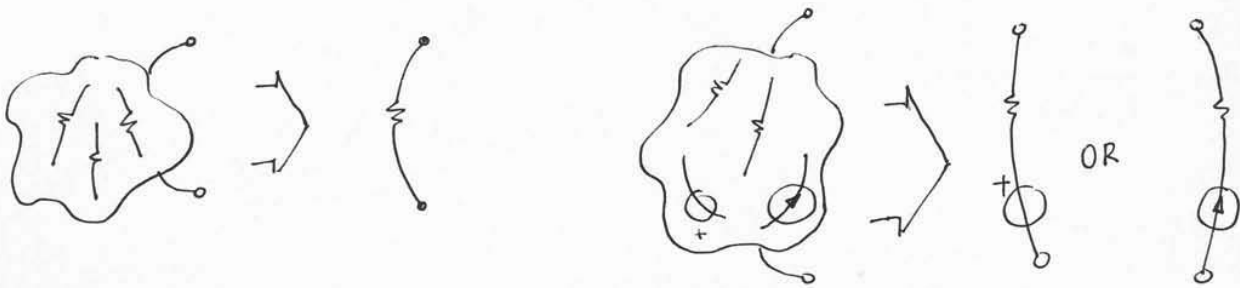IT IS A GENERALIZATION OF EQUIVALENT RESISTANCE




ANY WELL-DEFINED (IT DOES NOT CONTAIN CIRCUIT ELEMENTS THAT ARE COUPLED TO SOME PHYSICAL VARIABLES OUTSIDE), 2-TERMINAL CIRCUIT ELEMENT β THAT IS COMPOSED BY LINEAR, TIME-INVARIANT, RESISTIVE ELEMENTS AND THAT LEADS TO A ONE-SOLUTION CIRCUIT WHEN DRIVEN BY AN IDEAL CURRENT SOURCE

1) HAS THE FOLLOWING CHARACTERISTIC

$$v = R_E i + V_0$$

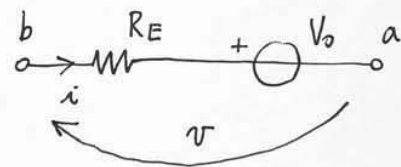2) IS EQUIVALENT TO THE FOLLOWING 2-TERMINAL ELEMENT (THEVENIN EQUIVALENT)



ALLOW TO REPLACE A COMPOSITE LINEAR RESISTIVE 2-TERMINAL ELEMENT BY THE SERIES CONNECTION OF ONE RESISTOR AND ONE VOLTAGE SOURCE


DEMONSTRATION

IT IS BASED ON SUPERPOSITION THEOREM

β CONTAINS $\frac{1}{s}$, $\frac{1}{s^2}$, $\frac{1}{s^3}$, ETC. AND

IT RESPECTS THEVENIN'S HYPOTHESIS

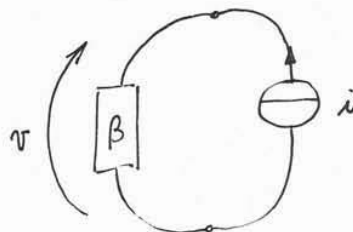
(WELL-DEFINED \equiv CLOSED, \neq SOLUTION, ...)



SUPERPOSITION THEOREM : $v = K_i \cdot i + v_0 \Rightarrow v = R_E i + v_0$

SAMPLE 1

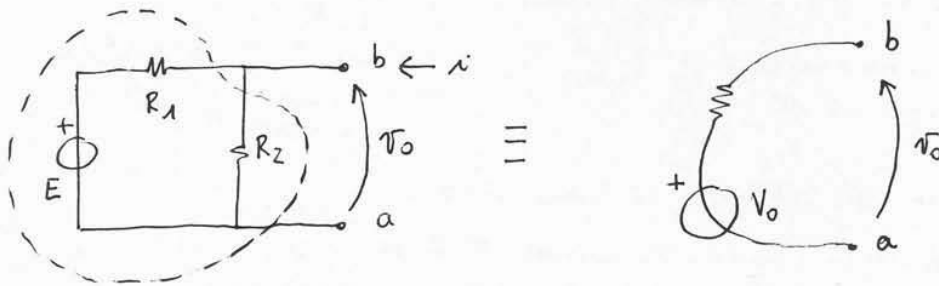DETERMINE THE THEVENIN'S EQUIVALENT CIRCUIT AT TERMINALS b-a




ONE STEP COMPUTATION

APPLYING MILLMAN


$$V = (G_1 E + i) / (G_1 + G_2)$$

LET'S CHANGE THE FORM TO OBTAIN THEVENIN'S EQUIVALENT
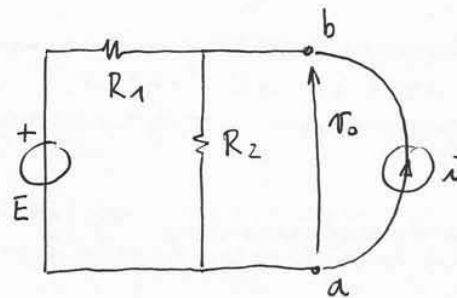
$$V = \underbrace{\frac{1}{G_1 + G_2}}_{R_E} i + \underbrace{\frac{G_1}{G_1 + G_2}}_{V_0} E$$



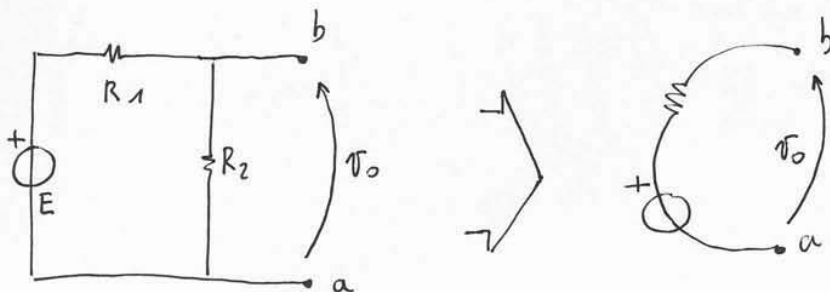
TWO STEP COMPUTATION (MORE EFFICIENT METHOD)



ONE LEAVES THE TERMINALS OPEN (NO CURRENT THROUGH THEM)

LEAVING TERMINALS OPEN TRANSFORM CONNECTION INTO SERIES => VOLTAGE DIVIDER



$$v_0 = E R_2 / (R_1 + R_2)$$

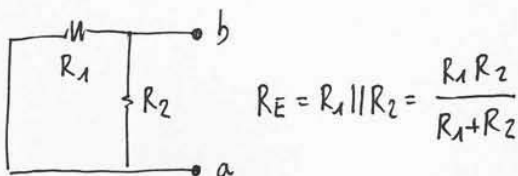


$$V = \frac{R_1 R_2}{R_1 + R_2} i + \frac{E R_2}{R_1 + R_2}$$

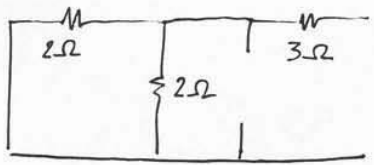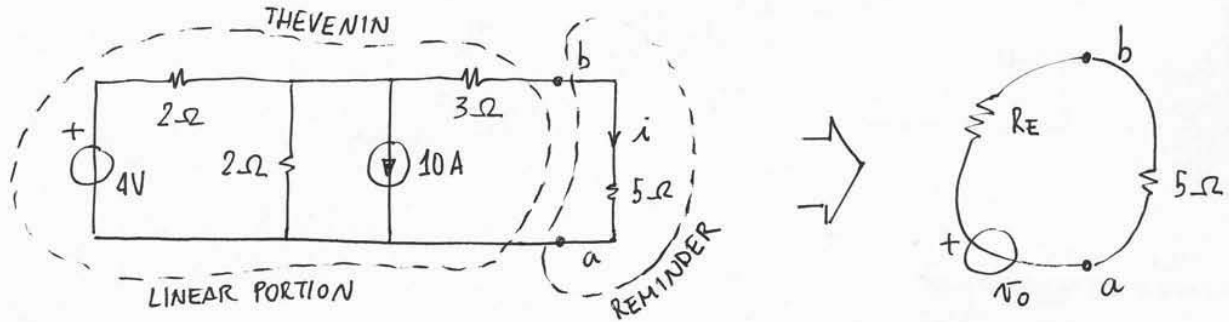PROBLEM 1

DETERMINE THE CURRENT i BY REDUCING THE 2-TERMINAL ELEMENT ATTACHED TO THE 5Ω RESISTOR TO ITS THEVENIN EQUIVALENT



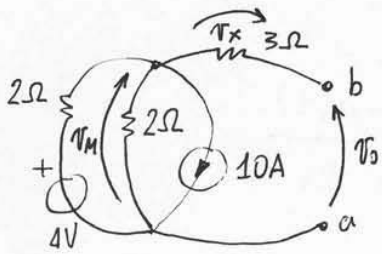
$$\Rightarrow R_E = (2 \parallel 2) + 3 = 4\Omega$$



$$V_M = V_0 = \frac{\frac{1}{2} \cdot 4 - 10}{\frac{1}{2} + \frac{1}{2}} = -8V$$

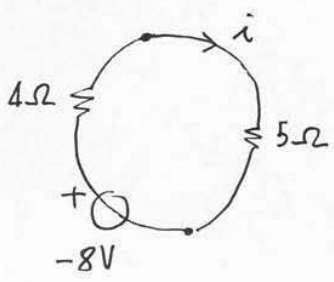
V_x ACROSS $R=3\Omega$ IS NULL BECAUSE TERMINALS ARE LEFT OPEN



$$i = \frac{-8V}{4\Omega + 5\Omega} = -\frac{8}{9}A$$


SAMPLE 1

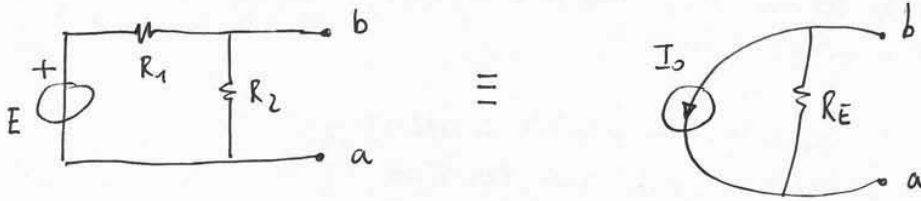DETERMINE THE NORTON EQUIVALENT CIRCUIT AT TERMINALS b-a



ONE STEP COMPUTATION


LET'S APPLY NODE EQUATION

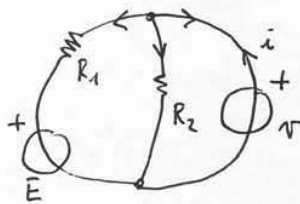


$$i = G_2 v + G_1 (v - E)$$

$$i = \underbrace{(G_1 + G_2)}_{G_E} v - \underbrace{G_1 E}_{I_0}$$

TWO-STEP COMPUTATION (MORE EFFICIENT)

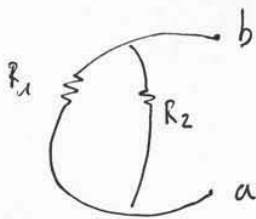

$$G_E = G_1 + G_2 = \frac{1}{R_E}$$

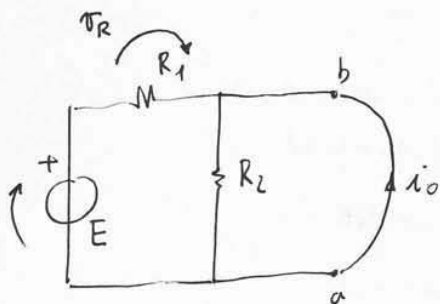

LOOP EQUATION

$$E + v_R = 0 \Rightarrow v_R = -E$$

$$i_R = G_1 v_R$$



$$\Rightarrow i_0 = i_R = -G_1 \cdot E$$

CURRENT THRU R2 IS NULL BECAUSE R2 IS SHORT CIRCUITED

$$i = (G_1 + G_2) v - G_1 E$$

CONVERSION OF EQUIVALENTS

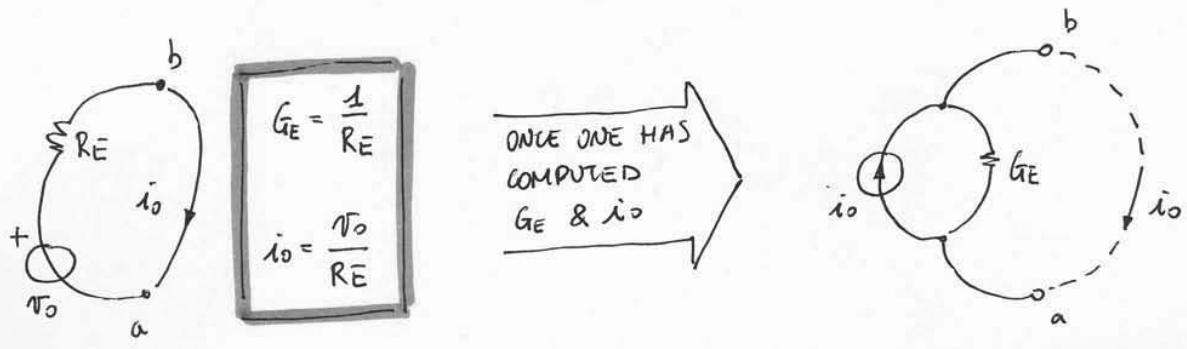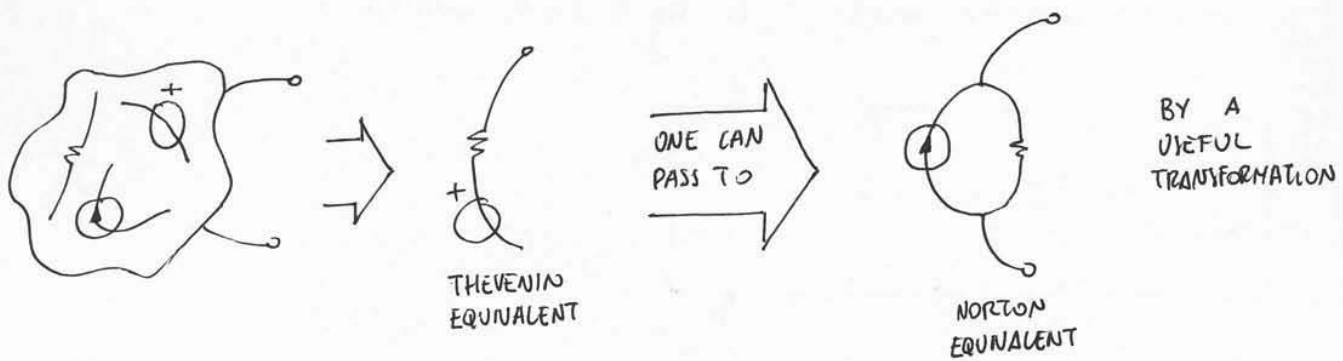BUILD THE DUAL EQUIVALENT OF ONE THAT IS GIVEN



EVEN THE OPPOSITE PROCEDURE IS ALLOWED

$$R_E = 1/G_E \quad \& \quad V_o = i_o / G_E$$

THE CURRENT SOURCE HAS TO BE DIRECTED AS i_o IN THIS FIGURE

R_E MUST BE $\neq 0$ OTHERWISE WE CANNOT COMPUTE ~~the~~ IT

EXISTANCE OF EQUIVALENTS

PRACTICAL CONDITIONS FOR ELEMENTS COMPOSED OF RESISTORS & INDEPENDENT SOURCES

• IF $|R_E| < \infty$ & $R_E \neq 0 \Rightarrow$ BOTH THE 2 EQUIVALENTS EXIST

• IF $R_E = 0$, THE THEVENIN EQUIVALENT IS $V_o = \mathcal{V}$ & NORTON EQUIVALENT DOES NOT EXIST


• IF $|R_E| = \infty$ ($G_E = 0$), THE NORTON EQUIVALENT IS $i = i_o$ & THEVENIN EQUIVALENT DOES NOT EXIST

APPLICATION OF THEVENIN: MAXIMUM POWER TRANSFER


MAXIMUM POWER OBTAINED

APART FROM SPECIAL CASES, ONE USES THEVENIN'S EQUIVALENT

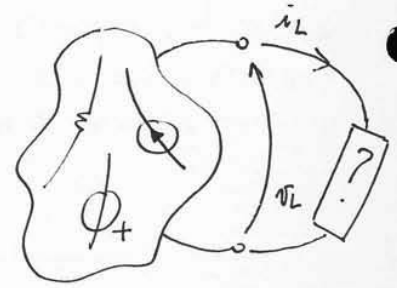PROBLEM: FIND MAX OF $p(t) = v_L i_L$ WHERE $L = \text{LOAD}$



ONE CAN COMPUTE v_L AND i_L

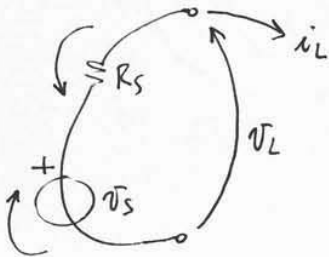

$$v_{RES} = R_s i_L$$

$$v_L = v_s - R_s i_L$$

LET'S COMPUTE THE POWER


$$p = \underbrace{(v_s - R_s i_L)}_{v_L} i_L$$

POWER \equiv QUADRATIC FUNCTION OF LOAD

IF $i_L = 0 \Rightarrow$ OPEN CIRCUIT AS UTILIZER

IF $i_L = v_s / R_s \Rightarrow$ SHORT CIRCUIT AS UTILIZER

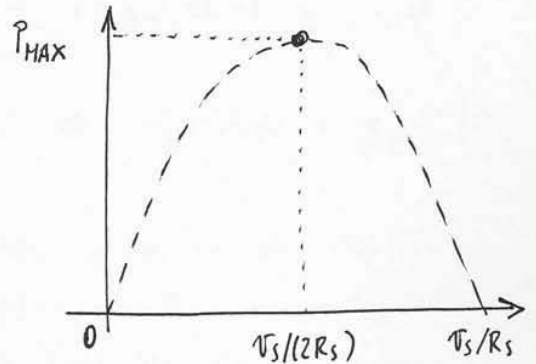P IS NULL IN THESE ~~ABOVE~~ 2 POINTS ABOVE MENTIONED




MAXIMUM POWER (READ ON PARABOLIC GRAPH)

$$P_{MAX} = \left(v_s - R_s \frac{v_s}{2R_s} \right) \cdot \frac{v_s}{2R_s}$$

$$P_{MAX} = \frac{v_s^2}{4R_s}$$

MAX POWER

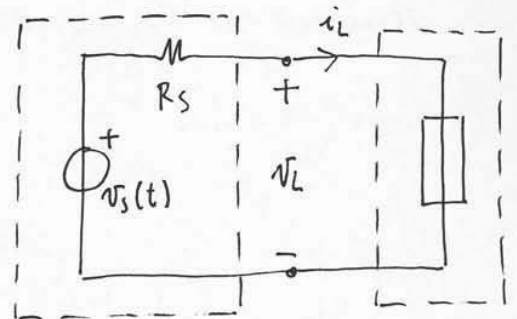

$$R_L = R_s$$

MATCHING LOAD

WHEN A SOURCE DELIVERS MAX POWER, ONE SAYS THAT IT IS MATCHED





IN OUR CASE, $v_L = v_s / 2$ = SMALL VALUE OF VOLTAGE; FOR EXAMPLE, IN CASE OF BATTERIES IT IS NOT GOOD TO BE AT LOW ~~v~~ v_L IN COMPARISON WITH v_s (NOT IN WORKING ZONE)

ANALYSIS VIA CIRCUIT TRANSFORMATION

- MODIFY THE CIRCUIT TOPOLOGY, GROUP AND REPLACE ELEMENTS TO REDUCE THE CIRCUIT TO A SINGLE LOOP OR SINGLE-NODE-PAIR CIRCUIT (NOT ALWAYS POSSIBLE)
- SOLVE THE SIMPLIFIED CIRCUIT BY DIVIDER EQUATIONS OR MILLMAN'S EQUATION

THERE IS NO ALGORITHM, IT REQUIRES EXPERIENCE **!**


SAMPLE 1

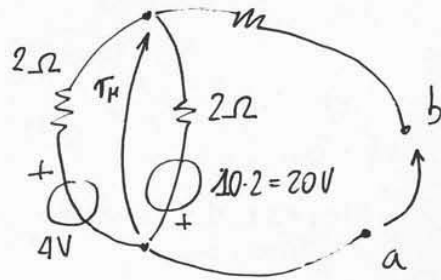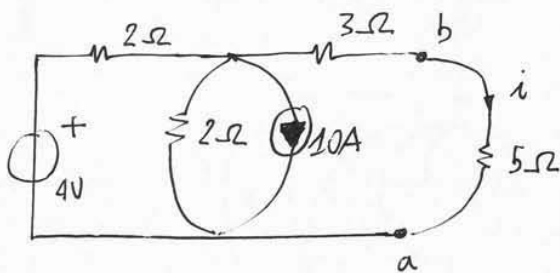

LET'S BUILD THEVENIN EQUIVALENT

1st STEP : $R_E = \cancel{2\Omega + 3\Omega} (2\parallel 2) + 3 = 4\Omega$

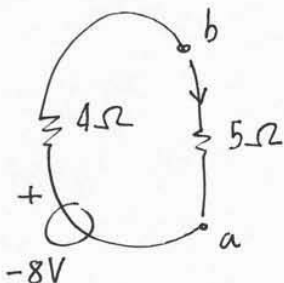$V_{th} = V_o = \frac{4 \cdot 1/2 - 20 \cdot 1/2}{1} = -8V$ 2nd STEP




$$i = -\frac{8V}{9} = -\frac{8}{9} A$$

4- CONTROLLED SOURCE AND 2-PORT ELEMENTS





CONTROLLED SOURCES ARE IDEAL SOURCES (VOLTAGE SOURCE OR CURRENT ONE) FORCING VOLTAGES AND CURRENTS THAT ARE FUNCTIONS OF OTHER CIRCUIT VARIABLES; THEY DEPEND ON SOMETHING ELSE, THEY ARE NOT INDEPENDENT



LET'S DEAL WITH LINEAR CONTROLLED SOURCES

4 KINDS

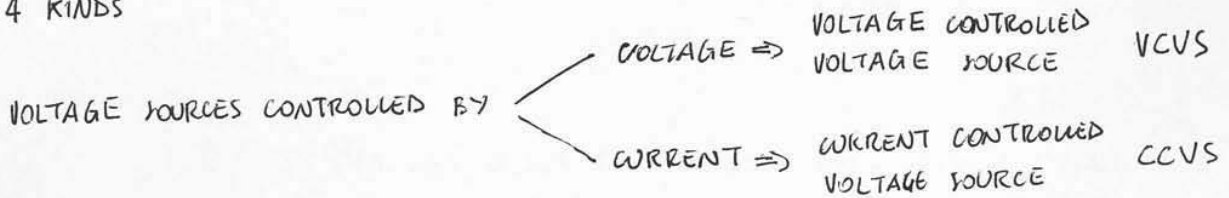

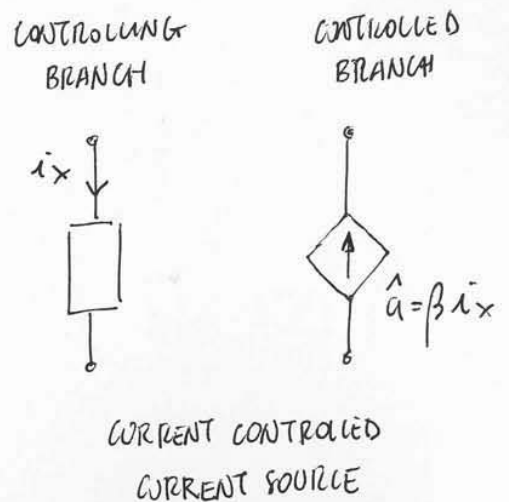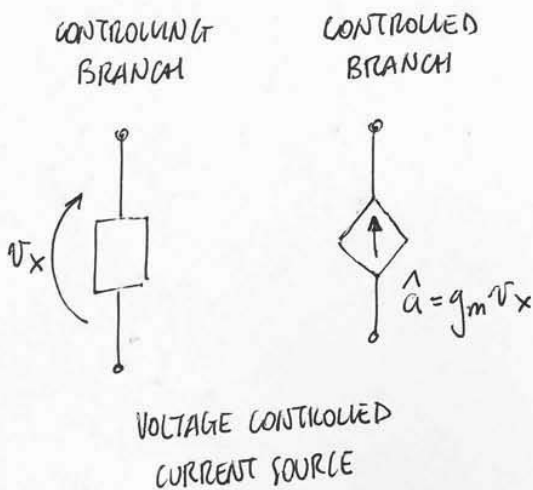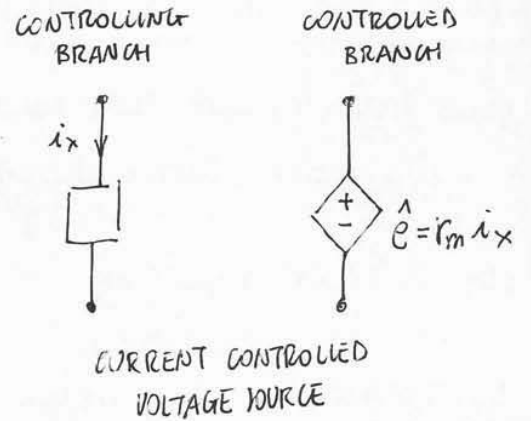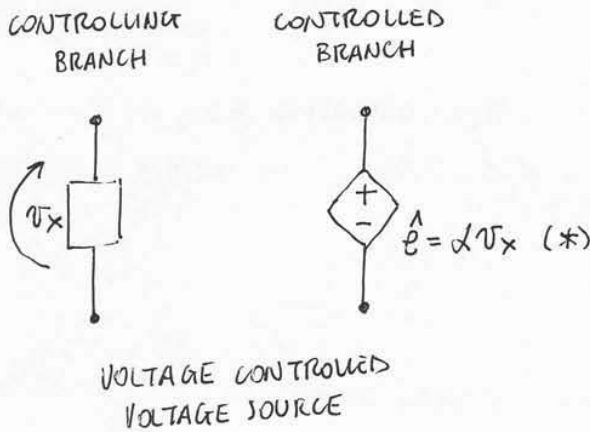(*) IT DEFINES THE BEHAVIOUR OF THE ELEMENT; VOLTAGE IS LINEAR FUNCTION OF CONTROLLING VOLTAGE v_x



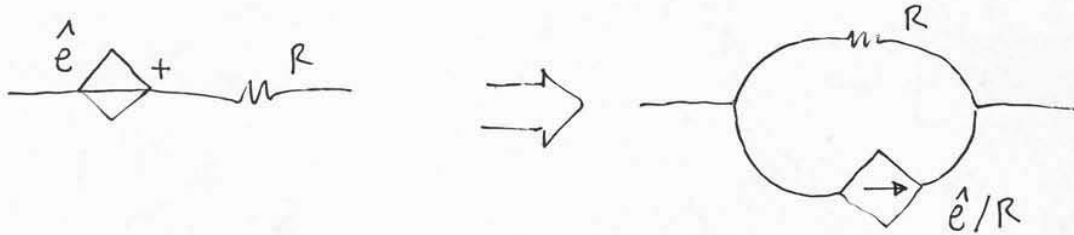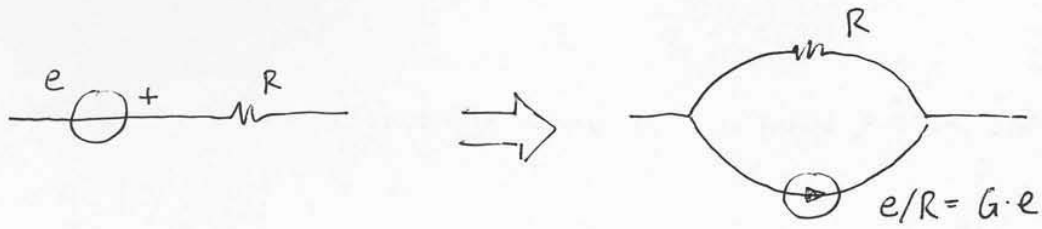

2) FOR THE RESULTING RESISTOR C-SOURCE CIRCUIT, USE

$$[G_n]_{kk} = \sum G_k \quad \text{RESISTORS CONNECTED TO NODE } k$$

$$[G_n]_{hk} = [G_n]_{kh} = -\sum G_n \quad \text{RESISTORS BETWEEN NODES } k \text{ \& } h$$

$$[A]_k = \sum a_k \quad \text{CURRENT INJECTED INTO NODE } k$$

NODAL ANALYSIS REVISITED, CONT'D


NODAL MATRIX EQUATION FROM MATRIX ELEMENTS, CURRENT CONTROLLED ELEMENTS CASE

- 1) SHORT CIRCUITS ONLY \Rightarrow JUST REMOVE THEM
- 2) VOLTAGE SOURCE: USE MNA (TREAT AUXILIARY CURRENTS AS FORCING TERMS)

$$[A]_k = \sum a_k + \sum i_{ek} \quad \begin{array}{l} \text{CURRENTS INJECTED} \\ \text{INTO NODE } k \end{array}$$

... THEN MOVE AUXILIARY CURRENTS ON LEFT-HAND SIDE AND CAST IN MATRIX FORM !

EXAMPLE

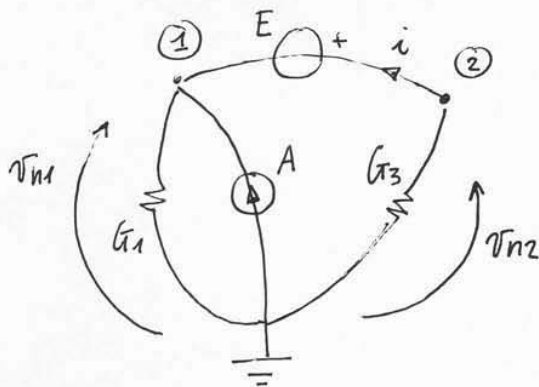

NO SERIES TOPOLOGY

VOLTAGE SOURCE: FORBIDDEN ELEMENT
LET'S DEFINE AUXILIARY CURRENT i
THROUGH THE VOLTAGE SOURCE AND
THEN APPLY THE RULES ONE
HAS JUST SEEN

ACTUAL VECTOR OF SOURCE TERM

$$\begin{bmatrix} G_1 & 0 \\ 0 & G_3 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \begin{bmatrix} A+i \\ -i \end{bmatrix} = \begin{bmatrix} A \\ 0 \end{bmatrix} + \begin{bmatrix} 1 \\ -1 \end{bmatrix} i$$

SET OF UNKNOWNNS $\{ v_{n1}, v_{n2}, i \}$



VECTOR OF SOURCES
DEPENDING ON THE
UNKNOWN i

$$\begin{bmatrix} \begin{bmatrix} G_1 & 0 \\ 0 & G_3 \end{bmatrix} & \begin{bmatrix} -1 \\ 1 \end{bmatrix} \\ \begin{bmatrix} -1 & 1 \end{bmatrix} & \begin{bmatrix} 0 \end{bmatrix} \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \\ i \end{bmatrix} = \begin{bmatrix} A \\ 0 \\ E \end{bmatrix}$$

ANALYSIS OF CIRCUITS WITH CONTROLLED SOURCES

- BY NODAL ANALYSIS OR MODIFIED NODAL ANALYSIS ONLY
- 2 STEPS
 - TREAT CONTROLLED SOURCES FORCING TERMS AS KNOWN: IMPLICIT MATRIX EQUATIONS
 - EXPRESS FORCING TERMS AS FUNCTIONS OF UNKNOWN VARIABLES: EXPLICIT EQUATIONS
- SYMMETRY PROPERTIES ARE LOST
- CURRENT SOURCES AFFECT THE MATRIX OF THE NA EQUATION ONLY

SAMPLE 1

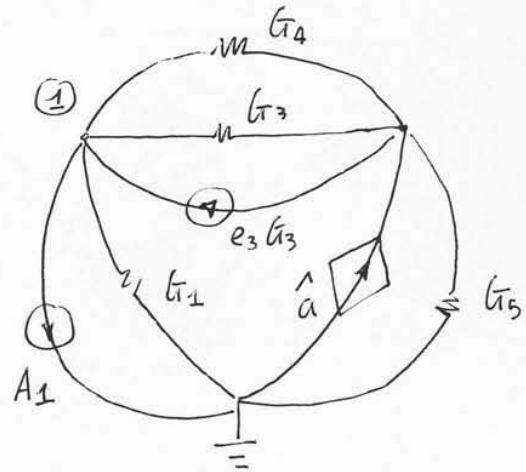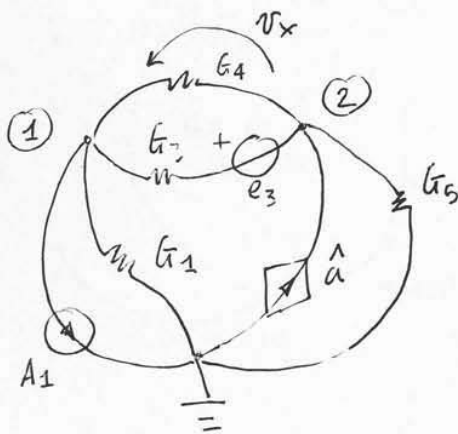

$$\begin{bmatrix} G_1 + G_3 + G_4 & -(G_3 + G_4) \\ -(G_3 + G_4) & G_4 + G_3 + G_5 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \begin{bmatrix} -a_1 + G_3 e_3 \\ -G_3 e_3 + \hat{a} \end{bmatrix}$$

$$v_x = v_{n1} - v_{n2} \Rightarrow \hat{a} = g_m (v_{n1} - v_{n2})$$

$$\begin{bmatrix} G_1 + G_3 + G_4 & -(G_3 + G_4) \\ -(G_3 + G_4) & G_4 + G_3 + G_5 \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix} = \begin{bmatrix} -a_1 + G_3 e_3 \\ -G_3 e_3 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ +g_m & -g_m \end{bmatrix} \begin{bmatrix} v_{n1} \\ v_{n2} \end{bmatrix}$$


$$\begin{bmatrix} 1/3 + 1/2 & -1/3 \\ -1/3 + 4/3 & 1/4 + 1/2 - 4/3 \end{bmatrix} \begin{bmatrix} \bar{v}_{n1} \\ \bar{v}_{n2} \end{bmatrix} = \begin{bmatrix} 9 \\ 0 \end{bmatrix} \quad \text{EXPLICIT EQUATION}$$

$$\underbrace{\begin{bmatrix} 5/6 & -1/3 \\ 1 & 5/4 \end{bmatrix}}_{\bar{G}_n} \begin{bmatrix} \bar{v}_{n1} \\ \bar{v}_{n2} \end{bmatrix} = \begin{bmatrix} 9 \\ 0 \end{bmatrix}$$


$$\begin{bmatrix} \bar{v}_{n1} \\ \bar{v}_{n2} \end{bmatrix} = \bar{G}_n^{-1} \begin{bmatrix} 9 \\ 0 \end{bmatrix}$$

STEP BACK TO THE ORIGINAL CIRCUIT


$$i = \frac{1}{2} (\bar{v}_{n1} - 12)$$

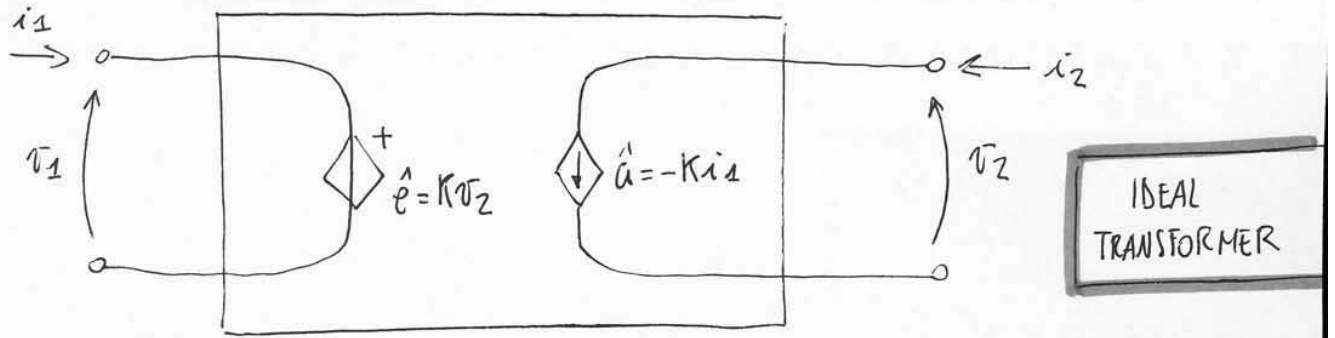

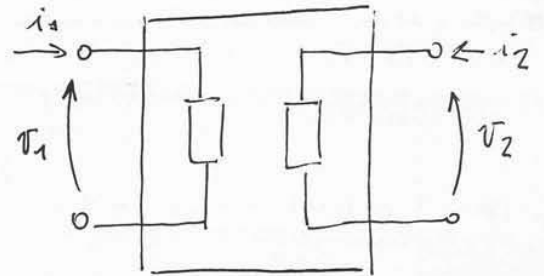
- AN INTRINSIC TWO PORT ELEMENT IS A 4-TERMINAL ELEMENT WITH AN INTERNAL STRUCTURE THAT GUARANTIE THE EXISTANCE OF PORT WURRENTS, E.G.



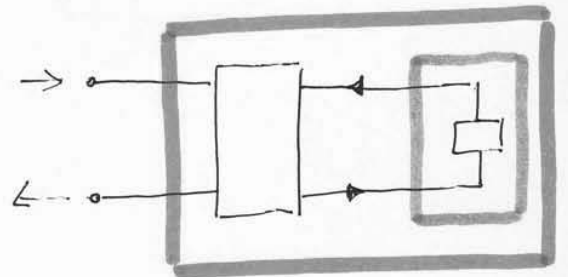- ANY FOUR-TERMINAL ELEMENT WITH TWO TERMINALS TERMINATED BY A TWO-TERMINAL ELEMENT OPERATES AS TWO PORT



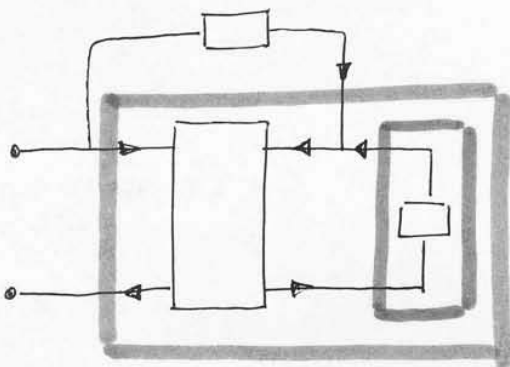
- DEFINES A WT-SET
CURRENT ENTERING = CURRENT EXITING
- DEFINES A WT-SET
CURRENT ENTERING = CURRENT EXITING



■ CURRENT ~~ENTER~~ ARE NOT THE SAME; NO LONGER GUARANTEE THEIR EQUIVALENCE

PROPERTY NO LONGER HOLD
2-TERMINAL NO LONGER FORMS A WT-SET

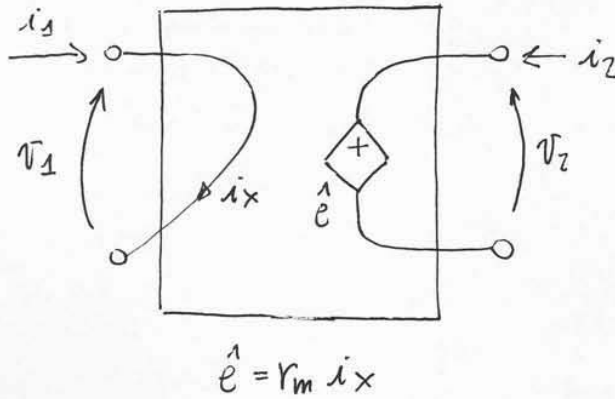CONTROLLED SOURCE : BASIC 2-PORT ELEMENTS



$v_1 = 0$ REGARDLESS CURRENT
 $v_2 = r_m i_1$ REGARDLESS i_2 SINCE ONE HAS A VOLTAGE SOURCE

$$\underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} v_1 \\ v_2 \end{bmatrix}} + \underbrace{\begin{bmatrix} 0 & 0 \\ -r_m & 0 \end{bmatrix}}_B \underbrace{\begin{bmatrix} i_1 \\ i_2 \end{bmatrix}} = \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_C$$

NEXT STEP: WRITE THE EXPLICIT CHARACTERISTIC

- 6 DIFFERENT POSSIBLE COMBINATIONS FOR 2-PORT ELEMENTS
- 2 DIFFERENT POSSIBLE COMBINATIONS FOR 1-PORT ELEMENT

$$A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + B \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = -C$$

CONDITION OF EXISTANCE: MATRIX INVERSION IS INVOLVED !

ONCE PROVIDED INVERSE OF MATRIX A EXISTS

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = -A^{-1} B \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + A^{-1} C$$

NOT SURPRISING RESULT: 2 PORT ELEMENT IS GENERALIZATION OF 1 PORT ELEMENT !

$$v = R \cdot i + v_0$$

NAMING

$$V = R i + V_0$$

↑ OPEN CIRCUIT MATRIX RESISTANCE


OPEN CIRCUIT VOLTAGE

$$i = G V + i_0$$


↑ SHORT CIRCUIT CONDUCTANCE MATRIX

SHORT CIRCUIT CURRENTS

SAMPLE 1

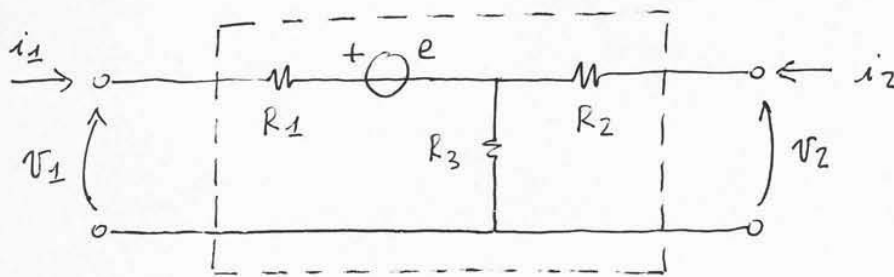

COMPUTE THEVENIN CHARACTERISTIC

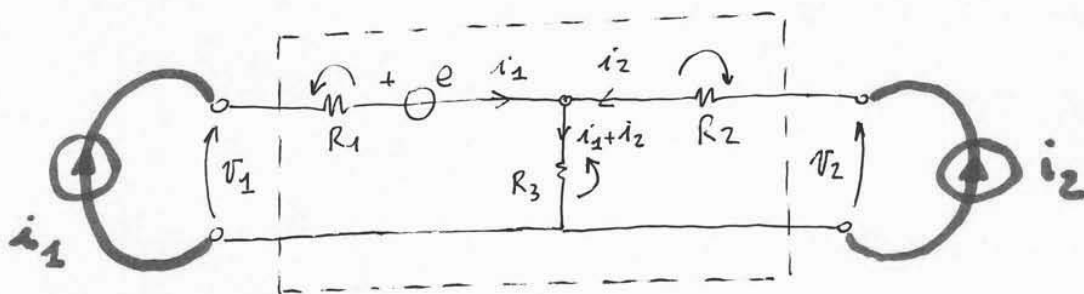


$$\begin{aligned} v_{R1} &= R_1 i_1 \\ v_{R3} &= R_3 (i_1 + i_2) \\ v_{R2} &= R_2 i_2 \end{aligned} \quad \begin{cases} v_1 = R_1 i_1 + e + R_3 (i_1 + i_2) \\ v_2 = R_2 i_2 + R_3 (i_1 + i_2) \end{cases}$$


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix}}_R \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \underbrace{\begin{bmatrix} e \\ 0 \end{bmatrix}}_{V_0}$$

EQUIVALENT CIRCUIT OF 2-PORT ELEMENTS

1-PORT ELEMENT

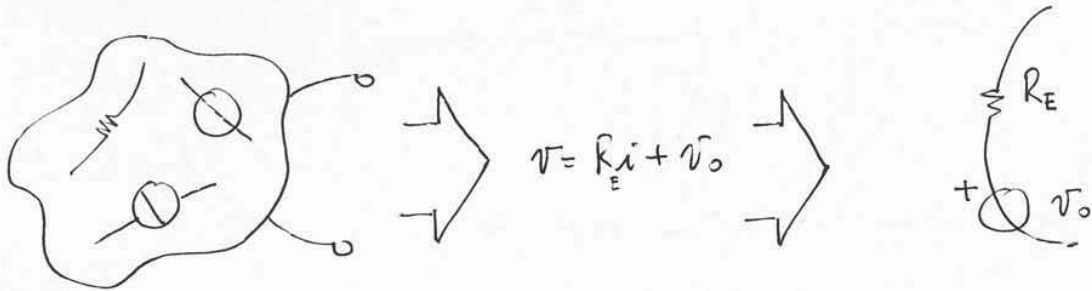

2-PORT ELEMENT

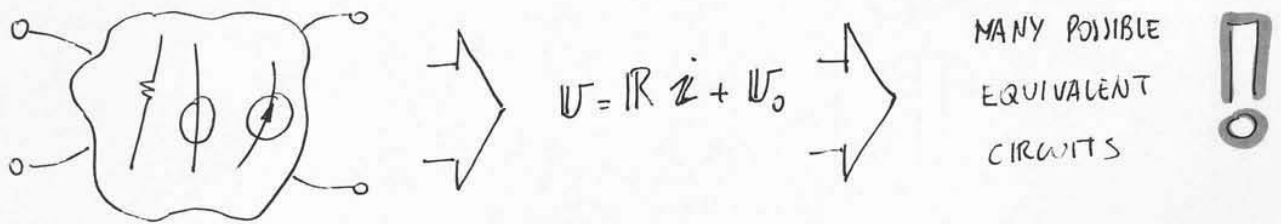


THEVENIN

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} v_{01} \\ v_{02} \end{bmatrix}$$

$$v_1 = \underbrace{R_{11} i_1}_{v_a} + \underbrace{R_{12} i_2}_{v_b} + \underbrace{v_{01}}_{v_c}$$

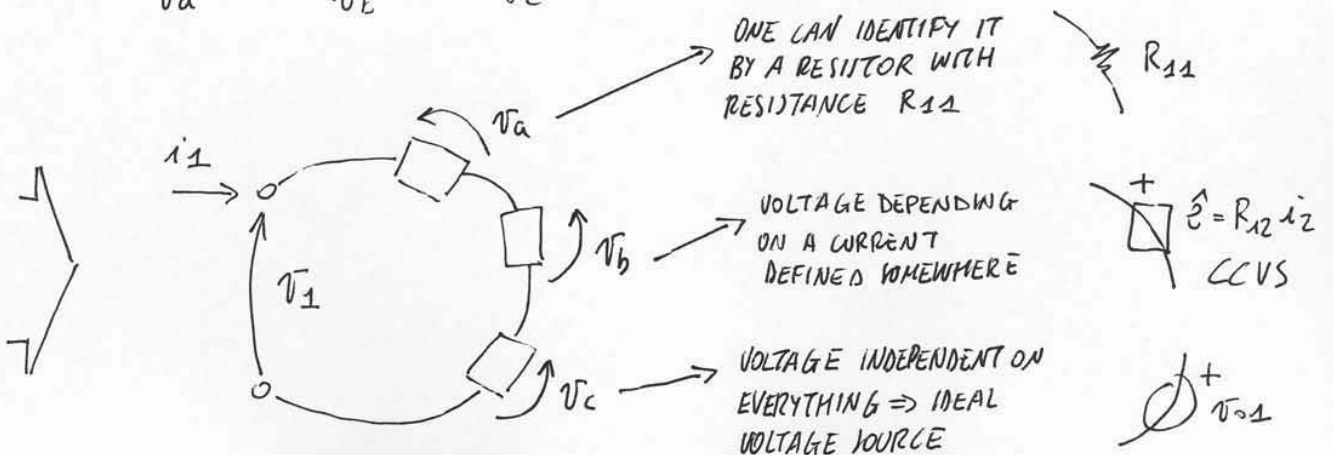3 VOLTAGE CONTRIBUTIONS SUMMED UP TO OBTAIN v_1



5 - FUNDAMENTALS OF DYNAMIC CIRCUITS

LET'S DEAL WITH LINEAR DYNAMIC CIRCUITS

DYNAMIC ELEMENT: ANY CIRCUIT ELEMENT DEFINED BY A CONSTITUTIVE RELATION WITH MEMORY; IT CHARACTERISTIC HAS A MEMORY AND ALSO THE PREVIOUS STEP OF VOLTAGE AND CURRENT ARE INVOLVED, NOT ONLY THE INSTANTANEOUS VALUES


3 ELEMENTAL DYNAMIC ELEMENTS TIME INVARIANT

- CAPACITOR
- INDUCTOR
- COUPLED INDUCTOR

DYNAMIC CIRCUIT: ANY CIRCUIT CONTAINING ONE OR MORE DYNAMIC ELEMENTS

DYNAMIC ELEMENTS

CAPACITOR (IDEAL)

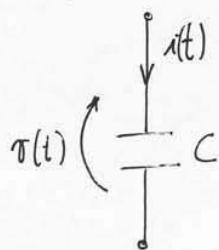


$$\begin{cases} q = C \cdot v(t) \\ i(t) = \frac{d}{dt} q(t) = C \frac{d}{dt} v(t) \end{cases}$$

EQUATION DESCRIBING BEHAVIOR OF CAPACITOR

← CAPACITANCE [Farad, F], $1F = 1C/V$

INDUCTOR (IDEAL)

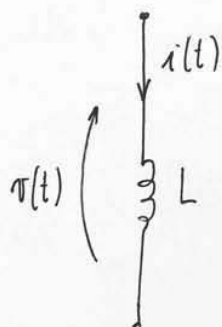


$$\begin{cases} \psi(t) = L i(t) \\ v(t) = \frac{d}{dt} \psi(t) = L \frac{d}{dt} i(t) \end{cases}$$

← MAGNETIC FLUX [Weber, W]

← INDUCTANCE [henry, H], $1H = 1Wb/A$



CONTINUITY OF CAPACITOR VOLTAGE

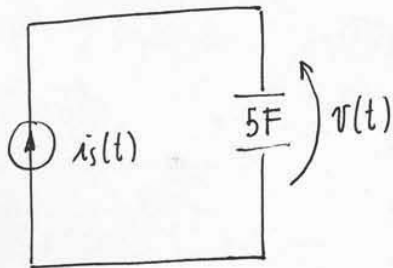FOR ANY CURRENT FUNCTION BOUNDED IN A CLOSED INTERVAL $[t_a, t_b]$
 THE CAPACITOR VOLTAGE IS A CONTINUOUS FUNCTION IN THE
 OPEN INTERVAL (t_a, t_b)



$$v(t) = \frac{1}{C} \int_{-\infty}^t i_s(t') dt'$$
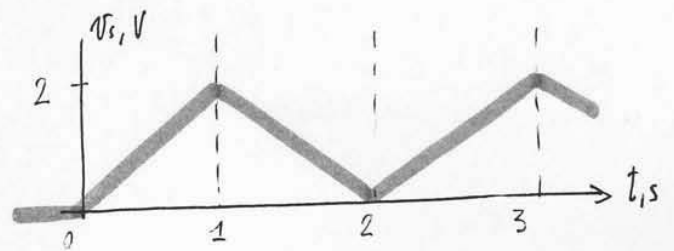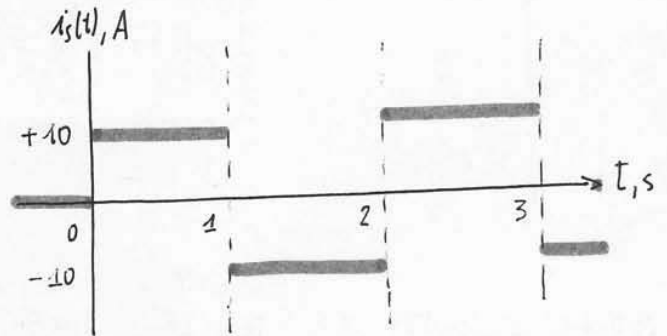
$$v(t) = \frac{1}{5} \int_{-\infty}^t i_s(t') dt'$$




LET'S CARRY OUT THE INTEGRATION GRAPHICALLY

$$v(t) = \begin{cases} 0 & t \leq 0 \\ 2t & 0 \leq t \leq 1 \\ -2t & 1 \leq t \leq 2 \end{cases}$$


linear function growing in time from 0

! DISCONTINUITY IN CURRENT FLOW BUT CONTINUITY IN VOLTAGE ACROSS THE CAPACITOR

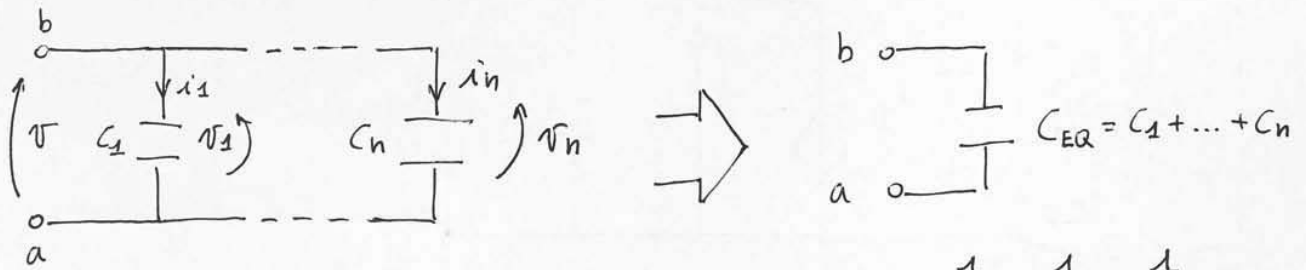SERIES AND PARALLEL CONNECTIONS OF CAPACITORS



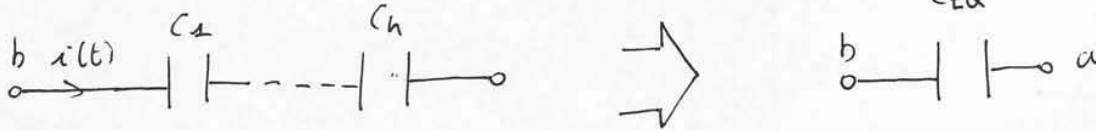
$$\frac{1}{C_{EQ}} = \frac{1}{C_1} + \frac{1}{C_n}$$




THE CAPACITANCE PARAMETER BEHAVES LIKE THE CONDUCTANCE PARAMETER
 THE INDUCTANCE PARAMETER BEHAVES LIKE THE RESISTANCE PARAMETER


SAMPLE 1

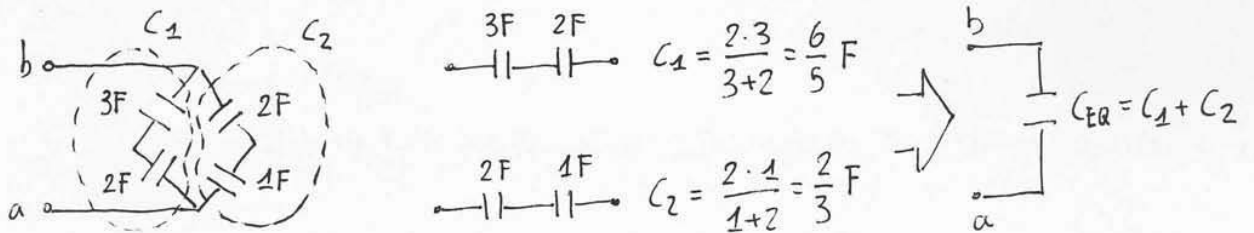

PROBLEM 1

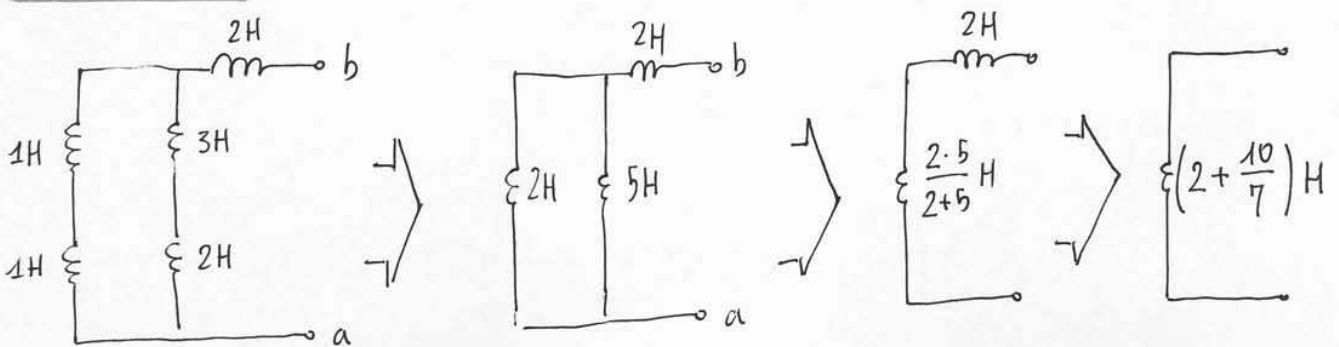

PROBLEM

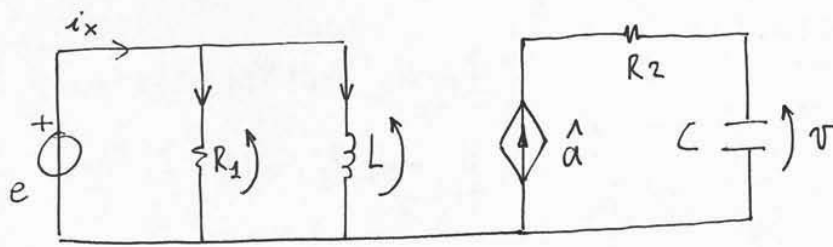

$$e = u(t) \text{ V}$$

$$\hat{a} = \beta i_x$$


$$i_x = G_1 e + \frac{1}{L} \int_{-\infty}^t e(t') dt'$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t \hat{a}(t') dt' = \frac{\beta}{C} \int_{-\infty}^t (G_1 e + \frac{1}{L} \int e) = \beta \frac{G_1}{C} \int_{-\infty}^t u(t') dt' + \beta \frac{1}{LC} \int_{-\infty}^t \int_{-\infty}^t u(t') dt' dt'$$

COUPLED INDUCTORS

COUPLED INDUCTORS ARE A MODEL FOR COUPLED WINDINGS (REAL TRANSFORMERS)

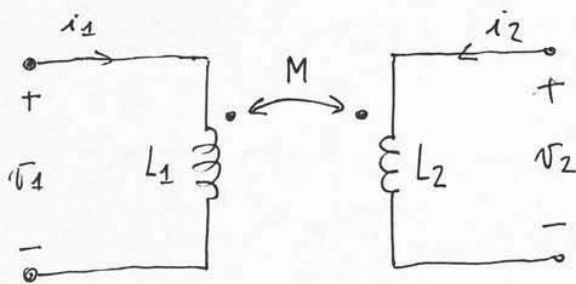COUPLED INDUCTORS ARE INTRINSIC 2-PORT ELEMENT



$$v_1(t) = L_1 \frac{d}{dt} i_1(t) + M \frac{d}{dt} i_2(t)$$

$$v_2(t) = M \frac{d}{dt} i_1(t) + L_2 \frac{d}{dt} i_2(t)$$

CONDITIONS: $L_1 > 0; L_2 > 0; M \leq \sqrt{L_1 L_2}$

M COUPLES THE TWO PORT; IT IS NAMED MUTUAL INDUCTANCE

$$\mathbb{L} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \text{ INDUCTANCE MATRIX}$$


USEFULL TO DEFINE IT USING COEFF. L_1, L_2, M IN THIS WAY

$$v(t) = \mathbb{L} \frac{d}{dt} \vec{i}(t)$$

VECTOR EQUIVALENT OF SCALAR EQUATION THAT HOLDS FOR 1 INDUCTOR (1 PORT ELEMENT)

$$v = L \frac{di}{dt}$$

LTI DYNAMIC CIRCUITS: ANALYSIS

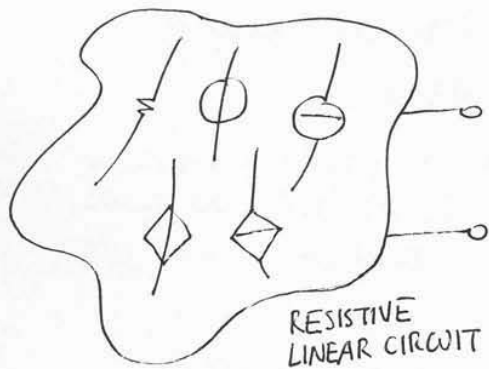

$$\sum a_k v_k = 0 \quad \text{KVL}$$

$$\sum \beta_k i_k = 0 \quad \text{KCL}$$

$$a_n v_k + b_n i_k + c_n = 0$$

SYSTEM OF LINEAR ALGEBRAIC EQUATIONS

IF THERE IS SOMETHING DYNAMIC LIKE A CAPACITOR



$$i = C \frac{dv}{dt}$$

LINEAR ALGEBRAIC EQUATIONS

⊕
DIFFERENTIAL EQUATIONS

DIFFERENTIAL ALGEBRAIC EQUATION

IMPORTANT TO DECIDE THE BEST METHOD TO SOLVE THE PROBLEM



MIXED SYSTEMS ARE DIFFICULT TO BE SOLVED: THE ISSUE IS THE SOLUTION OF DAE


LET'S DEFINE THE DIFFERENT CASES AND THE BEST METHODS FOR EACH ONE

- PROBLEM REDUCIBLE TO PURE ALGEBRAIC OR DECOUPLED DIFFERENTIAL EQUATIONS INVOLVING EITHER THE UNKNOWN OR THEIR DERIVATIVES/INTEGRALS ONLY

- ALGEBRAIC SOLUTION OR ALGEBRAIC + INTEGRATION/DIFFERENTIATION (SELDOM HAPPENS)

- REDUCIBLE TO A FIRST ORDER COMPLETE DIFFERENTIAL EQUATION (PARTICULARLY IMPORTANT CASE)

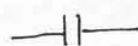- PARAMETRIC FORM OF THE SOLUTION: IT HAPPENS WHEN THE CIRCUIT HAS JUST 1 CAPACITOR OR 1 INDUCTOR OR THEIR EQUIVALENTS



USING THE PARAMETER τ

$$\frac{dv}{dt} + \frac{1}{\tau} v = \frac{1}{\tau} v_0(t)$$

THIS IS THE EQUATION TO BE SOLVED

TO SOLVE IT, ONE HAS TO \rightarrow INCLUDE INITIAL CONDITIONS I.C.

\hookrightarrow SPECIFY $v_0(t)$

$$v_0(t) = E m(t)$$


THE PROBLEM CAN BE SPLIT IN THIS WAY

$$\begin{cases} \frac{dv}{dt} + \frac{1}{\tau} v = \frac{1}{\tau} E & t > 0 \\ v(0^+) = v(0^-) \end{cases}$$

INITIAL CONDITION DESCRIBING THE PROBLEM; REMEMBER THAT VOLTAGE ACROSS CAPACITOR IS A CONTINUOUS FUNCTION

FOR $t < 0$ VOLTAGE APPLIED BY THE VOLTAGE SOURCE IS 0 \Rightarrow SHORT CIRCUIT

LET'S REPRESENT THE CIRCUIT

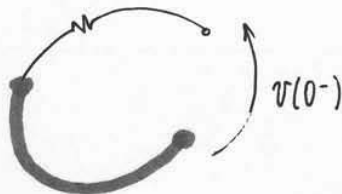

CAPACITOR IS IN STEADY STATE CONDITIONS \Rightarrow OPEN CIRCUIT

RESISTOR CONNECTED TO OPEN CIRCUIT \Rightarrow NO CURRENT IS FLOWING

\Rightarrow VOLTAGE ACROSS THE RESISTOR IS 0 $\Rightarrow v(0^-) = 0$



THE SOLUTION OF THE PROBLEM IS

$$v(t) = \begin{cases} 0 & t \leq 0 \\ -E e^{-t/\tau} + E & t \geq 0 \end{cases}$$

ONCE ONE HAS THIS SOLUTION, HE DOES NOT NEED TO WRITE ANYMORE THE DIFFERENTIAL EQUATION


IN MORE COMPACT FORM $v(t) = -E m(t) e^{-t/\tau} + E m(t)$

STEP RESPONSE FROM NON ZERO I.C.

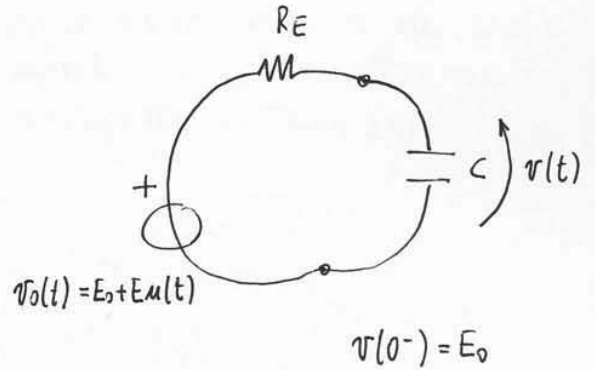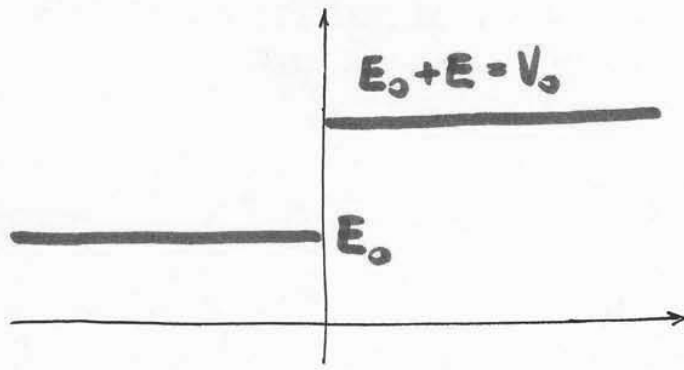

ONE CAN SPLIT THE SOURCE AS DEPICTED BELOW; IN THIS CASE, SUPERPOSITION THEOREM HOLDS \Rightarrow ONE IS GOING TO CONSIDER 2 DIFFERENT PROBLEMS

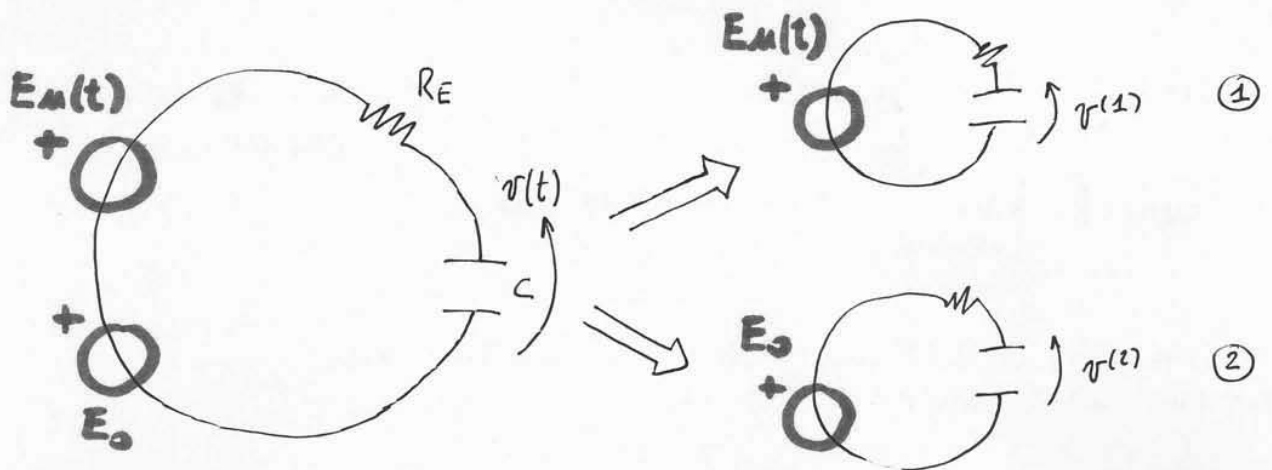THE VOLTAGE ACROSS THE CAPACITOR WILL BE THE SUM OF THE VOLTAGES COMPUTED IN THE 2 PROBLEMS !!



LET'S CONSIDER PROBLEM (1) : ZERO-STATE RESPONSE COMPUTED BEFORE $v^{(1)} = -E e^{-t/\tau} + E \quad t \geq 0$

LET'S CONSIDER PROBLEM (2) : SOURCE HAS NO DISCONTINUITY : AT A FIXED TIME, ONE IS LOOKING FOR THE FINAL VALUE AND IT IS E_0




$\Rightarrow v^{(2)} = E_0$

$\Rightarrow v(t) = -E e^{-t/\tau} + E + E_0 = -E e^{-t/\tau} + V_0$

!! ONCE IS KNOWN $v(0^-)$ AND TIME CONSTANT PART ONE DOES NOT NEED TO WRITE DIFF. EQUATION




SINCE $E = V_0 - E_0 \Rightarrow v(t) = (E_0 - V_0) e^{-t/\tau} + V_0 \quad t \geq 0$

SAMPLE 1 COMPUTE & PLOT $v_c(t)$

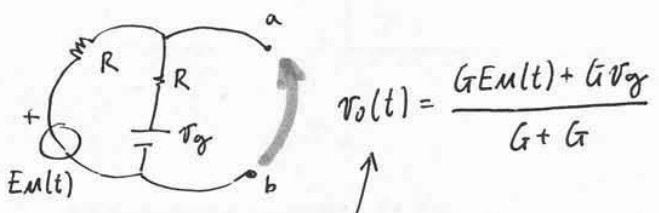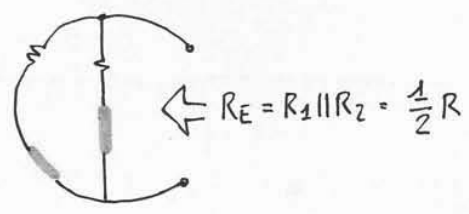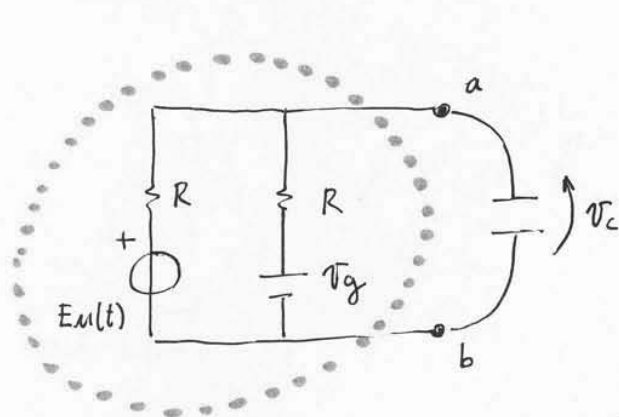

SINCE ONE IS LOOKING FOR v_c , HE IS NOT FREE TO DEFINE THIS ONE.

LET'S FOCUS THE ATTENTION ON THE PROBLEM

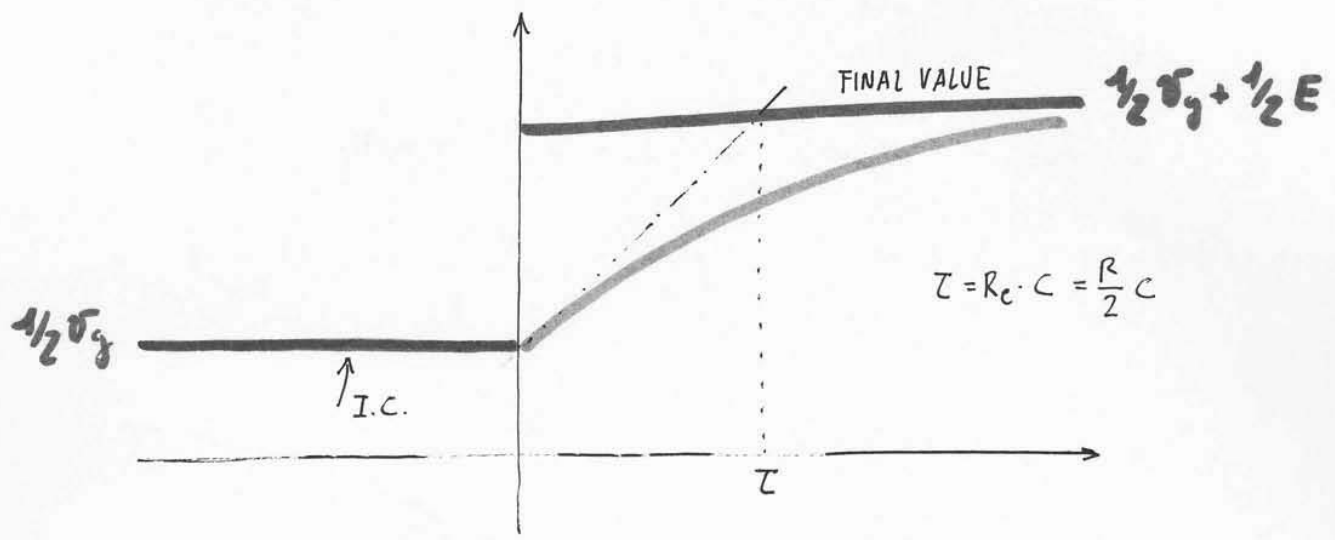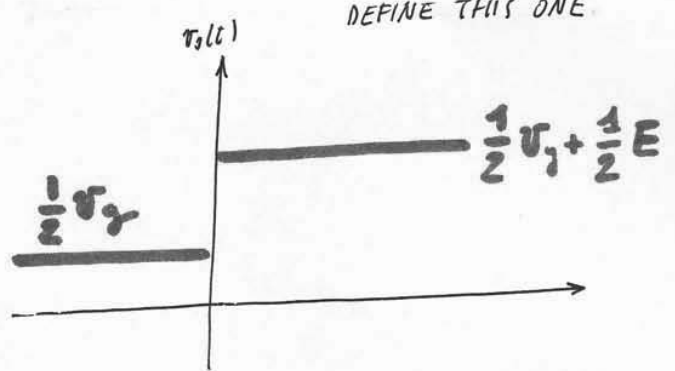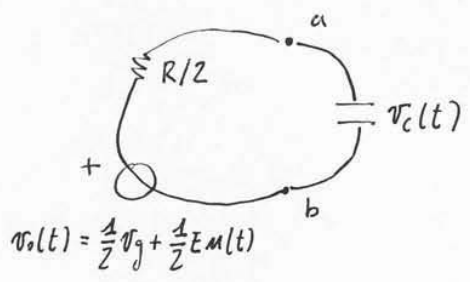

$$v(t) = \begin{cases} \left(\frac{1}{2} v_g - \frac{1}{2} v_g \right) e^{-(t-\infty)/\tau} + \frac{1}{2} v_g = \frac{1}{2} v_g & t < 0 \\ \left[\frac{1}{2} v_g - \left(\frac{1}{2} v_g + \frac{1}{2} E \right) \right] e^{-(t-0)/\tau} + \left(\frac{1}{2} v_g + \frac{1}{2} E \right) & t \geq 0 \end{cases}$$

FINAL VALUE

PROBLEM 2



COMPUTE AND PLOT $v_c(t)$

$a = 2 [u(t) - u(t-T)]$ A


$T > 0$


$v_c(-1) = V_0$

SERIES EQUIVALENT DOES NOT EXIST

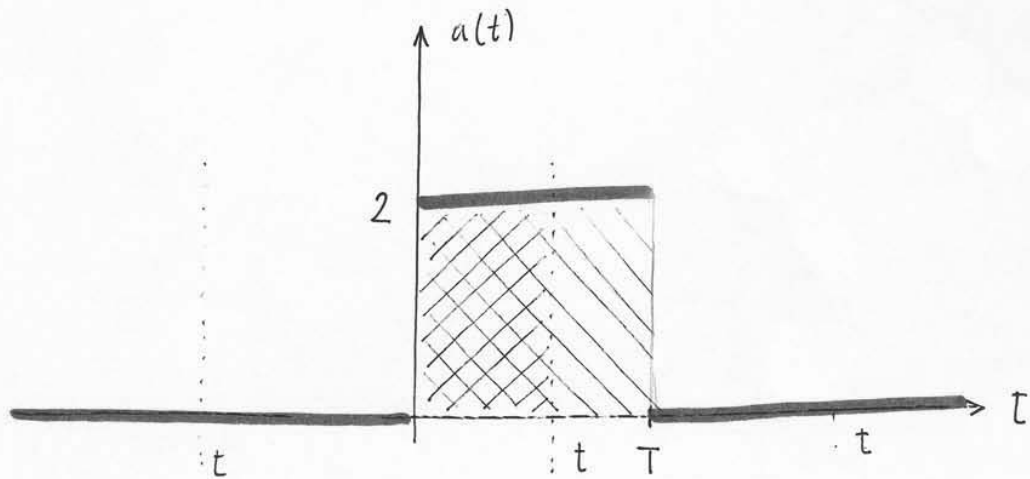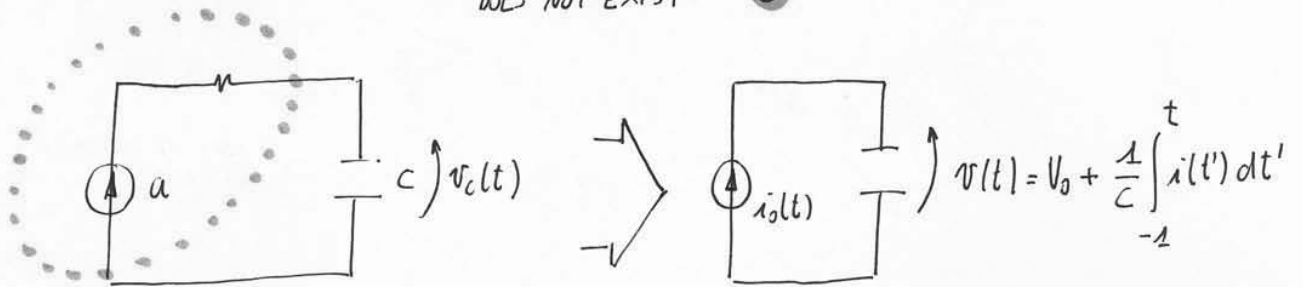
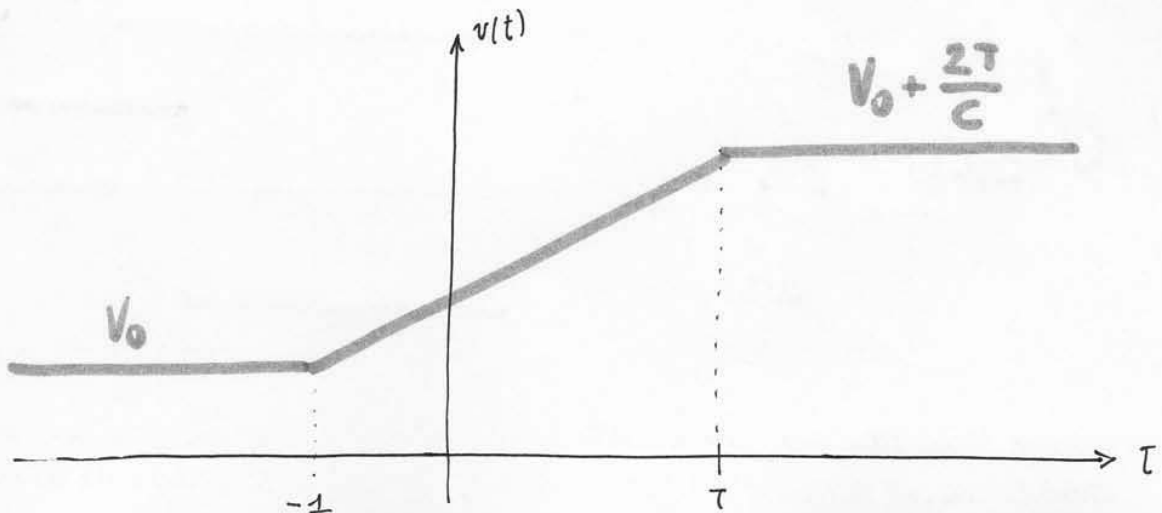
$$v(t) = V_0 + \frac{1}{C} \int_{-1}^t a(t') dt' = \begin{cases} V_0 & -1 < t < 0 \\ V_0 + \frac{2}{C} t & 0 \leq t \leq T \\ V_0 + \frac{2}{C} T & t \geq T \end{cases}$$



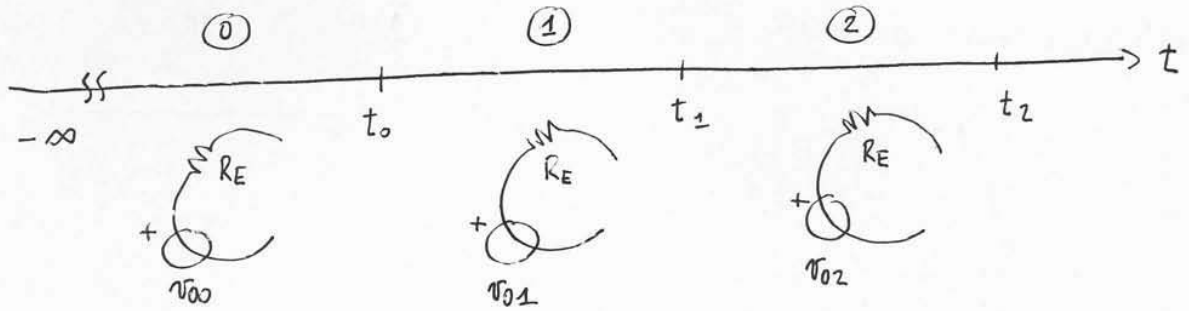

$$v(t) = v_{00}$$

$$v_1(t) = (v_{00} - v_{01}) e^{-\frac{(t-t_0)}{\tau}} + v_{01} \quad t_0 \leq t \leq t_1$$

$$v_2(t) = (v_1(t_1) - v_{02}) e^{-(t-t_1)/\tau} + v_{02}$$





DEPENDING ON THE LENGTH OF INTERVAL AND ON THE VALUE OF τ , THE FUNCTION CAN REACH OR NOT THE FINAL VALUE

FIRST ORDER DYNAMIC CIRCUIT, RECIPE




- 1) PLOT SOURCE WAVEFORMS AND WBDIVIDE TIME AXIS IN INTERVALS WHERE SOURCES ARE CONSTANT
- 2) FOR EACH TIME INTERVAL, BUILD THE SERIES/PARALLEL EQUIVALENT OF THE RESISTIVE COMPOSITE ELEMENT DRIVING THE CAPACITOR/INDUCTOR
- 3) FOR EACH TIME INTERVAL, WRITE THE SOLUTION USING THE PARAMETERS OF THE EQUIVALENT OF THE INTERVAL

PROBLEM

COMPUTE AND PLOT $v_c(t)$

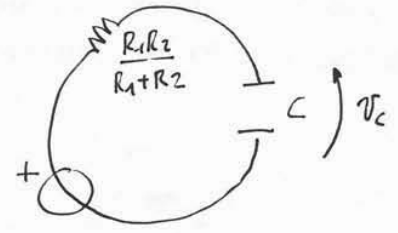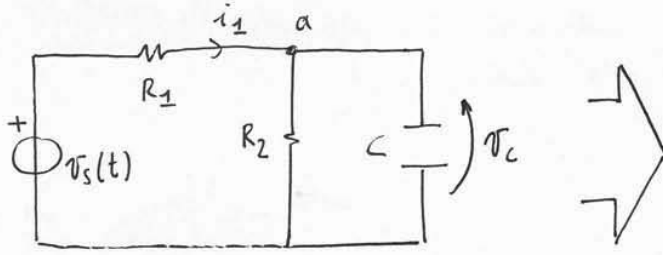
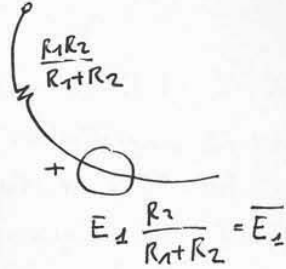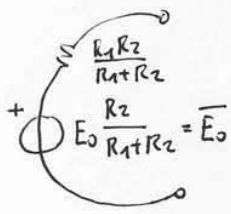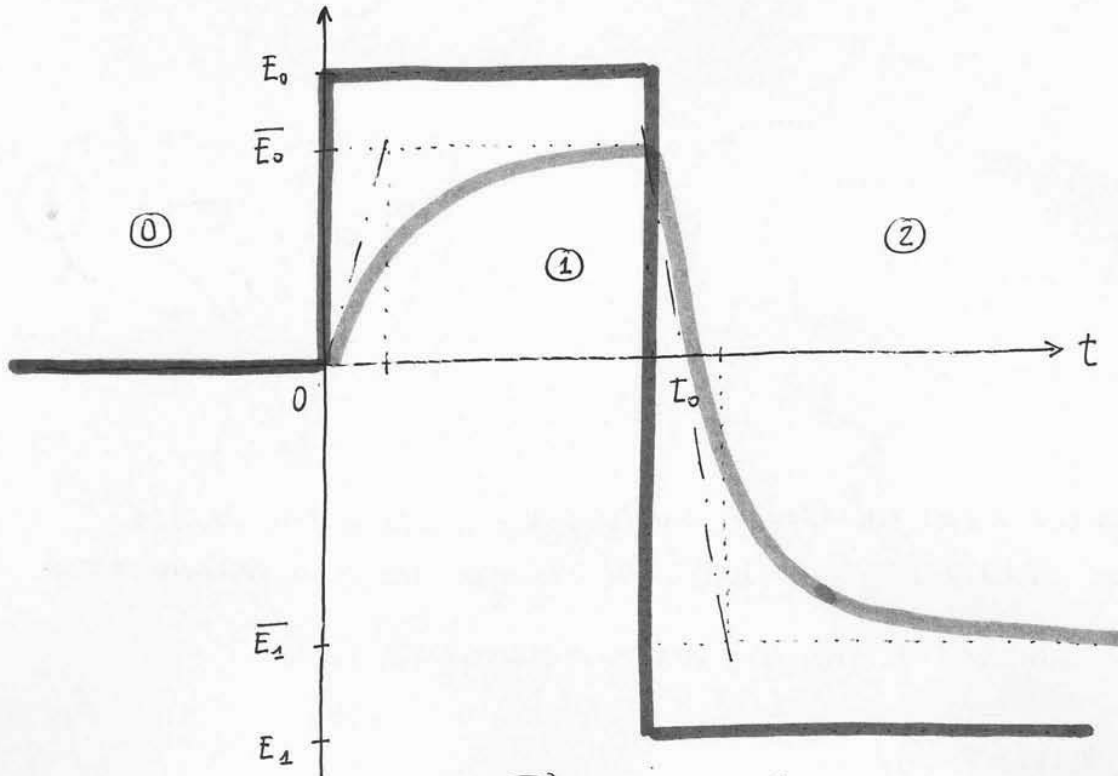
$$\frac{G_1 v_s}{G_1 + G_2} = v_s \frac{R_2}{R_1 + R_2}$$



① $v_{c0} = 0$


① $v_{c1} = \left(0 - E_0 \frac{R_2}{R_1 + R_2} \right) e^{-\frac{(t-t_0)}{\tau}} + E_0 \frac{R_2}{R_1 + R_2}$

② $v_{c2} = \left(v_{c1}(t=t_0) - E_1 \frac{R_2}{R_1 + R_2} \right) e^{-\frac{(t-t_0)}{\tau}} + E_1 \frac{R_2}{R_1 + R_2}$

$\tau = R_E \cdot C$

let's suppose $\tau = \frac{1}{5} t_0$

IDEAL SWITCHES

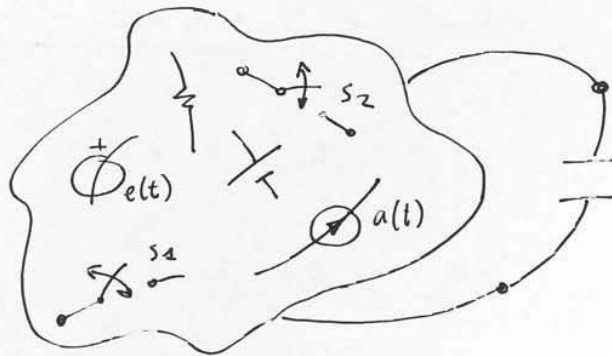


EVERYTHING AS BEFORE
 SAME CONSIDERATIONS
 SAME PROCEDURES



ONE THING TO BE UPDATED: ONE HAS TO DIVIDE TIME AXIS
 INTO INTERVALS WITH \rightarrow CONSTANT SOURCE VALUE
 \hookrightarrow CONSTANT SWITCH STATE

ONE MINOR DIFFERENCE: WHEN SWITCH CHANGES ITS STATE,
 ALSO TOPOLOGY OF DRIVING ELEMENT CHANGES; CONSEQUENTLY,
 ALSO EQUIVALENT RESISTANCE CAN CHANGE

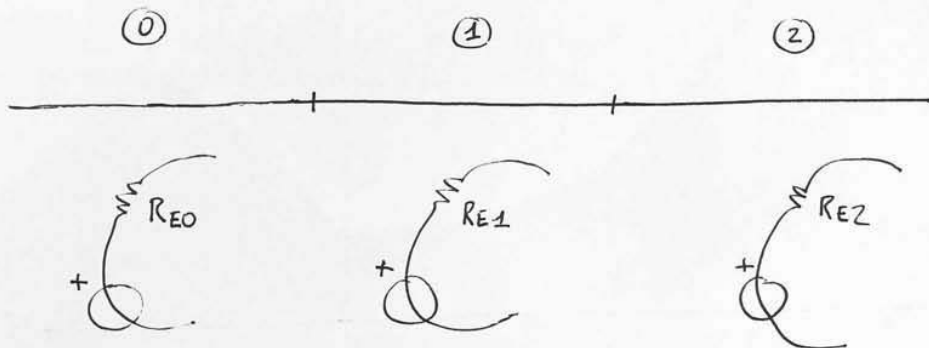TIME CONSTANT IS DEFINED FOR EACH TIME INTERVAL; NO
 LONGER CONSTANT VALUE; R_E CHANGES $\Rightarrow \tau$ CHANGES



SOLUTION HAS THE SAME FORM AS BEFORE

6- GENERAL DYNAMIC CIRCUITS

SINGLE SIDED LAPLACE TRANSFORM


ARBITRARY # OF CAPACITOR & INDUCTORS

INTEGRAL LINEAR TRANSFORMATION

$$F(s) = \mathcal{L}[f(t)] = \int_{0^-}^{\infty} f(t) e^{-st} dt$$


$$s = \sigma + j\omega$$

↑
COMPLEX NUMBER: COMPLEX FREQUENCY

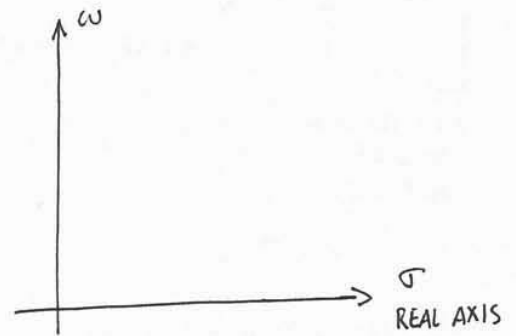

COMPLEX VARIABLE \Rightarrow COMPLEX RESULTS

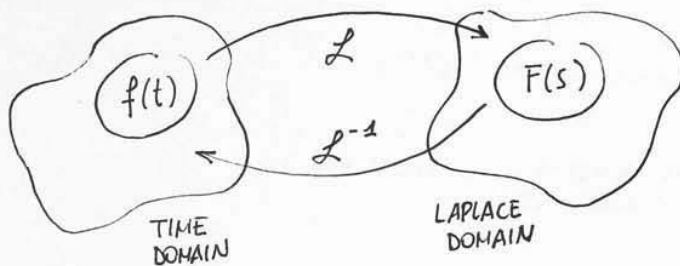WHEN THE INTEGRAL IS DEFINED, 1 TO 1 CORRESPONDENCE
THE ELEMENTS ARE PAIRED



! SINGLE SIDED BECAUSE THE
INTEGRAL IS DEFINED $[0, +\infty)$
 0^- INCLUDED TO ALLOW
FUNCTION TO WORK PROPERLY
WITH THE TRANSFORMATION OF dt
 $0^- = 0 - \epsilon$

$\{f(t), F(s)\} =$ LAPLACE TRANSFORM PAIR

↑
LOWER CASE LETTER
FUNCTION OF TIME

↑
UPPER CASE
FUNCTION OF FREQUENCY

KEY PROPERTY

$$\mathcal{L}[f(t)] = F(s) \quad \text{TRANSFER OF THE FUNCTION}$$

! DIFFERENTIAL OPERATOR
IN TIME DOMAIN
BECOMES LINEAR ALGEBRAIC
IN FREQUENCY DOMAIN

$$\mathcal{L}\left[\frac{d}{dt} f(t)\right] = sF(s) - f(0^-) \quad \text{SIMPLY LINEAR ALGEBRAIC EQUATION}$$

REAL RATIONAL FUNCTIONS

- RATIO OF POLYNOMIALS

- $a_m, b_n \dots$ ARE REAL COEFFICIENTS

$$F(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0}$$

$n > m$
 $\{a_m, b_n\}$ Real

$$F(s) = \frac{N(s)}{D(s)} \leftarrow \begin{array}{l} \text{REPRESENTING THE POLYNOMIAL ON NUMERATOR} \\ \text{REPRESENTING THE POLYNOMIAL ON DENOMINATOR} \end{array}$$

IF $n < m$, NUMERATOR CAN BE DIVIDED BY DENOMINATOR AND THE FUNCTION CAN BE WRITTEN IN THIS WAY

$$F(s) = \sum_k C_k s^k + G(s) \leftarrow \begin{array}{l} \text{REAL RATIONAL FUNCTION} \\ \text{PROPER FUNCTION} \end{array}$$


↑
RESULT OF DIVISION

ROOTS OF POLYNOMIALS : n -ROOTS IN COMPLEX PLANE FOR BOTH NUMERATOR AND DENOMINATOR

ROOTS OF POLYNOMIALS WITH REAL COEFFICIENTS CAN BE REAL OR IN PAIR COMPLEX CONJUGATES

THE ZEROS OF $N(s)$ ARE ALSO ZEROS OF THE FUNCTION

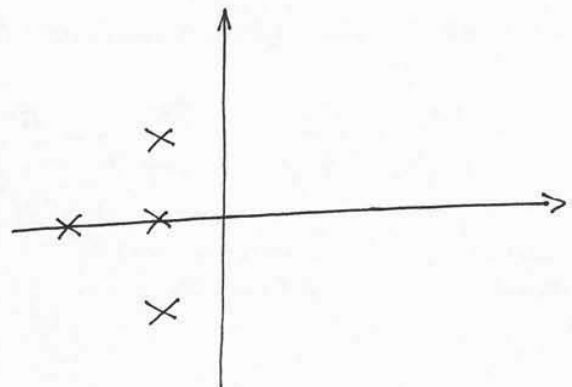THE ZEROS OF $N(s) \Rightarrow$ ZEROS OF FUNCTION NAMED ZEROS



THE ZEROS OF $D(s) \Rightarrow$ POINTS OF COMPLEX PLANE WHERE FUNCTION

DIVERGES, GOES TO INFINITY; THEY ARE NAMED POLES

↑
AT EVERY ZERO OF $D(s)$, ONE HAS SINGULARITY OF $F(s)$

THE 2 CONTRIBUTION ARE LUMPED IN SINGLE CONTRIBUTION OF THIS FORM

$$\frac{K_3}{s-p_3} + \frac{K_3^*}{s-p_3^*} \Rightarrow \frac{K_{31}s + K_{30}}{(s-\sigma_3)^2 + \omega_3^2}$$

DIMOSTRABILE COME DIFFERENZA DI QUADRATI

ONE KEEPS CONTIGUOUS TOGETHER \Rightarrow THIS PRODUCT IS REAL

TO COMPUTE THE COEFFICIENT OF THE RESIDUES \Rightarrow MANY TECHNIQUES


THE SIMPLEST ONE IS TO EQUATE $\frac{K}{s-p_1} = \frac{K_{21}}{s-p_2}$

ONE UTILITY CAN BE FOUND ON www.quickmath.com

THE LAPLACE METHOD (EAVISIDE ~ 1900)

SOLUTION PROCEDURE

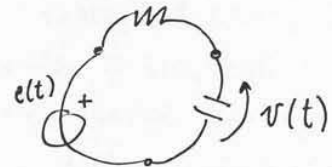
SUPPOSE THIS IS THE GIVEN PROBLEM: ONE DOES NOT NEED TO WRITE EQUATIONS IN TIME DOMAIN



(1) TRANSFORMED CIRCUIT

REPLACE ORIGINAL CIRCUIT WITH THE TRANSFORMED ONE; IN TRANSFORMED CIRCUIT, EVERY ELEMENT HAS ALGEBRAIC CHARACTERISTIC

\Rightarrow PLANE LINEAR ALGEBRAIC

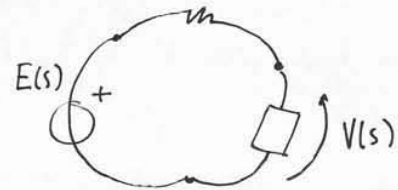

(2) ANALYSIS $V(s) = \dots$

ANY METHOD FOR LINEAR RESISTIVE CIRCUIT (OF COURSE, THE MOST CONVENIENT FOR THE PROBLEM ONE HAS)

(3) INVERSE TRANSFORMATION OF SOLUTIONS

$$\mathcal{L}^{-1}[V(s)] = v(t)$$