



Corso Luigi Einaudi, 55 - Torino

Appunti universitari

Tesi di laurea

Cartoleria e cancelleria

Stampa file e fotocopie

Print on demand

Rilegature

NUMERO: 1493A -

ANNO: 2015

A P P U N T I

STUDENTE: Beccaria

MATERIA: Guiding Electromagnetic System + temi + Eserc.
Prof. Pirinoli

Il presente lavoro nasce dall'impegno dell'autore ed è distribuito in accordo con il Centro Appunti.

Tutti i diritti sono riservati. È vietata qualsiasi riproduzione, copia totale o parziale, dei contenuti inseriti nel presente volume, ivi inclusa la memorizzazione, rielaborazione, diffusione o distribuzione dei contenuti stessi mediante qualunque supporto magnetico o cartaceo, piattaforma tecnologica o rete telematica, senza previa autorizzazione scritta dell'autore.

**ATTENZIONE: QUESTI APPUNTI SONO FATTI DA STUDENTIE NON SONO STATI VISIONATI DAL DOCENTE.
IL NOME DEL PROFESSORE, SERVE SOLO PER IDENTIFICARE IL CORSO.**


Assignment N°1

BECCARIA MICHELE (Kwdll n° 209013)

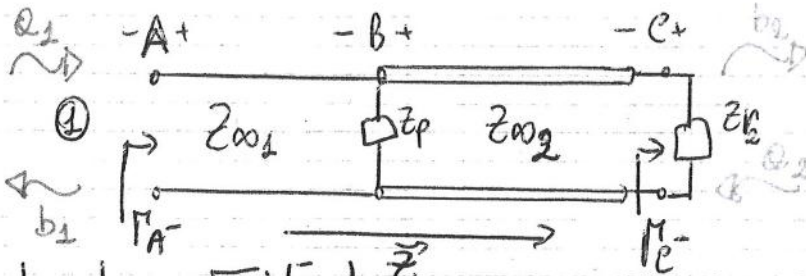Problem N°1

1st sheet

To compute S_{11} parameter I have to use this circuit:



$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \left. \frac{\sqrt{Z_0} V_{A^-}}{\sqrt{Z_0} V_{A^+}} \right|_{V_{C^+}=0} = \Gamma_{A^-}$$

To find Γ_{A^-} I started from C:

$$\Gamma_{C^-} = \frac{Z_{L2} - Z_{02}}{Z_{L2} + Z_{02}} = 0 \quad \text{matched condition}$$

So I have that:

$$\Gamma_{B^+} = \Gamma_{C^-} e^{-52klbe} = 0 \quad \implies Z_{B^+} = 60 \Omega$$

$$Z_{B^-} = Z_{B^+} \parallel Z_p = \frac{(60 \cdot 60) \Omega^2}{(60 + 60) \Omega} = 30 \Omega$$

Now I compute Γ_{B^-}

$$\Gamma_{B^-} = \frac{Z_{B^-} - Z_{01}}{Z_{B^-} + Z_{01}} = 0$$


Again I have that:

$$\Gamma_{A^+} = \Gamma_{B^-} = 0 \quad \text{This implies} \quad \implies Z_{A^+} = 30 \Omega$$

Finally I compute Γ_{A^-}

$$\Gamma_{A^-} = \frac{Z_{A^+} - Z_{01}}{Z_{A^+} + Z_{01}} = 0$$

So I found that $S_{11} = 0$

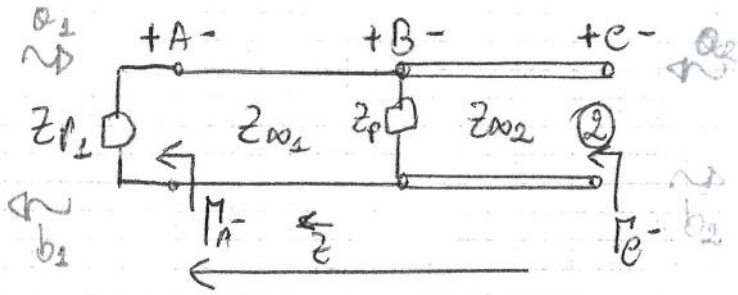

Starting to compute S_{22} :

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \left. \frac{V_e^- / \sqrt{Z_{r2}}}{V_c^+ / \sqrt{Z_{r2}}} \right|_{V_{A^+}=0} = \Gamma_e^-$$

As for the previous calculus I will have:

$$\Gamma_{A^-} = \frac{Z_{r1} - Z_{\infty 1}}{Z_{r1} + Z_{\infty 1}} = 0$$

$$\Gamma_{B^+} = \Gamma_{A^-} e^{-j2kl_{AB}} = 0 \implies Z_{B^+} = 30 \Omega$$

$$Z_{B^-} = Z_{B^+} \parallel Z_p = \frac{(30 \cdot 60) \Omega^2}{(30+60) \Omega} = 20 \Omega$$

$$\Gamma_{B^-} = \frac{Z_{B^-} - Z_{\infty 2}}{Z_{B^-} + Z_{\infty 2}} = -0,5$$

$$\Gamma_{e^+} = \Gamma_{B^-} e^{-j2kl_{Be}} = -0,5 e^{-j2k \frac{\pi}{8} \cdot \frac{3}{8} \lambda} = -0,5 j$$

$$Z_{e^+} = Z_{\infty 2} \cdot \frac{1 + \Gamma_{e^+}}{1 - \Gamma_{e^+}} = \cancel{20 \Omega} (36 - j48) \Omega$$

$$\Gamma_{e^-} = \frac{Z_{e^+} - Z_{r2}}{Z_{e^+} + Z_{r2}} = -j0,5$$

$$S_{22} = -j0,5 = -0,5 e^{-j270^\circ}$$


Because this circuit is made only with passive components the circuit is reciprocal, so $S_{21} = S_{12}$ but to demonstrate it I will compute however S_{12}

BECCARIA Michele 209013 Assignment N°1

2nd sheet

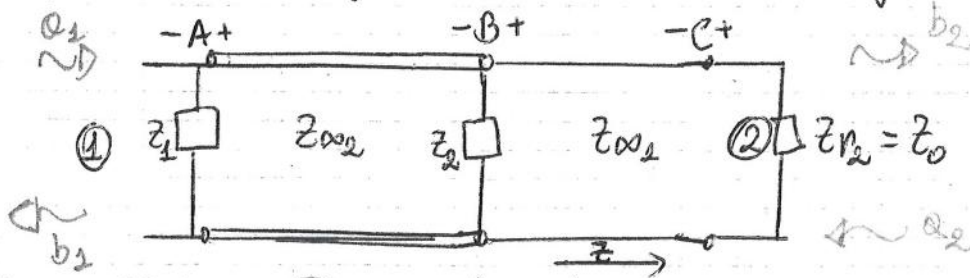Problem N°2

I transformed the given circuit in the following one:



(For the notation the reader has to see the complete circuit only to understand how I computed z_1 and z_2)

• z_1

Because we have an open circuit $\Gamma_D = 1$

$$\Gamma_{AD} = \Gamma_D e^{-j\beta k l_{AD}} = 1 \cdot e^{-j \frac{\pi}{2} \cdot \frac{5}{8} \lambda} = -j$$

$$z_{AD} = z_1 = z_{\infty 3} \cdot \frac{1 + \Gamma_{AD}}{1 - \Gamma_{AD}} = -j \frac{z_0}{2}$$

• z_2

$$\Gamma_E = \frac{z_E - z_{\infty 1}}{z_E + z_{\infty 1}} = \frac{j z_{\infty 1} - z_{\infty 1}}{j z_{\infty 1} + z_{\infty 1}} = \frac{j-1}{j+1} = j$$

~~$$\Gamma_{BE} = \frac{z_{BE} - z_{\infty 2}}{z_{BE} + z_{\infty 2}} = 1$$~~

$$\Gamma_{BE} = \Gamma_E e^{-j\beta k l_{BE}} = 1$$

$$z_{BE} = z_{\infty 2} \cdot \frac{1 + \Gamma_{BE}}{1 - \Gamma_{BE}} = \infty \Rightarrow Y_{BE} = 0 \Rightarrow z_2 = \infty, Y_2 = 0$$

Now I can compute S_{11}

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \left. \frac{V_{A^-} / \sqrt{Z_{\infty 2}}}{V_{A^-} / \sqrt{Z_{\infty 1}}} \right|_{V_{C^+}=0} = \Gamma_{A^-}$$

$$= V_{A^+}^+ \frac{(1 + \Gamma_{B^-})}{(1 + \Gamma_{B^+})} (1 + \Gamma_{e^-}) e^{-\gamma K(l_{AB} + l_{BC})} =$$

$$= \frac{V_{A^+}^+}{1 + \Gamma_{A^+}^+} \frac{(1 + \Gamma_{B^-})}{(1 + \Gamma_{B^+})} (1 + \Gamma_{e^-}) e^{-\gamma K(l_{AB} + l_{BC})} =$$

$$= V_{A^-}^+ \frac{(1 + \Gamma_{A^-})}{(1 + \Gamma_{A^+})} \frac{(1 + \Gamma_{B^-})}{(1 + \Gamma_{B^+})} (1 + \Gamma_{e^-}) e^{-\gamma K(l_{AB} + l_{BC})}$$

So we have:

$$S_{21} = \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{(1 + \Gamma_{A^-})}{(1 + \Gamma_{A^+})} \frac{(1 + \Gamma_{B^-})}{(1 + \Gamma_{B^+})} (1 + \Gamma_{e^-}) e^{-\gamma \frac{8\pi}{\lambda} \left(\frac{5}{\sqrt{2}} x\right)}$$

$$= \downarrow 1 \cdot \frac{(1 + 0,9 e^{-j127^\circ})}{1 + \frac{11}{13}} \cdot \frac{1 + \frac{11}{13}}{1 + \frac{1}{3}} \left(1 - \frac{1}{3}\right) \cdot e^{-\gamma \frac{5}{2} \pi}$$

$$= -0,36 - j0,22 = 0,42 e^{-j148^\circ}$$

$$S_{11} = 0,9 e^{-j127^\circ}$$


$$S_{21} = 0,42 e^{-j148^\circ}$$

BECCARIA MICHELE 209013

3rd sheet

... continue Problem 3

To find P_A I consider this circuit

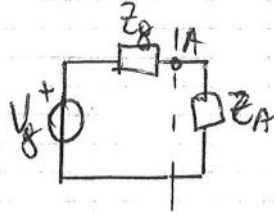

Where Z_A is:


$$Z_A = Z_{A1} \cdot \frac{1 + \Gamma_A^+}{1 - \Gamma_A^-} = Z_0 \cdot \frac{1 + 0,25}{1 - 0,25} = 1,67 Z_0$$

$$P_A = \frac{1}{2} \operatorname{Re}\{Z_A\} |I_A|^2 = \frac{1}{2} \operatorname{Re}\{Z_A\} \cdot \left| \frac{V_g}{(Z_A + Z_g)} \right|^2 = \frac{1}{2} \cdot 1,67 Z_0 \cdot \frac{100 V^2}{4,708 Z_0} =$$

$$= \frac{17,73}{Z_0} V^2$$

$$P_e = P_A \cdot 0,68 = \frac{12,09}{Z_0} V^2$$

Problem 4

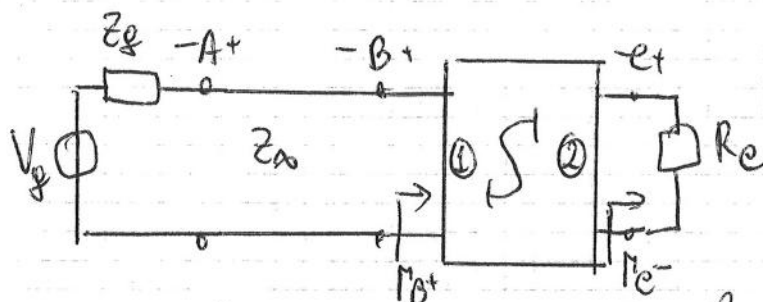

To compute the maximum power in the load R_e taking into account the maximum reflected power that the generator can withstand I'll do this:
Considering that

$$\frac{P_e}{P_B = P_A} = \frac{|S_{22}|^2}{|1 - S_{22} \Gamma_e|^2} \cdot \frac{(1 - |\Gamma_e|^2)}{(1 - |\Gamma_B^+|^2)}$$

BECCARIA MICHELE
ENROLL NUMBER 209013

ASSIGNMENT N° 2

Problem n° 4

To design a Low Pass filter with maximally flat response we use Butterworth filter. We start to find the prototype filter:


$$\Omega = \frac{\omega}{\omega_c} = \frac{2\pi \cdot 3,75 \text{ GHz}}{2\pi \cdot 2,5 \text{ GHz}} = 1,5$$

$$|\Omega| - 1 = 0,5$$

We use the graph shown us in theory lesson that plots the frequency behaviour of P_{LR} out of pass-band and we find the value of the point $(|\Omega| - 1, IL)$, in order to find the order N of the filter

$N = 5$ (actually the point would be $N = 4$ but to respect the specification of $IL \geq 15 \text{ dB}$, we choose $N = 5$)

So, using T-network I have:

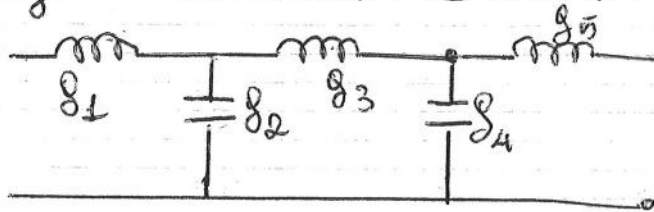


In theory lessons we saw that to find values of g_N we have to see the table in which are located these values corresponding every order of the filter N .
For $N = 5$

$$g_1 = g_5 = 0,618 \quad g_3 = 2$$

$$g_2 = g_4 = 1,618$$

Now ~~we~~ we can find ~~the~~ the circuit with lumped elements:

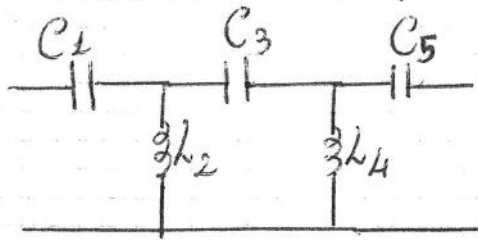So Now I transform The prototype with the real high pass filter:



Where:

$$C_1 = C_5 = \frac{1}{\omega_c R_0 g_1} = 0,36 \text{ pF}$$

$$L_2 = L_4 = \frac{R_0}{\omega_c \cdot g_2} = \cancel{4,17} \text{ mH}$$

$$C_3 = \frac{1}{\omega_c R_0 g_3} = \cancel{0,28} \text{ pF}$$

Problem n° 3

I use a Butterworth filter because of "maximally flat response". I shall compute Ω_1 and Ω_2

$$\omega_1 = 2\pi \cdot f_1 = 15,08 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\omega_0 = \sqrt{\omega_1 \cdot \omega_2} = 15,39 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\omega_2 = 2\pi \cdot f_2 = 15,71 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\omega_{R1} = 2\pi \cdot f_{R1} = 12,06 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\omega_{R2} = 2\pi \cdot f_{R2} = 18,85 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\Omega_1 = \frac{\omega_0}{\omega_2 - \omega_1} \cdot \left(\frac{\omega_{R1}}{\omega_0} - \frac{\omega_0}{\omega_{R1}} \right) = -12,06$$

$$\Omega_2 = \frac{\omega_0}{\omega_2 - \omega_1} \cdot \left(\frac{\omega_{R2}}{\omega_0} - \frac{\omega_0}{\omega_{R2}} \right) = 10$$

$$|\Omega_1| - 1 = 11,06$$

$$|\Omega_2| - 1 = 9$$

So even if I have two specifications and 1 grade of degree I however have $N=2$

ASSIGNMENT 3

MICHELE BECCARIA 209013

SHEET 1Problem 1 - Low Pass filter


With microstrip technology we work in this way:

$$\Omega = \frac{\omega}{\omega_c} = 1,5$$

$$|\Omega| - 1 = 0,5$$

So, from the table of Butterworth filter we use $N=5$ (because of maximally response)

The prototype will be:

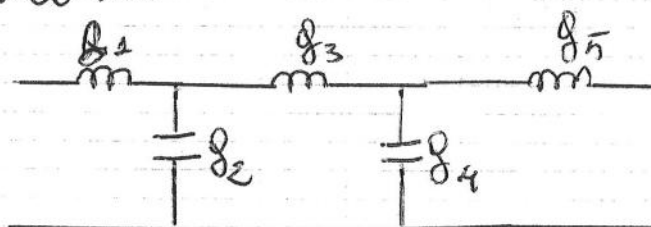

$$g_1 = g_5 = 0,6180$$

$$g_2 = g_4 = 1,6180$$

$$g_3 = 2$$

So now we compute the parameters of the microstrip to realize this filter with stepped impedance:

$$d = 1,8'' = 3,175 \text{ mm}$$

$$\left(\frac{W}{d}\right)_{\min} = 0,1575 \quad \left(\frac{W}{d}\right)_{\max} = 4,7244$$

So now we compute ϵ_{eff} for every values of $\frac{W}{d}$:

$$\epsilon_{\text{eff}_2} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \cdot \frac{1}{\sqrt{1 + 12 \left(\frac{d}{W}\right)_{\min}}} = 1,77 + 0,77 \cdot 8,76 \cdot 10^{-2} = 1,857$$


$$\epsilon_{\text{eff}_1} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \cdot \frac{1}{\sqrt{1 + 12 \left(\frac{d}{W}\right)_{\max}}} = 1,77 + 0,77 \cdot 0,409 = 2,180$$

$$l_2 = l_4 = \frac{\theta_2}{\beta_1} = 1,45 \text{ cm}$$

$$l_3 = \frac{\theta_3}{\beta_2} = 8,10 \text{ mm}$$

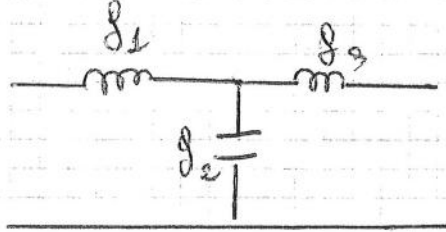Problem 2


To design a band pass filter using three resonant $\lambda/4$ stub, we ~~we~~ know that $N=3$ in fact from the prototype




We have Chebyshev filter with:

$$g_1 = g_3 = 1,5963$$

$$g_2 = 1,0967$$

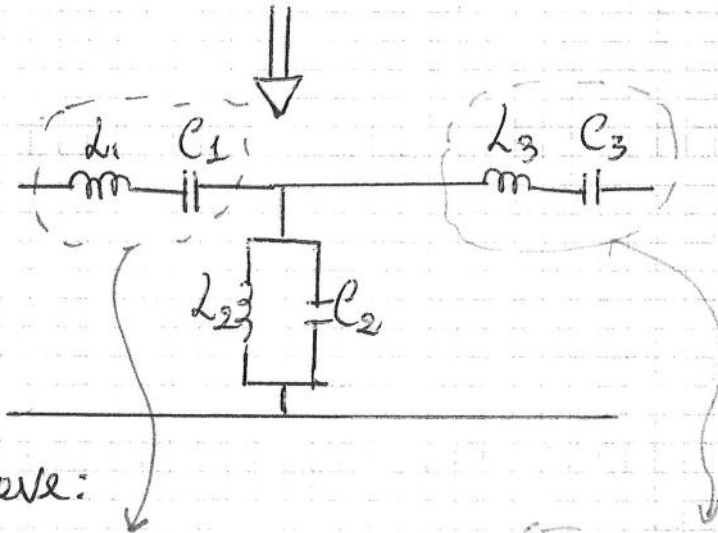


And we have:

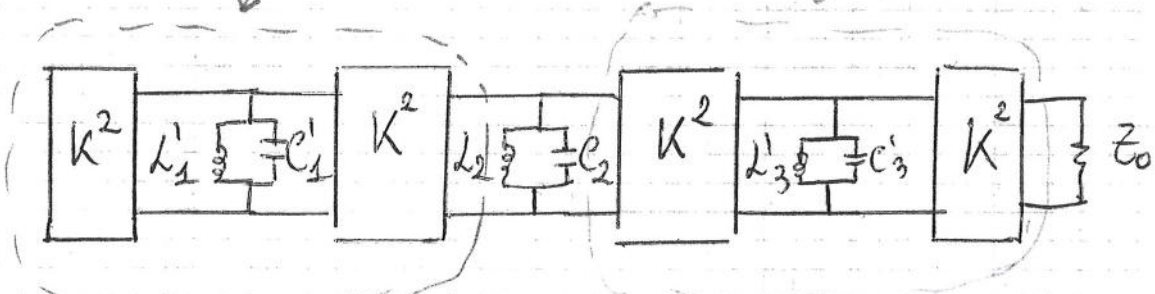

Where $K = Z_0$ and is a quarter wave impedance inverter


Finally we have: $\lambda/4$

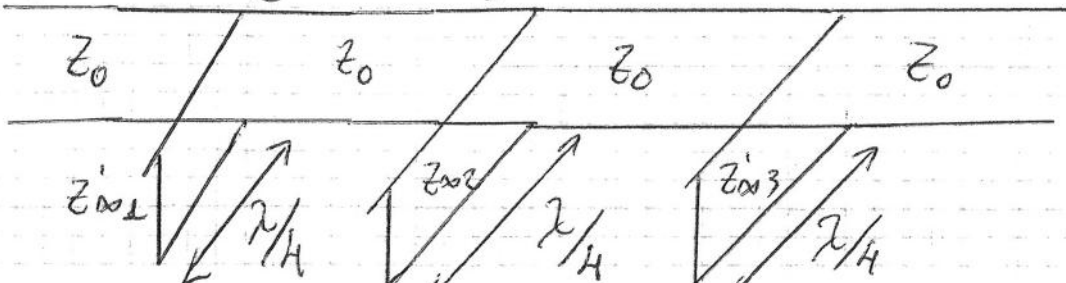

SHEET 2 ASSIGNMENT 3 MICHELE BECCARIA

... continuing Problem 3

We transform the previous circuit as:

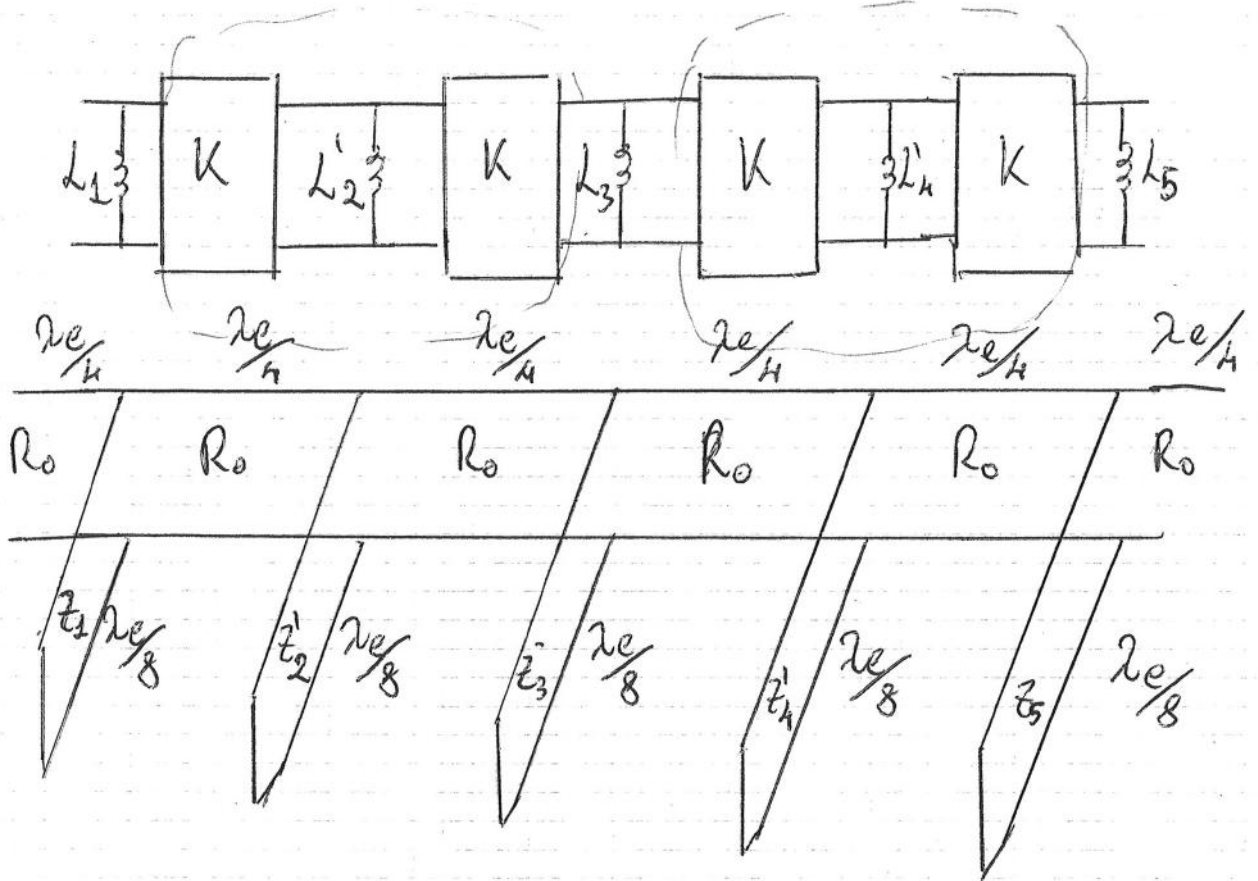

$$Z_1 = Z_5 = \omega_c L_1 = 81,7 \Omega$$

~~$$Z_1 = \omega_c L_1 = 81,7 \Omega$$~~

$$\bar{Z}'_2 = C_2 \cdot Z_0^2 = \frac{1}{g_2 \cdot Z_0 \cdot \omega_c} \cdot Z_0 \Rightarrow \omega_c \cdot \bar{Z}'_2 = \frac{Z_0}{g_2 \cdot \omega_c} = 30,9 \Omega$$

$$Z_3 = \omega_c L_3 = 24,81 \Omega$$

$$Z_{in2} = \frac{4 Z_0}{g_2 \pi \lambda} = 387 \Omega$$

The computation of Z_e and Z_h for microstrip technology were the same of the previous assignment and we found:


$$Z_e = 34,82 \Omega$$

$$Z_h = 172,97 \Omega$$

for this reason we can't use this technology because the impedances are different.

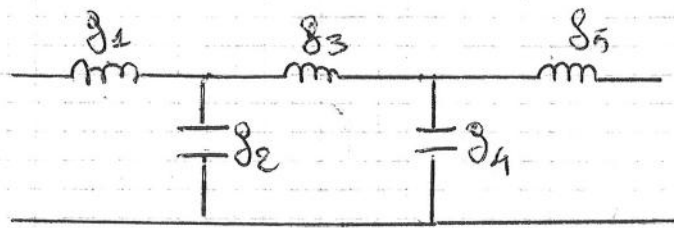Problem 2 - Low Pass filter

Starting from the prototype: ($N=5$, 0,5 dB ripple response)



$$g_1 = 1,7058 = g_5$$


$$g_2 = g_4 = 1,2296$$

$$g_3 = 2,5408$$

~~The~~

$$l = \lambda/8$$

We have

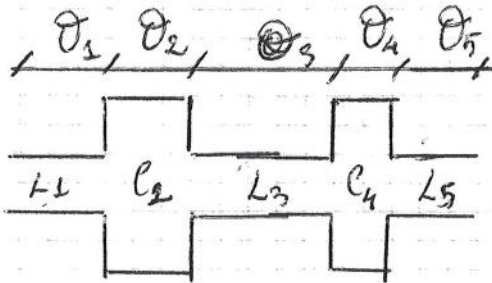


$$\theta_1 = \frac{\beta \pi}{\alpha} \cdot \frac{l}{g_4} = \frac{\pi}{4} = \theta_2 = \theta_3 = \theta_4 = \theta_5$$

$$Z_{h1} = \frac{g_1 \cdot R_0}{\theta_1} = 108,6 \Omega = Z_{h5}$$

$$Z_{e2} = Z_{e4} = \theta_2 \cdot \frac{R_0}{g_2} = 32 \Omega$$

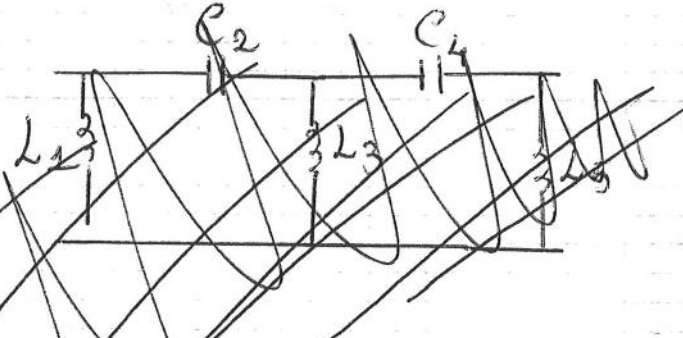Problem 4

As for the previous ~~one~~ assignment, ex n° 2 I have (lumped elements):



Where:


$$L_1 = L_4 = 2,6 \text{ mH}$$

$$L_3 = 0,79 \text{ mH}$$


$$C_2 = C_4 = 0,393 \text{ pF}$$

$$\delta_1 = \delta_3 = 1,5963$$

$$\delta_2 = 1,0967$$

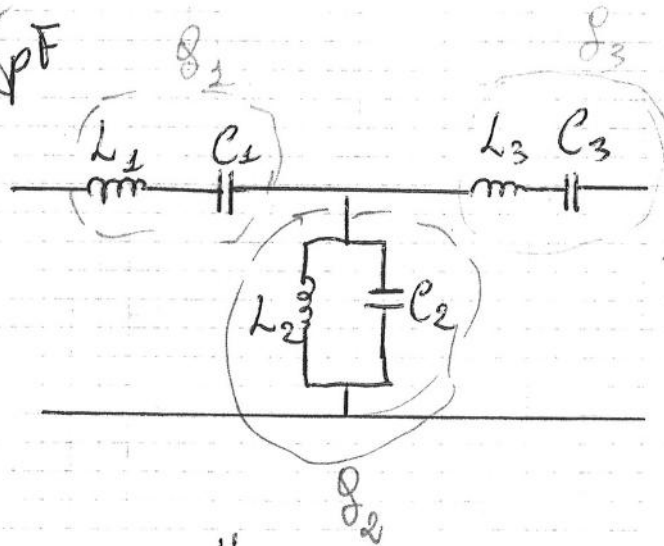

$$\Delta = 0,154$$

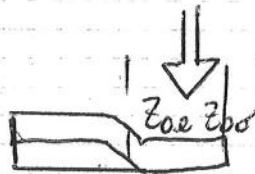

$$\gamma Z_{01} = \sqrt{\frac{\pi \Delta}{2\delta_1}} = 0,389$$

$$\gamma Z_{02} = \frac{\pi \Delta}{2\sqrt{\delta_1 \delta_2}} = 0,182$$

$$\gamma Z_{03} = \frac{\pi \Delta}{2\sqrt{\delta_2 \delta_3}} = 0,182$$

$$\gamma Z_{04} = \sqrt{\frac{\pi \Delta}{2\delta_3 \delta_4}} = 0,389$$

$$\begin{cases} Z_{\infty e1} = Z_0 \cdot [1 + \gamma Z_{01} + \gamma^2 Z_{01}^2] = 77 \Omega \\ Z_{\infty o1} = Z_0 \cdot [1 - \gamma Z_{01} + \gamma^2 Z_{01}^2] = 38,1 \Omega \end{cases} \begin{cases} Z_{\infty e2} = 60,83 \Omega = Z_{\infty e3} \\ Z_{\infty o2} = 42,518 \Omega = Z_{\infty o3} \end{cases}$$

Considering Γ_2 :

$$\Gamma_2 = \frac{b_2}{a_2}$$

$$b_2 = S_{23} a_3 = S_{23} \Gamma_3 b_3 = S_{23} \Gamma_3 S_{31} a_1 = S_{23} \Gamma_3 S_{31} \Gamma_1 b_1 = S_{23} \Gamma_3 S_{31} \Gamma_1 S_{12} a_2$$

$$\Gamma_2 = S_{23} \Gamma_3 S_{31} \Gamma_1 S_{12}$$

$$\frac{P_3}{P_2} = \frac{|S_{31}|^2 \cdot |\Gamma_1|^2 |S_{12}|^2 (1 - |\Gamma_3|^2)}{(1 - |S_{23}|^2 |\Gamma_3|^2 |S_{31}|^2 |\Gamma_1|^2 |S_{12}|^2)}$$

~~$$\Gamma_1' = \frac{z_a - z_{T1}}{z_e + z_{T1}} \xrightarrow{(z_e = 50 \Omega)} 0$$~~

$$\Gamma_1'' \xrightarrow{(z_e = 70 + j30 \Omega)} 0,21 + j0,19$$


$$|\Gamma_1''|^2 = 0,084$$

$$\left(\frac{P_3}{P_2}\right)_{TX} (z_e = 50 \Omega) = 0$$

$$\left(\frac{P_3}{P_2}\right)_{TX} (z_e = (70 + j30) \Omega) = 7,95 \cdot 10^{-2}$$

continues
→

PROBLEM 2

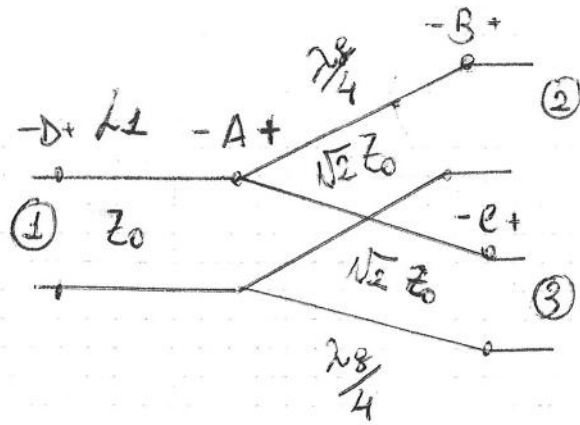


a) Scattering matrix

$$[S] = \begin{pmatrix} S_{11} & S_{12} & S_{12} \\ S_{12} & S_{22} & S_{23} \\ S_{12} & S_{23} & S_{22} \end{pmatrix}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1, a_3=0} \quad S_{22} = \frac{b_2}{a_2} \Big|_{a_1, a_3=0} \quad S_{23} = S_{32} = \frac{b_3}{a_3} \Big|_{a_1, a_2=0}$$

for simplicity I draw the circuit as:

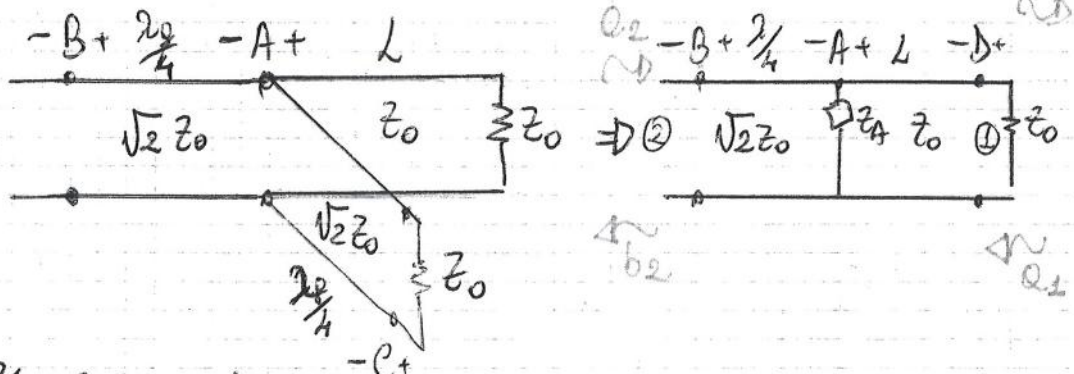

~~$$\Gamma_{e+} = \frac{Z_0 - \sqrt{2}Z_0}{Z_0 + \sqrt{2}Z_0} = \frac{1 - \sqrt{2}}{1 + \sqrt{2}} = -\frac{1 - \sqrt{2}}{1 + \sqrt{2}}$$~~

$$Z_A = \frac{2Z_0^2}{Z_0} = 2Z_0 \Rightarrow \text{because the line is } \frac{\lambda_0}{4}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1, a_3=0} = \frac{V_{D+} / \sqrt{Z_0}}{V_{B+} / \sqrt{Z_0}} =$$

$$V_{D+} = \frac{V_{D+}}{1 + \Gamma_{D+}} = V_{D-} = \cancel{V_{B-}} (1 + \Gamma_{B-}) = V_{A+} (1 + \Gamma_{B-}) e^{-j\beta L} =$$

$$\frac{V_{A+}}{1 + \Gamma_{A+}} (1 + \Gamma_{B-}) e^{-j\beta L} = V_{A-} \frac{(1 + \Gamma_{A-})}{(1 + \Gamma_{A+})} (1 + \Gamma_{B-}) e^{-j\beta L} \rightarrow \text{continue}$$

$$\frac{P_2}{P_1} = \frac{|S_{21}|^2}{1 - |M_2|^2} = \frac{1}{2}$$

$\hookrightarrow 0$

$$\frac{P_3}{P_1} = \frac{|S_{31}|^2}{1 - |M_3|^2} = \frac{1}{2}$$

$\hookrightarrow 0$

d) Find z_{03} and z_{02} with $P_2/P_3 = -2\text{dB}$

$$\begin{cases} \frac{1}{z_0} = \frac{z_0}{z_{02}^2} + \frac{z_0}{z_{03}^2} & z_{02} = x \quad z_{03} = y \\ \frac{z_{03}^2}{z_{02}^2} = 0,631 \end{cases}$$

$$\begin{cases} \frac{1}{z_0} = \frac{z_0}{x^2} + \frac{z_0}{y^2} & \begin{cases} \frac{z_0}{x^2} + \frac{z_0}{0,631x^2} - \frac{1}{z_0} = 0 \\ y^2 = 0,631x^2 \end{cases} \\ \frac{y^2}{x^2} = 0,631 \end{cases}$$

$$\frac{z_0 \cdot 0,631x^2 + z_0^2 x^2 - 0,631x^4}{x^2 \cdot 0,631x^2 \cdot z_0} = 0$$


$$0,631x^2 = 1,631z_0x^2$$

$$x = 1,60 \sqrt{z_0} \Rightarrow 1,60 \cdot 50 \Omega = 80,4 \Omega$$

$$y = 2,05 \sqrt{z_0} \Rightarrow 2,05 \cdot 50 \Omega = 102,5 \Omega$$

ASSIGNMENT 6 *Becassis Michele* 209013

Problem 1

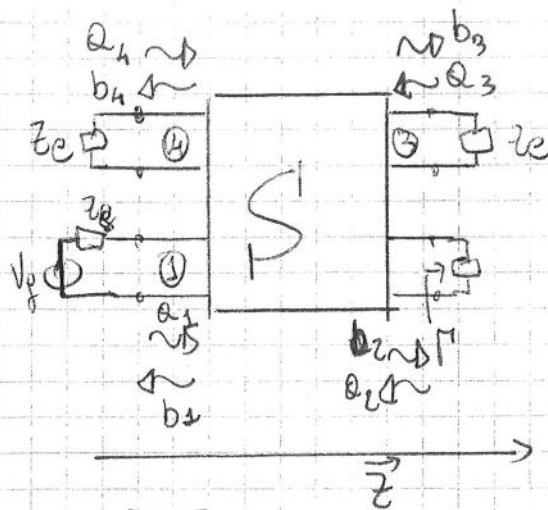

$$\left| \frac{V_4}{V_3} \right| = 0,6$$

$$\angle \frac{V_4}{V_3} = \frac{\pi}{8}$$

$$[S] = \begin{pmatrix} 0 & \sqrt{1-K^2} & 5K & 0 \\ \sqrt{1-K^2} & 0 & 0 & 5K \\ 5K & 0 & 0 & K \\ 0 & 5K & K & 0 \end{pmatrix} \quad \text{where } K = 10^{-\frac{3}{20}} = \frac{\sqrt{2}}{2}$$

Knowing that:

$$\frac{V_4}{V_3} = \frac{b_4}{b_3} \quad \text{because} \quad \begin{cases} V_4 = (1 + \frac{M_1}{4}) V_4^+ = V_4^+ = b_4 \\ V_3 = (1 + \frac{M_3}{3}) V_3^+ = V_3^+ = b_3 \end{cases}$$

$$\begin{cases} b_4 = S_{43} a_3 + S_{42} a_2 = S_{42} a_2 = S_{42} M_2 b_2 \\ b_3 = S_{34} a_4 + S_{31} a_1 = S_{31} a_1 \\ b_2 = S_{21} a_1 + S_{24} a_4 = S_{21} a_1 \end{cases}$$

$$\frac{b_4}{b_3} = \frac{S_{42} M_2 (b_2)}{S_{31} (a_1)} \Rightarrow M_2 = \frac{b_4}{b_3} \cdot \frac{S_{31}}{S_{42} S_{21}} = 0,6 \cdot \frac{5 \sqrt{2}}{2} \cdot \frac{5 \sqrt{2}}{2} \cdot \frac{1}{\sqrt{2}} = 0,818 \cdot 2 = 1,636$$


Looking for the worst case we compute:

$$|S_{34}^2| = -6,247\text{dB} \quad \Rightarrow \text{This is the worst case}$$

$$|S_{31}S_{34}| = -6,223\text{dB}$$

$$|S_{31}^2| = -6,199\text{dB}$$

Problem 3

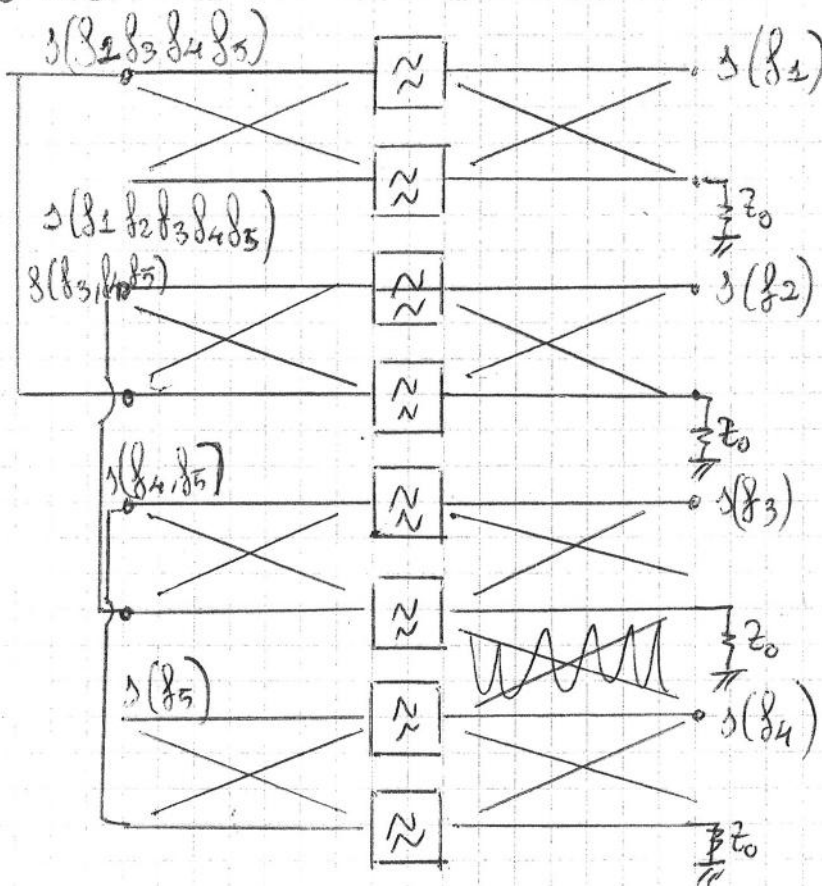

$$|S_{11}|^2 = 0,95$$

$$|S_{12}|^2 = 0,98$$

$$I_{L1} = |S_{12}|^2 = 0,98$$

$$I_{L2} = |S_{11}|^2 |S_{12}|^2 = 0,931$$

$$I_{L3} = |S_{11}|^4 |S_{12}|^2 = 0,884$$

$$I_{L4} = |S_{11}|^6 |S_{12}|^2 = 0,840$$

$$I_{L5} = |S_{11}|^8 = 0,814$$

BECCARIA MICHELE 209013



1.2

Points 21
Smith radius 1
f 5.8000 GHz
□ S11 0
× S21 -3.81dB 98.8°
◇ S24 -3.81dB -98.8°
+ S33 0


Time 2.3 secs

F3 : PARTS
a tline 70.710Ω 270°
b tline 50Ω 98°
c tline 70.710Ω 98°
d
e
f
g
h
i

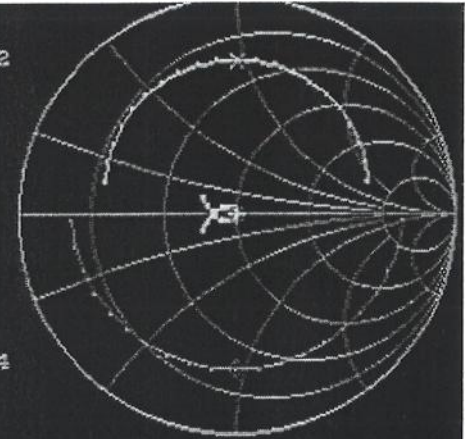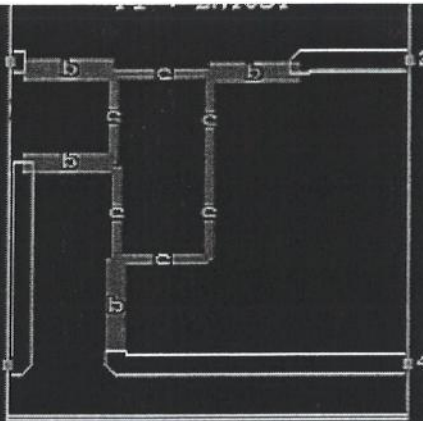F4 : BOARD
zd 50.000 Ω
fd 5.000 GHz
er 10.200
h 1.270 mm
s 25.400 mm
c 19.000 mm
Tab microstrip




file : homework7.2

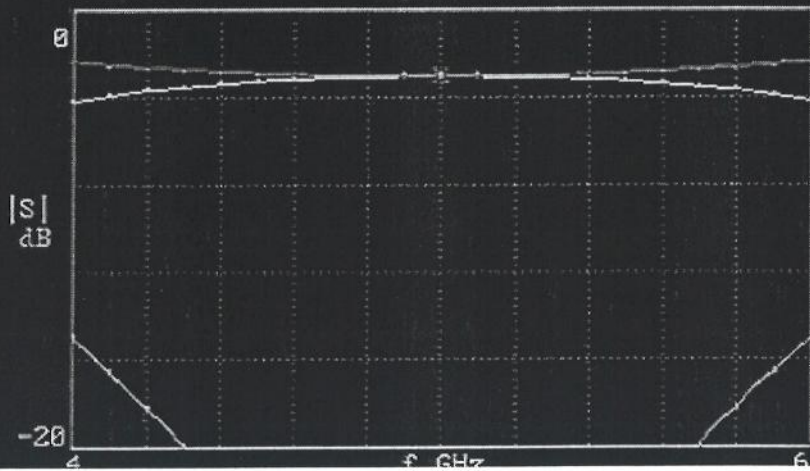

ASSIGNMENT N°7 BECCARIA MICHELE S209013

Problem 2

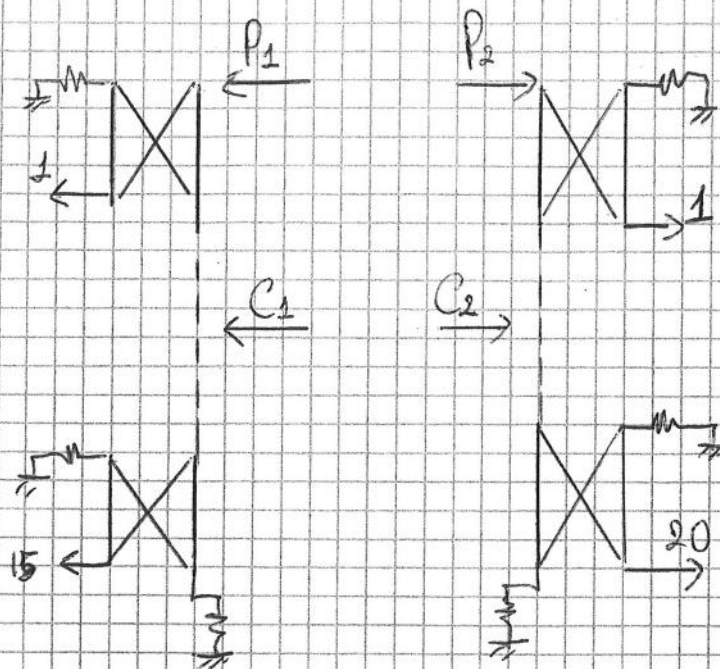

For both lines we have:

$$A_L = 10^{\frac{-3}{10}} = 0,501$$

$$I_L = 10^{\frac{-12}{10}} = 0,063$$

The receiver sensitivity has -35 dBm that are equal to -65 dB. So we have

$$P_N = -65 \text{ dB} + 5 \text{ dB} = -60 \text{ dB} = 10^{-6} \text{ W}$$


$$C_1 = \frac{1 - I_L}{N_1} = 6,24 \cdot 10^{-2}$$

$$C_2 = \frac{1 - I_L}{N_2} = 0,0468$$

$$P_{iN_1} = \frac{P_N}{C_1 A_L (1 - C_1 - I_L)^{1/4}} = 209 \mu\text{W} = -36,8 \text{ dB} = \underline{\underline{-6,8 \text{ dBm}}}$$

$$P_{iN_2} = \frac{P_N}{C_2 A_L (1 - C_2 - I_L)^{1/4}} = 389 \mu\text{W} = -34,1 \text{ dB} = \underline{\underline{-4,10 \text{ dBm}}}$$

Problem 2

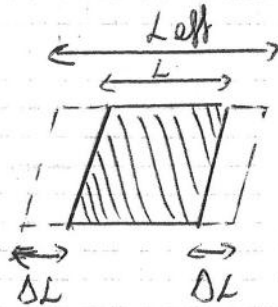

$$\epsilon_r = 2,33$$

$$h = 1/15'' = 0,17 \text{ cm}$$

$$f_0 = 20 \text{ GHz}$$

$$W = \frac{c}{2 f_0} \sqrt{\frac{2}{\epsilon_r + 1}} = 5,68 \text{ cm}$$


$$\epsilon_{\text{eff}} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \cdot \frac{1}{\sqrt{1 + 12 \frac{h}{W}}} = 2,664$$

$$L_{\text{eff}} = \frac{2L}{2} = \frac{1}{2} \frac{c \sqrt{\epsilon_{\text{eff}}}}{f_0} = 4,49 \text{ cm}$$

~~$$\frac{\Delta L}{h} = 0,514$$~~

$$\Delta L = 0,514 \cdot h = 0,87 \text{ mm}$$
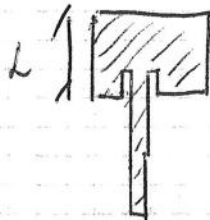
$$L = L_{\text{eff}} - 2\Delta L = 4,31 \text{ cm}$$




I used this formula because $\frac{W}{h} > 1$

$$Z_{00} = \frac{120\pi}{\sqrt{\epsilon_{\text{eff}}} \left[\frac{W}{d} + 1,393 + 0,667 \ln \left(\frac{W}{h} + 1,444 \right) \right]} = 6,21 \Omega$$

The equivalent transmission line model is:

ASSIGNMENT N°9 BECCARIA Michele 209013

Problem 1

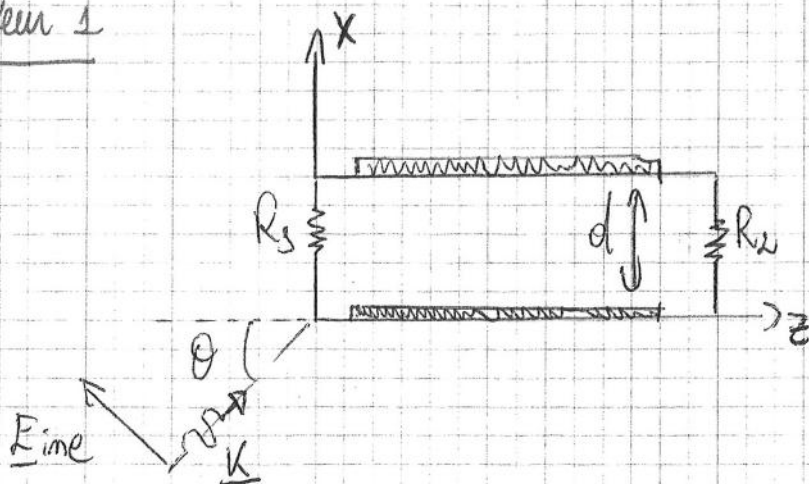

Starting to compute K and the other parameters:

$$\underline{K} = K_0 (\cos \theta \hat{z} + \sin \theta \hat{x}) = K_0 \left(\frac{z}{2} + \frac{\sqrt{3}}{2} \hat{x} \right) = \frac{K_0}{2} (\hat{z} + \sqrt{3} \hat{x})$$


$$\underline{E} = \cancel{E_0} = E_0 [\hat{x} \sin(90^\circ - \theta^{inc}) - \hat{z} \cos(90^\circ - \theta^{inc})] =$$

$$= E_0 \left[\frac{1}{2} \hat{x} - \frac{\sqrt{3}}{2} \hat{z} \right] = \frac{E_0}{2} [\hat{x} - \sqrt{3} \hat{z}]$$

$$\underline{H} = \frac{1}{Z_0} \hat{K} \wedge \underline{E} = \frac{1}{Z_0} \cdot \frac{E_0}{4} \begin{vmatrix} \hat{x} & \hat{y} & \hat{z} \\ \sqrt{3} & 0 & 1 \\ 1 & 0 & -\sqrt{3} \end{vmatrix} = \frac{1}{Z_0} \cdot \frac{E_0}{4} (\hat{y} + 3\hat{y}) = \frac{E_0}{Z_0} \hat{y}$$

$$\lambda = \frac{c}{f} = \frac{3 \cdot 10^8 \frac{m}{s}}{100 \text{ MHz}} = 3 \text{ m} \gg 15 \text{ cm}$$

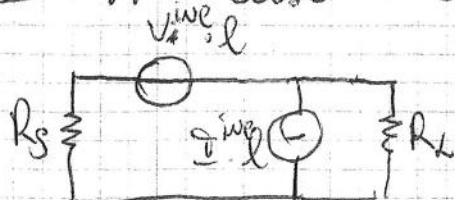In this case I can use the short line approximation:



$$V^{inc} \cdot l = -\int \omega_0 \mu_0 l \cdot d \cdot \vec{H} \cdot \hat{m}$$

$$I^{inc} \cdot l = -\int \omega_0 \epsilon_0 l \cdot d \cdot \vec{E}^{inc} \cdot \hat{c}$$


$$\hat{m} = \hat{y}$$

$$\hat{c} = \hat{x}$$

$$V^{inc} \cdot l = -52\pi \cdot 1 \cdot 10^8 \cdot 4\pi \cdot 10^{-7} \cdot 0,15 \cdot 5 \cdot 10^{-3} \cdot \frac{10}{120\pi} = -515,708 \text{ mV}$$

$$I^{inc} \cdot l = -53\pi \cdot 1 \cdot 10^8 \cdot 20 \cdot 10^{-2} \cdot 15 \cdot 10^{-2} \cdot 5 \cdot 10^{-3} \cdot \frac{10}{120\pi} = -594,942 \text{ uA}$$

Problem 3

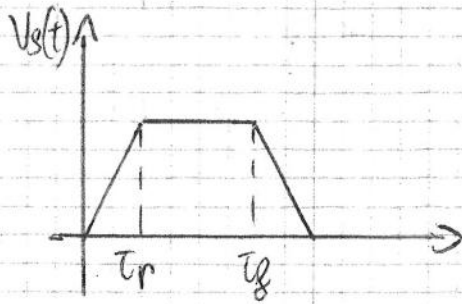

We know that:


$V_{FE} = -j\omega \{M_{FE}^{IND} + M_{CAP}\} V_3$ in ~~the~~ ^{frequency} domain,
in time domain we have:

$$V_{FE}(t) = -\frac{d}{dt} V_3(t) \cdot \{M_{FE}^{IND} + M_{CAP}\}$$

$$V_{FE}(t) = -\frac{d}{dt} V_3(t) \cdot \{M_{FE}^{IND} + M_{CAP}\}$$

$$V_{FE\text{MAX}} = \frac{5}{50 \cdot 10^{-9}} \{ \pi \cdot 10^{-9} + 6,25 \cdot 10^{-9} \} = 1,125 \text{ V}$$

Problem 4

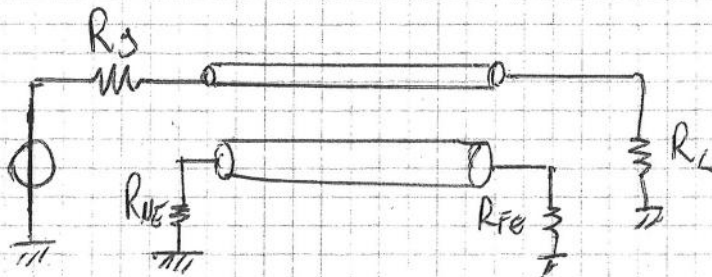

$\lambda = \frac{c}{f} = 300 \text{ m} \gg 2 \text{ m} \rightarrow$ I can use short line approximation:

$$\tau_S = \frac{L_{SH}}{R_{SH}} = 16 \mu \Rightarrow \omega = 2\pi f = 6,283 \cdot 10^6 \frac{\text{rad}}{\text{s}}$$

$$\frac{1}{\tau_S} = 62,5 \cdot 10^3 \frac{\text{rad}}{\text{s}} \ll \omega$$

Thus:

$$\frac{1}{1 + j\omega\tau_S} \approx \frac{1}{j\omega\tau_S}$$