



**appunti**  
www.centroappunti.it

Corso Luigi Einaudi, 55/B - Torino

**Appunti universitari**

**Tesi di laurea**

**Cartoleria e cancelleria**

**Stampa file e fotocopie**

**Print on demand**

**Rilegature**

NUMERO: 1520A -

ANNO: 2015

# APPUNTI

STUDENTE: Lacirignola

MATERIA: Power Electronics + Eserc. Prof. Maddaleno

Il presente lavoro nasce dall'impegno dell'autore ed è distribuito in accordo con il Centro Appunti.

Tutti i diritti sono riservati. È vietata qualsiasi riproduzione, copia totale o parziale, dei contenuti inseriti nel presente volume, ivi inclusa la memorizzazione, rielaborazione, diffusione o distribuzione dei contenuti stessi mediante qualunque supporto magnetico o cartaceo, piattaforma tecnologica o rete telematica, senza previa autorizzazione scritta dell'autore.

ATTENZIONE: QUESTI APPUNTI SONO FATTI DA STUDENTI E NON SONO STATI VISIONATI DAL DOCENTE.  
IL NOME DEL PROFESSORE, SERVE SOLO PER IDENTIFICARE IL CORSO.

What is power electronics? We have power electronics every time that we are concerning with the **EFFICIENCY**.

In this field we have electrical energy conversion. So, we can have different types of conversion :

1. DC → DC (CONVERTER)
2. DC → AC (INVERTER)
3. AC → DC (RECTIFIER)
4. AC → AC (CYCLOCONVERTERS)

We are interested in ① and ③.

EFFICIENCY DISTINGUISHES POWER ELECTRONICS FROM NOT POWER ELECTRONICS.

What is efficiency?


$$\eta = \frac{P_o}{P_{im}}$$

It's important for:

- money, cost

(If  $\eta > 1$  we invent perpetual motion :)

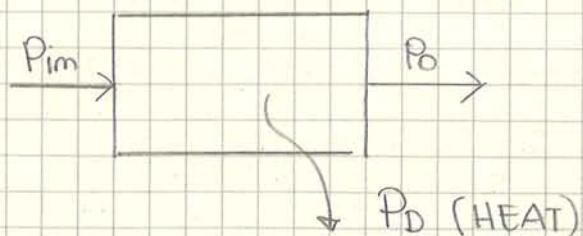$P_{im} - P_o$  → this difference is the power that stays inside; the dissipated power  $P_d$ .



NB: the relation  $P_{im} - P_o$  is not instantaneous.

② Let's consider AC adaptors. How many AC adapt. exist in Europe?

### POWER SAVING

③ How much does electric energy for the main cost?

20 cents for  $\text{kW}/\text{hours}$

But! The energy of batteries is more expensive! Three order of magnitude than the energy from the mains. ( $20 \$/\text{kWh}$ )

Our devices must have an high battery efficiency.


### PORABLE DEVICES

### LONGER ENDURANCE


Let's start to analyze two type of conversion, their advantages and disadvantages.

The standard way is to use a standard transistor working in linear region:

### LINEAR "POWER SUPPLY"

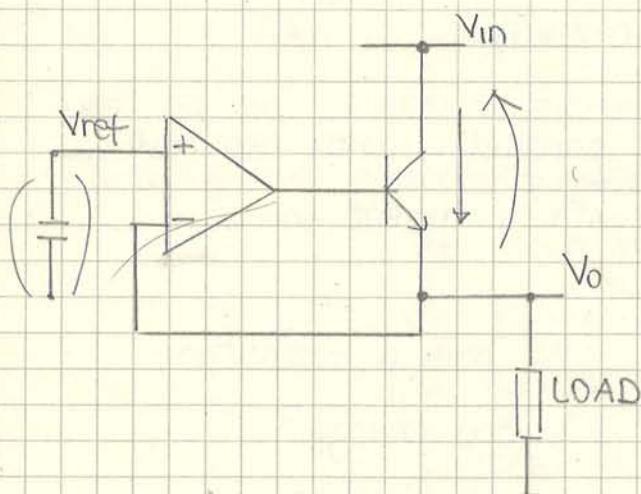

- |   |   |         |
|---|---|---------|
| <ul style="list-style-type: none"><li>- efficiency</li><li>- <math>V_o</math> RELATED <math>V_{in}</math></li></ul> | } | DISADV. |
| <ul style="list-style-type: none"><li>+ EASY</li><li>+ FAST</li><li>+ E.M. NOISE LOW</li></ul>                      | } | ADV.    |

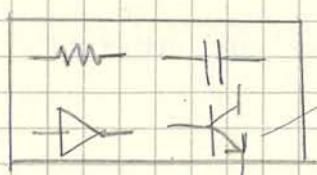

→ This transistor works in linearity; in RAD zone we have a power dissipation ( $V \cdot I$  is power!)

What are the differences between switch mode conversion and linear power supply?  $\oplus$  advantages of switch mode ;  $\ominus$  disadvantages:

- $\oplus$  efficiency (we have no elements wasting power)  
( weight, cost, temperature, life ... )
- $\oplus$   $V_o$  not related in magnitude and sign with the input voltage  
( we can have  $V_o$  larger smaller, with opposite sign respect to  $V_{in}$  )
- $\oplus$  Multiple outputs


NEGATIVE POINTS :

- $\ominus$  complicated
- $\ominus$  They are a speedy feedback system. An important parameter is the crossover frequency ( smaller than linear system)
- $\ominus$  Slow system ( slower than linear system)
- $\ominus$  Electromagnetic noise ( very high )

NB: we need to use inductors ( in order to have high efficiency ).

Can we use synthesize inductors? No.

First of all groundend inductor:

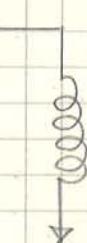


The main reason is that a generator needs of an OP-AMP. That's fine. An inductor carries a current that the order of AMPS ( large current ) so we need a POWER OP-AMP.

But this component has a very bad efficiency.  $\Delta$

## BASIC TOPOLOGIES - REFRESH -

## HYPOTHESES :

- IDEAL SWITCHES

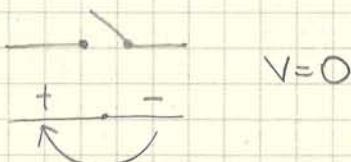

$$V=0$$

- $RC$  or  $\frac{L}{R}$  TIME CONSTANTS ( $\tau$ )

$$\tau \gg T_{sw}$$

What does it mean? It means that waveform linear; otherwise exponential. → EQUATIONS EASIER


(NB: R can be the load; the parass. of the L)

→ EFFICIENCY = 1 ( IDEAL CASE )

So, for the beginning  $\eta = 1$

- OUTPUT VOLTAGE (OF A POWER CONVERTER) IS CONSTANT.

NO RIPPLE

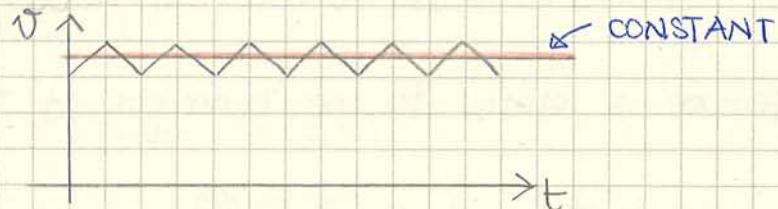

- There is a sort of "steady state"; sort because there is a switch that open and close). → It's called CYCLO STATIONARY CONDITION (each cycle is equal to the other one),

(It's equal to the DC bias point for linear circuit)

## TWO BASIC TOPOLOGIES :

- BUCK

$$\frac{V_o}{V_i} < 1$$

DUAL  $\rightarrow (V_o < V_i)$  BUT DON'T WRITE IN THIS WAY!  
 $|V_o| < |V_i|$

- BOOST

$$\frac{V_o}{V_i} > 1$$

There are 2 more topologies :

- BUCK-BOOST (FLY BACK)

$$\frac{V_o}{V_{in}} < 0$$


$V_o$  OPPOSITE POLARITY OF  $V_{in}$

We can do the average of voltage:

$$\bar{U}_L = \overline{L \frac{d i_L}{d t}} \longleftrightarrow = L \frac{d \bar{i}_L}{d t}$$

LINEAR  
OPERATOR

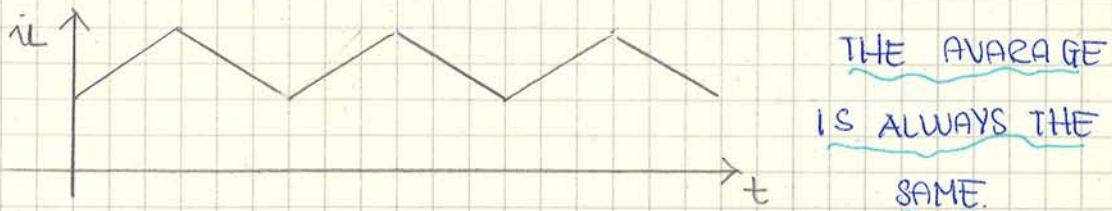If we consider cyclostationary conditions ( $\bar{i}_L$  is equal in each cycle) :



The average is the DC component of the current.

In cyclost. cond. the average is the same; so the derivative is

zero :

$$\bar{U}_L = 0 \quad \left( \frac{d \bar{i}_L}{d t} = 0 \right)$$


An inductor for DC component is a piece of wire; a real inductor has a resistance. (short circuit)

$$\bar{i}_C = C \frac{d \bar{U}_C}{d t} = 0 \quad (\text{OPEN CIRCUIT})$$


What happens if we apply a constant voltage to C and we have a constant current?  $\rightarrow$  C is failed. It's time to change it.

$$\left. \begin{array}{l} \bar{U}_L = 0 \\ \bar{i}_C = 0 \end{array} \right\} \text{CYCLOSTATIONARY CONDITION.}$$

We can find out  $i_L(t)$

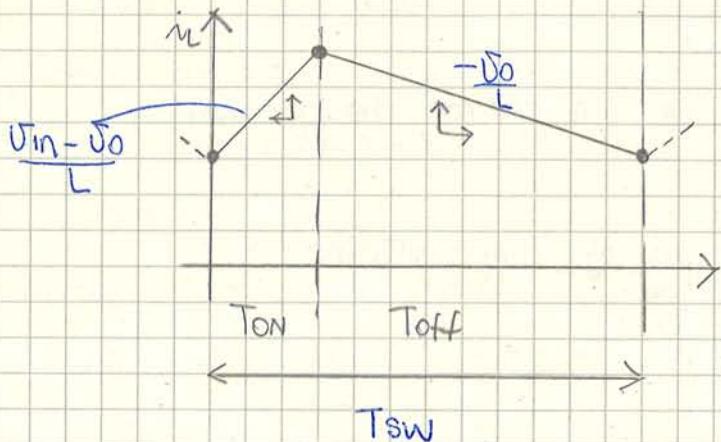

①

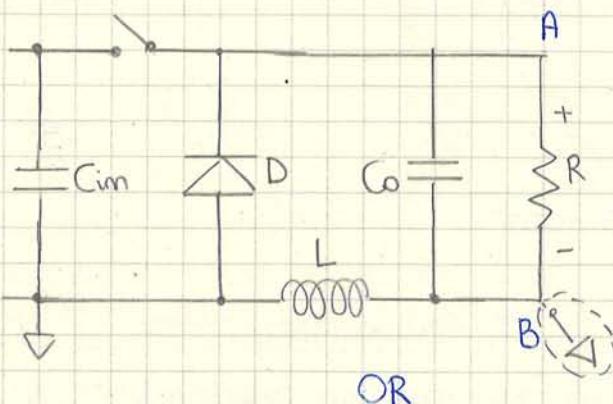

$$V_o = V_{in} \cdot D$$

SW ON

$$A \rightarrow V_{in} \quad B \rightarrow V_{in} - V_o$$

SW OFF


$$A \rightarrow 0$$

$$B \rightarrow -V_o$$

(NO)

OR

②

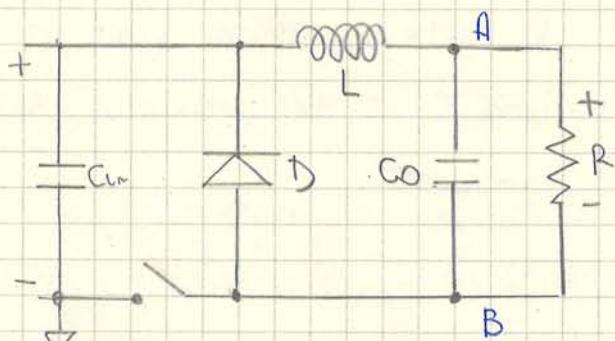

SW ON

$$A \rightarrow V_o \quad B \rightarrow \emptyset \vee$$


SW OFF

$$A \rightarrow V_{in} + V_o$$

(NO)

OR

③

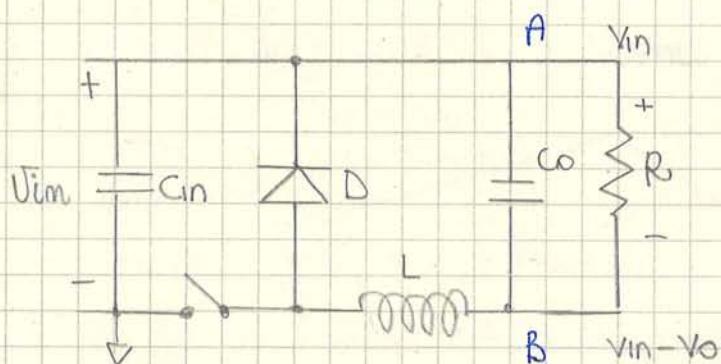

$$A \rightarrow V_{in}$$

$$B \rightarrow V_{in} - V_o$$

BOTH IN  
SW ON AND  
SW OFF

The potential is constant!

(OR)

①, ② e ③ are all buck converters.

Voltage reference is usually connected to a large part of PCB; it could be connected to metal box, (GROUND). Let's see circuit ① what happens? If we look to the output voltage refers to ground we see that there is a swing up and down ( $V_{in}$ ) very fast.

↳ High speed changing voltage; so it's generate a lot of electromagnetic noise (the load goes up and down of quantity equal to  $V_{in}$ ).

For solving this problem I can connect B to the ground, L became a short circuit!

We see that the equations are different.

$$\frac{V_{in} - V_{sw} - V_o}{T_{sw}} \cdot \frac{T_{on}}{T_{sw}} - \frac{V_D + V_o}{T_{sw}} = 0$$

$\Downarrow D$

$$\frac{T_{off}}{T_{sw}} = 0$$

$\Downarrow 1-D$

NB : If  $V_o$  doesn't depend on  $L$ , I can put  $L=0$ ? No! If we shorts the inductor ; in the moment that we close the switch <sup>to the air</sup> we apply  ~~$V_{in} - V_o$~~ , and it's not a good idea. And  $L$  can't be  $0$ ; it's in the denominator!

So, solving the equation, we find out  $V_o$ :

- $V_o = \frac{(V_{in} - V_{sw})D}{V_D (1-D)}$

$\sim$

NB The presence of  $-$ , because  $V_o$  is smaller than the ideal


And the real duty cycle:

- $D_{\text{REAL}} = \frac{V_o + V_D}{V_{in} - V_{sw} + V_D}$  ( $D_{\text{REAL}} > D_{\text{IDEAL}}$ )


If  $V_o \gg V_D$  And  $V_{in} \geq V_{sw} + V_D$  there is a sort of cancellation.

But if  $V_{in}$  is 0.9 V this is not valid!

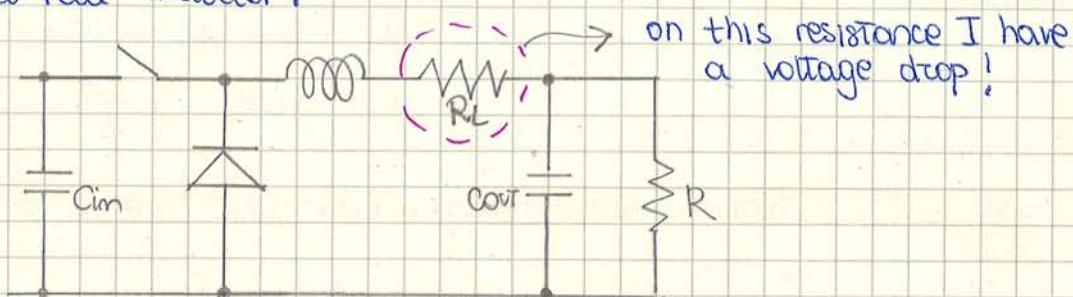If we have losses our output voltage is smaller. By the way, If we have a real inductor:




Let's see how our converter works :

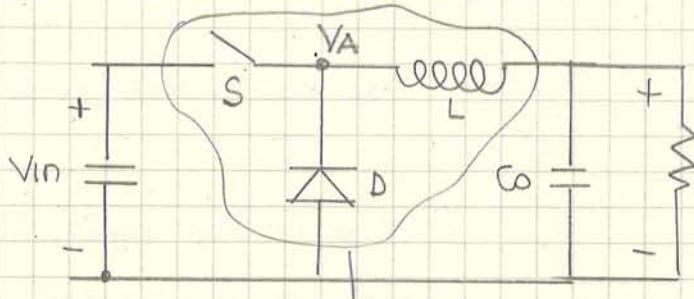


The buck conv. is just this part!

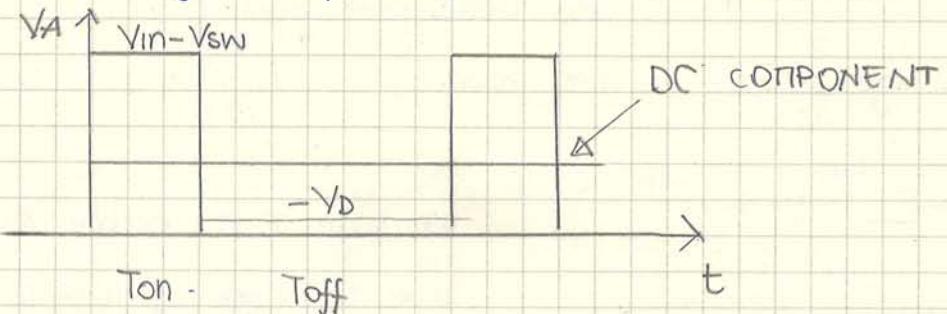NB: I can't change the polarity because of diode! ⚠



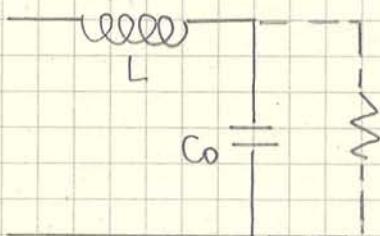Let's see the 2<sup>nd</sup> part of the circuit:




This is a resonance circuit.

Low pass filter (II order)


↳ AC component is stopped.

So, this low pass filter passes the DC component of VA. (the average!)

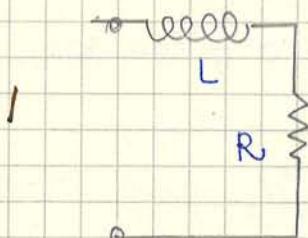
If I want to make a 1<sup>st</sup> order.



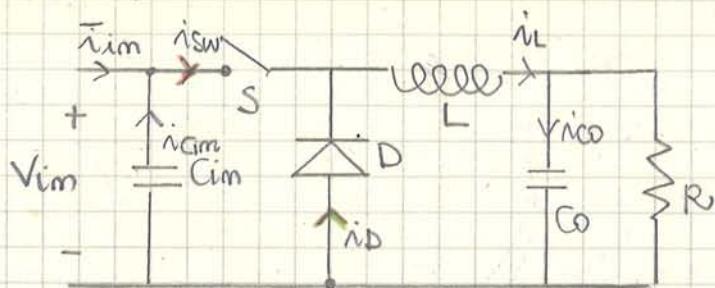In this case if I want the same frequency capability of the II order  $\rightarrow$  L is large and large ...




WRITE WAVEFORMS  
IN THE CIRCUIT.

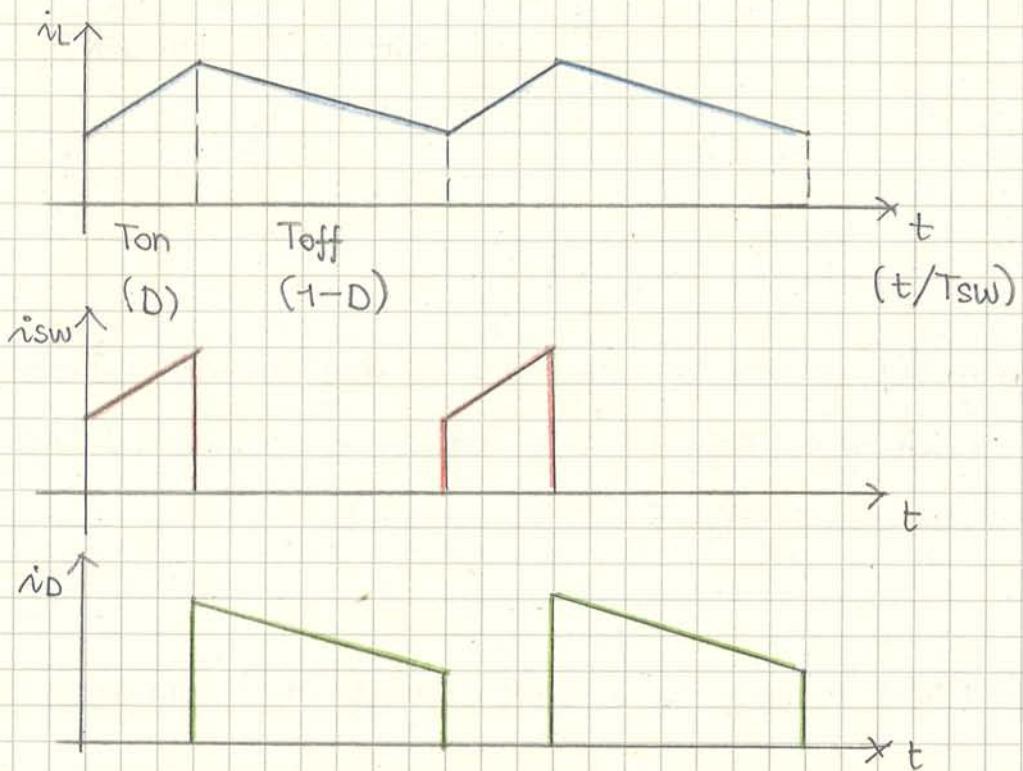

EQ: I forgot to put the diode? what happens to the circuit?


Or if I put the diode reversed? (cc Vin)

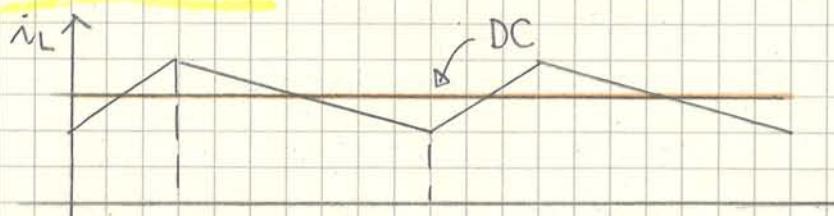Let's go to see current in  $C_ico$ . If the output voltage is constant  $V_{ico} = \emptyset$ . But  $V_o$  is not constant! There is ripple.




The DC component goes in R.

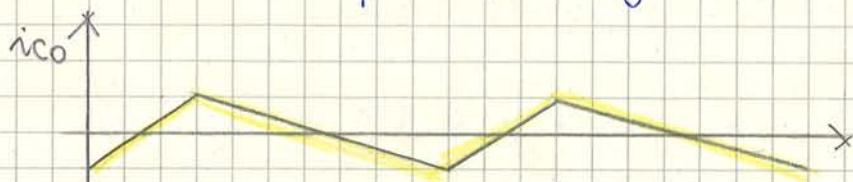What about AC component? It goes in  $C_ico$ .



Can we use current divider rule? No.


Why?

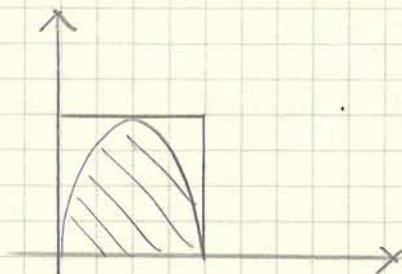

PARABOLA

$$x(1-x)$$

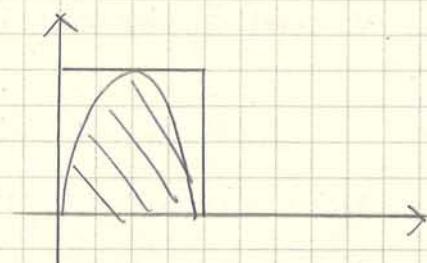
$$A_{\text{PAR}} = \frac{2}{3} \cdot b \cdot h$$




SINUSOIDAL

$$A_{\text{SIN}} = \frac{2}{\pi} b \cdot h$$

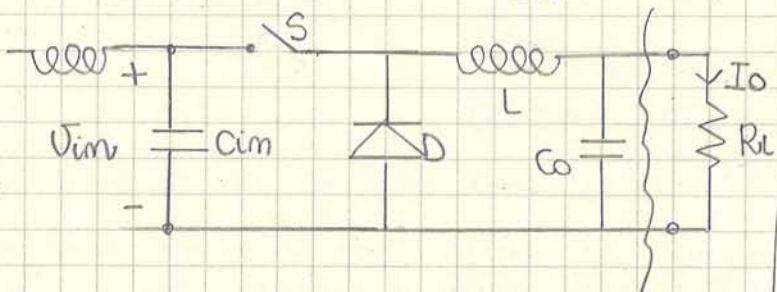Let's take our standard configuration of buck converter:



In other case we can represent it as:

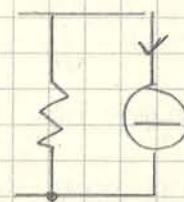


NORTON

EQUIVALENT


(or non-linear load)

Remember that  $V_{in}$  is not ideal, otherwise  $C_{in}$  is useless!

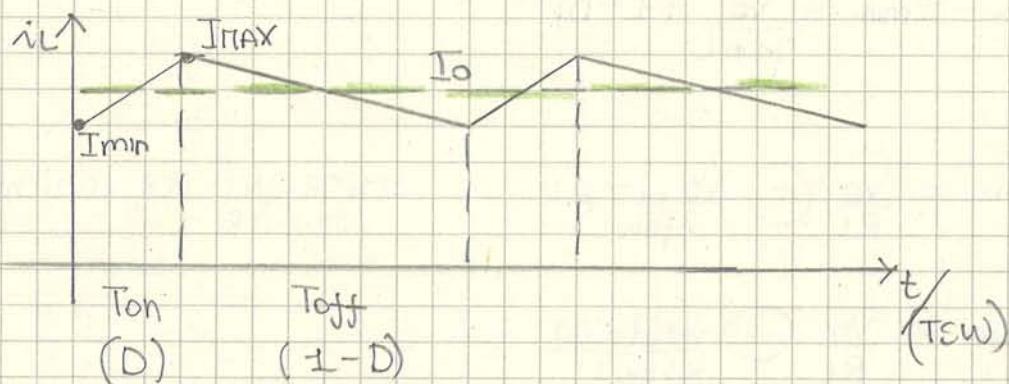The inductor at the input is one part of the E.M. filter and it's designed by E.M. engineers.  
we know that the inductor current in CCM :




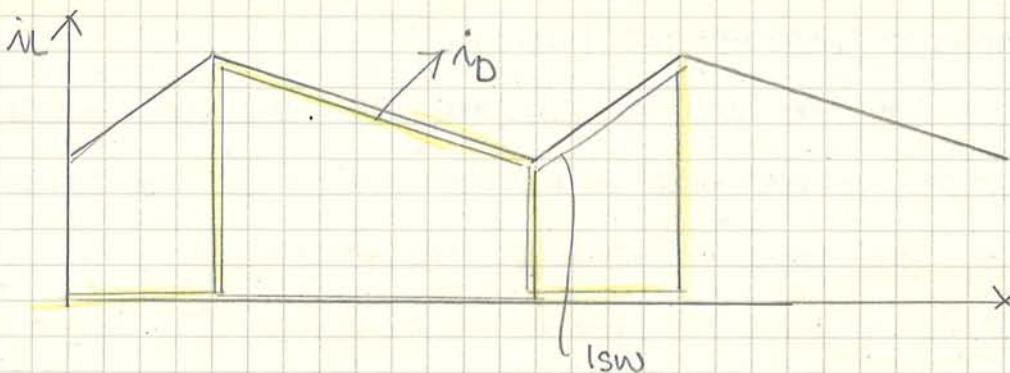In order to find  $i_L$ , I need to find out  $I_{\text{MAX}}$  and  $I_{\text{MIN}}$ . I need it because of the stress; for example  $I_{\text{max}}$  is the peak current flowing to the L, that is the peak flowing to the switch; and so on.



Let's try to derive the only design equation for buck converter.

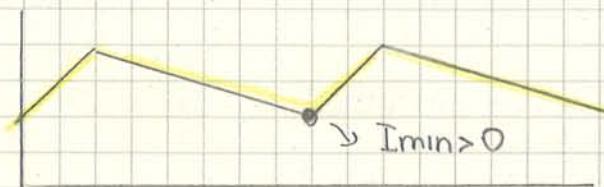In general, we want to work it in CCM (because it's easy to control it). CCM means that  $i_L$  must be larger than  $0$ .




So, in order to be sure that our buck converter works in CCM we must guarantee that  $I_{min}$  is larger than  $0$ .

So,  $I_{min} > 0$ :

$$\frac{V_0}{R_L} - \frac{V_0(1-D)}{2fsWL} > 0$$

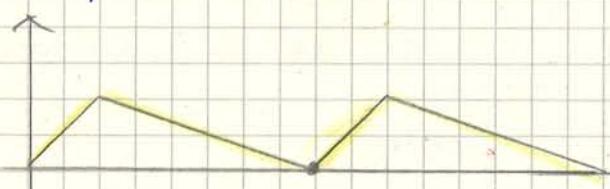We have to find the critical condition; the boundary between CCM and DCM; and this condition is:



$$\frac{V_0}{R_L} - \frac{V_0(1-D)}{2fsWL} = 0$$

$$\frac{1}{R_L} - \frac{1-D}{2fsWL} = 0$$

→ if it is satisfied we have the boundary between CCM and DCM.

$R_L$  is not under our control! The customer decides how much current he wants. What about  $D$ ?

$$D = \frac{V_0}{V_{in}} \rightarrow D \text{ is not our degree of freedom!}$$

I want to find D and R that guarantee ~~that~~ the value of L for staying still in CCM.

I want  $I_{min} > 0$  in the worst case.

$$I_{min} = \frac{V_0}{R_L} - \frac{V_0(1-D)}{2f_{sw}L} > 0 \quad (\text{I take the smallest possible})$$

$\hookrightarrow R_{LMAX}$  and  $D_{min}$

CCM

So:

$$L_{CRIT} = \frac{(1-D_{min})R_{MAX}}{2f_{sw}} \rightarrow \text{IT'S THE ONLY DESIGN EQUATION OF BUCK CONVERTER}$$

If I want to design a buck converter working in DCM, this situation is reversed considering  $R_{min}$  and  $D_{MAX}$ ; and L should be smaller.

And if we remove load from the converter?

$I_{MAX} \rightarrow \infty$ ; and L should be  $\infty$ ! Too much expensive!

(And then we pass from CCM to DCM) GUARANTEED!

On the contrary if R becomes smaller and smaller we stay in CCM.

What about switch and diode? We have a range. (No stress)

What about  $C_{im}$  and  $C_{out}$ ? They have a value, a stress!

We need to find :

- PEAK CURRENT
- AVERAGE CURRENT
- RMS CURRENT



Stressed depends on :

$V$  ← electric field

$I_{PK}$  ← critical for bonding wires in transistor

(magnetic saturation)

$I_{AVE}$

$I_{RMS}$

→ DISSIPATED POWER HEAT

What is important is :

$$p(t) = V(t) \cdot i(t)$$

Let's go into details:



INSTANTANEOUS  $\Sigma i(t)$

$i$  → AVERAGE CURRENTS  $\bar{\Sigma} i = \bar{i} = 0$   
 (we have already done it!)


RMS  $\Sigma i_{\text{RMS}} = 0 ?$

IS IT TRUE? **NO.** THE SQUARE IS NOT LINEAR.

$$\text{RMS}(\bar{i}) = 0$$

We can use a sort of KCL for RMS current.

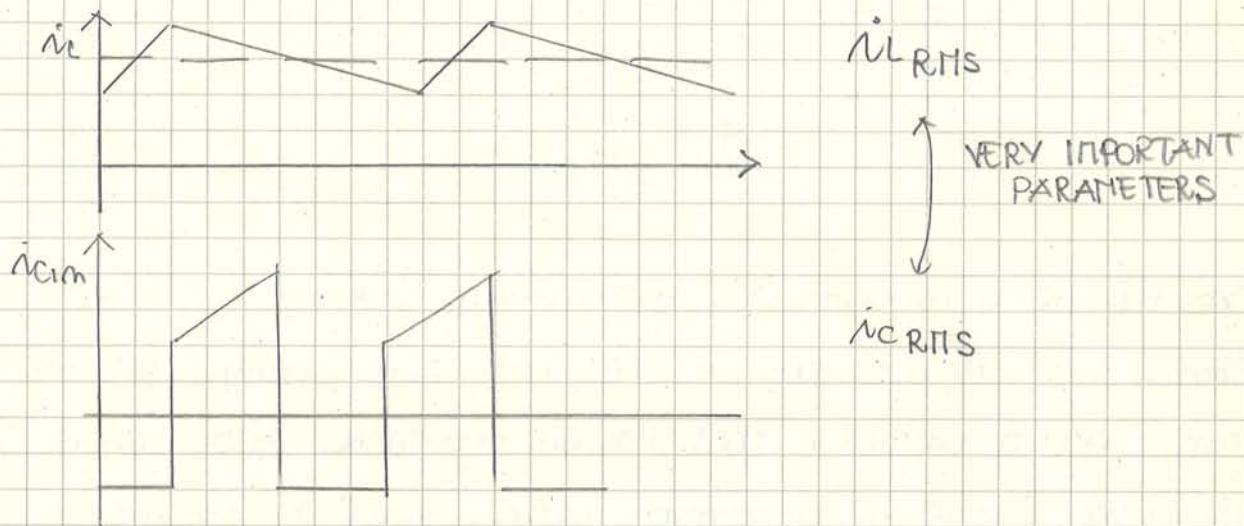Let's consider  $i_{\text{AC}}$  and  $\bar{i}_L$ :



It's hard to find RMS. We can do something better. Let's consider:

$$i(t) = I_{\text{DC}} + i_{\text{AC}}(t)$$

$$\bar{i}_{\text{AC}}(t) = 0$$


So, we try to find out RMS value from  $i(t)$ :

$$\text{RMS}[i(t)]^2 = \frac{1}{T_{\text{SW}}} \int_0^{T_{\text{SW}}} (I_{\text{DC}} + i_{\text{AC}}(t))^2 dt$$

$$= \frac{1}{T_{\text{SW}}} \int_0^{T_{\text{SW}}} I_{\text{DC}}^2 dt + \frac{1}{T_{\text{SW}}} \int_0^{T_{\text{SW}}} 2I_{\text{DC}} \cdot i_{\text{AC}}(t) dt + \int_0^{T_{\text{SW}}} i_{\text{AC}}^2 dt$$

$\cancel{\phi}$  ( $\bar{i}_{\text{AC}}$  is  $\phi$ )

Zoom to iAC:

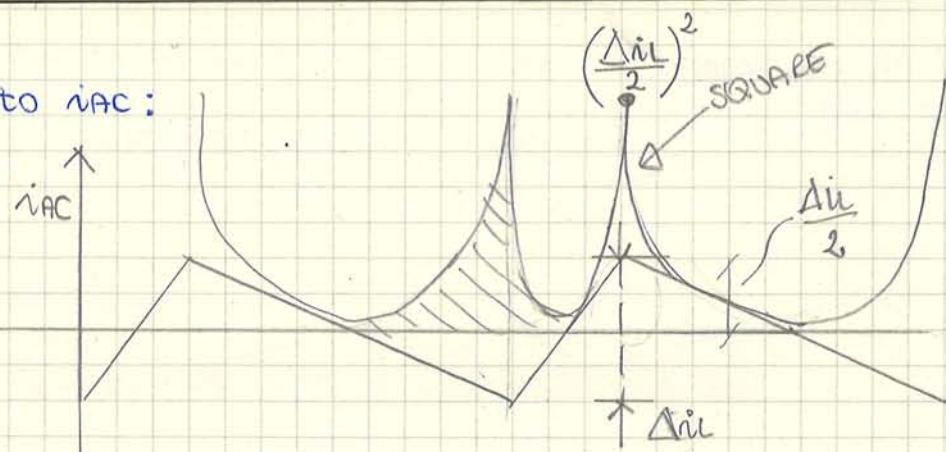


In order to find RMS value:

- square waveform
- evaluate the peak
- Find the area and spread it over one cycle

$$\text{AREA : } \frac{\text{BASE}}{3} \left( \frac{\Delta iL}{2} \right)^2$$

$$\text{• AVERAGE : } \frac{\text{BASE}}{3} \left( \frac{\Delta iL}{2} \right)^2 \cdot \frac{1}{\text{BASE}}$$

So, without integrals we find out:

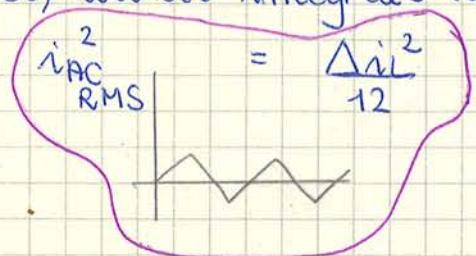

(why equation  $\star$  works? DC component and AC component are function in Hilbert space; so  $I_{DC}$  and  $I_{AC}$  are orthogonal.)

Substituting:

$$I_L^2_{RMS} = I_0^2 + \frac{\Delta iL^2}{12}$$

$$I_L_{RMS} = \sqrt{I_0^2 + \frac{\Delta iL^2}{12}}$$

in case of CCM

this term is negligible

NB  $\Delta$  we did an assumption:  
all the AC component flows to  $C_0$   
(Not totally true)

True if there isn't ripple

$$I_L_{RMS} \approx I_0$$


! CCM

No. We can't do it.  $I_{L_{RMS}}^2$  and  $I_o^2$  are very close each other.


So, this calculation has no meaning.

$$I_{L_{RMS}} \approx I_{L_{AVE}} \quad CCM$$

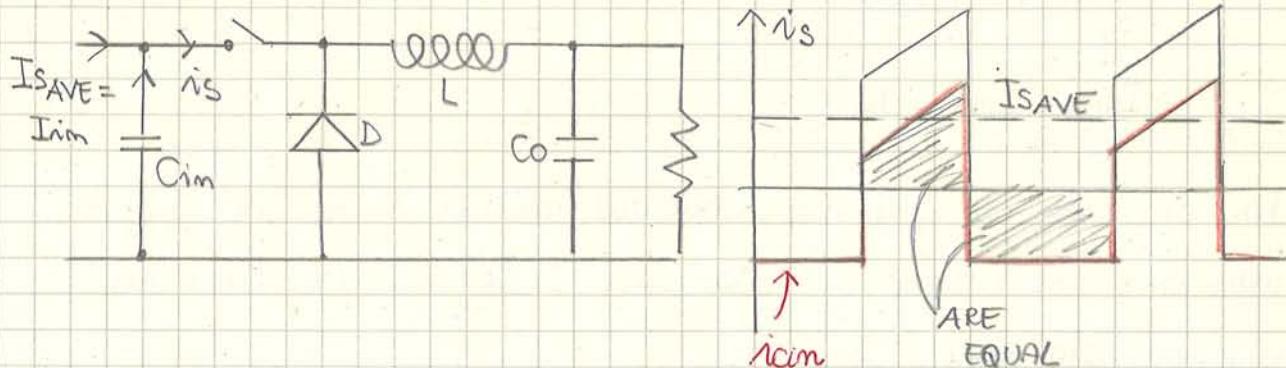Let's analyze the input of the buck converter:




Let's start to evaluate  $I_{S_{AVE}}$ :

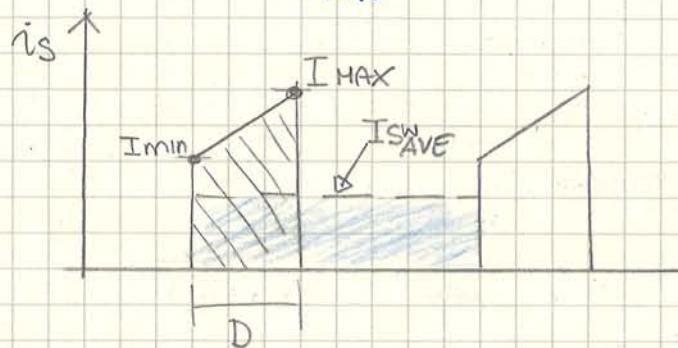

(Remember: the average is the area)

$$I_{S_{AVE}} = \frac{I_{min} + I_{max}}{2} \cdot D = I_o \cdot D = I_{im}$$

IMPORTANT:

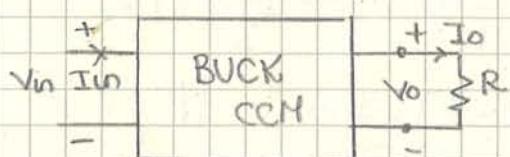

$$V_o = V_{im} \cdot D \quad \leftarrow \text{IT LOOKS LIKE}$$

$$I_{im} = I_o \cdot D \quad \text{A TRANSFORMER!}$$

$$I_o = I_{im} \cdot \frac{1}{D}$$

$$V_o \cdot I_o = V_{im} \cdot I_{im}$$

POWER CONSERVATION

It's not true! we have losses!

We use these equations not to design our circuit but to check it.

$$I_{AC} = ? \quad \text{Can we use } I_{AC} = \sqrt{I_{TOT}^2 - I_{DC}^2} \quad ?$$


RMS Cim

In this case, we haven't numerical cancellation.

Cim is UNDER HEAVY STRESS

$$I_{AC} = \sqrt{(I_0 \cdot \sqrt{D})^2 - I_0^2 D^2} = I_0 \sqrt{D - D^2}$$

$$= I_0 \sqrt{D(1-D)}$$

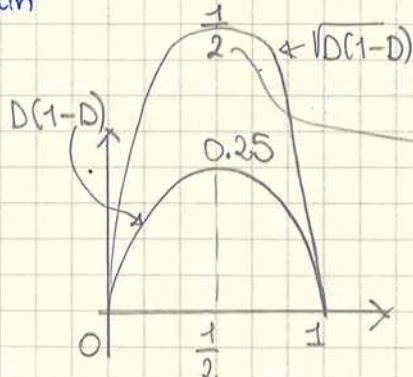


Bad news! Very strong stress for the Cim.

Suppose:

$$I_0 = 1,9 \text{ A}$$

$$\Delta i_L = 0,2$$

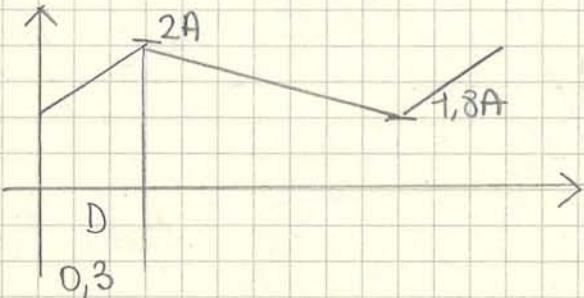

- $I_{CO} = \frac{\Delta i_L}{\sqrt{12}} = 57 \text{ mA}$
- $I_{Cim} \approx \frac{1}{2} I_0 \approx 0.95 \text{ A}$  !! VERY HIGH CURRENT


Cim VERY STRESSED

Without approximation:

$$1.9 \text{ A} \sqrt{0.3 \times 0.7} = 0.87 \text{ A}$$


D 1-D

Let's find now the stress of the diode:

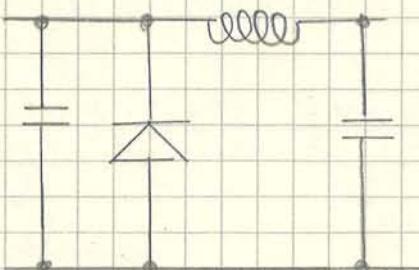

DCM has a larger average value than CCM. (with the same duty cycle).

If the load is very light :

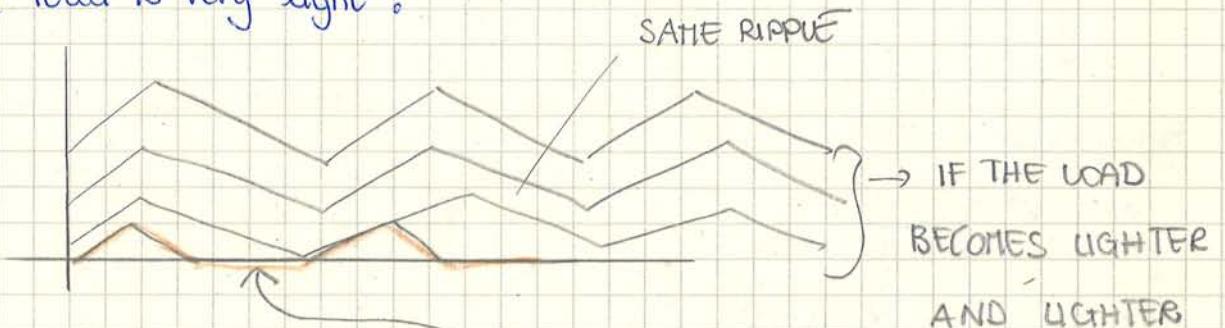


If I make the load still lighter  $\rightarrow$  DCM

- CCM HEAVY MODE
- DCM LIGHT MODE

(Also called in this way)

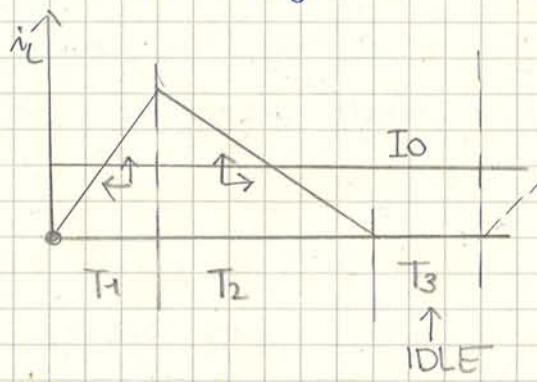If we want to analyze our circuit in DCM we have to consider :



$$\frac{V_{in} - V_o}{L} T_1 + -\frac{V_o}{L} T_2 = 0$$

$$\frac{V_o}{V_{in}} = \frac{T_1}{T_1 + T_2} \neq T_{SW}$$

$T_1 + T_2 < T_{SW}$  because of  $T_3$

So, we don't solve the problem and we need a II equation.

Idle is not useful because the circuit doesn't work in this time;  
we lose effectiveness.

1)  $M = \frac{V_o}{V_{in}} = \frac{T_1}{T_1 + T_2}$

ALWAYS

We decide how long is  $T_2$ ; but  
we don't know  $T_2$ .

In many cases we found a relationship between  $I_O$  and  $i_L$ .  $I_O$  is the DC component of  $i_L$ . So :

2)  $I_O = \frac{T_1 + T_2}{2 T_{SW}} \cdot \left( \frac{V_{in} - V_o}{L} \right) T_1 = \frac{V_o}{R}$

$i_{LMAX}$

(AREA SPREADS IT  
OVER ONE CYCLE)

AVERAGE OF  
 $i_L$

what  $D = 1$  mean? It means <sup>that</sup> the switch is closed all the time, does

$D$  is  $1 \rightarrow V_o = V_m$ . This means that we are not in DCM and the last equation found doesn't help me! (We are in CCM)


what happens if  $R \rightarrow \infty$  (I remove the load)?  $\frac{V_o}{V_m} = 1$ .

we are still in DCM because through inductor there is no current.

So the equation can be used.

M IS DIMENSIONLESS!

why we don't use buck converter in DCM?

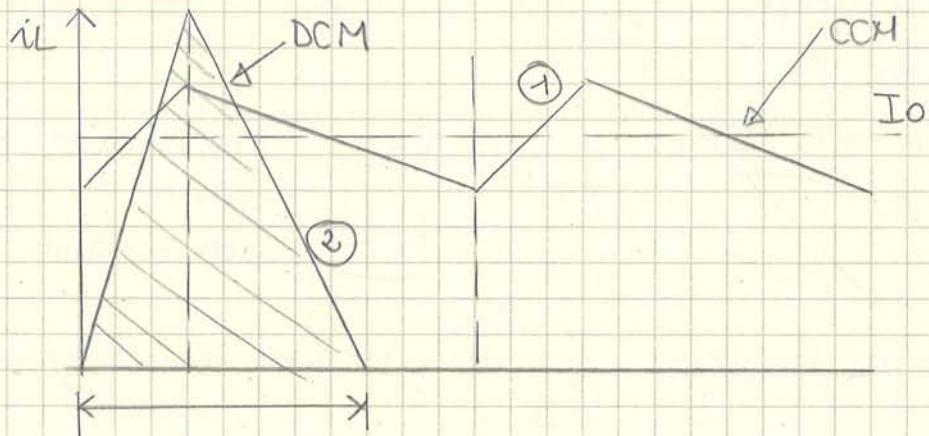

② Curve of DCM design @ same parameters of CCM.

① CCM

The average value in DCM is still  $I_o$ , but the peak is at least twice the peak of CCM (because we want to have the same area). This is a real strong stress for each component.

There is a possible advantage (but very very small):

$$L_{CRIT} = \frac{R(1-D)}{2f_{sw}}$$

CCM  $L > \frac{R_{max}(1-D_{min})}{2f_{sw}}$

DCM

$$L < \frac{R_{min}(1-D_{max})}{2f_{sw}}$$

$L_{DCM} < L_{CCM}$  ← ADVANTAGE OF DCM

$$V_o = \frac{V_{in} 2}{1 + \sqrt{1 + \frac{8L f_{sw}}{D^2} \frac{(V_o)}{(I_o)}}}$$

$\rightarrow R$

So, if we want to find the derivative we have to find out  $V_o$  and then find derivative


$V_o = f(f_{sw}, D, L, I_o)$  and then find out the output resistance

There is another way

① Numerically :


② Dini's Theorem

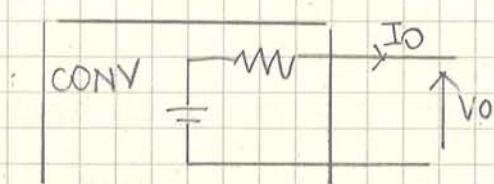Most of the time when we get the derivative we obtain a negative value of resistance  $R < 0$ . It means that :



$I_o \uparrow \quad \left. \begin{array}{l} R \text{ negative. Why?} \\ V_o \downarrow \end{array} \right\} \text{Sign convention.}$

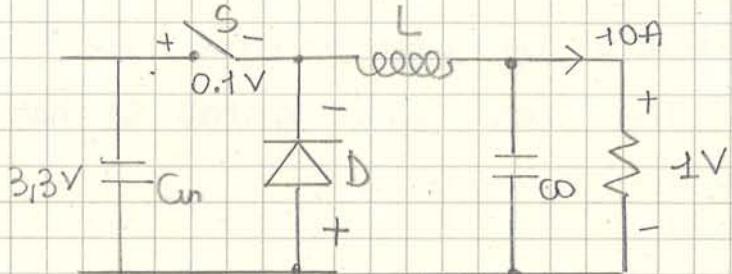
Let's consider a buck converter with some topological changes:





$$D = \frac{1V}{3,3V} = 0,3$$

maybe not! Because if  $V_o$  is so low the voltage drop at diode starts to be important. !


Let's suppose  $I_o = 10A$

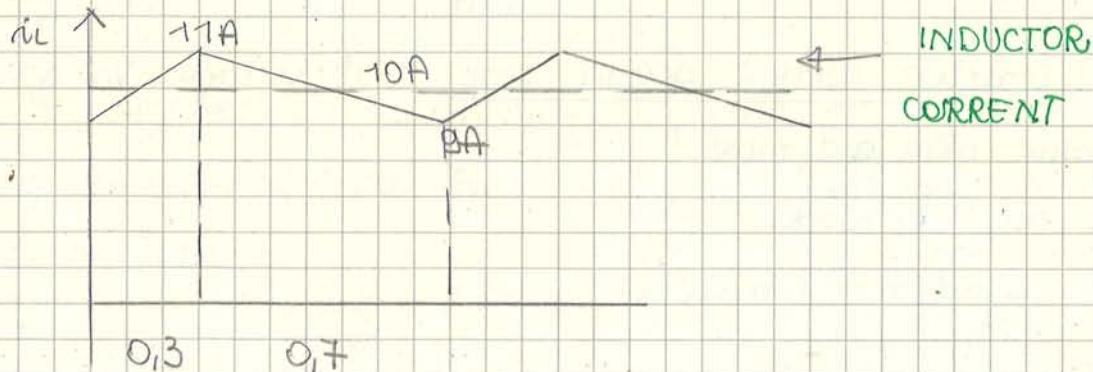

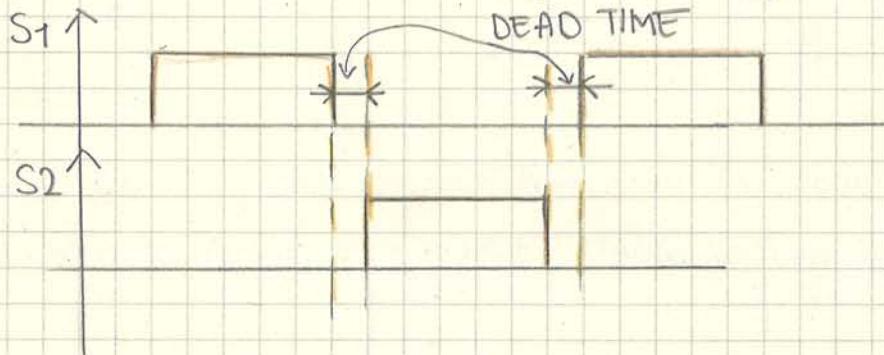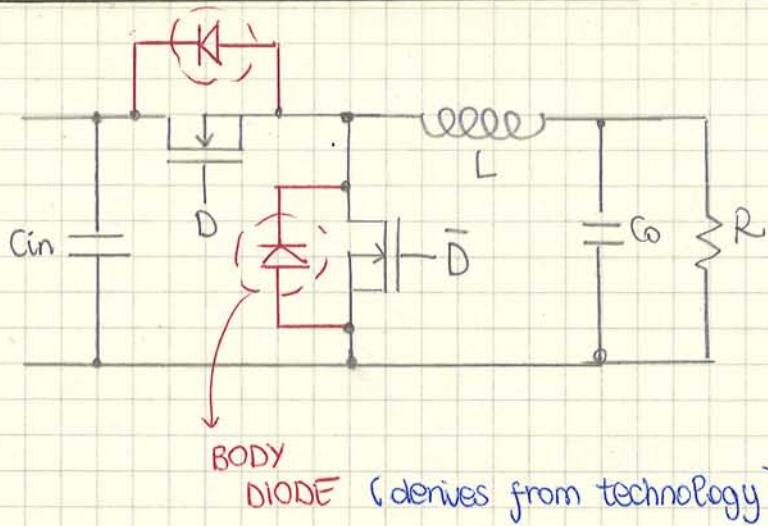

what happens in dead time? The current flows to the body diode and produces a voltage drop of  $\pm 1\text{V}$  but for a very short time!

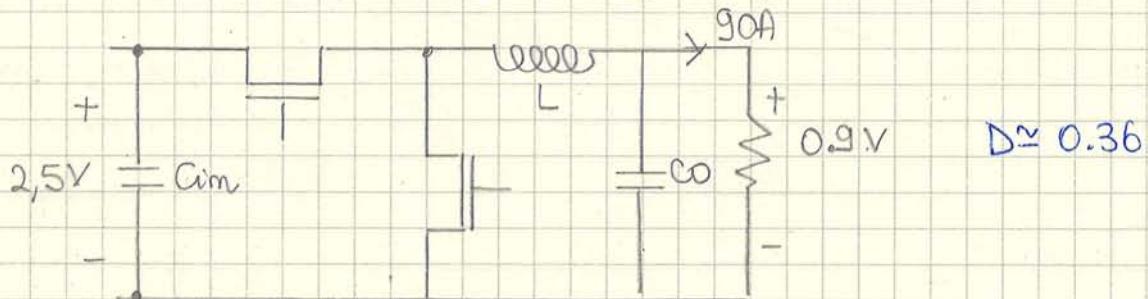On the other hands, let's try to design a buck like this:




The main problem is: how much current flows through  $C_{in}$ ? more or less 45 A. It's a lot! There are capacitors able to support this value but are large, expensive! And also L must carry 90 A!

Instead of having 1 converter able to support 90 A we can have 3 converters (30 A each) in parallel.

Smaller components, but 3 of them! In this way we reduce the stress.



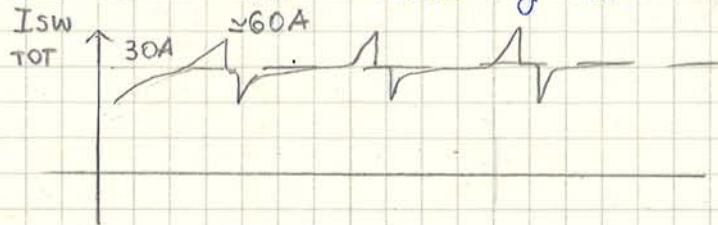if the switches conduct together  
So, the total current is something like this:



If I have D of 36% and we have 3 circuits together this overlap will be 0.03%.

The RMS value of this current is quite low because the duty cycle should be the D of DC component and D of the small parts  $\rightarrow$  OVERLAP.

So the RMS current through C is very reduced.


This is the way that uses motherboard to supply processors.  
This way is called MULTIPHASE. (low voltage very high current)

## BOOST (STEP UP)

$\frac{V_o}{V_{in}} \geq 1$  The output voltage is larger than the input voltage. (Yeah!)


The bad part is that it's very difficult to control it

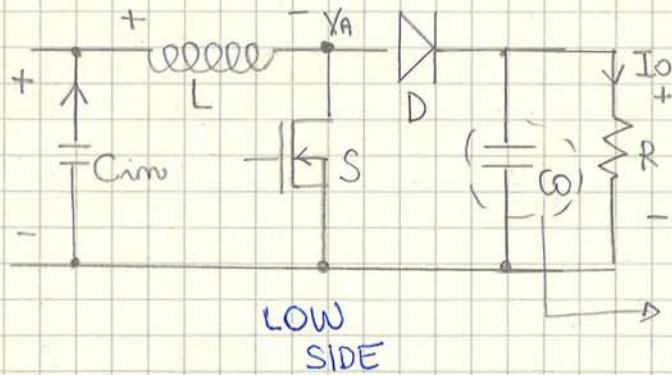In many cases (high power) we use other type of converter; but boost converter for example has many applications like mp3.



IN THIS CASE  $C_o$  IS A PART OF CIRCUIT.

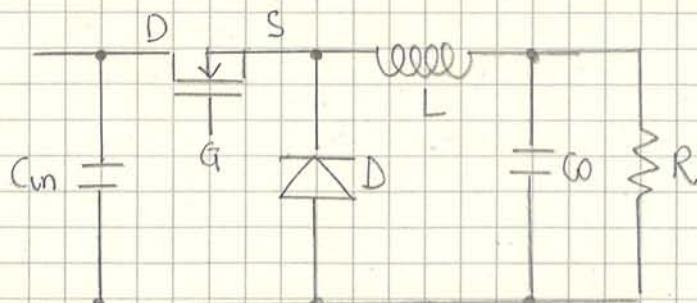Let's compare it with the buck converter:



With nMOS


- $T_{on} \rightarrow$  switch is closed; so the voltage drop on L is  $V_{in}$ . If we want to be more precise  $V_L = V_{in} - V_{sw} - V_{RES\_PAR}$

$\downarrow$   
of the wire



- $T_{off} \rightarrow$  through L the voltage drop is  $V_{in} - V_o - V_d$   
 $V_{in} - V_o$  is negative!

Deriving the other waveforms:

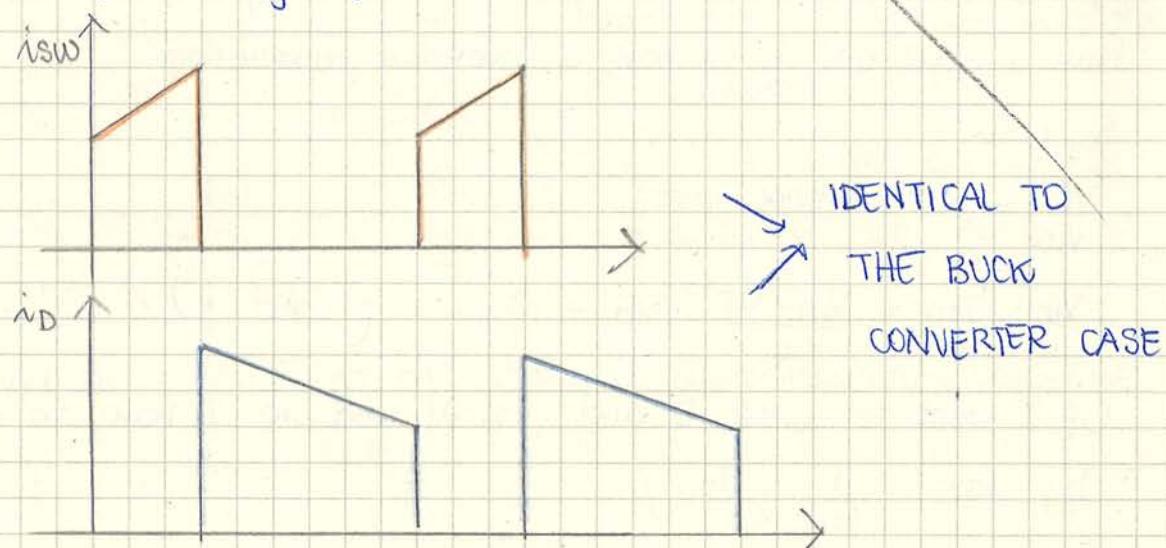


$i_{inm}$  and  $i_{co}$  are different.


If we want to be very precise, if  $V_{inm}$  is ideal,  $i_{inm} = 0$ ; but:



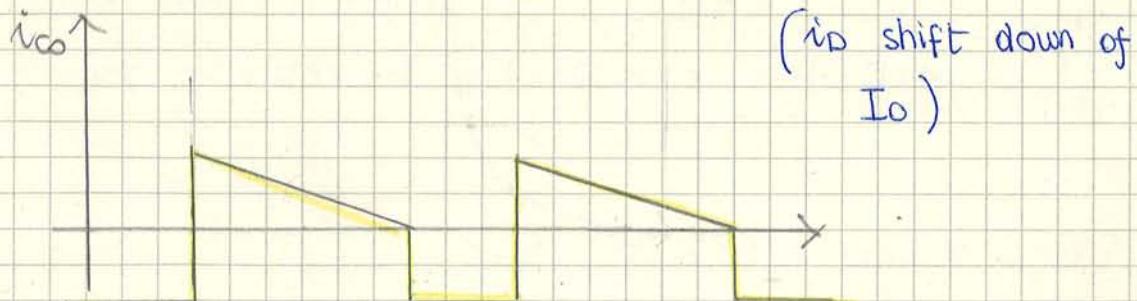And  $i_{co}$  that is the AC comp. of the current flowing to the diode:




Let's consider an ideal boost:

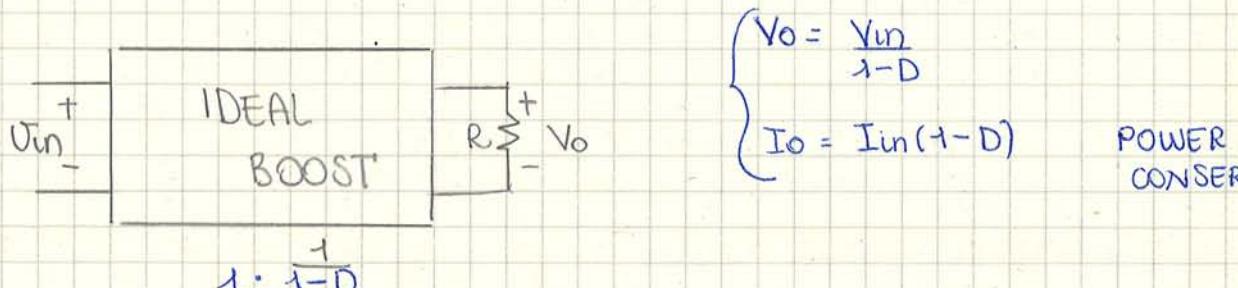

↑ like a transformer!

But let's consider for example one parasitic element (R<sub>IND</sub> of the wire),


I have:

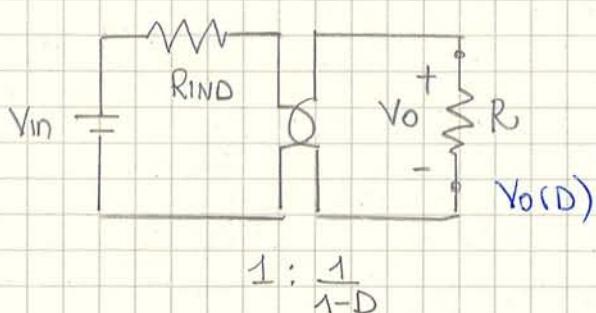

transformer that transform the DC component.

If D = 1 I have an infinite output voltage. No!

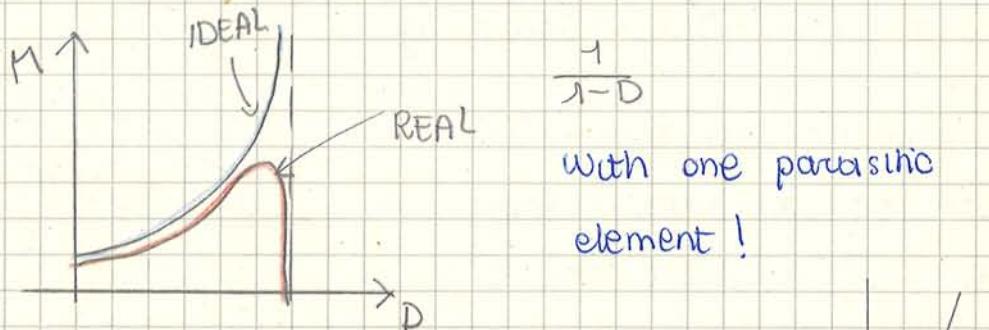If we find out V<sub>O(D)</sub> we get that it can't reach any value we want:



$$\frac{1}{1-D}$$

with one parasitic element!

In our boost converter we want to stay in this area:

where losses are not important yet.

So now we can find the three derivatives:

$$\bullet \quad \frac{\partial V_o}{\partial D} = \frac{\partial}{\partial D} \left( V_{in} \cdot \frac{1}{1-D} \right) = \frac{V_{in}}{(1-D)^2} \cdot (+1) = \frac{V_{in}}{(1-D)^2}$$

If I want to express it if function of V<sub>O</sub>

$$\left( \frac{V_o}{V_{in}} = \frac{1}{1-D} \right)$$

$$= \frac{V_o}{1-D} = V_o \cdot \frac{V_o}{V_{in}} = \frac{V_o^2}{V_{in}}$$

→ If V<sub>O</sub> is constant I can see what happens if V<sub>in</sub> changes.

Boundary condition:

$$\underbrace{I_{min} = 0}_{\sim} \Rightarrow \frac{\frac{V_o}{R(1-D)}}{2f_{sw}} = \frac{D(1-D)V_o}{2f_{sw}L}$$

- fsw degree of freedom

- D :  $M = \frac{1}{1-D} \rightarrow D = \frac{M-1}{M}$  → IT'S A CONSTRAIN !

- R is a constrain of the customer.


So, fixed fsw we can derive L : (or the contrary).

$$L_{CRIT} = \frac{D(1-D)^2 R_{MAX}}{2f_{sw}} \rightarrow CCM$$

$L > L_{CRIT}$	CCM
$L < L_{CRIT}$	DCM

And what about D?  $D_{max}$  or  $D_{min}$ ? What is the worst case?

(DCM is good for low power application)

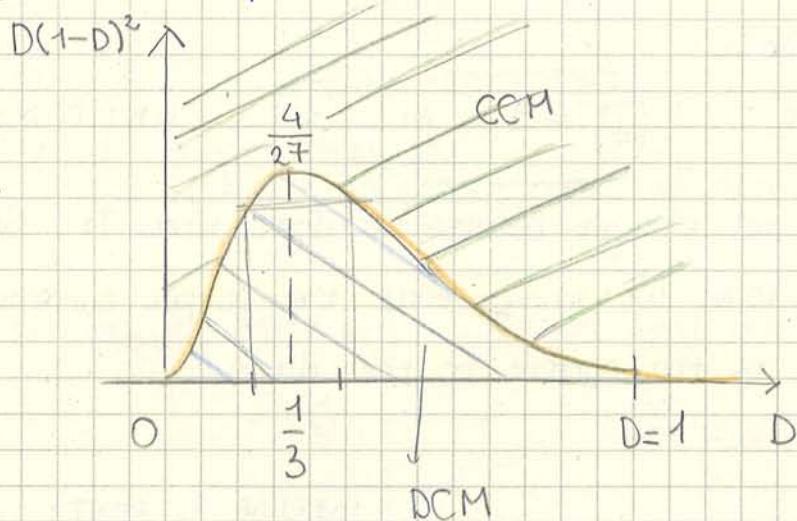

So, we have  $L_{CRIT} = \frac{D(1-D)^2 R}{2f_{sw}}$

If we want  $\frac{V_o}{V_i} > 1$  we have to stay in DCM. BUT in this mode the stress is very high, it's not respecting CCM and so we have to use it in low power voltage. If we need a large power we need to use other topology.

Now analyze the boost converter in DCM.

So we obtain :

$$\frac{M}{R} = \frac{1}{2} \frac{D}{L} \frac{T_1}{M-1} \quad \left( \frac{D}{L_{fsw}} = T_1 \right)$$

$$M(M-1) = \frac{1}{2} R \frac{D^2}{L_{fsw}}$$

$$M^2 - M - \frac{RD^2}{2L_{fsw}} = 0$$

LARGEN THAN 1

$$M = \frac{1 \pm \sqrt{1 + \frac{2RD^2}{L_{fsw}}}}{2}$$

I can't take the negative sign

because the second quantity is larger than 1.

NB: In every DCM mode  $M$  depends on  $R$  ! This means that it's not an ideal voltage source (like CCM mode).


So we can evaluate the derivatives:

- $\frac{\partial V_o}{\partial V_{in}} = M$

- $\frac{\partial V_o}{\partial I_o} \neq 0 < 0$  OUTPUT RESISTANCE


$$\left( \frac{V_o}{V_{in}} = \frac{1 + \sqrt{1 + \frac{2V_o D^2}{I_o L_{fsw}}}}{2} \text{ and we derive } \frac{\partial V_o}{\partial I_o} \dots \right)$$

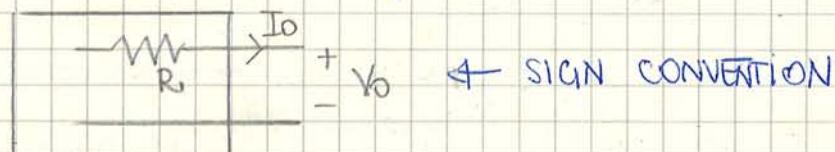It's not a negative resistance! It's just found out with these signs:



- $\frac{\partial V_o}{\partial D} = \text{GAIN} (V_{in}, R, D, \dots)$

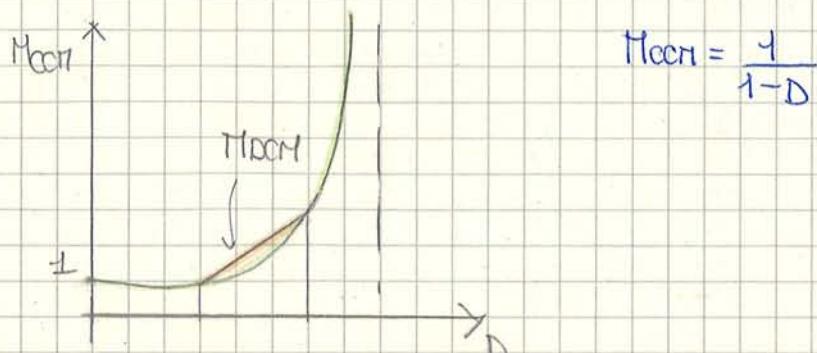
Let's see what happens if I want to compare the  $M$  in CCM and the  $M$  in DCM



Unfortunately our circuit is not protected by S.C.


If the switch is opened there is a current that flows into the circuit. So we have no protection. Not good!

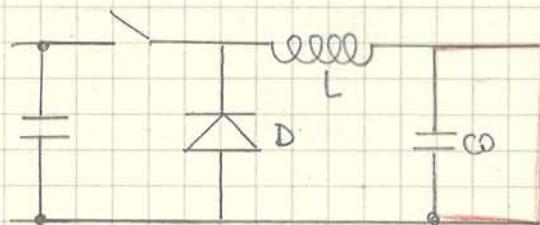For the buck converter is totally different:




If we have a S.C at the output we can open the switch and we isolate the input from the short.

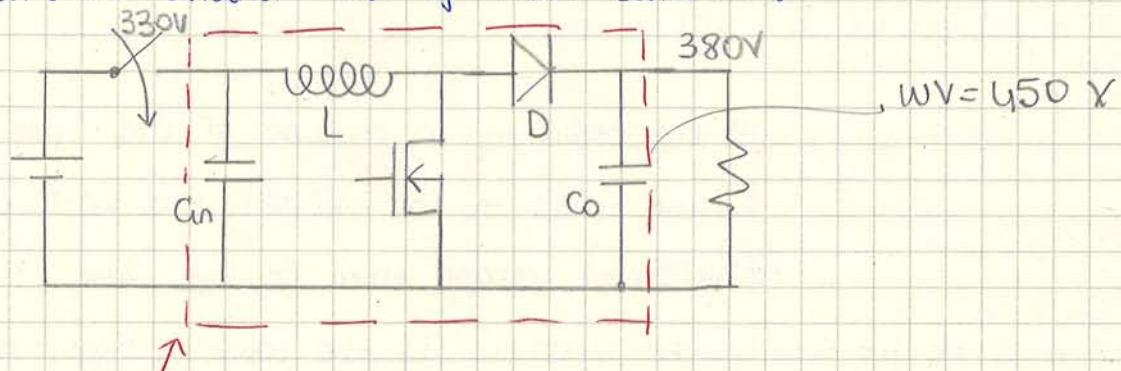
Let's consider another issue of boost converter:



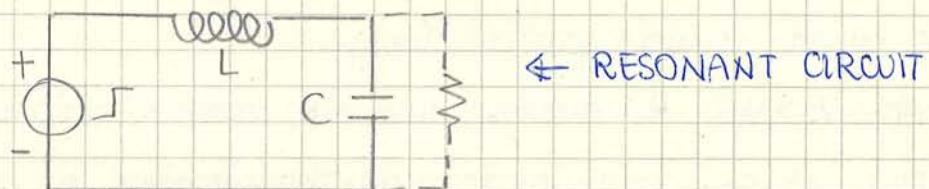
We apply a voltage step  $\Delta$  to this circuit:



And at capacitor voltage:

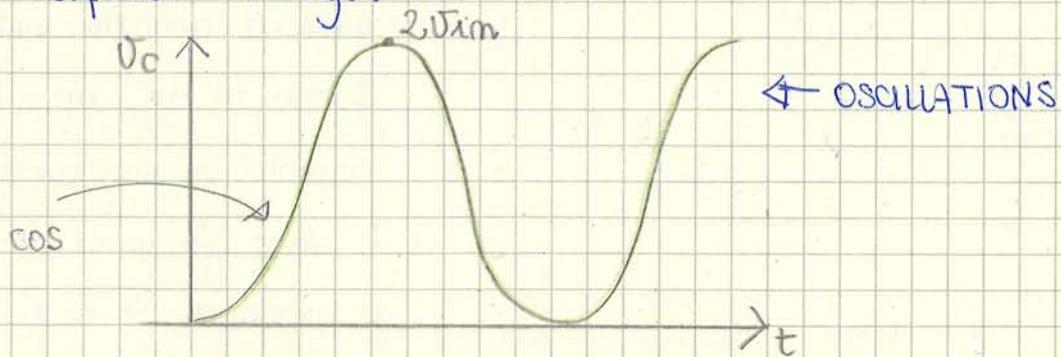

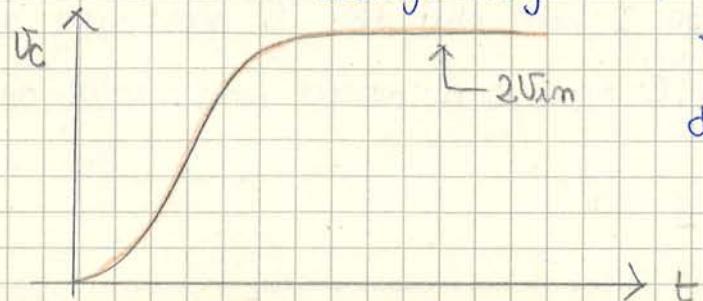
But we have diode and the voltage stays at  $2V_{im}$ :



The capacitor doesn't discharge.


When it is HOT, the resistance of this component goes down and its power is negligible.

A second solution used for large power :

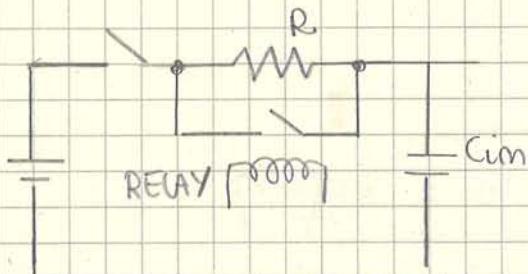

RELAY  $\rightarrow$  I can close and open the switch. But this costs.  
If our converter works with many loads, we have to wait in order to relay works.

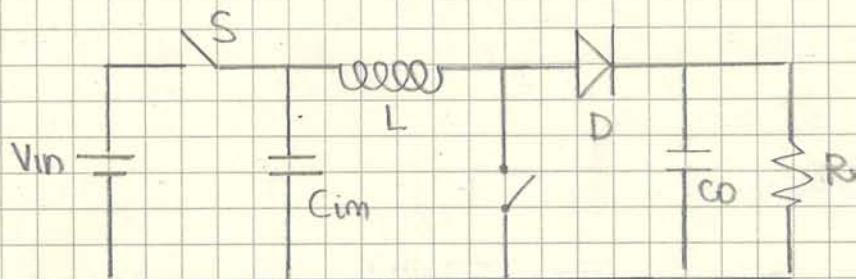There is another way to avoid the over voltage at the output side.



$$\sqrt{LC} \approx \tau$$


TIME CONSTANT  
OF THE PULSE

$$\tau \gg T_{SW}$$

$T_{SW} = 200 \text{ KHz}, 5 \mu\text{s} \rightarrow \tau$  must be of the order of 50 ms


It means that the current goes up forever and when switch is opened we have a saturation of L and  $C_0$ !

Let's make some changes:

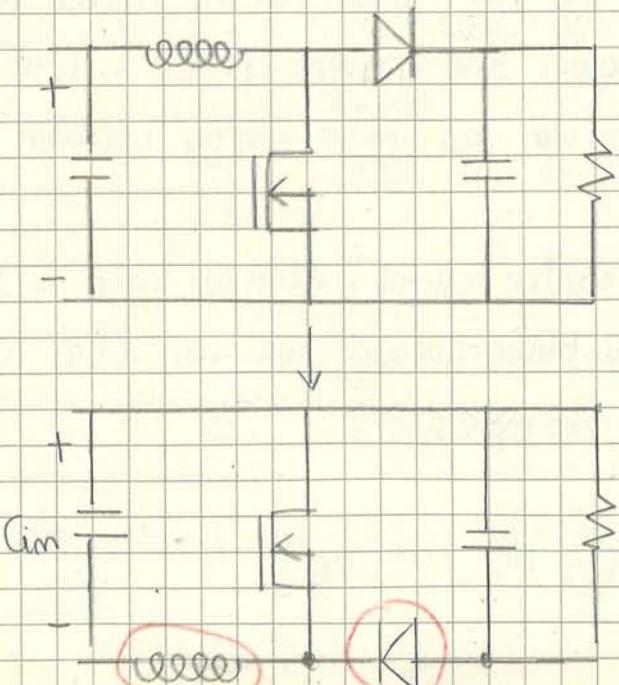


I have to move both!  
But it's not a good idea!  
The output voltage is always the same.

Or:

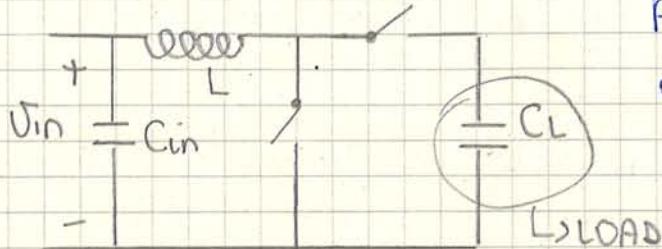


A boost converter only for charging or discharging a capacitance.

Or:

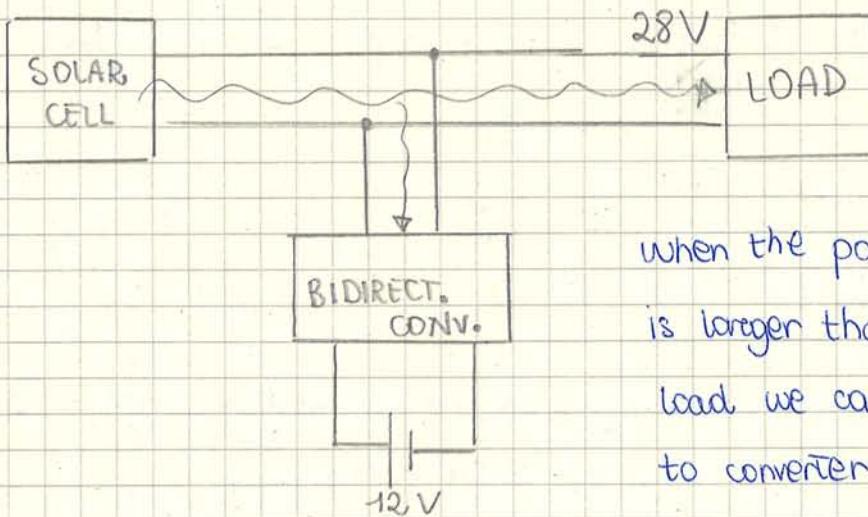

when the power of solar cell is larger than the power of the load we can have a flow power to converter.

One question:

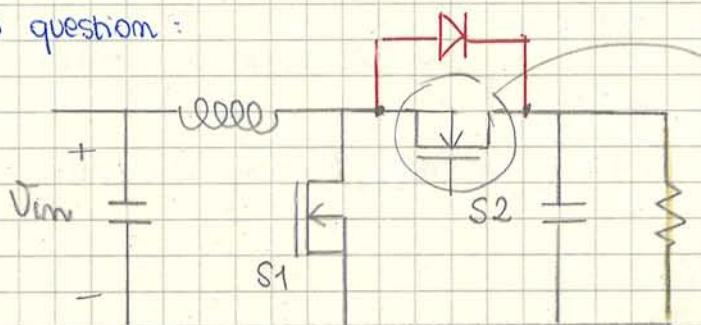

If I open this switch can I handle a s.c. to the output? No! Because of body diode

I closed

IDEAL SWITCH

V opened

nMOS SWITCH  $\rightarrow$  current both directions

VOLTAGE only one direction

I

SCR (we can't switch it off until current goes to zero)

V

For having an ideal switch behaviour we can have 2 nMOS in series :


What is the disadvantage of the inverter?

During  $\sqcap$  we have a period of time which both of MOS conducts at the same time (CROSS-CONDUCTION or SHOOT-THROUGH). So we need to apply some kind of delay.

However, most of the time I prefer to use nMOS transistor because they have better electrical characteristics of pMOS transistor.


pMOS has  $L$  larger than nMOS because of mobility.


Let's come back to boost converter:

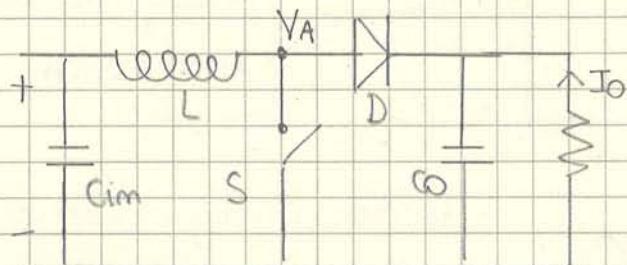


Let's find the waveforms.

• CCM

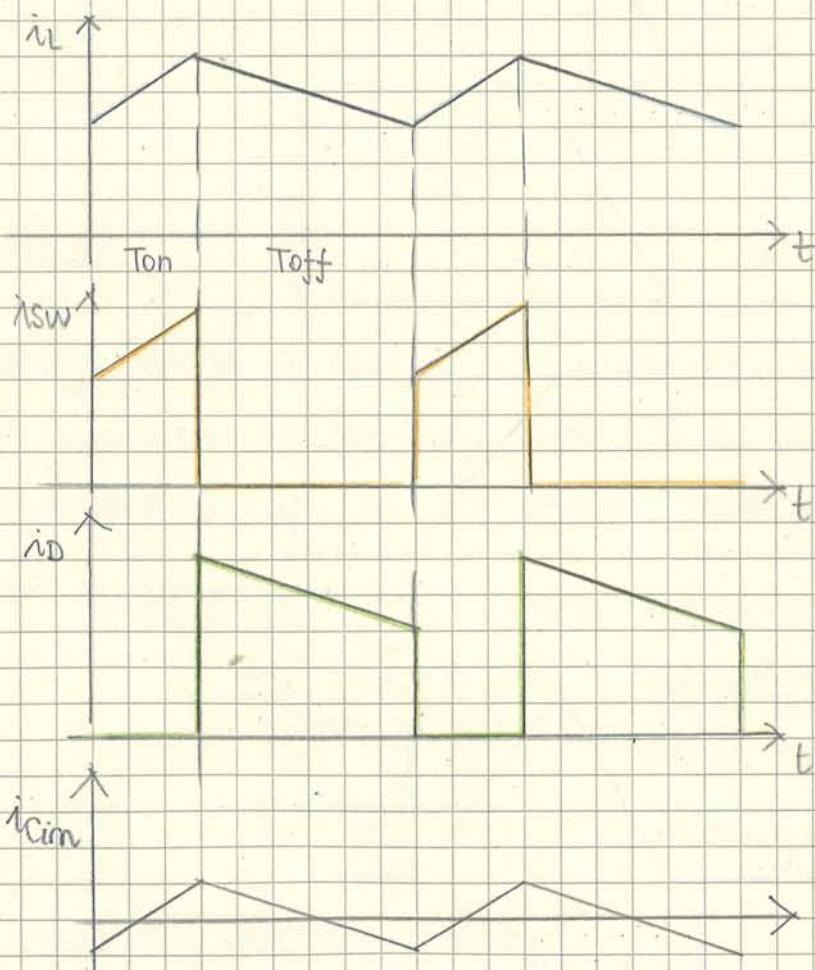

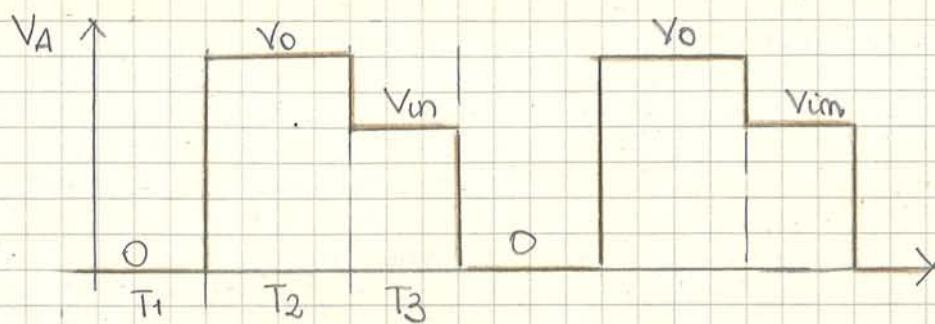


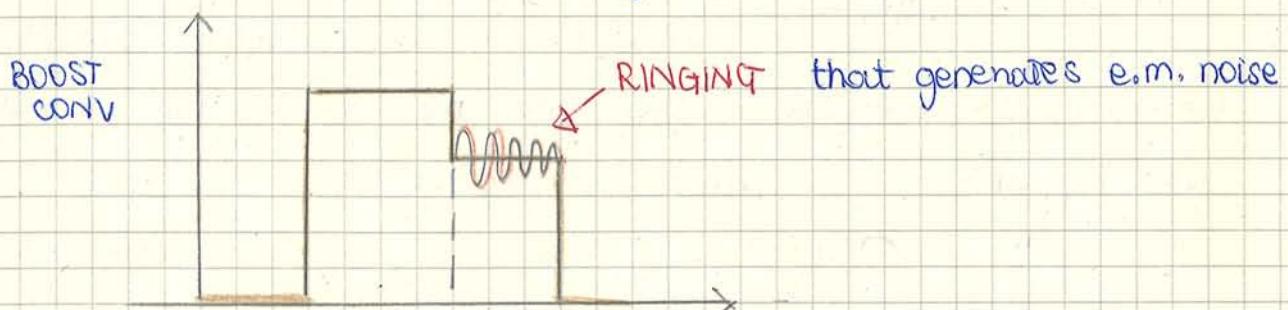We saw this waveform: (like any converter)



How is this ringing generated?


Switch and diode open:

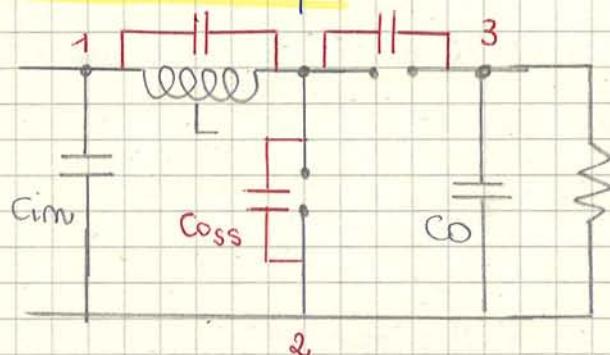

PARASITIC CAPACITANCE

All these 3 paras. caps are in parallel.

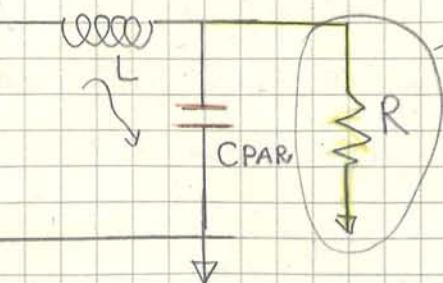The voltage across a cap is not important. What is important is the variation voltage. So node 3 is constant (like 2 and 1). So the 3 caps are in parallel and give me a resonator:




For avoid this oscillation we put a resistor (in parallel) But it takes a lot of DC component

So we have an important quantity :

$$f_{RES} = \frac{1}{2\pi\sqrt{LC}}$$

→ RESONANCE FREQUENCY

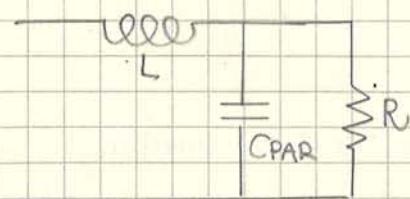


$$Z_0 = \sqrt{\frac{L}{C_{PAR}}}$$

And now we can find R:

$$Q = \frac{Z_0}{R} \quad \text{OR} \quad Q = \frac{R}{Z_0} \quad ? \quad \text{Are both correct.}$$

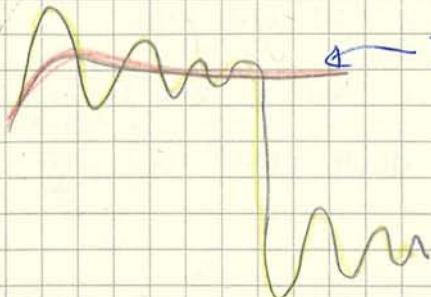if in my circuit  $R \rightarrow \infty$ ,  $Q \rightarrow \infty$  and then:  $Q = \frac{R}{Z_0}$




I want a Q something like this

$$\text{So } Q = 0,7 \rightarrow 1$$

and I derive R.

$\hookrightarrow$  that is  
R<sub>sn</sub>

But I have a capacitor in series:

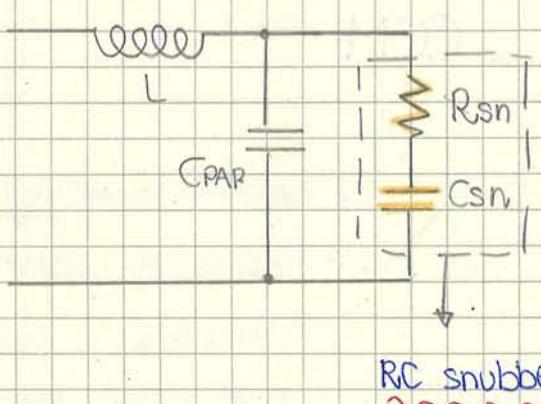


3<sup>rd</sup> order circuit

For minimize loss power.


- If  $C_{sn} \rightarrow 0$ ,  $R_{sn}$  doesn't work ;

- If  $C_{sn} \rightarrow \infty$  ( $C_{sn}$  SC) and so I have DC power dissipation.

$$C_{sn} = 6 \rightarrow 8 C_{PAR}$$

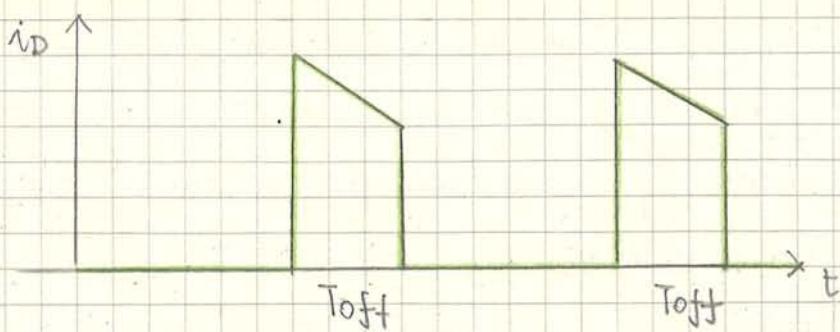


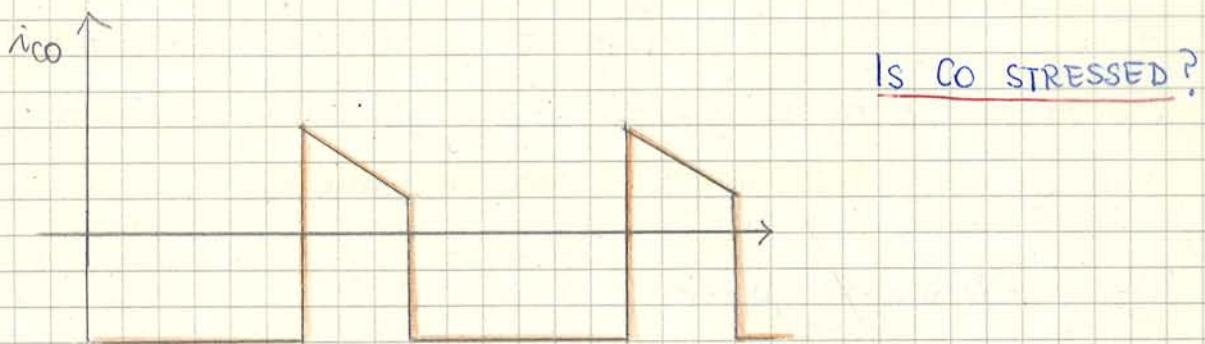what is  $i_{CO}$  current? It's the current through the diode minus the DC component.




The current through  $C_O$  has not a small oscillation! It's an impulsive current exactly like the one of the boost converter. So  $C_O$  is under heavy stress.

what about  $C_{im}$ ?

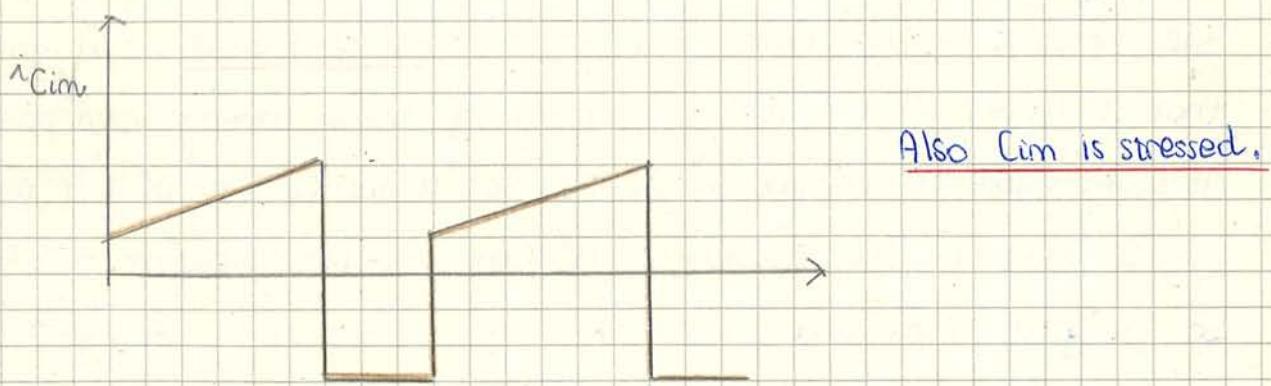

And  $V_A$ ?

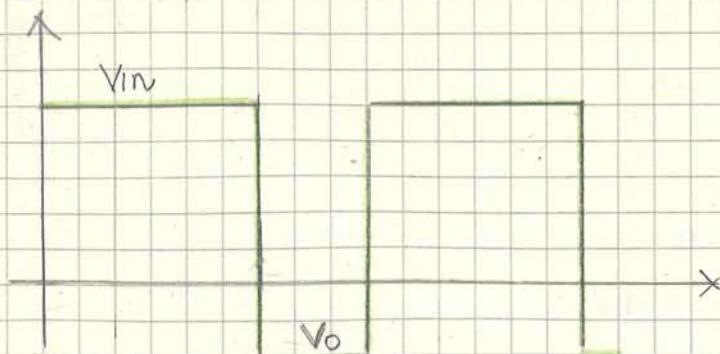

$$\left\{ \begin{array}{l} I_{MAX} - I_{min} = \frac{V_{in}}{L} \cdot T_{on} = - \frac{V_o}{L} \cdot T_{off} \\ OR \\ \frac{V_o}{R} = - \bar{i}_D = - \frac{I_{MAX} + I_{min}}{2} \end{array} \right.$$

Because we need  $I_{MAX} - I_{min}$   
(e' lo wche ci vu)

↓  
the direction is opposite!

$$\left\{ \begin{array}{l} I_{MAX} - I_{min} = - \frac{V_o}{f_{sw} L} (1-D) \\ I_{MAX} + I_{min} = - \frac{2V_o}{R(1-D)} \end{array} \right.$$

$$I_{MAX} = - \frac{V_o}{R(1-D)} - \frac{V_o(1-D)}{2f_{sw}L}$$

$$I_{min} = - \frac{V_o}{R(1-D)} + \frac{V_o(1-D)}{2f_{sw}L}$$

$$I_{min} = 0 = - \frac{V_o}{R(1-D)} + \frac{V_o(1-D)}{2f_{sw}L}$$

What are my degrees of freedom?  $f_{sw}$  and  $L$ . We usually choose  $f_{sw}$  and then find out  $L$ . (Remember that  $|V_o|$  can be  $>$  or  $<$  than  $V_{in}$ !).

So:


$$L_{CRIT} = \frac{R(1-D)^2}{2f_{sw}}$$

→ it's a monotonic expression; if  $D \uparrow$ ,  $L \downarrow$ , always!

CCM →  $L > L_{CRIT}$

DCM →  $L < L_{CRIT}$  →  $L < \frac{R_{min}(1-D_{MAX})^2}{2f_{sw}}$


Now consider:

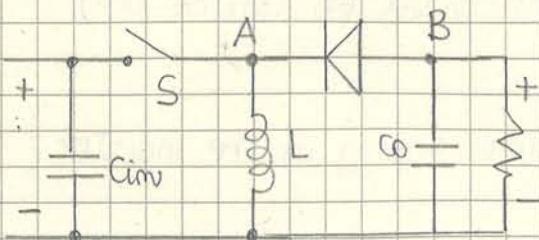


We can use quadratic KCL for both A and B. (Because we don't have smooth current).

Then :

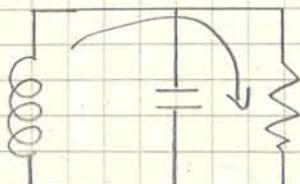
$T_{off}$  → SWITCH OPEN, AND THE ENERGY STORED INSIDE INDUCTOR MOVES TO THE OUTPUT (and input is disconnected)



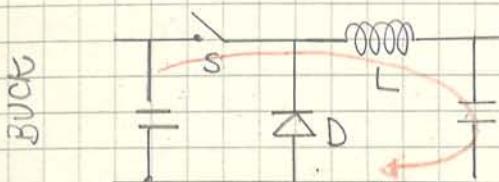It's different for buck and boost converter :



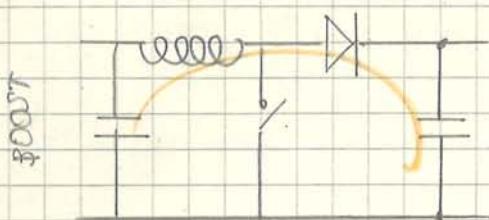During Ton we put energy to inductor  
but at the same time energy goes to  
the output !




Same story for this.

Buck and boost converter are called DIRECT CONVERTER.

On the other hand, in a buck-boost converter we have 2 separate phases : charge and store energy and then deliver energy → INDIRECT CONVERTER.

L CHARGING

$$\mathcal{E}_L = \frac{1}{2} L I^2$$

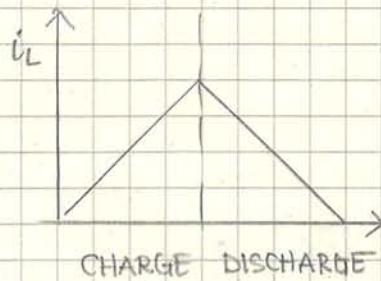

NB: we have to use the maximum current because the energy is given by peak current.

$$\text{So: } \mathcal{E}_L = \frac{1}{2} L \left( \frac{V_{in} \cdot T_{on}}{L} \right)^2 = \frac{1}{2} \frac{V_{in}^2 D^2}{L f_{sw}} = \frac{V_{in}^2 D^2}{2 L f_{sw}^2}$$


ENERGY STORED IN L IN ONE CYCLE

Instead of  $\frac{V_{in}}{V_0}$ :

$$\frac{\Delta V_0}{\Delta I_0} = - \frac{D^2 R^2}{2 f_{SW} L} \cdot \frac{2 f_{SW} L}{D^2 R} = -R$$

$$\frac{1}{\pi^2}$$

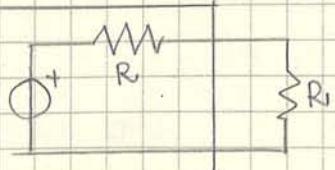The internal resistance of our converter is equal to the load resistance?




Is this means that the efficiency is 50%?


In circuit theory yes; but on the other hand if we reduce  $R_{int}$  we can increase efficiency. But how can it be possible? They are equal, we derive it!

$R_{int} = R$  comes out from a derivative; it's a DIFFERENTIAL RESISTANCE, not linear! It has nothing to do with power dissipation.

Let's go back to DCM mode:

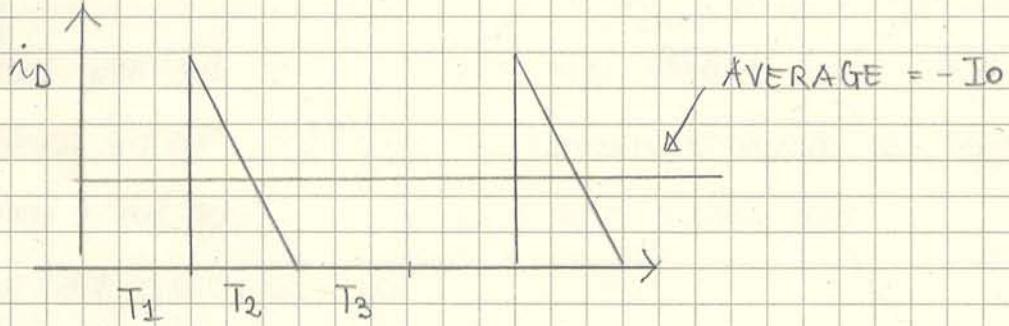

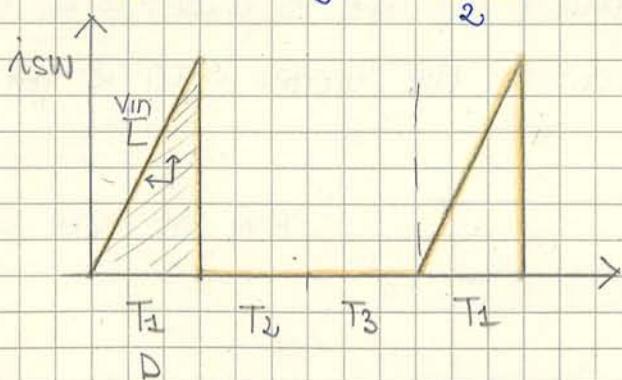How can we find average?  $\frac{T_2 \cdot I}{2}$



from DC current coming input  
 $i_{SW} = T_1 \cdot \frac{V_{in}}{L} \cdot \frac{T_1}{2} \cdot \frac{1}{T_{SW}} =$

$$= \frac{V_{in} D^2}{2 f_{SW} L} \quad (\textcircled{A}) \text{ EQ}$$


Why it's called buck-boost converter?

It's a merge of buck and boost.


Let's consider a buck followed by boost.

How can we go from this topology to the standard one?

During Ton:

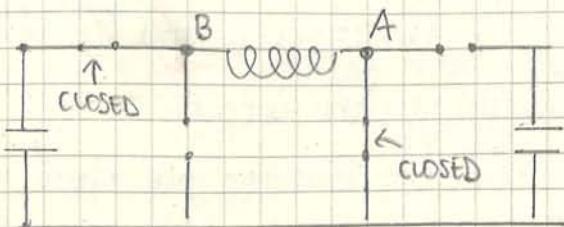


During Toff:

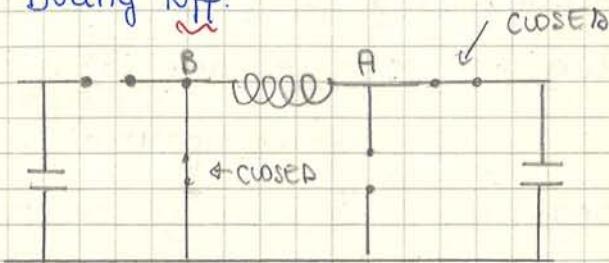

Energy stored from input to L

During Ton A is connected to the ground; during Toff B is connected to ground.

So we can re-draw the circuit like this:

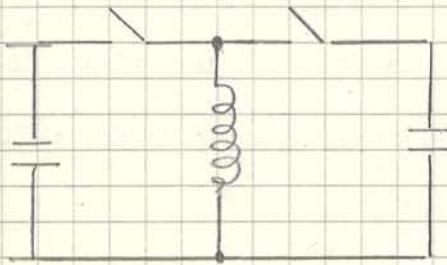


### STANDARD BB CONVERTER

The difference between the previous circuit is that L, now, doesn't flip up and down. And this means that  $V_o$  has negative sign respect  $V_{in}$ .

And what about the boost-buck?

### CUK CONVERTER

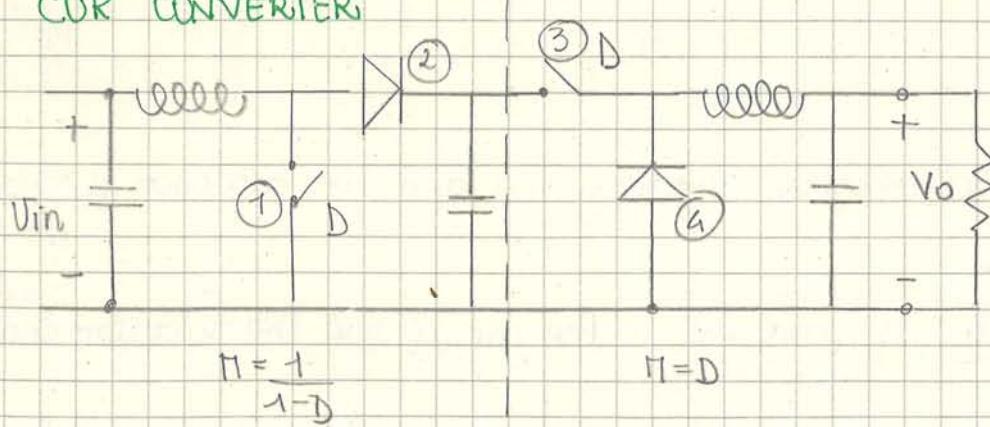

$$M_{TOT} = \frac{D}{1-D}$$

$V_o$  has the same sign of  $V_{in}$ .

Both of input and output currents are smooth current. However, it's a sort of boost, so it's difficult to drive.


We have 2L, 4 switches and the capacitor doesn't care

Good news: the two inductors can be done on the same magnetic core.

Bad news: it's complicated to do.

## OVERVIEW OF DIFFERENT TOPOLOGIES


BUCK

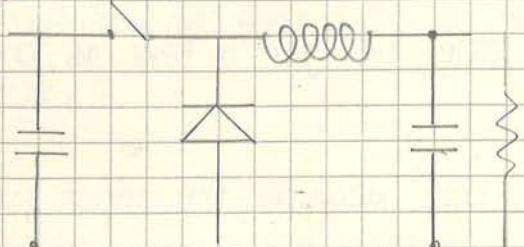

- Cin STRESSED, Co NOT STRESSED
- OVERVOLTAGE: NO SURVIVE
- OUTPUT SC: OK
- CL: OK (There is the switch)
- SOFT START: OK

(D)


BOOST

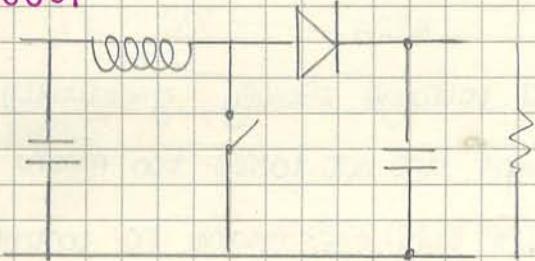

- Cin UNSTRESSED, Co STRESSED
- OVERVOLTAGE: survive
- OUTPUT SC: NO
- CL: NO
- SOFT START: NO

$\frac{1}{1-D}$


BUCK-BOOST

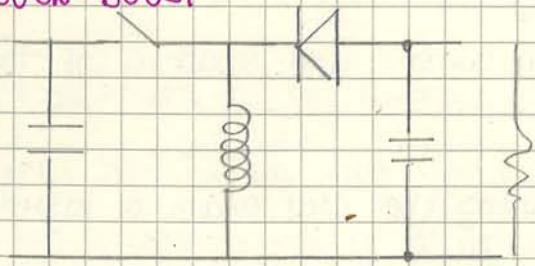

- Cin STRESSED, Cout STRESSED
- OVERVOLTAGE: NO SURVIVE
- OUTPUT SC: OK
- CL: OK
- SOFT START: OK

$\frac{D}{D-1}$


CUK

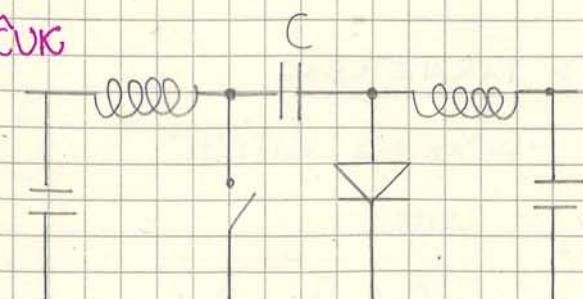

- Cin UNSTRESSED, Co UNSTRESSED
- OVERVOLTAGE: SURVIVE
- OUTPUT SC: C is like an open circuit, so OK
- CL: NIH...OK
- SOFT START: OK

$\frac{D}{D-1}$

In DCM :

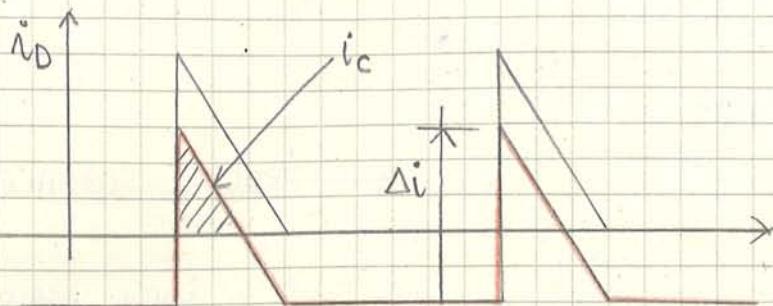

If the cap is electrolytic I have to specify the ESR to control the output ripple :

$$\boxed{V_{\text{OUT}} \text{ RIPPLE PP} = \Delta i \cdot \text{ESR}}$$

What about if I use a film or ceramic caps? ESR is not a issue.

So I need to specify C:

$$\frac{\Delta V}{\text{RIPPLE}} = \frac{\Delta Q}{C} \quad \text{AREA} \quad \left( \begin{array}{l} \text{IN CCII} \\ \text{BUCK} \end{array} \right) \quad C = \frac{\Delta i L}{\Delta V_c \cdot 8 f_{SW}}$$

## ELECTROLYTIC CAP




$$C = \epsilon \frac{A}{d}$$

$$\epsilon_{\text{AIR}} \approx 1$$

$$\epsilon_{\text{PLAST}} \approx 2 \div 2,5 \quad (\text{depends on plastic})$$

(water has a big dielectric constant.) There are some ceramic materials that have a big value of  $\epsilon_r$ .

Let's take a foil of aluminium :

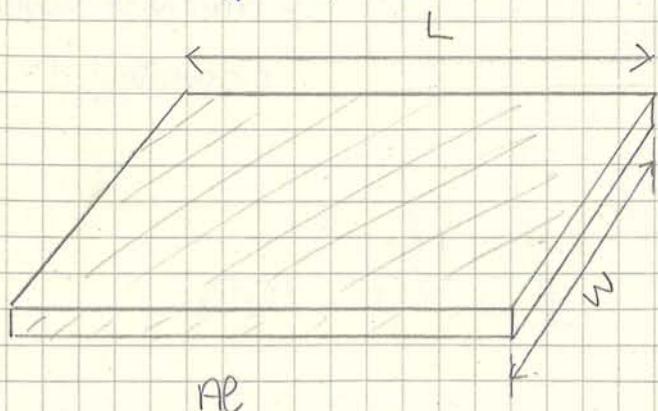

If we use this foil for doing capacitor, we compute the area as :  $W \cdot L$ .  
we discover that it is low

How can we have more area? We can stretch it.


why electr. cap has a positive and negative sign?

$\text{Al}_2^+ \text{O}_3^- \rightarrow$  The down side must be positive and the other side negative

→ In order to have this we want that the oxygen must be on the  
Aluminum oxide.

If we reverse the polarity the cap is destroyed.

Tantalum caps are similar:

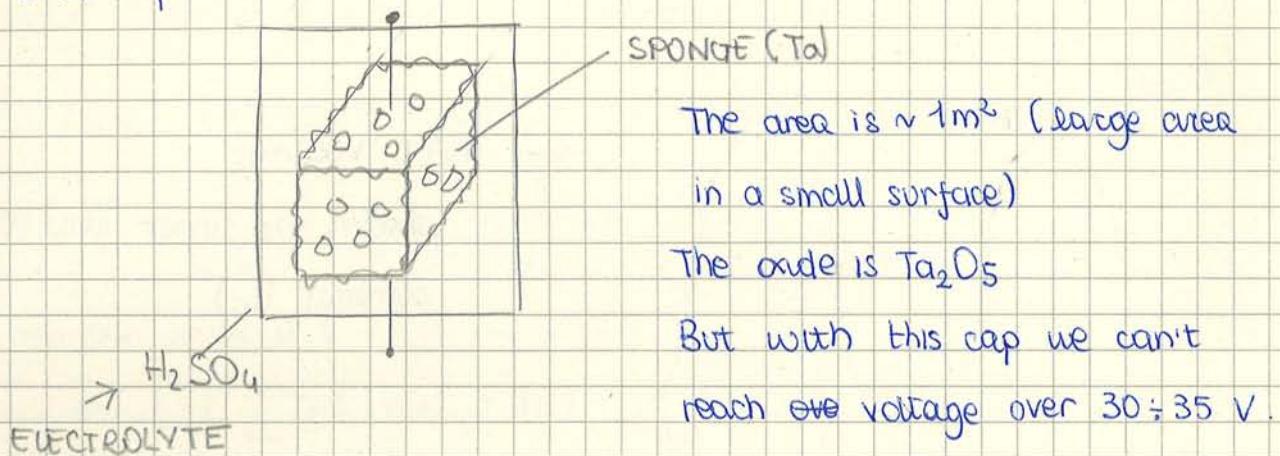

$$v(t) = V_{PK} \cos(\omega t) \rightarrow 2\pi \cdot 50 \text{ Hz}$$

$i_c$  is a periodic waveform and we can use Fourier series:

$$i_t = \sum_{n=1}^{\infty} I_{nPK} \cos(n\omega t + \phi_n) \leftarrow \text{INPUT CURRENT}$$

$$I_{RMS}^2 = \frac{1}{T} \int_0^T i(t)^2 dt \quad \leftarrow \text{we measure with the scope}$$

OR:

$$I_{RMS}^2 = \frac{1}{T} \int_0^T \left( \sum_{n=1}^{\infty} I_{nPK} \cos(n\omega t + \phi_n) \right)^2 dt$$

We have  $(\omega t \ 2\omega t \ 3\omega t \ \dots) \times (\omega t \ 2\omega t \ 3\omega t \ \dots)$

$$(\cos(2\omega t))^2 = \frac{1 + \cos 4\omega t}{2}$$

So we can write it:


$$= \frac{1}{T} \int_0^T \sum \cos(n\omega t + \phi_n) + \frac{1}{2} (- - -)$$

So now swapping:

$$\sum \frac{1}{T} \int_0^T (I_j I_k \cos(n\omega t) + \frac{1}{2} I_{nPK}^2) dt \rightarrow = 0$$

the RMS current is given by the sum of all harmonics.
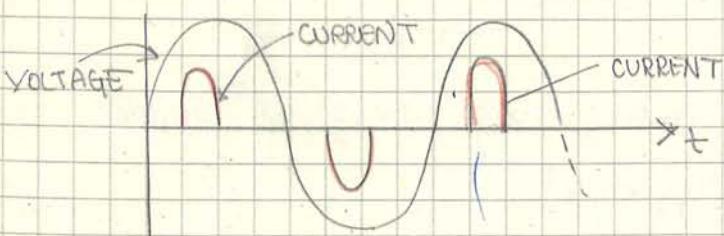
$$I_{RMS}^2 = \sum \frac{1}{T} \int_0^T \frac{1}{2} I_{nPK}^2 dt = \sum_{n=1}^{\infty} \frac{1}{2} I_{nPK}^2$$





$$\begin{cases} V_{PK} \cos \omega t = v \\ \sum I_{nPK} \cos(n\omega t + \phi_n) = i \end{cases} \rightarrow \text{we can find the average power}$$

AVERAGE POWER

$$\bar{P} = \frac{1}{T} \int_0^T v \cdot i dt = \frac{1}{T} \int_0^T V_{PK} \cos \omega t \cdot \sum I_{nPK} \cos(n\omega t + \phi_n) dt$$



$$= \frac{1}{T} V_{PK} \int_0^T \cos \omega t \sum_{n=1}^{\infty} I_{nPK} \cos(n\omega t + \phi_n) dt =$$

## THREE-PHASE SYSTEM

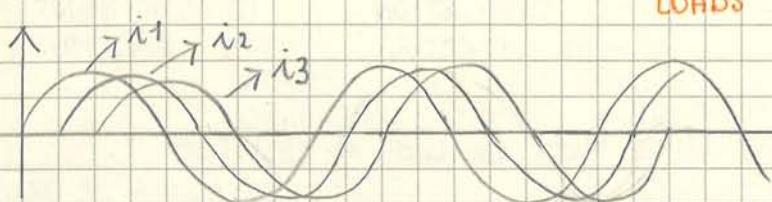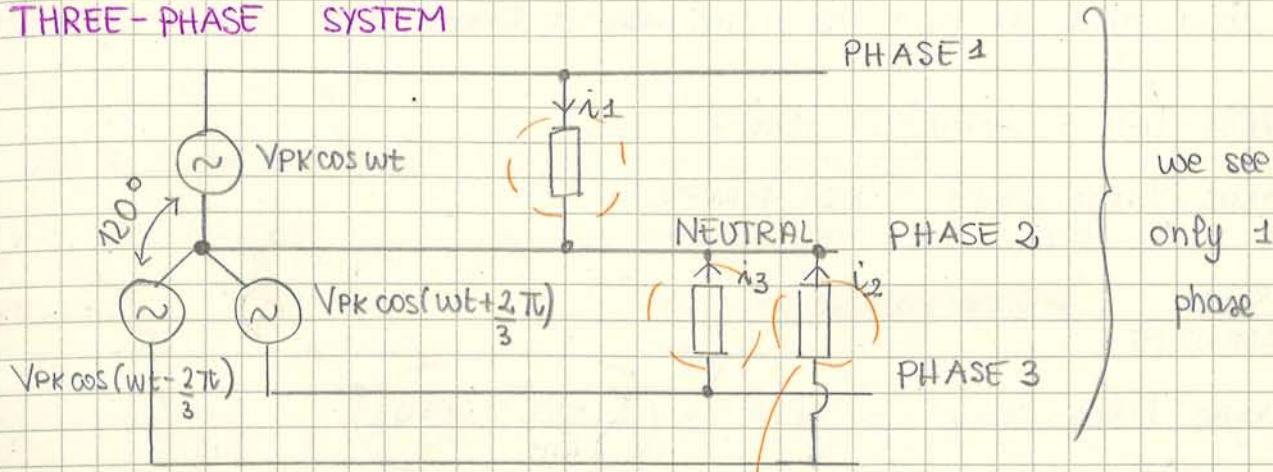

If we sum these currents  
they cancelled out  
(in the node of neutral)

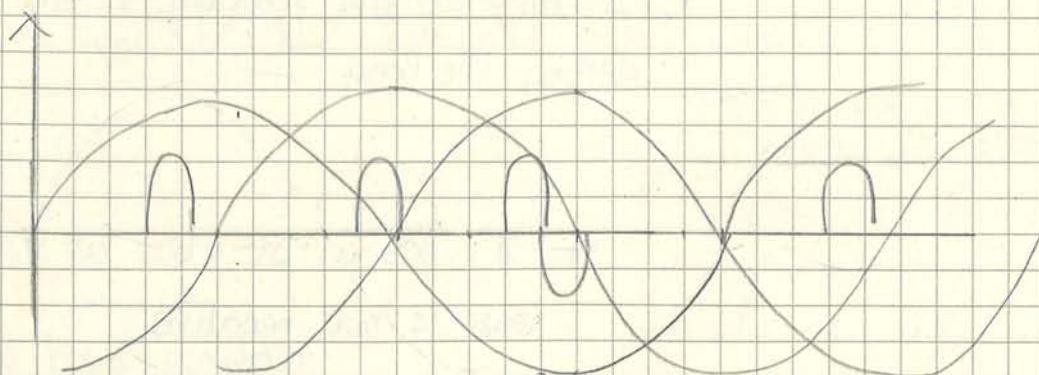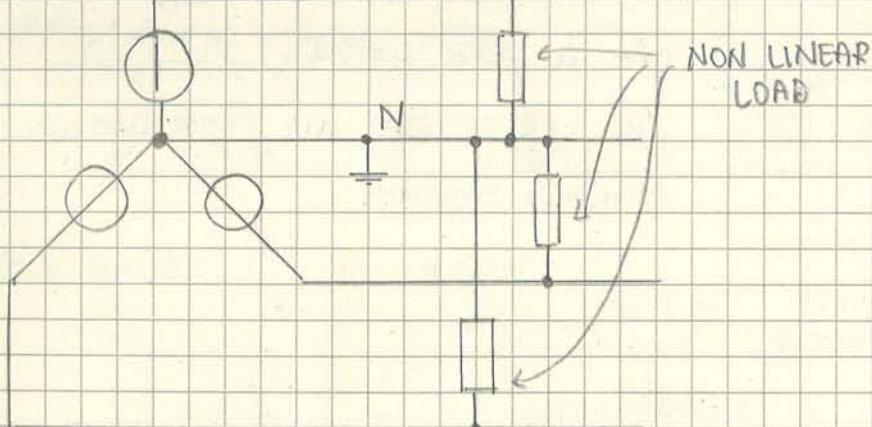What happens if we have a non-linear load?




Currents are out of phase and they don't cancel out.

1) The voltage is not a DC voltage

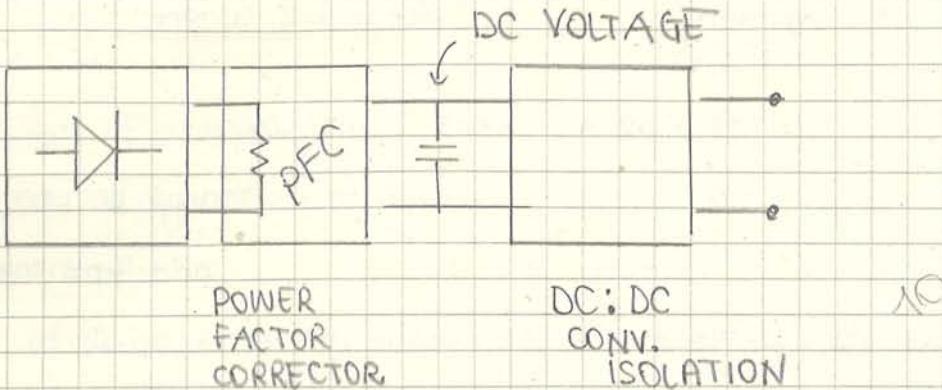2) It's not isolated.


But if I put the load, it's not generates harmonics.

We need to have a DC voltage and we need to introduce an isolation.




Now we're looking to PFC.


Input voltage to PFC is:

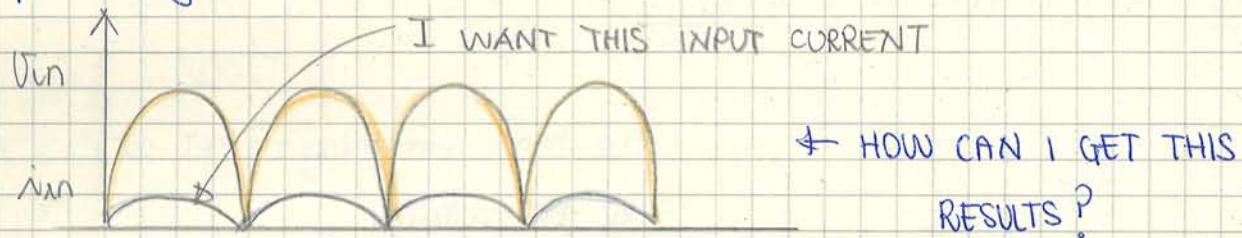


Let's consider a buck converter:

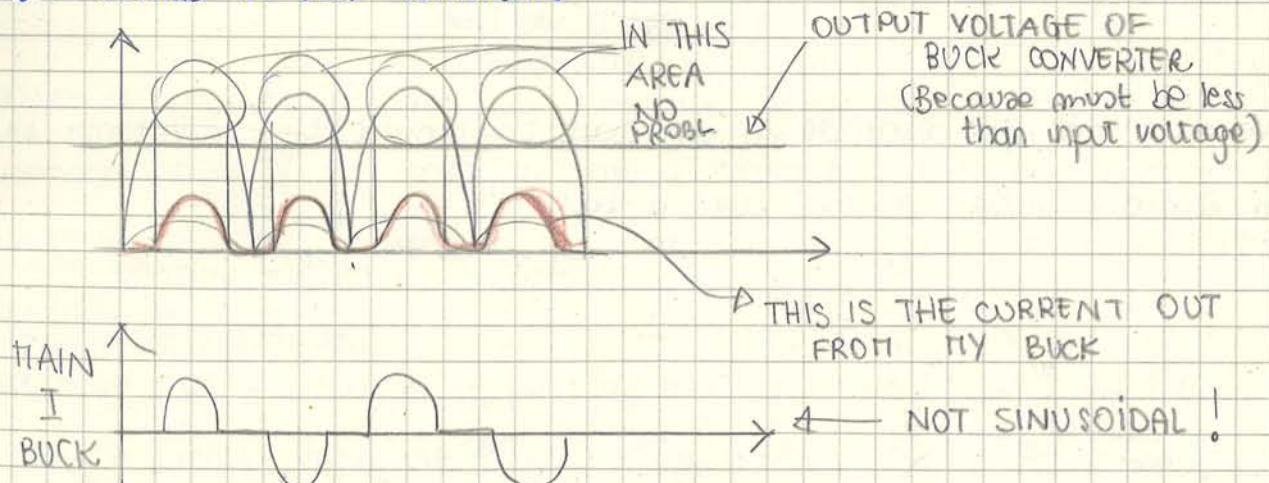

Now boost converter:

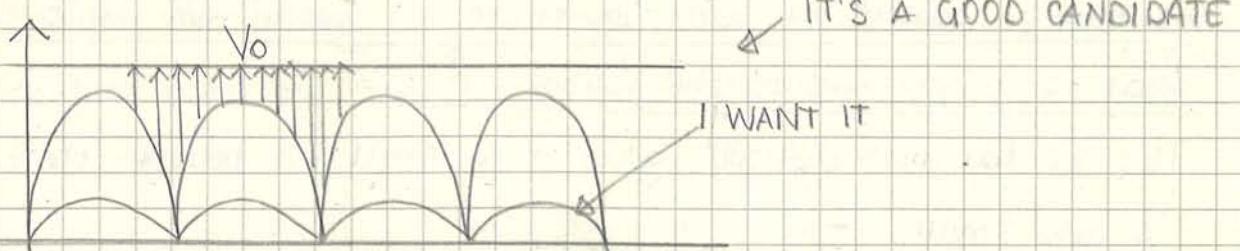


And what about buck-boost?

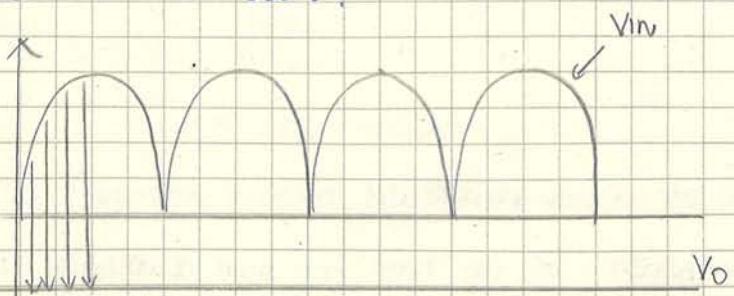

It is also a good candidate for PFC.

The problem of boost is that  $V_o$  is very high. BB hasn't this problem; then it is OK. (we change only the reference). What is the problem of BB as PFC?

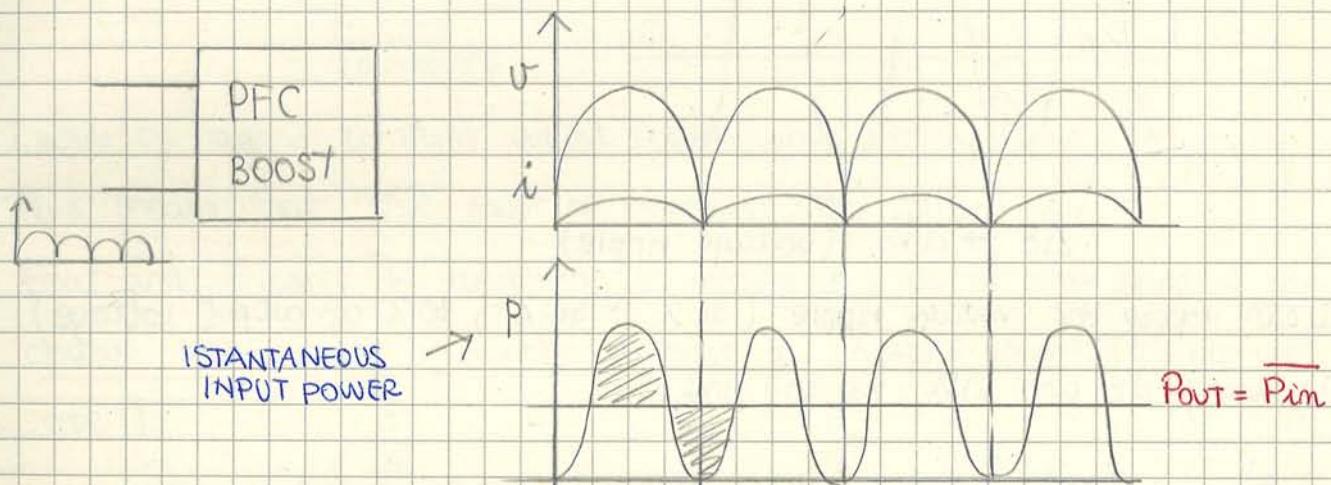BB has a pulsating input current that generates noise. So in general we prefer boost, and if the voltage is too much high we work in ECM because we have less stress.



power is not constant! Too bad. Because after PFC we have a DC-DC converter, and if we want to have a constant voltage the input power must be constant! So we can say that the output power is equal to the average of input power.

We have that for the first part of the cycle there is some ~~some~~ power that is greater than the average and in the second part is smaller. But, the 2 areas are equals.

How can we store energy? CAPACITOR ( $C_0$ ) that is used to store energy for the first part and then releases in the second part of the cycle.


$$= \frac{1}{4f_{LINE}} \cdot P_{OUT} \cdot \left( \frac{2}{\pi} \right) = \frac{P_{OUT}}{2\pi f_{LINE}} \rightarrow \text{And then we find } C_0$$

↓ SINUSOIDAL FUNCTION

Other way to solve it is to say that cap has a reactance and :

$$V_{RIPPLE} = \frac{I_{RIPPLE}}{j\omega C} L \cdot 2\pi \cdot f_{SW}$$


HOW WE CONTROL IT ?

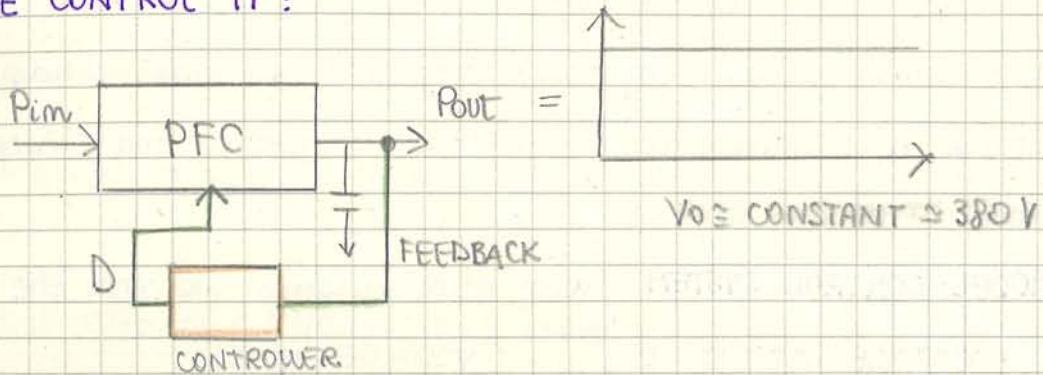

I want to have a constant output power when the input is

This means that  $V_o \cdot i$  must be constant. The voltage is

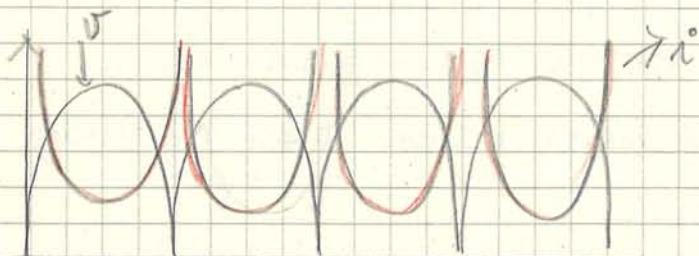that and I can't do anything to modify it. On the other hand, I can change the current in order to have a constant power. (It's the opposite!)



So, I need that the output voltage has some ripple because this ripple makes the difference between a PFC and a standard DC-DC converter. How can I control the output voltage but not the ripple? Filter, (L.P. FILTER). The bandwidth of the loop gain must be narrow otherwise I correct the output ripple. So the crossover frequency is very small (~10 Hz) (Boost has a RHP and so we have to cross before).

If I need to design this compensator (the transfer function of circuit) what do I need? I need to know the dynamic relationship between  $V_o$  and  $D$ . It's not  $V_o = V_{in} \cdot D$  this is for steady state!

I need to know the transfer function! In order to get a stable system.

I need Laplace transform  $\frac{V_o}{D}$  in this domain!

Our converter has switches, so it's time variant circuit (the schematic changes). And the relationship is not linear. ⚠


How can we find transfer function?

- STATE SPACE AVERAGING (MIDDLEBROOK) - CCM - eq. differential

- SWITCH AVERAGING (VORPERIAN) easier to apply for many topologies.

- CIRCUIT AVERAGING it's not a method, even if is very easy to apply


Why averaging?

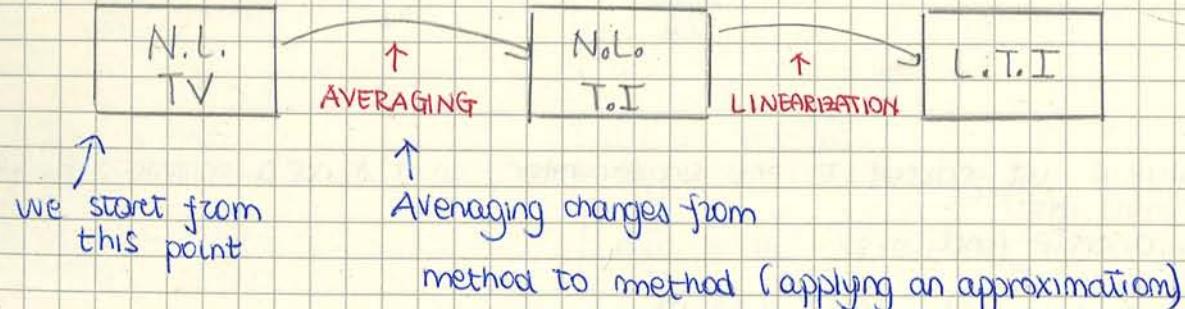

For example we can have:


$$\bar{x}(t) = \frac{1}{T_{SW}} \int_t^{t+T_{SW}} x(\tau) d\tau \rightarrow \text{MOVING AVERAGE}$$

↑ time continuous average

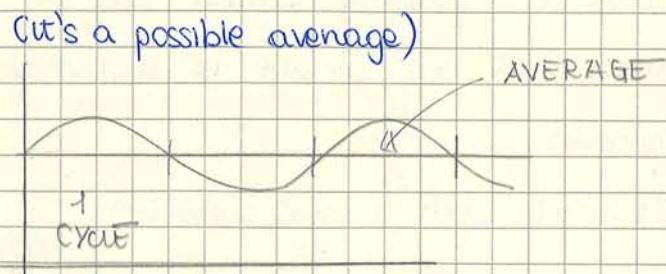

In CCM we have:

MIDDLEBROOK

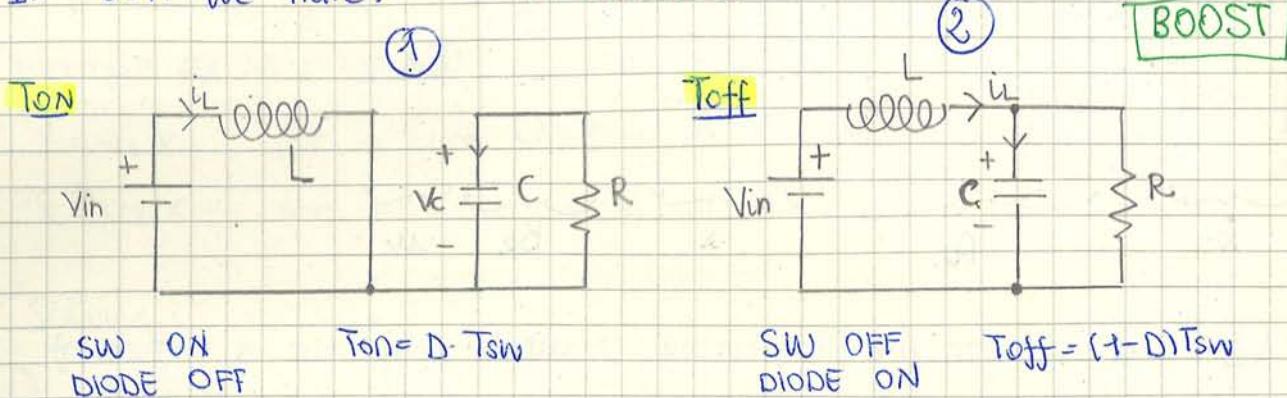

Both of them are linear and time invariant.

For describing these circuits we can use differential equation. The basic equations are:

$$\begin{cases} \dot{x} = Ax + Bu & \text{STATE} \\ y = Cx + Du & \text{INPUT} \\ \quad | & \text{MATRIX} \end{cases}$$

The state variables are  $i_L$  and  $V_C$  (that is the output voltage across  $R$ )

OUTPUT

$$\begin{cases} L \frac{di_L}{dt} = V_{in} \\ C \frac{dV_C}{dt} = -\frac{V_C}{R} \end{cases}$$

(1)

$$\begin{cases} L \frac{di_L}{dt} = V_{in} - V_C \\ C \frac{dV_C}{dt} = i_L - \frac{V_C}{R} \end{cases}$$

(2)

$$\begin{cases} \frac{di_L}{dt} = \frac{V_{in}}{L} \\ \frac{dV_C}{dt} = -\frac{V_C}{RC} \end{cases}$$


$$\begin{cases} \frac{di_L}{dt} = \frac{V_{in} - V_C}{L} \\ \frac{dV_C}{dt} = \frac{i_L}{C} - \frac{V_C}{RC} \end{cases}$$

→ From them we have to write down matrixes

$$(1) \quad \begin{bmatrix} \dot{i}_L \\ \dot{V}_C \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & -1/RC \end{bmatrix}}_{A_1} \begin{bmatrix} i_L \\ V_C \end{bmatrix} + \underbrace{\begin{bmatrix} 1/L \\ 0 \end{bmatrix}}_{B_1} V_{in}$$

NB: If I have on the output:

$I_o$  is an input!

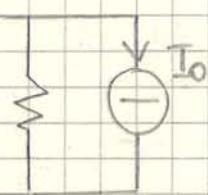

Let's consider (for a moment) if our result is reasonable or not. For example let's consider a simple system :

$$\dot{x} = a_1 x \quad \text{for a time } D \cdot T_{SW}$$

$$\dot{x} = a_2 x \quad \text{for a time } (1-D)T_{SW}$$

SOLUTION :  $\begin{cases} x(t) = x(0) e^{at} \\ \dot{x} = ax \end{cases}$

Solving :

$$1) \quad x(DT_{SW}) = x(0) e^{a_1 DT_{SW}}$$

$$2) \quad x(T_{SW}) = \underbrace{x(0) e^{a_1 DT_{SW}}}_{\text{INIT. COND.}} \cdot e^{a_2 (1-D) T_{SW}} = x(0) e^{[a_1 D + a_2 (1-D)] T_{SW}}$$

$a$  is the reciprocal of time constant ; it's an average like that we found first! So, is it true? Does it work? No, it's wrong. Why?

Solution must be something like :

$$e^{A_1 DT_{SW}} \cdot e^{A_2 (1-D) T_{SW}} \quad \times \quad e^{(A_1 D + A_2 (1-D)) T_{SW}}$$

IT'S VALID ONLY FOR SCALAR, NOT  
FOR MATRICES !

But in this case it works. Let's consider :

$$e^{A_1 DT_{SW}} = I + A_1 DT_{SW} + \frac{1}{2} (A_1^2 D^2 T_{SW}^2) + \dots$$

$$e^{A_2 (1-D) T_{SW}} = I + A_2 (1-D) T_{SW} + \frac{1}{2} A_2^2 (1-D)^2 T_{SW}^2 + \dots$$

If we multiply these two :

$$e^{(A_1 D + A_2 (1-D)) T_{SW}} = I + \underbrace{A_1 DT_{SW}}_{\text{1st term}} + \underbrace{A_2 (1-D) T_{SW}}_{\text{2nd term}} + A_1 A_2 D (1-D) T_{SW}^2$$

Remember our assumption  $T \gg T_{SW}$ ; in our expression we have time constants, so we can neglect the other terms (we have  $T_{SW}^2$  etc..etc..). So :

$$e^{(A_1 D + A_2 (1-D)) T_{SW}} \approx I + A_1 DT_{SW} + A_2 (1-D) T_{SW}$$

← IT'S COMMUTATIVE

↑  
IT'S A GOOD APPROXIMATION.

$$\begin{cases} \frac{d\bar{I}_L(t)}{dt} = \frac{d-1}{L} \bar{V}_C(t) + \frac{\bar{V}_{in}}{L} \\ \frac{d\hat{V}_C(t)}{dt} = \frac{1-d}{C} \bar{I}_L(t) - \frac{\bar{V}_C}{RC} \end{cases} \rightarrow \text{NON LINEAR}$$

what is advantage? Matlab can solve it very faster because it's time continuous differential equation. we can't put it in spice, we can't apply LaPlace transf. (not in easy way); so we have to linearize it considering small variations around all the variables. How can we do it?

### SMALL SIGNAL MODEL :

- Taylor series
- Different approach; for each part:

$$\begin{array}{l} \bar{I}_L = I_L + \hat{I}_L \\ \uparrow \quad \uparrow \quad \downarrow \\ \text{TOTAL} \quad \text{DC VALUE} \quad \text{VAR.} \end{array} \quad d = D + \hat{d} \quad V_C = V_C + \hat{V}_C$$

$$\bar{V}_{in} = V_{in} + \hat{V}_{in}$$

$$\begin{cases} \frac{d(I_L + \hat{I}_L)}{dt} = \frac{D + \hat{d} - 1}{L} (V_C + \hat{V}_C) + \frac{V_{in} + \hat{V}_{in}}{L} \\ \frac{d(V_C + \hat{V}_C)}{dt} = \frac{1-D-\hat{d}}{C} (I_L + \hat{I}_L) - \frac{(V_C + \hat{V}_C)}{RC} \end{cases} \quad \text{NON LINEAR}$$

$$\hat{I}_L = \hat{i}_L \quad \text{if } \hat{i}_L \ll I_L \quad \text{SMALL SIGNAL CONDITIONS}$$

When I multiply 2 terms of small signal, I can neglect them.

For example  $\hat{i}_L \cdot \hat{d}$  (2<sup>nd</sup> order terms)

Let's write DC terms:

$$\begin{cases} \frac{dI_L}{dt} = \frac{(D-1)}{L} V_C + \frac{V_{in}}{L} = 0 \rightarrow V_C = \frac{V_{in}}{1-D} \rightarrow V_{in} = V_C(1-D) \\ \frac{dV_C}{dt} = \frac{(1-D)}{C} I_L - \frac{V_C}{RC} = 0 \rightarrow \frac{V_C}{R} = I_L(1-D) \end{cases}$$

STEADY STATE

SOLUTION

(ONLY FOR CHECKING)

$I_L$  and  $V_C$  are  
constants

$$I_L = \frac{V_{in}}{R(1-D)^2}$$

How can we solve it? LaPlace transform ( $\mathcal{L}$ ) :

$$\begin{cases} \hat{s}\hat{i}_L(s) = \hat{V}_C(s) \frac{D-1}{L} + \hat{d} \frac{\hat{V}_C}{L} \\ s\hat{V}_C(s) = \hat{i}_L(s) \cdot \frac{1-D}{C} - \frac{\hat{V}_C(s)}{RC} - \hat{d}(s) \frac{I_L}{C} \end{cases} \quad \frac{\hat{V}_C(s)}{\hat{d}(s)} = ?$$

NB: we don't need initial condition because if we have to find transfer function we don't need it.

For exercise let's check dimension.

Substituting  $\frac{1-D}{C}$  in the 2<sup>nd</sup> equation:

$$s\hat{V}_C = \frac{1-D}{C} \left[ \hat{V}_C(s) \frac{D-1}{sL} + \hat{d} \frac{\hat{V}_C}{sL} \right] - \frac{\hat{V}_C}{RC} - \hat{d}(s) \frac{I_L}{C}$$

$$\text{with: } V_C = \frac{V_{in}}{1-D} \text{ and } I_L = \frac{V_{in}}{R(1-D)^2}$$

We obtain:

$$s\hat{V}_C = \hat{V}_C \left( -\frac{(1-D)^2}{sLC} - \frac{1}{RC} \right) + \hat{d} \left( \frac{V_{in} \hat{d}}{(1-D)sLC} - \frac{V_{in}}{RC(1-D)^2} \right)$$

Dividing and multip. for SLC :

$$\hat{s}LC\hat{V}_C = V_C(-\frac{(1-D)^2}{sLC}) - \frac{sL}{R} + \hat{d} \left( V_{in} - \frac{sL}{R} \frac{V_{in}}{(1-D)^2} \right)$$


$$\hat{V}_C \left( s^2LC + (1-D)^2 + \frac{sL}{R} \cdot \frac{1}{(1-D)^2} \right)$$

$$\frac{\hat{V}_C}{\hat{d}} = \frac{V_{in}}{(1-D)^2} \cdot \frac{1 - \frac{sL}{R} \cdot \frac{1}{(1-D)^2}}{s^2LC + \frac{sL}{R(1-D)^2} + 1}$$


SON OF A BOOST!

$$2 \text{ poles } f_p = \frac{1-D}{2\pi\sqrt{LC}}$$

Loop gain  $|T|$  is:

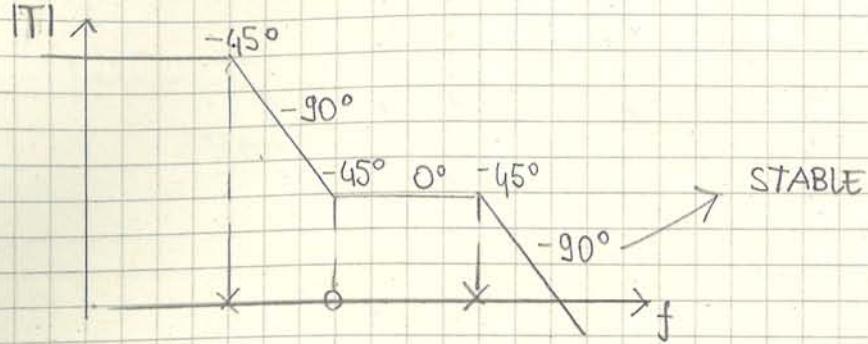

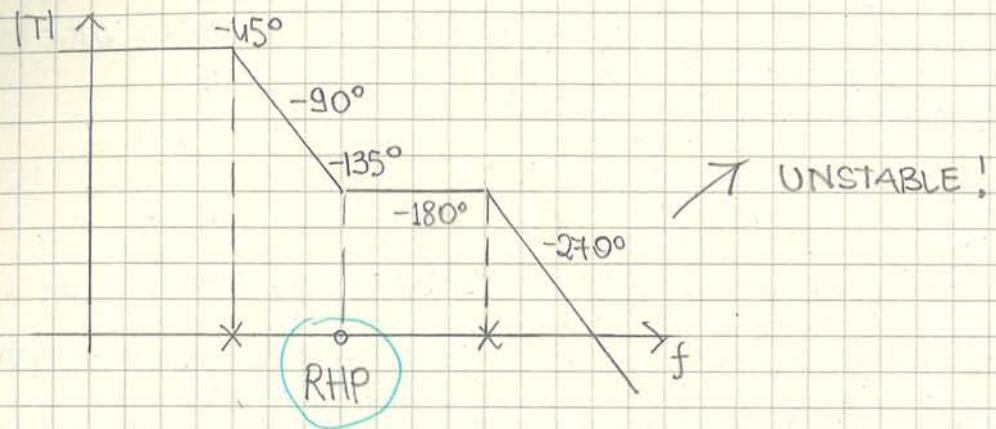
Now let's suppose that is an extra zero : (that is RHP zero)



Bad idea : putting a LHP in order to cancel RHP. It doesn't work! It works only for high precision system.

The only way to get it stable it's crossover before RHP. So we have to look for the minimum of this frequency  $f_z$  and crossover before. It happens for boost, buck-boost converter ... Boost is used as PFC ; in the PFC my bandwidth has to be less than the line frequency . For example I have to crossover at 10Hz maximum,

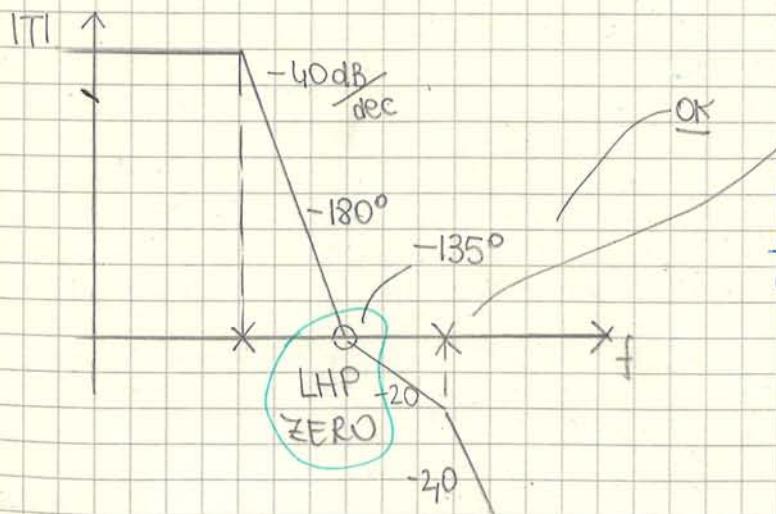
let's consider another transfer function:



If this pole is not too far from crossover frequency . This pole decrease my phase margin  $\rightarrow$  UNSTABLE


WHERE RHP zero coming from in a BOOST?

Let's consider diode current:

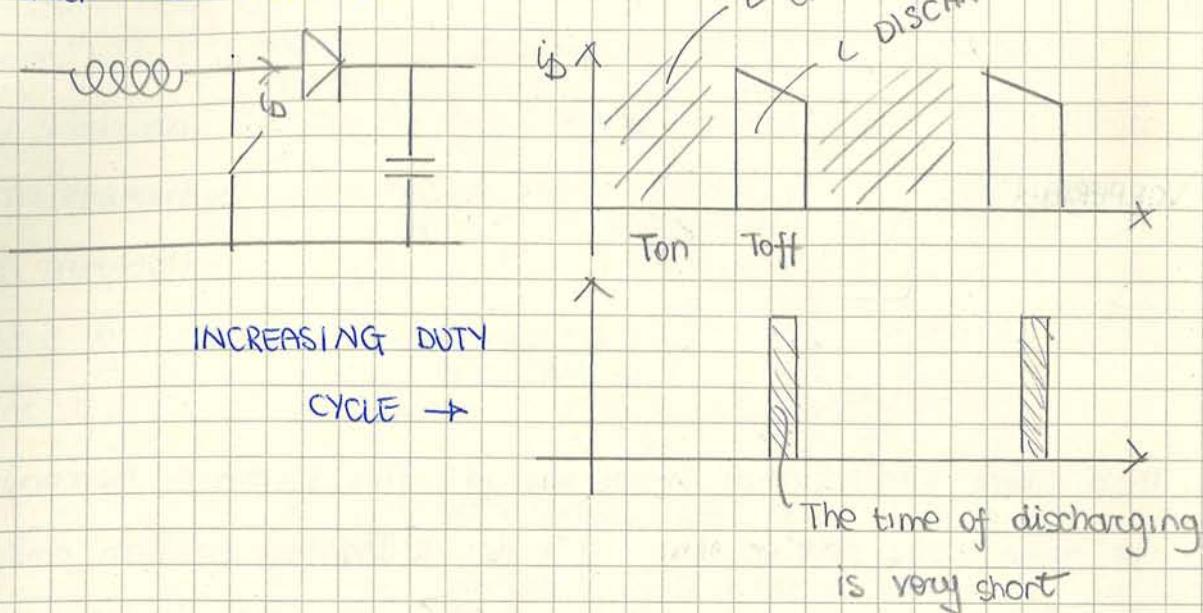




Let's change method to analyze our circuit in order to find transfer function. With the previous method we have to write down the differential equations for all part of the circuit and then we have to average it. We have to write down diff. equat. for switches that are non-linear and we to stabilize them.

For example if we have this circuit:

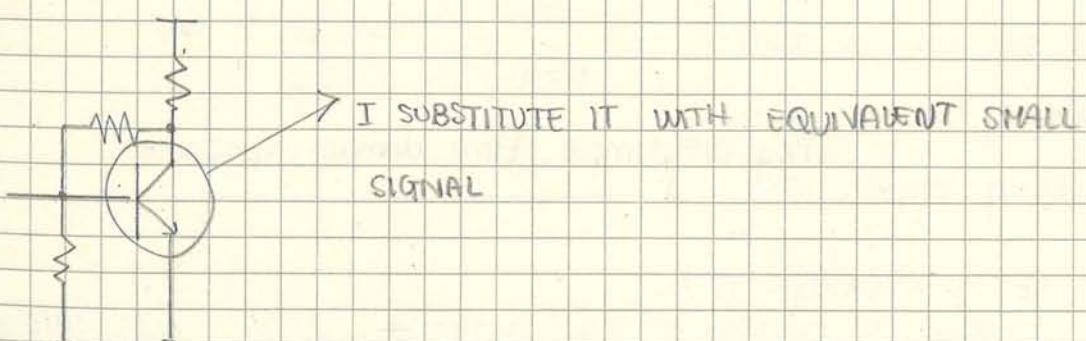

We do the same now with switches.

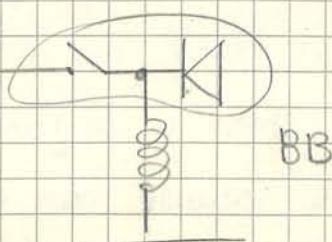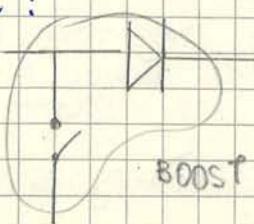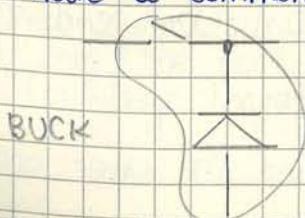In all topologies we find the same structure of switch and diode that have a common point:




frequency spectrum they are stat. independent. In our case  $i_c$  doesn't change too much ( $i$  is the current through the inductor). So we can do this approximation. During 1 cycle  $q$  changes and  $\bar{V}_{ap}$  and  $i_c$  not too much!  $\rightarrow$  Reasonable approximation for our circuit.

So:

$$\left\{ \begin{array}{l} \bar{V}_{cp} = \bar{V}_{ap} \cdot \bar{q} \\ \bar{i}_a = \bar{i}_c \cdot \bar{q} \end{array} \right. \quad \left\{ \begin{array}{l} \bar{V}_{cp} = \bar{V}_{ap} \cdot d(t) \\ \bar{i}_a = \bar{i}_c \cdot d(t) \end{array} \right. \quad (\bar{q} = d)$$


$\hookrightarrow$  NON LINEAR EQUATIONS,  $\bar{i}_c$  AND  $\bar{V}_{ap}$  CHANGE! (AND ALSO  $d$ )

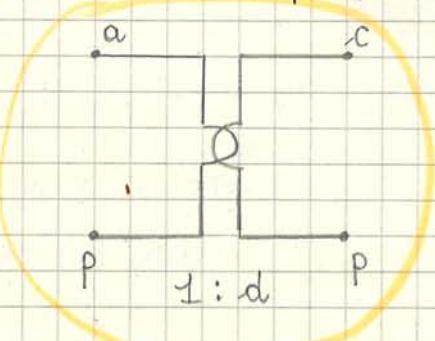what does represent these equations?  $\rightarrow$  TRANSFORMER



It's a strange transformer because the turn ratio  $d$  changes! (And it also transforms the DC)

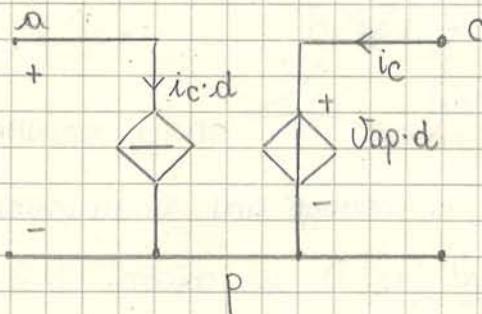we  
So we can model our tripole with a transformer; so it's easier doing computation with it. Better:



MODEL OF AN IDEAL TRANSF.  
that we can put in SPICE  
and simulate it faster  
than having switch and  
diode.


This is still NON LINEAR; but this isn't a problem for SPICE.

But it has no changes because there aren't switches.  $\rightarrow$  TIME INVARIANT.

Now we have to linearize it. What are advantages and disadvantages?


We can use LaPlace transform. But we lost generality because we study only one point and a small area around it.

let's see buck-boost :

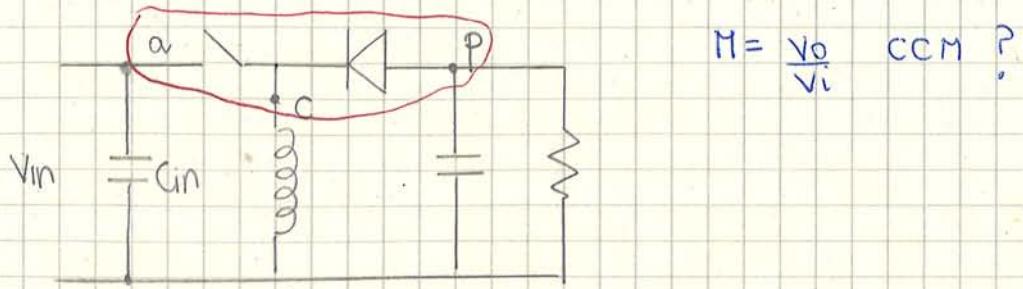


Substituting this tripole with transformer :

- DC (BUCK BOOST)

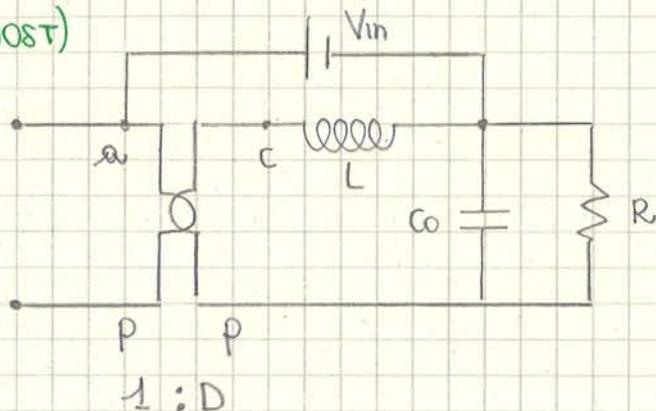


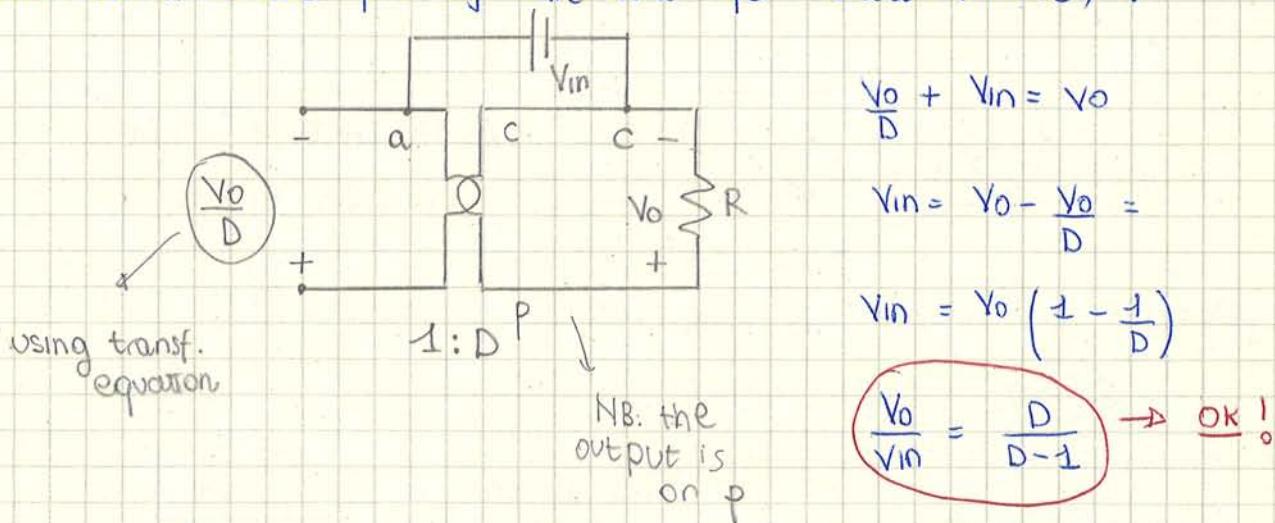But L and C are piece of wire and open circuit. (in DC) :



- AC (BUCK)

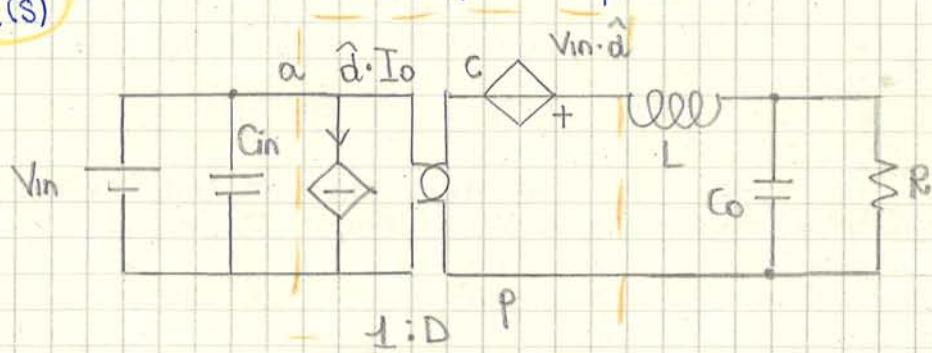$\frac{\hat{V}_o(s)}{\hat{a}(s)}$  ← this is the important point



So, removing bias voltage sources :

We haven't RHP zero! This is the reason why we design it in CCM


If we put Co ESR the mainly effect is:

$$\frac{\hat{U}_o(s)}{d(s)} = V_{in} \cdot \frac{1 + s \cdot C \cdot ESR}{s^2 LC + sL + \frac{1}{R}}$$


→ Actually we have ESR in these term, but it's negligible; so we MUST neglect them!

Bad news.

I assume an ideal voltage. Actually:

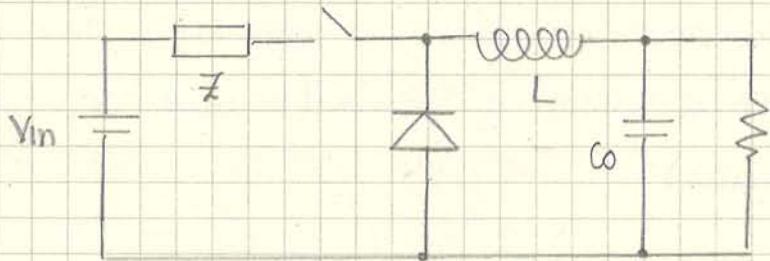

If I look small signal model:

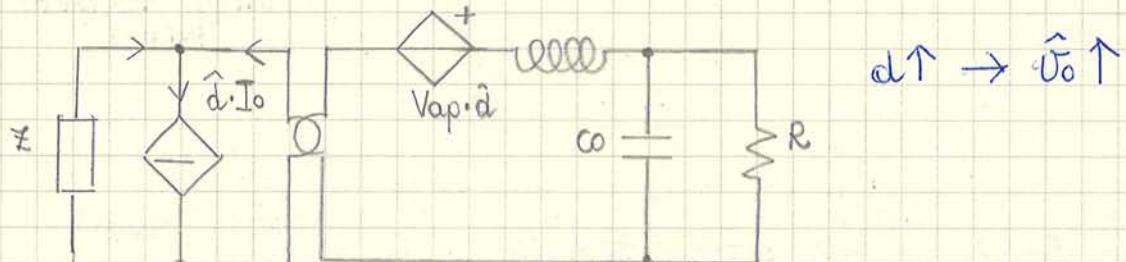

Using superposition and removing  $V_{ap} \cdot d$ , when  $\hat{d}$ , the current sinked is much more. The current comes from source and the primary; so on the secondary I have current flowing to the left and  $\hat{U}_o$  will decrease.

So:

- $V_{ap} \cdot \hat{d} \rightarrow d \uparrow, \hat{U}_o \uparrow$
- $\hat{d} \cdot I_o \rightarrow d \uparrow, \hat{U}_o \downarrow$

} SUPER POSITION

At high frequency it could happen that both of them are working


It could happen that  $\hat{d} \cdot I_o$  works at high frequency and  $V_{ap} \cdot \hat{d}$  at low frequency; so I have positive gain and negative gain. It means that there is a RHP zero. It could happen.

$$\bar{V}_{cp} = \bar{V}_{ap} \cdot D - (1-D) \text{ESR} \cdot \bar{i}_c \cdot D$$

EXTRA TERM

← what is an electrical representation of this equation?

This is still a transformer :

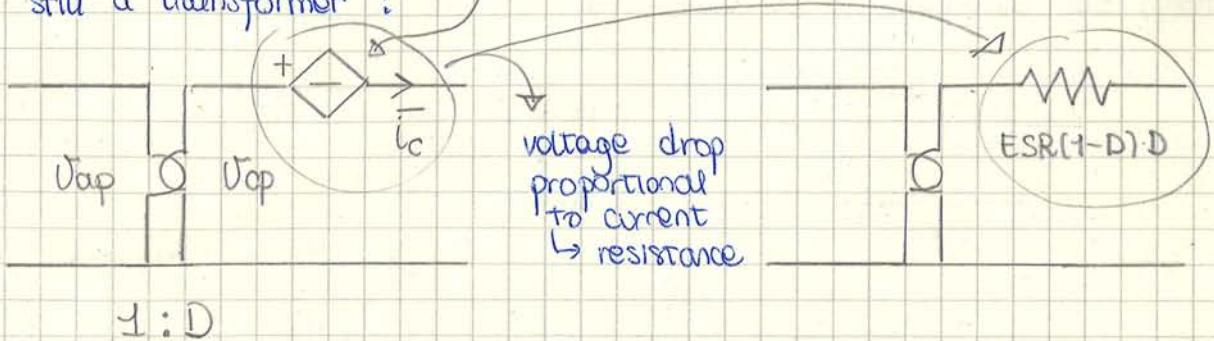


Resistance decrease Q factor of L-C circuit, who cares? Electrolytic caps have a toll of  $\pm 20\%$  and ESR isn't a very precise number and it goes up when cap becomes old. Also the inductor has  $\pm 20\%$ ; and its value decreases as DC current decreases (we are close to saturation). So this change of Q is negligible.

### Averaging DCM converter : CIRCUIT AVERAGE

As first study we use the most important topology used in DCM:

Buck-Boost :

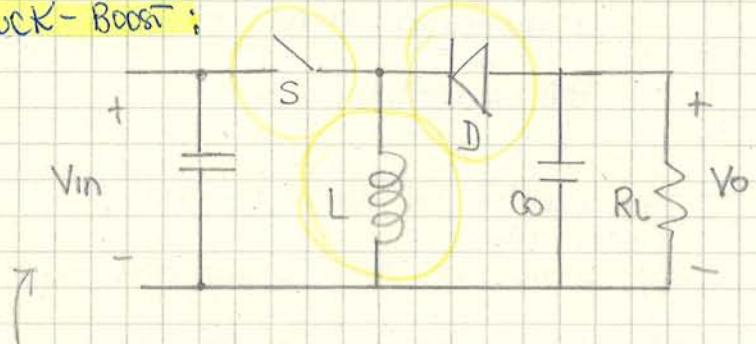

What happens for each component when it is averaged?


NO VARIATION

What is average of C → a capacitor! linear; time invariant.

// // // L → an inductor!

// // //  $R_{L}$  → is still output load!

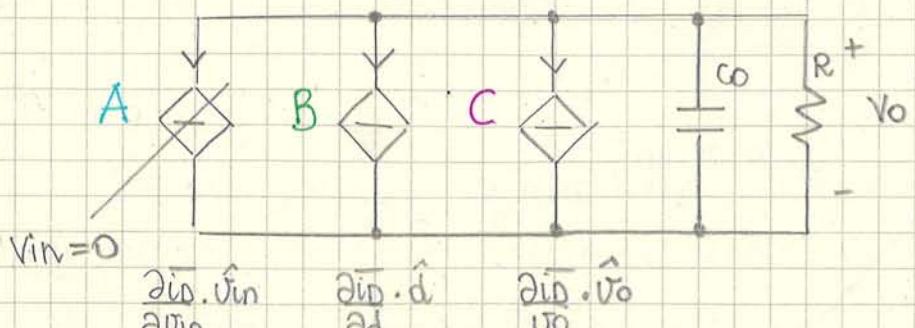And the diode and switch? This method is not systematic like previous method that we have seen; we need to substitute this diode (that is a switch on and off) with something that has a voltage across it and current through it. So it can be either a control current source or it could a control voltage source.



← LINEAR; so  
I can use superposition  
(Assuming  $V_{in}$  constant)

because I have to find  
out  $\frac{\hat{V}_o(s)}{d(s)}$

$$A) \frac{\partial \hat{V}_o}{\partial V_{in}} = A = -\frac{2 V_{in} \cdot d^2}{2 f_{SW} L \hat{V}_o} = -\frac{V_{in} d^2}{f_{SW} L \hat{V}_o} \quad (\text{A.S.})$$

$$B) \frac{\partial \hat{V}_o}{\partial d} = B = -\frac{2 V_{in}^2 \cdot d}{2 f_{SW} L \hat{V}_o} = -\frac{V_{in}^2 d}{f_{SW} L \hat{V}_o} \quad (\text{GAIN})$$

$$C) \frac{\partial \hat{V}_o}{\partial \hat{V}_o} = C = \frac{V_{in}^2 \cdot d^2}{2 f_{SW} L \hat{V}_o^2}$$


Remember that:  $\frac{\hat{V}_o}{V_{in}} = -D \sqrt{\frac{R}{2 f_{SW} L}}$  (FOUND WITH ENERGY)

$$\left(\frac{V_{in}}{\hat{V}_o}\right)^2 = \frac{2 f_{SW} L}{D^2 R}$$

And so I can write:

$$\frac{\partial \hat{V}_o}{\partial \hat{V}_o} = \frac{2 f_{SW} L d^2}{2 f_{SW} L d^2 R} = \frac{1}{R} \quad (\text{Actually is negative but the current in the load is coming down and it's ok})$$

So we have: NUMBER, CONSTANT

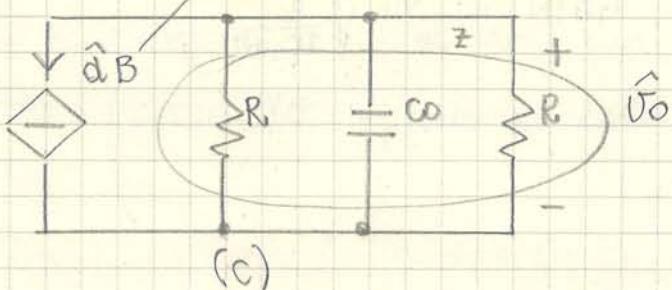

This is linear. I'm looking for  $\hat{V}_o$ . We can use Laplace transf.

$$\hat{V}_o(s) = -\hat{A}(s) \cdot B \cdot Z$$

$$\boxed{\frac{\hat{V}_o(s)}{\hat{A}(s)} = -B \cdot Z}$$

Let's see Bode function.

The pole frequency changes!

$$\frac{1}{2\pi C \left( \frac{ESR + R}{2} \right)}$$

→ NEGIGIBLE

So the pole frequency doesn't change too much.

ANALOGUE GAIN ↑

On the other hand, if  $R$  becomes lighter, the pole moves to the left.


What happens to gain? It changes with  $V_{IN}$  and  $R$ .

The zero is fixed but we don't know where it is. (And it moves because  $C$  becomes odd.)

Maybe there is something wrong. We have  $L$  and  $C$  but we have found only one pole (that related to capacitor). We "lost" the other one.

When we have a pole it means that is an element storing energy; it has memory; and I describe it with differential equation..

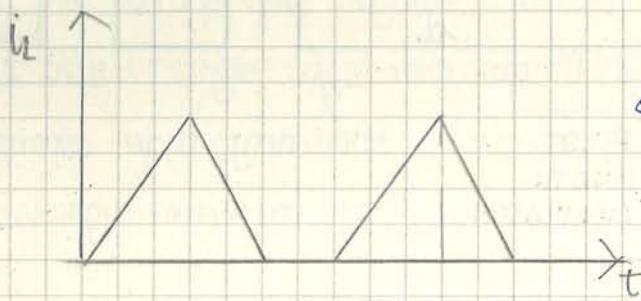
Let's consider inductor current in time domain:



It has memory, but it's limited to stay in 1 cycle.  
This memory is canceled before the end of the second cycle is above

This means that we have a pole; but it's a fast pole and it's  $\sqrt{\frac{1}{2}}$  of  $f_{SW}$  and we can't describe it. And we can neglect it because we work far below  $\frac{f_{SW}}{2}$ . For our issue all convert. working in DCM have only one pole.

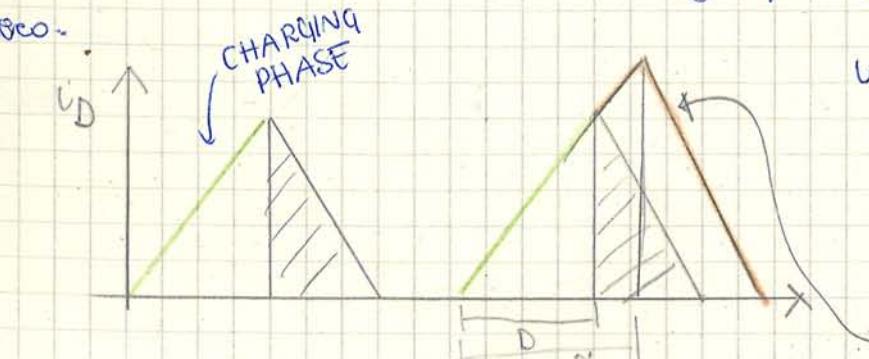
What about RHP zero? mathematically speaking this topology has RHP zero.



We are int. in  $i_D$  because energy goes to the output.

If we increase  $D$ , input current goes higher

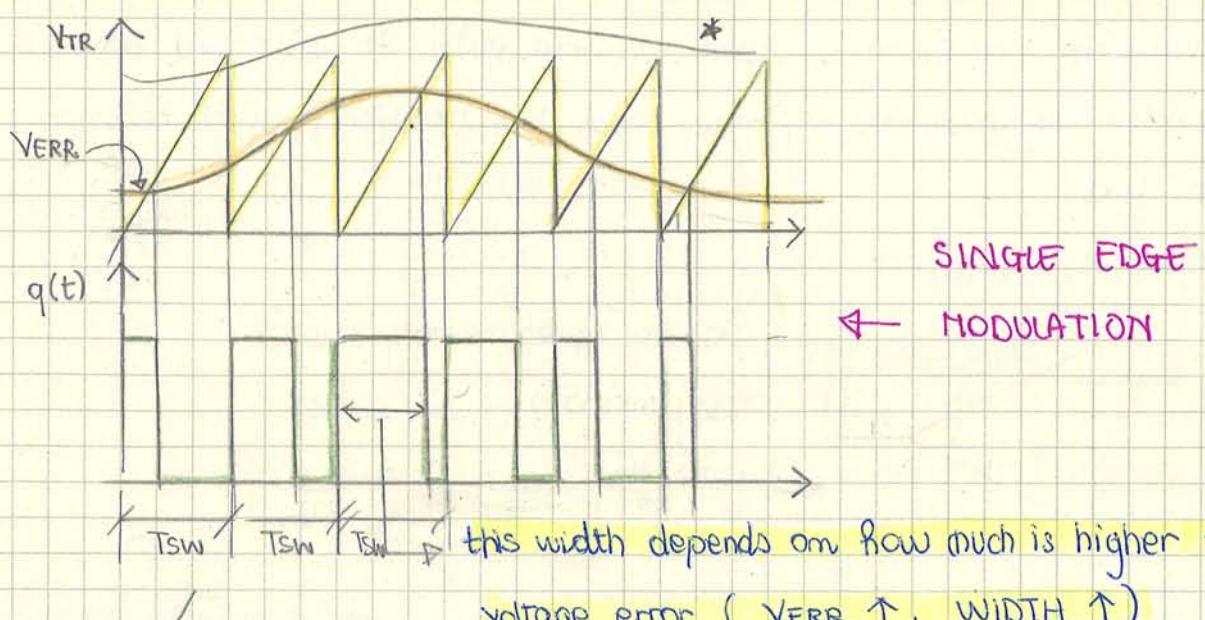So, if  $D \uparrow$ , the energy that goes to the load increases because peak current goes up.




PERIOD IS ALWAYS TSW  
(CONSTANT TIME)

(In each cycle the switch is on and off)

What happens if  $V_{in}$  goes above the peak? \* D goes to 1. }  
And the voltage goes negative? Below the zero? D becomes 0. } SATURATION

It is called single edge modulation because the time is periodic and the end of this pulses is modulated by the amplitude of the error signal.

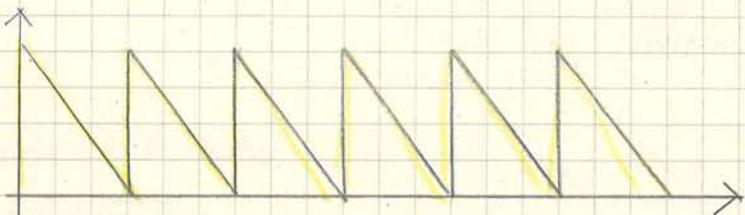
There is another way to use sawtooth; for example in this way:



It's still a single edge modulation.


(In the AC-DC converter they use symm. waves).

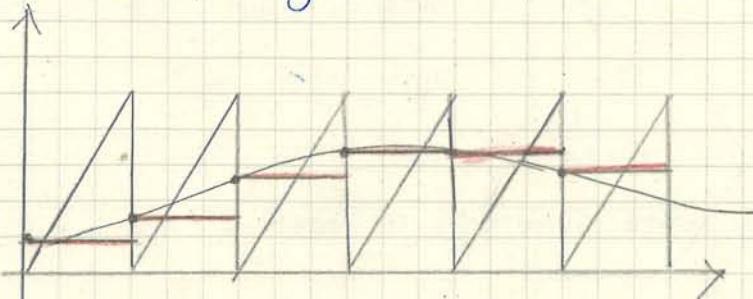In some cases, instead of having modulator, in order to avoid noise we can put on the error signal a S/H circuit. It keeps  $V_{ERR}$  constant for all full cycle. So we obtain:



It generates a lot of problems.

So, my system is something like this:

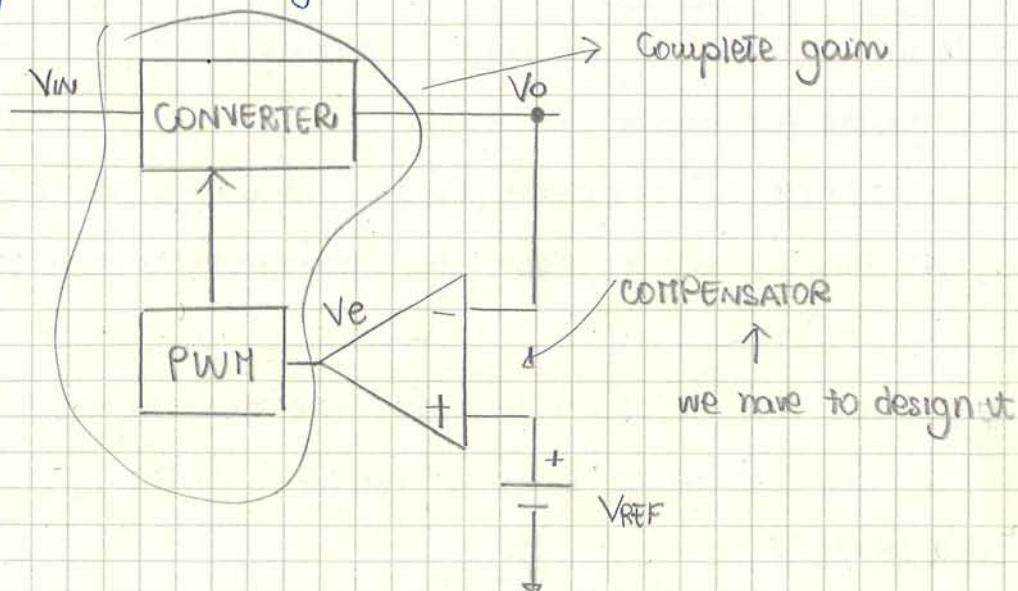

I want to close a loop because I want output voltage it's a fixed voltage, constant voltage. The important quantity that we have to study is:

LOOP GAIN  $|T|$ . We have to define what kind of  $|T|$  we want.

And for the loop gain the important parameters are:


- phase margin
  - steady state error → High gain DC means low steady state error → PRECISION (ACCURACY)
  - Bandwidth (speed of  $V_O$  when par. change; if the load changes quickly I need to recover fast).
  - (High bandwidth)
- STABILITY

So we want:

- High DC gain for precision;
- Phase margin for stability;
- Bandwidth for fast recovery;


Limitations : 1) There is  $\frac{f_{SW}}{2}$

Our model stops  
to work here

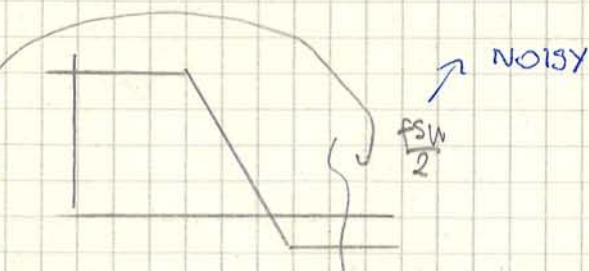



We have to stay quite lower than  $\frac{f_{SW}}{2}$ .

What are the problems? Pole is moving  $\rightarrow$  gain is moving. I have to look for the plant transf. function that gives me the maximum crossover frequency  $f_c$ . It depends on  $V_{in}, R$   $\rightarrow$  so I have to look for the worst case what happens to the curve ③ if  $V_{in}$  decreases? Curve shift down. And what about crossover frequency? It moves to the left. So the worst condition is:

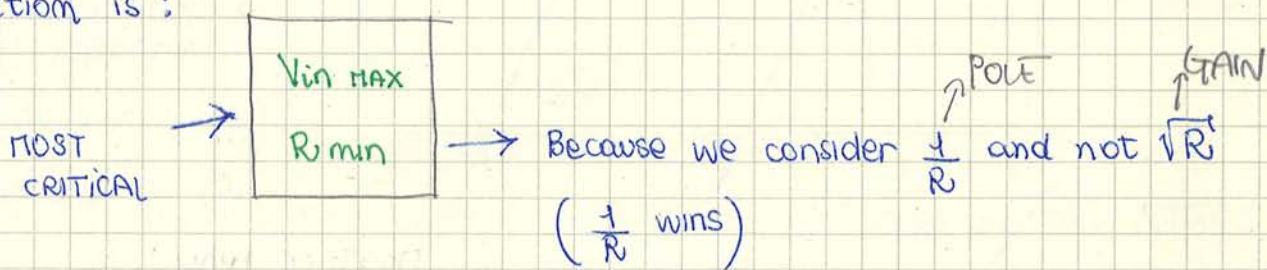

So, now looking for a circuit that give me a transfer function like this:


### COMPENSATOR TYPE 3

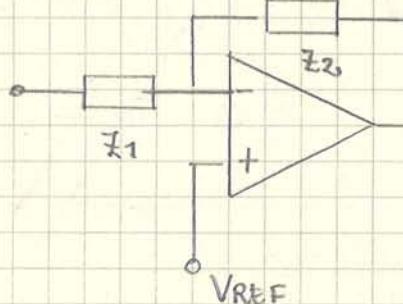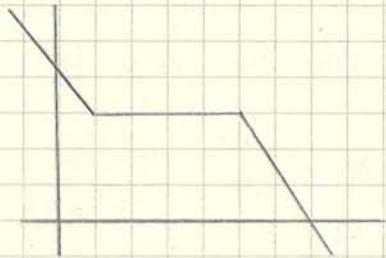

$$\frac{Z_2}{Z_1} = ?$$

2 poles; so  
I use 2 caps

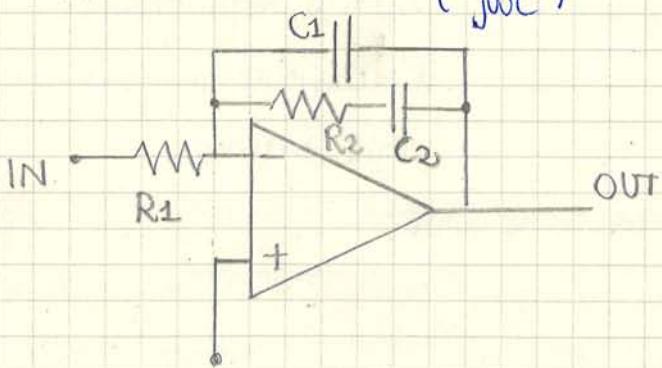I want to come down with 2 capacitors; they must be in  $Z_2$  because an impedance decreases  $(\frac{1}{j\omega C})$ . I want an integrator:



There isn't DC feedback.

We have to find 4 parameters; but we have  $\gg$  3 requirements:

- zero frequency;
- pole frequency
- Band gain


The last equation comes from values of the components.

- ① In low frequency band;  $C_2$  has an impedance that is larger than  $R_2$  and so we can neglect  $R_2$ .
- ② When frequency goes up,  $C_2$  impedance decreases and the branch is dominated by  $R_2$ .
- ③ The parallel is dominated by  $C_2$ .

- $f_z = \frac{1}{2\pi C_2 R_2} \rightarrow$  IS IT RIGHT? OR IS IT AN APPROXIMATION?

Zero means that function goes to zero, that there is no output (for a given frequency). What is the condition in the circuit that gives me zero output? When  $R_2$  and  $C_2$  become short circuit I have zero output. And when they become s.c? When  $C_2$  has an impedance that is opposite of  $R_2$ ; and when we find this frequency we obtain (when  $R_2 = -\frac{1}{sC_2}$ )
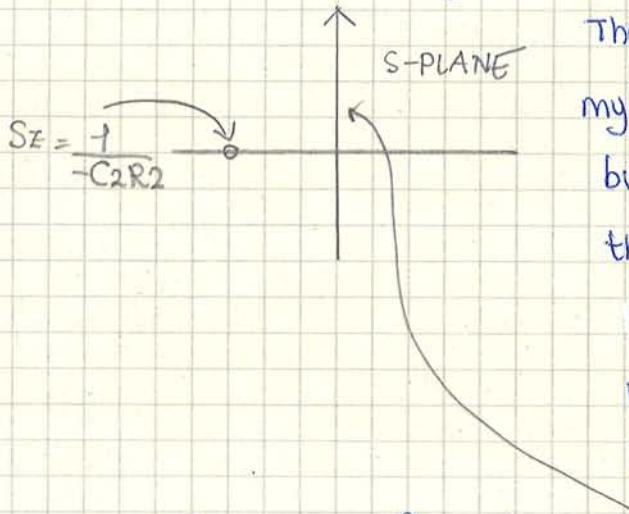
$$s_z = -\frac{1}{C_2 R_2} \rightarrow \text{There is something strange!}$$



There is negative sign; so my zero is in left plane; but how is it possible that our zero doesn't give us an output that is no zero if we look transf. function?



Because we're visiting s-plane only along the  $j\omega$  axis; we don't hit the zero; we don't pass through the zero. Zero is on real axis; and the effect of zero is that we have a slope of 20 dB/dec.

- $f_p = \frac{1}{2\pi C_1 R_2} \rightarrow$  IS IT RIGHT?

Yes. Because actually is

$$\frac{1}{2\pi \left( \frac{C_1 C_2}{C_1 + C_2} \right) R_2}$$

$\hookrightarrow \simeq C_1$

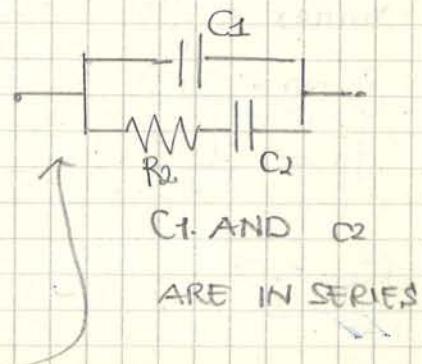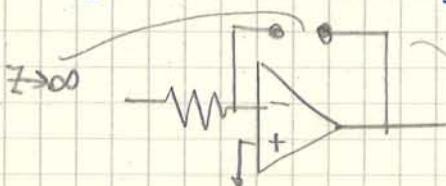


$f_Z$  : we have an idea of ESR if C is electrolytic. (At the exam we find ESR from output ripple and we estimate it.)  
 $f_Z$  can be  $\approx 3\text{ kHz}$  (about 3 decades from  $f_p$ ).

Is  $f_Z$  fixed? more or less. Is  $f_Z$  accurate? No; because it depends on the parasitic elements of capacitors.

$$\begin{aligned} \text{GAIN} : V_{in \text{ MAX}} &= \sqrt{\frac{R_{limin}}{2f_{sw}L}} \\ &= 18V \cdot \sqrt{\frac{2.6\Omega}{2 \cdot 200\text{ kHz} \cdot 22\mu\text{H}}} = 29.73 \approx 30V \end{aligned}$$

$$\frac{30V}{3V} \approx 10 \text{ times} \rightarrow 20 \text{ dB}$$

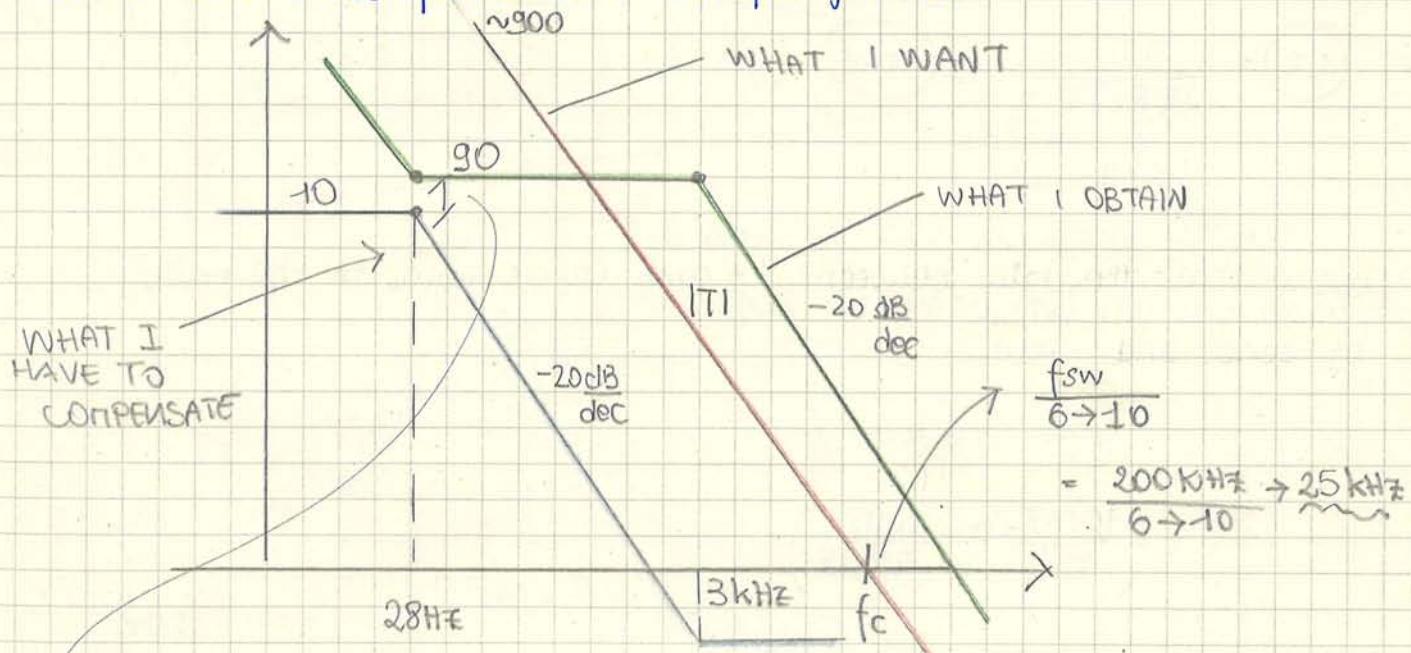So I have to compensate the transfer function.




$$\begin{aligned} \frac{f_{sw}}{6 \rightarrow 10} &= \frac{200\text{ kHz}}{6 \rightarrow 10} \rightarrow 25\text{ kHz} \end{aligned}$$

$$\left( \frac{25\text{ kHz}}{28\text{ Hz}} \right) = \frac{x}{1} \Rightarrow x = 900 \text{ (gain of T @ 28 Hz)}$$


$$\Delta \frac{900}{10} = 90 \rightarrow \text{gain of my curve} \quad (\text{DIFFERENCE; BUT I HAVE TO DIVIDE!})$$

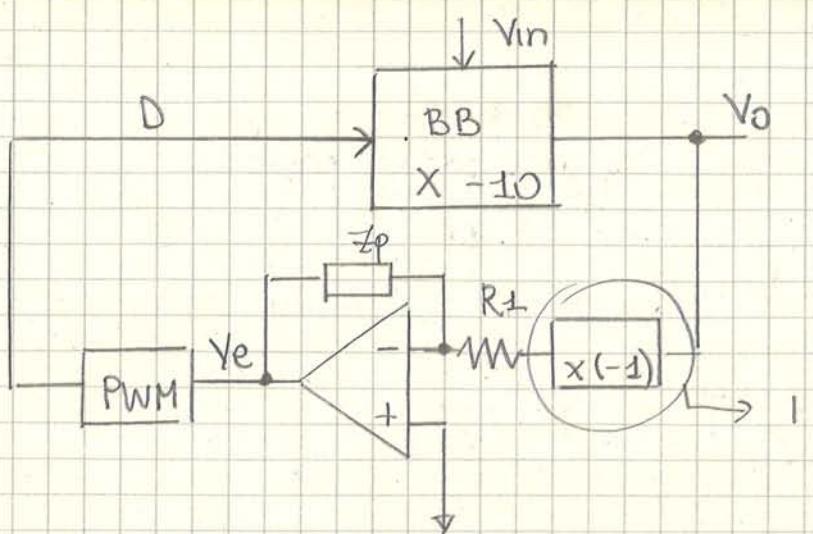And so, my compensator gives me a transfer function that is:




Now, how can I guarantee  $-12V$  at the output? There is nothing in this circuit that give me this!

I put  $R_1$  in a diff. position

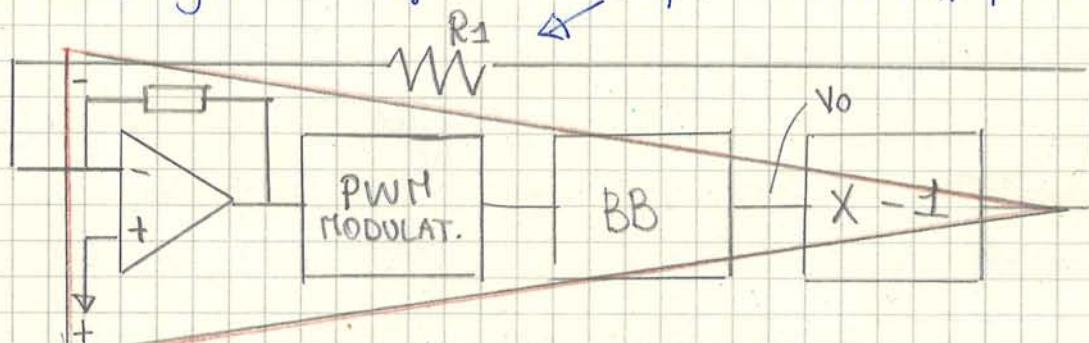

Instead of having a voltage follower I

have to use a N1 op-amp amplifier.

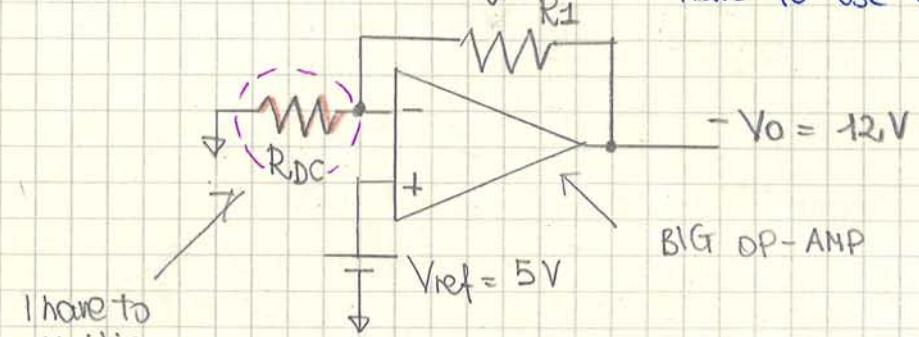


I have to  
put this  
resistance

R<sub>DC</sub> sets only DC gain.

Does R<sub>DC</sub> change my stability; phase margin, crossover frequency? No.

Look at the original OP-AMP:

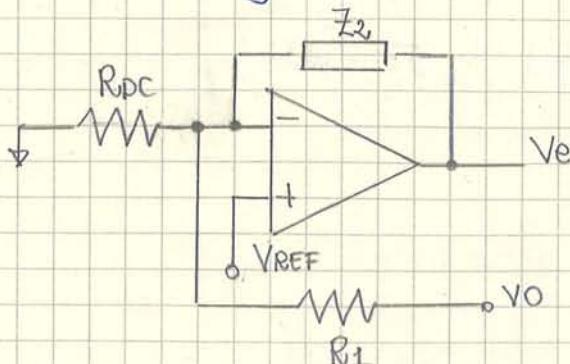


In order to analyse loop gain I need to analyse a feedback path starting from one point and arriving at the same point.

$$\frac{V_e}{V_0} = -\frac{Z_2}{R_1} \rightarrow \text{there isn't } R_{DC}$$

Since R<sub>DC</sub> there isn't in the calculation the gain doesn't change with R<sub>DC</sub> and so all our deals are valid.

However, adding R<sub>DC</sub> has a defect on this circuitry:

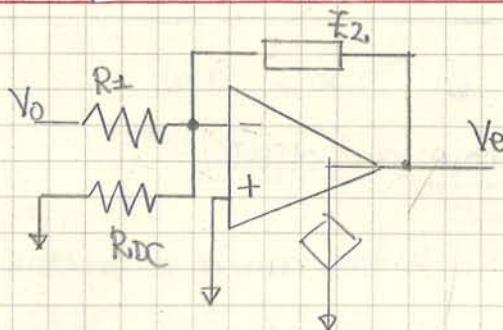let's consider in this system (simplified explanation) just the first op-amp; that give us a transfer function - what I get -, there is a feedback system. So I want to study how well this op-amp provides me the transfer function that I want:




What is the loop gain of this compensator:

$$\text{Ad. } \frac{R_1 // R_{DC}}{R_1 // R_{DC} + Z_2} !$$

What happens if R<sub>DC</sub> → 0? Very high DC gain.

↪ Loop gain → 0! So we don't have this transfer function anymore.

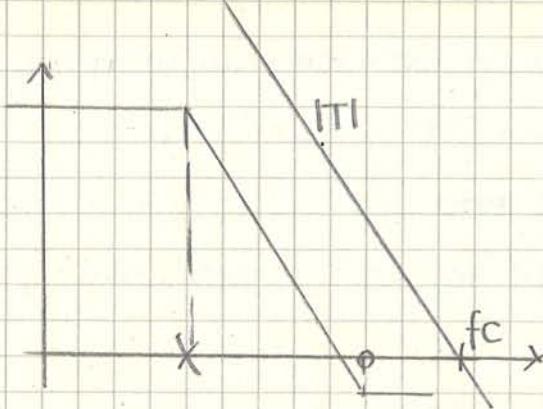
Let's suppose an output voltage = 400 V and V<sub>REF</sub> = 2.5 V → we need a gain factor that is 160! and R<sub>DC</sub> < R<sub>1</sub> and loop gain goes down; it means that the bandwidth of this compensator becomes smaller and smaller!




why we want an high fc? If I have only DC amplifier?

I want a system that recover from fast variation of output voltage.


So :

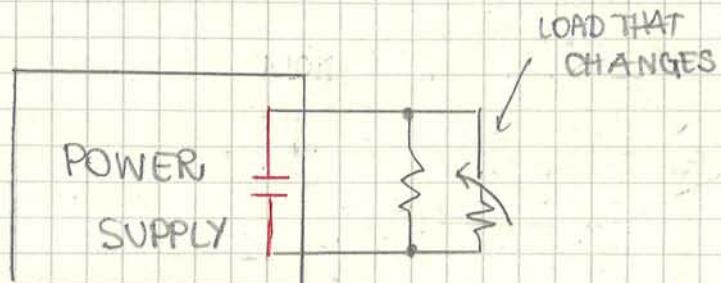

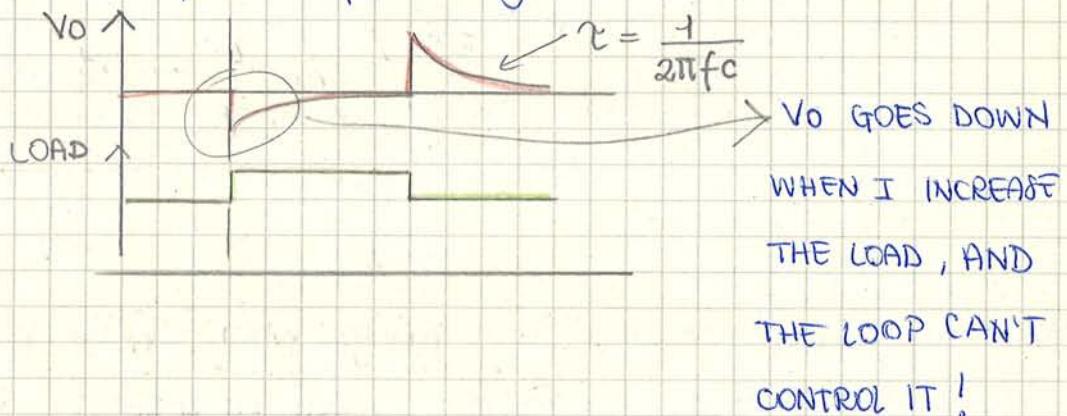If I change the load, the output voltage instead of constant is:



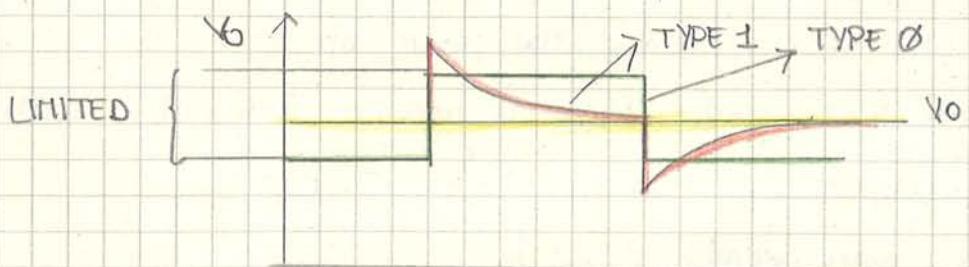There is a case when I don't like this kind of behaviour:




Which we prefer? It depends of what kind of load we have. If we look the integral of the area of Type 1 curve we have a short period of time when we have error; on the other hand the type 0 curve has a longer period of time when we have a constant error.

But I have the load at the end and it could be unhappy if it receives a peak of error!


What's next step? We want to compensate buck converter voltage mode:

### BUCK VM CCM

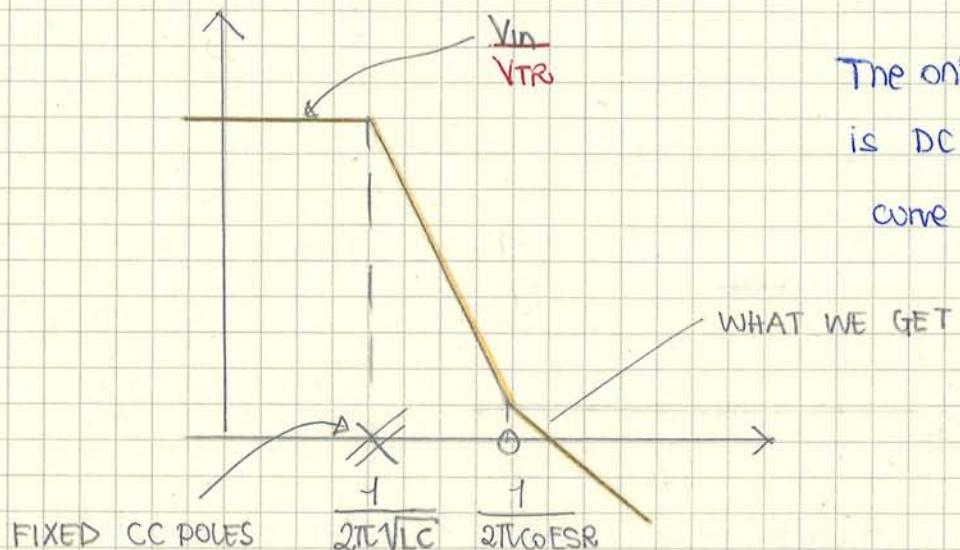

The only thing that changes is DC gain; so the curve moves up and down.  
(only shift).

So I want to compensate it:

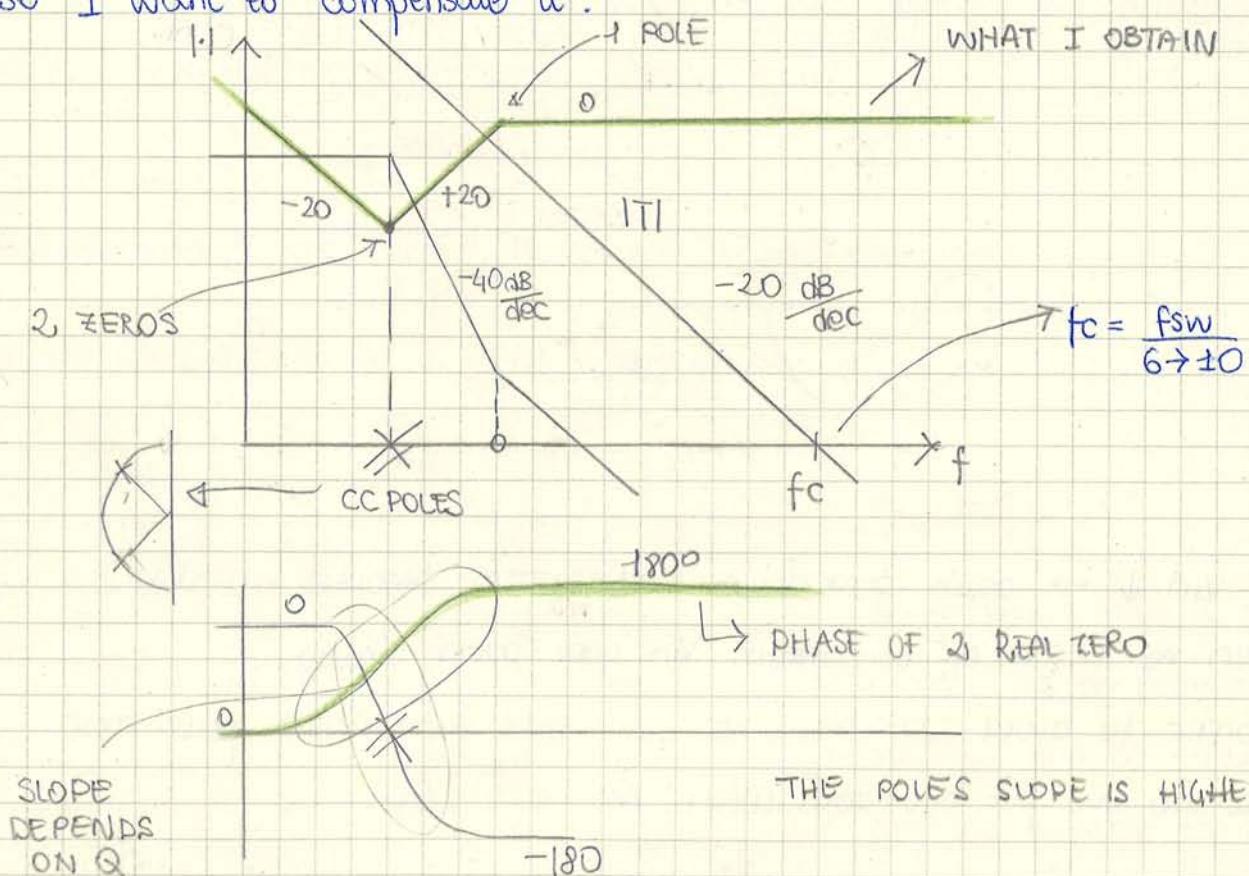

THE POLES SLOPE IS HIGHER

So we have a region when the phase is  $-180^\circ$  and the gain is greater than 1: →

So, to compensate a B.C. I need 3 poles  $\rightarrow$  TYPE 3 compensator :

- 1 POLE ORIGIN (in order to reduce steady state error)
- 1 POLE over the Co ZERO
- 1 CLOSURE POLE  $> 3f_C, < f_{SW}$  (NB:  $3 \cdot 2 = 6$  from  $\frac{f_{SW}}{6 \rightarrow 10}$ )

And 2 zeros :

- 1 ZERO @ POLES OF B.C
- 1 ZERO @  $\frac{1}{2}$  C.C. POLES OF B.C


When  $f_C$  moves to the left? When transfer function moves down. So the most critical case for stability is when the buck gain is its maximum.

When I have the maximum curve ; so :

$V_{IN MAX}$

And the load? who cares! It doesn't change the gain.

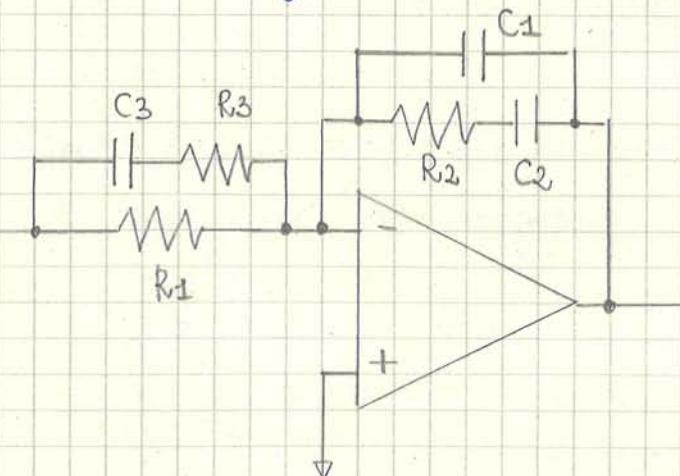So the schematic to get a TYPE 3 compensator :



$$GAIN : -\frac{Z_2}{Z_1}$$

For increasing gain I can increase  $Z_2$  or decrease  $Z_1$ .

- So  $Z_2$  can be  $-m$  no!
- or  $Z_1$  can be  $\frac{1}{T}$  ok!


{ 5 equations (not 6 because  $A_2/A_1 = f_H/f_L$  so I have only 5 indip.)  
6 elements

$\hookrightarrow$  + degree of freedom (we choose  $C_2$  [ $10\mu F \rightarrow +nF$ ])

What does zero mean? It means that there is nothing to the output. There is zero voltage at the output. In order to have it  $Z_2 \rightarrow 0$  (or at the input an infinite impedance).

$$Z_1 = R_1 \parallel \left( R_3 + \frac{1}{sC} \right) = \infty \rightarrow \text{so we find the s value and the zero.}$$

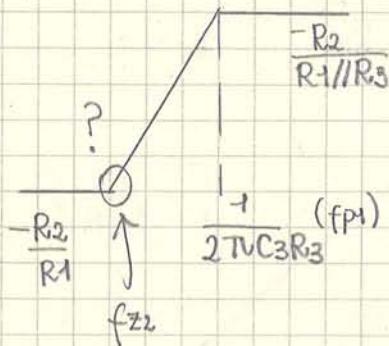Or I can say that I know the transfer function that I get :




The only unknown is  $f_{z2}$ :

$$\frac{-R_2}{R_1 \parallel R_3} = \frac{1}{2\pi C_3 R_3} f_{z2}$$

$$f_{z2} = \frac{1}{2\pi C_3 (R_1 + R_3)}$$

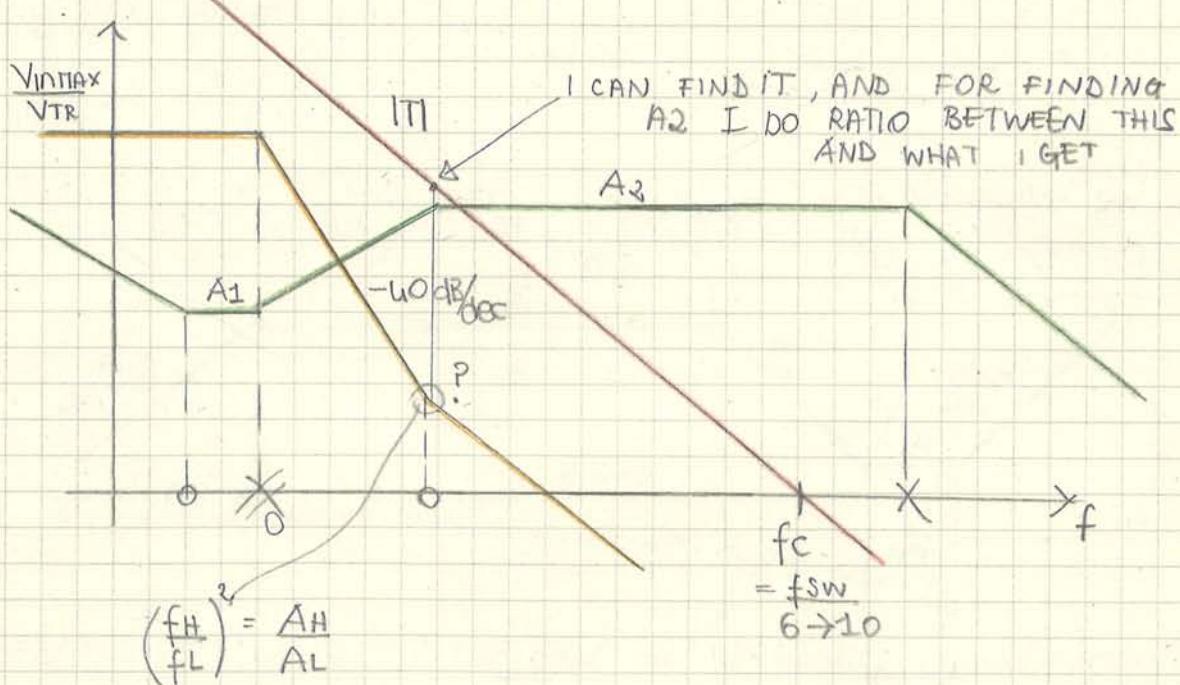NB: THIS IS EXACTLY (BECAUSE OP-AHP SEPARATES 2 IMP.)



Now let's find components values.

- Let's assume  $C_1 = \underline{100 \text{ pF}}$  (Don't use it at the exam)!

$$\bullet f_{p2} = \frac{1}{2\pi C_1 R_2} = 19 \text{ kHz} = \frac{1}{2\pi \cdot 100 \text{ pF} \cdot R_2} \Rightarrow R_2 = 83,7 \text{ k}\Omega$$

$$\hookrightarrow R_2 = \underline{82 \text{ k}\Omega}$$

$\rightarrow 5\%$  is OK

$$\bullet C_2 = \frac{1}{2\pi f_{p1} R_2} = \frac{1}{2\pi \cdot 170 \text{ Hz} \cdot 82 \text{ k}\Omega} = 11 \text{ nF}$$

$$\hookrightarrow C_2 = \underline{10 \text{ nF or } 12 \text{ nF}}$$

$\hookrightarrow$  zero moves little bit left

associated to first zero

$$\bullet R_1 = \frac{R_2}{A_1} = \frac{82 \text{ k}\Omega}{1,84} \approx \underline{47 \text{ k}\Omega} \quad \% \pm \text{ MUST BE PRECISE ! Because it determines the precision of output voltage !}$$

$$\bullet f_{p1} = \frac{1}{2\pi C_3 R_3} \quad f_{p2} = \frac{1}{2\pi C_3 (R_1 + R_3)} \quad \left. \right\} \text{ 2 EQUATIONS ; I HAVE TO FIND } R_3 \text{ AND } C_3$$

Dividing these equations :

$$\frac{3 \text{ kHz}}{340 \text{ Hz}} = \frac{R_1 + R_3}{R_3}$$

$$= 7,82 = \frac{R_1}{R_3} = \frac{47 \text{ k}\Omega}{R_3} \Rightarrow R_3 = \frac{47 \text{ k}\Omega}{7,82} = 6 \text{ k}\Omega$$

$$\hookrightarrow R_3 = \underline{6.2 \text{ k}\Omega}$$

$$\bullet f_{p2} = \frac{1}{2\pi C_3 (R_1 + R_3)}$$

$$C_3 = \frac{1}{2\pi \cdot 340 \text{ Hz} \cdot (47 \text{ k}\Omega + 6.2 \text{ k}\Omega)} = 8.8 \text{ nF}$$


$$\hookrightarrow C_3 = \underline{10 \text{ mF}}$$

It's better 10 nF because this cap gives me  $f_{p2}$  frequency (small period).

$$\text{Now let's check the gain : } \frac{R_2}{R_1 // R_3} = \frac{82 \text{ k}\Omega}{47 \text{ k}\Omega // 6.2 \text{ k}\Omega} = -16.9 \quad (A_2)$$

What is missing?  $R_{DC}$ .

So, we have to measure loop gain  $|T|$  ( $L$  for control guys) of our feed-back system. (for checking if it's ok). Let's consider any feedback system :

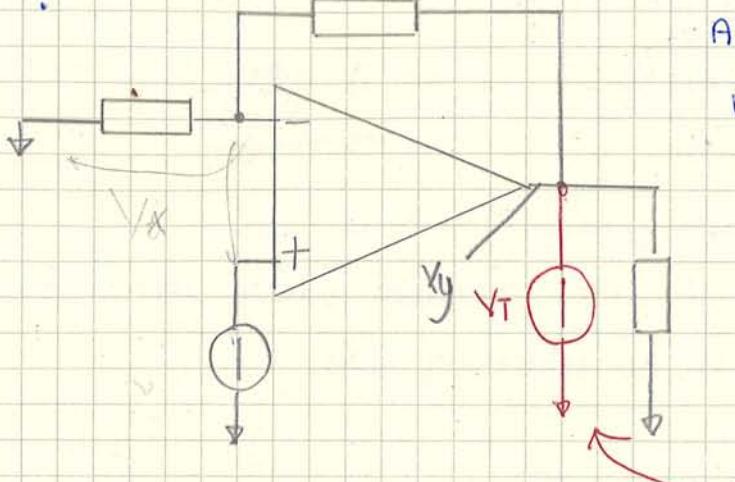


### AMPLIFIER WITH FEEDBACK.

We want to measure loop gain of this system. (it could be a compensator + pwm...). So, for do it we put a test signal  $V_T$  and we compute  $V_y$  :

$$-\frac{V_y}{V_x} = T \quad \text{CUTTING}$$

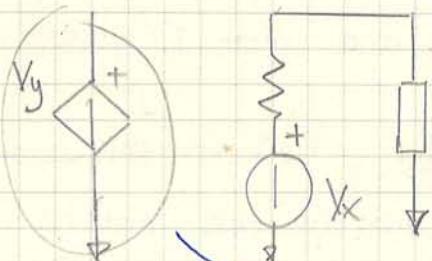On the other hand, if we cut our system saturate; I don't measure anything. There is another way to evaluate  $T \rightarrow$  Rosterstark method. Inside we have a current or voltage controlled source and I substitute it with an independent one and then the ratio between  $V_y$  and  $V_x$  is  $T$ .




$$T = -\frac{V_y}{V_x}$$

↳ this is right


Unfortunately this system can't be used because this is only a model; a symbol! And so it is not good for doing measure in the lab.

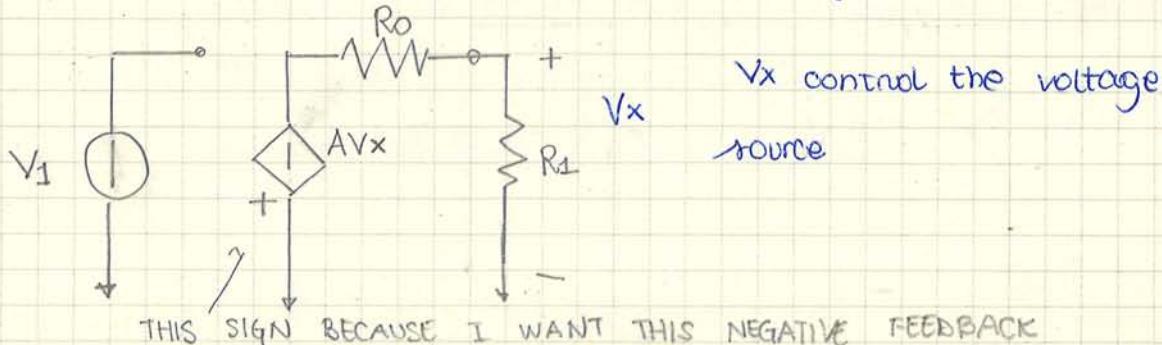Let's go to the details to see what feedback system is :



I put a voltage source  $V_Z = V_y - V_x$  that has exactly the same voltage between the 2 nodes and so nothing changes!

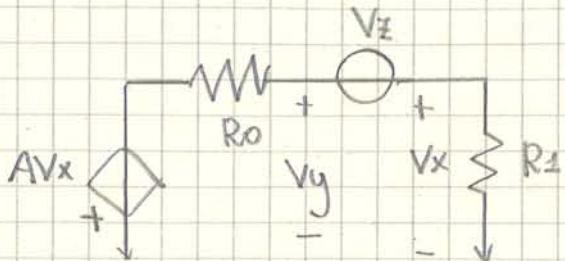The idea of Middlebrook is: if I remove  $V_x$  probably system is in the same position as before and  $T = -\frac{V_y}{V_x}$ . Is it true?



$V_y = -A V_x$  ? Not true, I have a current in  $R_0$ !

$$V_y = -AV_x - R_0 \cdot \frac{V_x}{R_1}$$


→ the current is the same!

$$V_y = -V_x \left( A + \frac{R_0}{R_1} \right)$$

And so:  $-\frac{V_y}{V_x} = T = A + \frac{R_0}{R_1}$  (3)

If  $\frac{R_0}{R_1} \ll A \rightarrow T_3 \approx T_2 \approx T_1$  GOOD APPROXIMATION

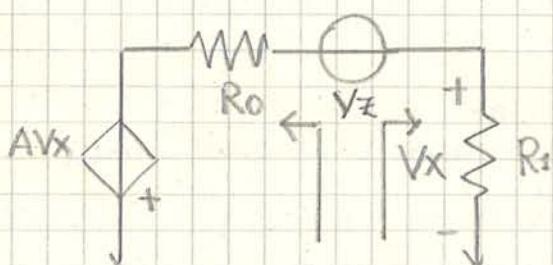This method works in the lab; and we found a method that is a good approximation. We can use this method if  $R_0 \ll R_1$  for passing from  $T_2$  to  $T_1$ ) and  $\frac{R_0}{R_1} \ll A$  (for passing from  $T_3$  to  $T_2$ ).




← It is still in linearity because I don't cut it.

- $\underline{\underline{R_0 \ll R_1}}$  (imp. looking backward far smaller than imp. looking forward). If it is true we can do the  $T$  measure in this way. In power electronics this condition is always satisfied.


Is it better ① or ②? From imp. mismatch both are ok. The offset is not a big deal because we do our measure in AC. The problem is the noise! We want to maximize  $\frac{S}{N}$ ! In ① we have almost  $\phi$ ; so it's not good!

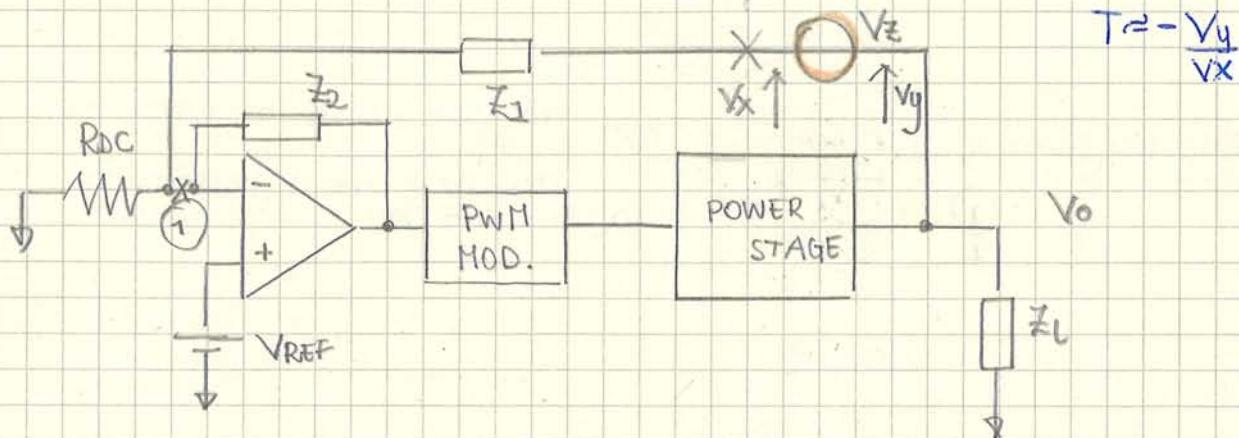And so our measurement is something like this:




There are cases where it's not too easy to measure. For example if we have high voltage we don't have voltage source that works with this voltage and in this case we have to use ①. So we need:

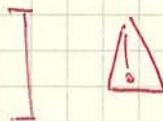
- 1) HOW TO INJECT  $V_z$
- 2) HOW TO MEASURE  $-\frac{V_y}{V_x}$



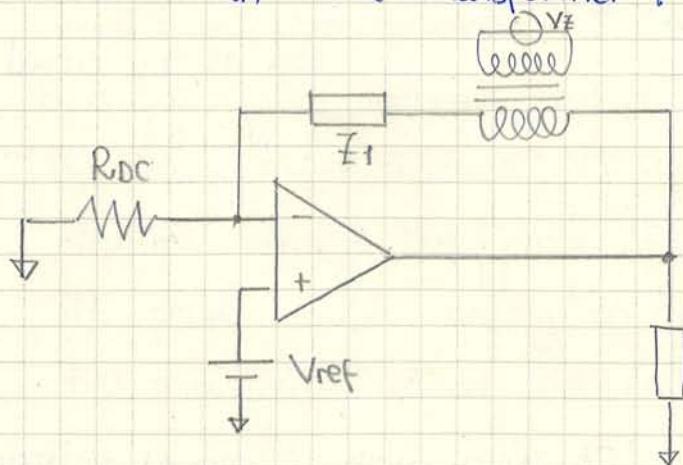1) We need a signal source and it must be floating.  
A solution can be a transformer:



But we have limitations.

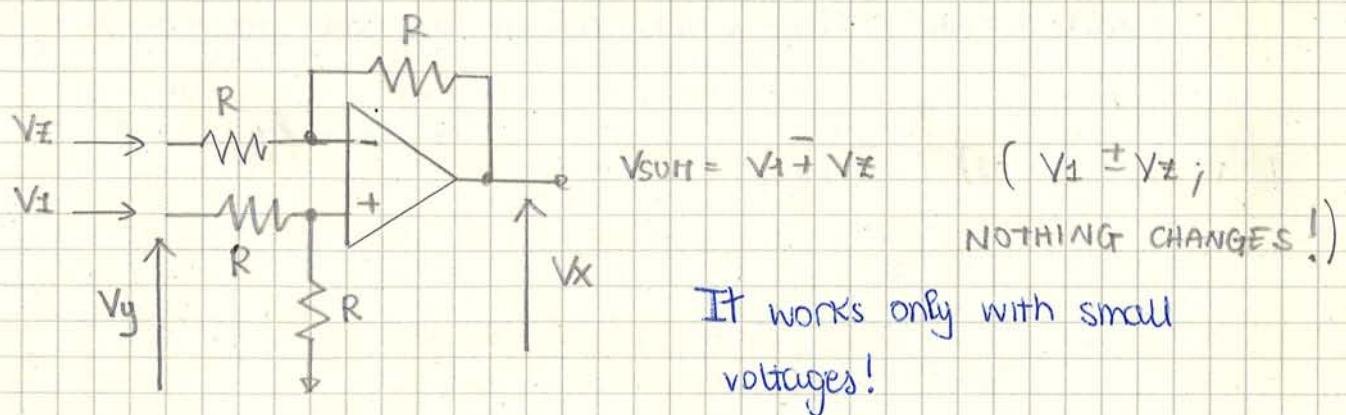


Let's try to make a transformer using op-amps and it must work exactly as a transformer. But it's more difficult.

2)  $T = -\frac{V_y}{V_x}$  ?

A)

LF NETWORK  
ANALYZER

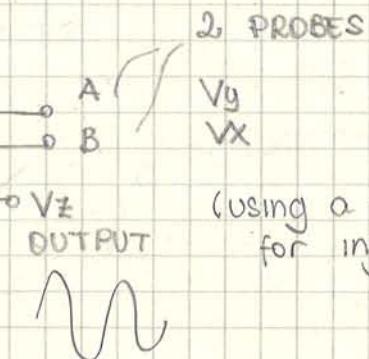

20 000 \$ !!! Very expensive.

- B) We have to measure the magnitude and the phase of 2 sinusoidal voltages. We can use the scope. It takes a long time! We have to repeat the procedure for many frequencies! It is nice to use when we have to determine the crossover freq. [it means  $|T| = 1$  and  $V_y$  and  $V_x$  has same amplitude; then we measure the phase diff @ fc and we find the phase margin directly on the scope (because we have the minus that cancel out  $180^\circ$ )]

There are other techniques for measure indirectly the loop gain.

$$AF = A_\infty \cdot \frac{T}{1+T} \quad \rightarrow \text{we find } T \text{ from this equation (after measured } AF \text{ and } A_\infty)$$

If  $|T| > 1$ , it's difficult to determine




THIS INPUT DOESN'T EXIST

What we could do instead of measuring the gain, we can try to measure the output impedance:


$$Z_{O(s)} = Z_D \cdot \frac{(1 + T_{sc})}{(1 + T_{oc})} \quad \text{BLACKMAN}$$

In frequency domain it's hard

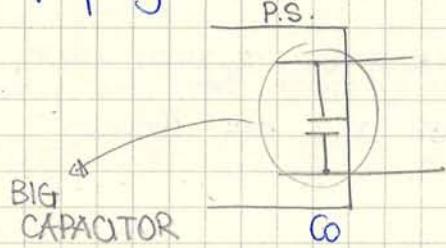


P.S.

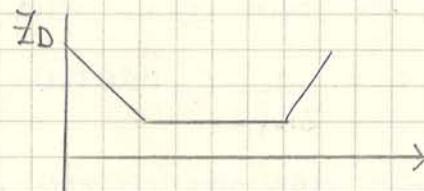This big capacitor has low impedance and it is modify by feedback



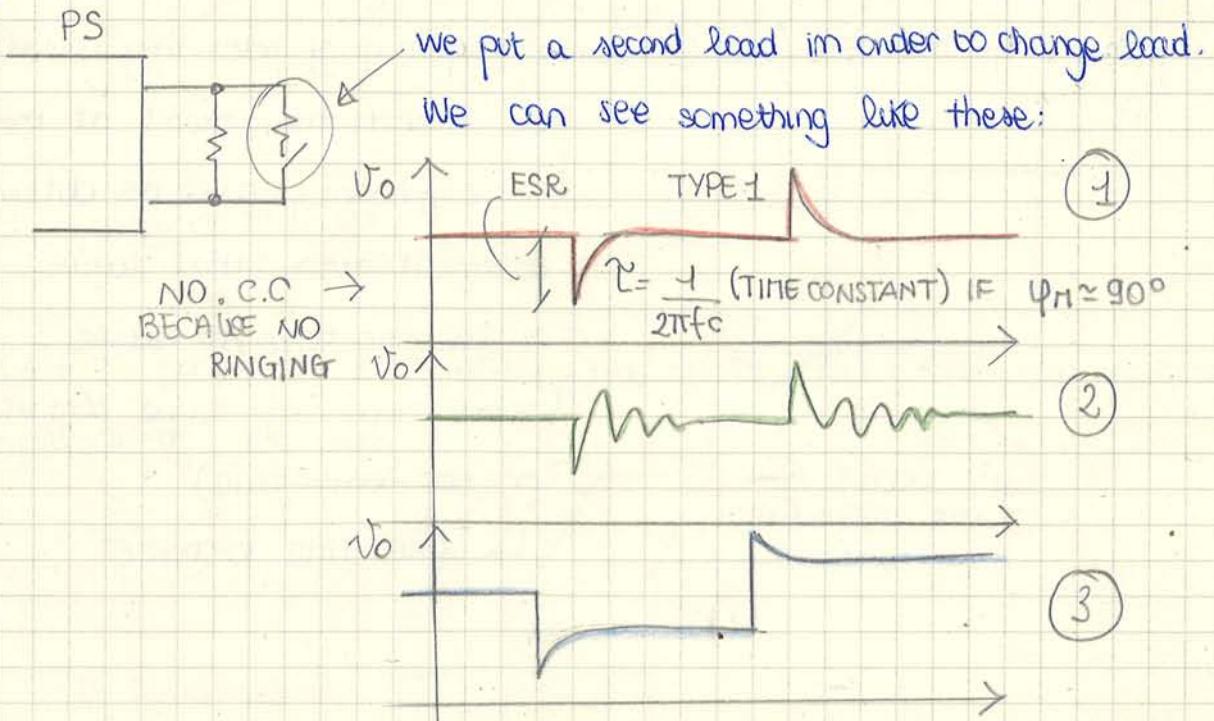
Another way is in time domain looking at the output voltage when load changes!



In ② we have open loop output impedance. Since we have a ringing it means that  $\eta_M$  is low

In ③ we have type φ system; it doesn't return to the nominal value

## CONTROL TECHNIQUES

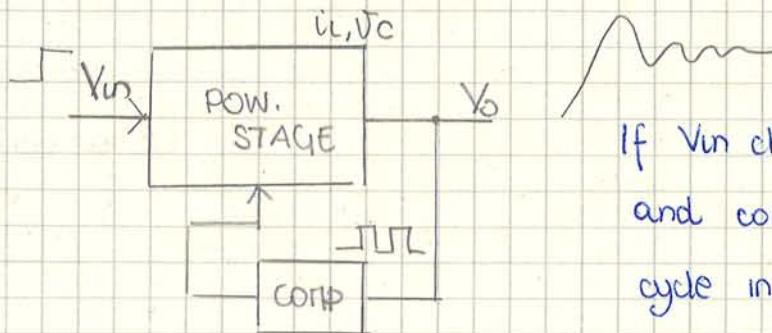

If  $V_{in}$  changes  $v_o$  changes and comp. decreases duty cycle in order to have  $v_o$  constant.


But for this method it takes sometimes before that control system recognized that there is something wrong; But there is a technique that "feel" the changes in real time and if we don't lose too much time and if:

$$V_{in} \uparrow \rightarrow D \downarrow$$

In some cases could be helpful. If we have PWM MODULATOR:



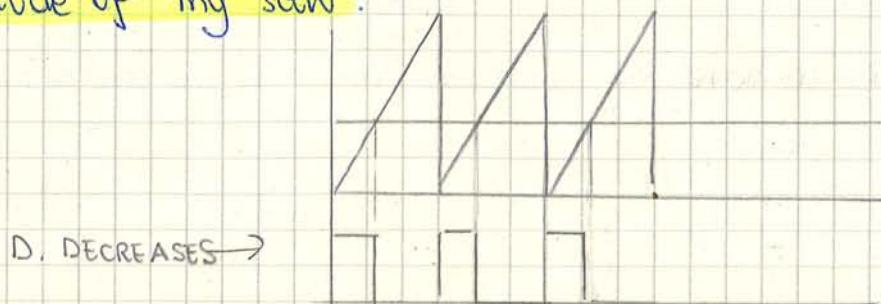
HOW CAN I DECREASE IMMEDIATELY THE DUTY CYCLE? We can increase the amplitude of my saw:



The next step is to measure the inductor current and the output voltage and we can design a better control system. Now see **CURRENT MODE**

The idea is:

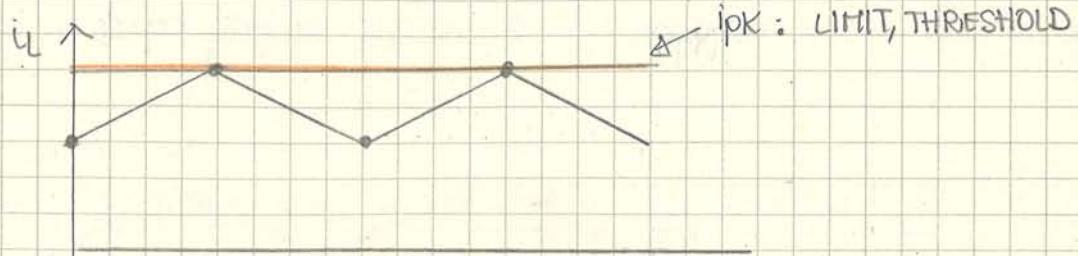If I consider inductor current in a buck converter :




When  $i_L$  reaches  $i_{pk}$  limit, I open the switch. Basic working steps are:

- AT THE BEGINNING OF THE CYCLE CLOSE THE SWITCH
- WAIT UNTIL  $i_L$  REACHES  $i_p$
- OPEN THE SWITCH
- WAIT UNTIL THE BEGINNING OF THE NEXT CYCLE

**STEPS  
FOR  
C.M.**

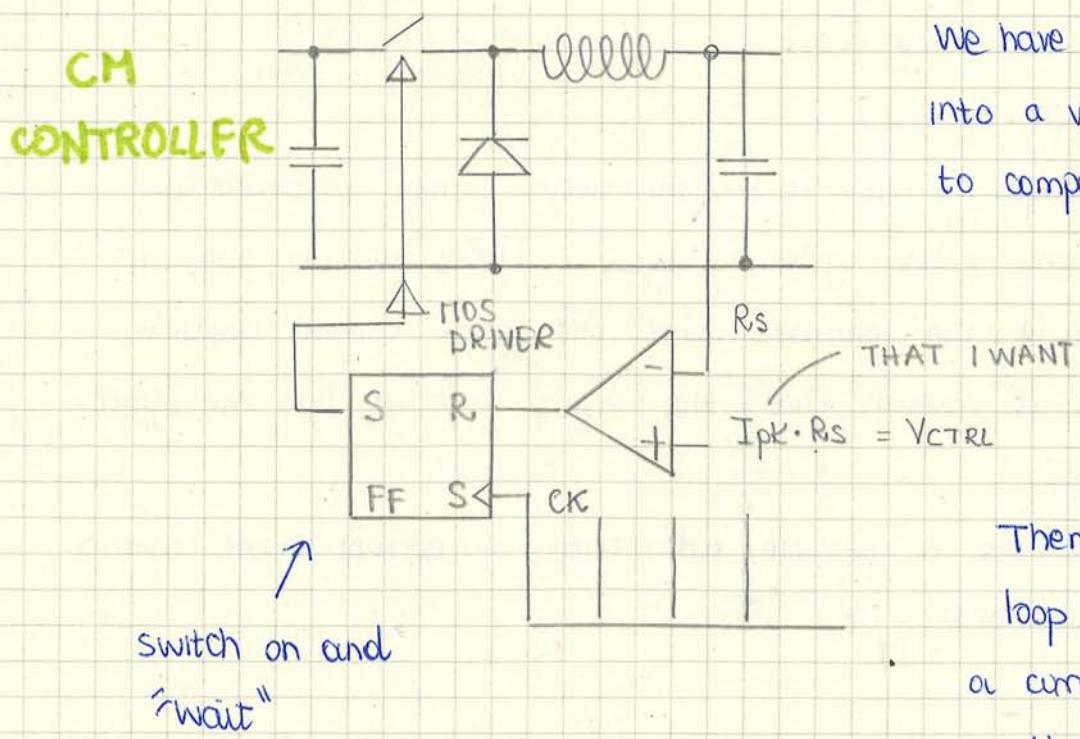
NB: we can assume that  $\bar{i}_L$  and  $i_{pk}$  are almost the same if ripple is very small. The circuit to implement this method (this behaviour) is : (it's valid for any topology). For example for BUCK:



It means that :

$$\frac{V_{CTRL}}{R_s} \approx \bar{i}_L$$

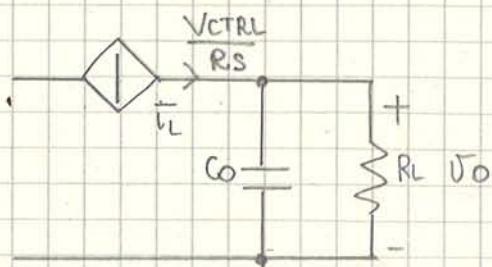the inductor becomes a controlled current source :



This is because I close a loop and it keeps my current constant.

So this is my system and inside the symbol there are all the other components.

$$V_O = \bar{i}_L \left( R_L \parallel \frac{1}{sC} \right) \approx \frac{V_{CTRL}}{R_s} \left( R_L \parallel \frac{1}{sC} \right)$$

$$= \frac{V_{CTRL}}{R_s} \cdot \frac{R_L}{1 + sCR_L} \Rightarrow \frac{V_O}{V_{CTRL}} = \frac{R_L}{R_s} \cdot \frac{\bar{i}}{1 + sCR_L}$$

Actually, I have to consider ESR and my transf. function becomes:

$$= \frac{1 + sCESR}{1 + sC(R + ESR)}$$

$\cancel{R \ll R}$

I need to have a L.T.I system!


We have done the steps for linearizing; one is this:  $\frac{V_{CTRL}}{R_s} \approx \bar{i}_L$

$\bar{i}_L$  is linear (already).

$$\text{So : } \frac{V_O}{V_{CTRL}} = \frac{R}{R_s} \cdot \frac{1 + sCESR}{1 + sCR_L}$$

→ TRANSF. FUNCTION BETWEEN  
OUTPUT VOLTAGE AND PEAK  
CURRENT



AVERAGE

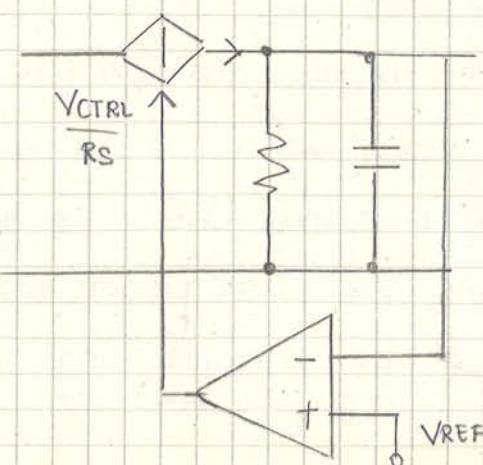

This has one pole and one zero.

The HF behaviour is independent from the load. (Yeah!) And from  $V_{IN}$ !

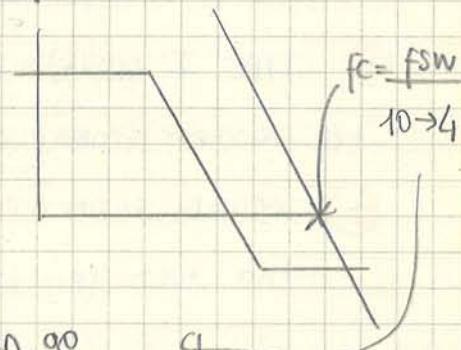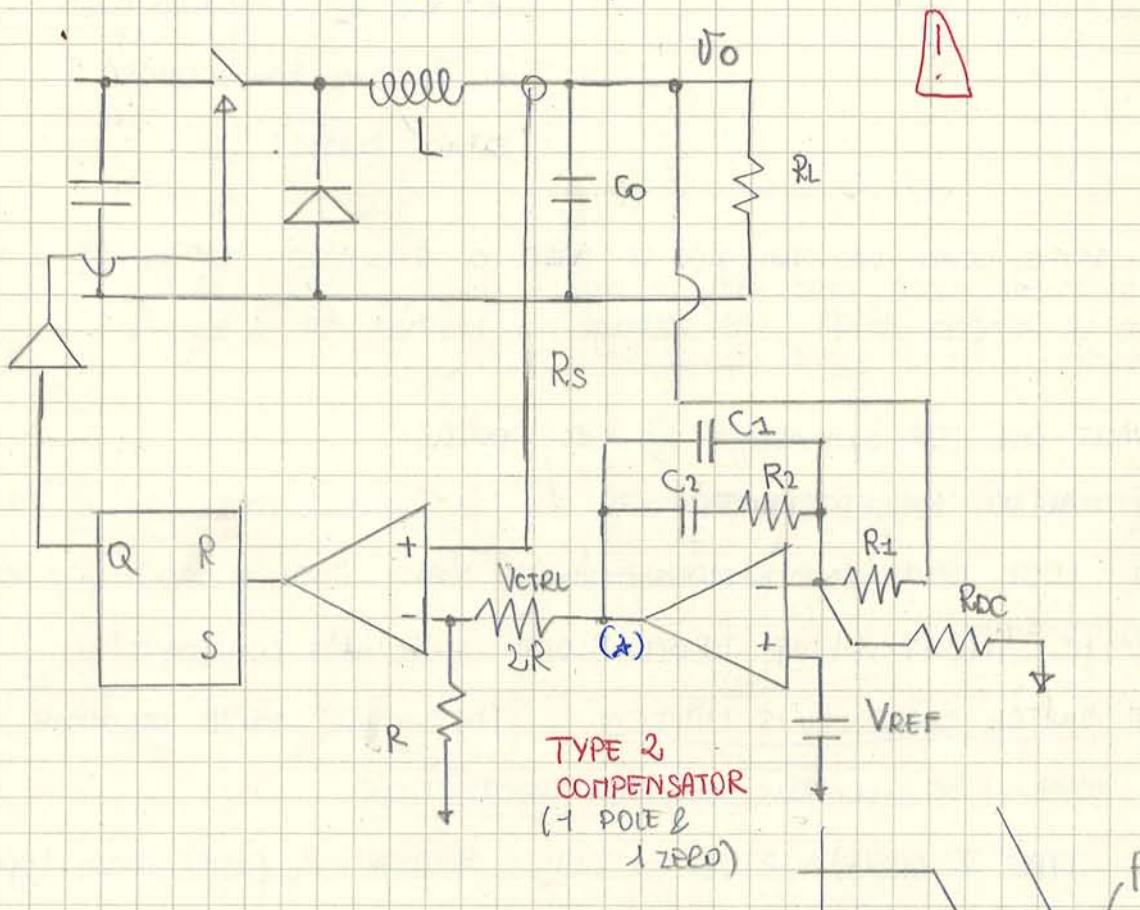So, let's go back to the original circuit:



How DOES IT WORK?

The clock put my switch on periodically.

$V_{CTRL}$  comes from the compensator and it adjusts the controlled current source go up or go down.

We have 2 loops: one fast (internal loop) and the other one is slow.  
NON LINEAR


I want a large voltage in (\*) because I have to compare it. In this way I haven't too much problem with noise. On the other hand I need a big voltage on  $R_S$ ! It means much losses. (large power dissipation on  $R_S$ ). The standard is  $i_L \cdot R_S MAX = \pm 1 V$ . So we put 2 resistors (a voltage divider); and the compensator can go up to 3V. In some cases we put a diode before 2R:

we can go higher because  $f_C$  is constant (more or less)

And disadvantages?

- COST (because we have to sense  $i_L$ )


- NOISE SENSITIVITY

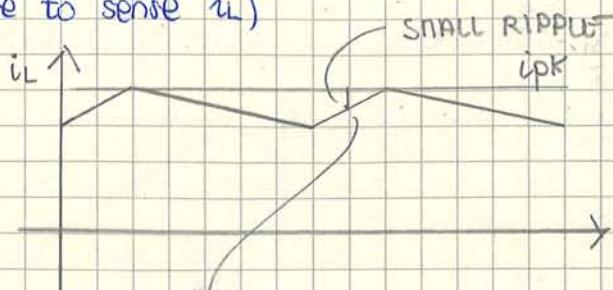


If I have a spike here, since the ripple is very small, if there is some noise immediately the switch is on!

It's not a big deal because if we decrease duty cycle the voltage starts to decrease and then the compensator adjust it.

-  $i_L \neq ipk$

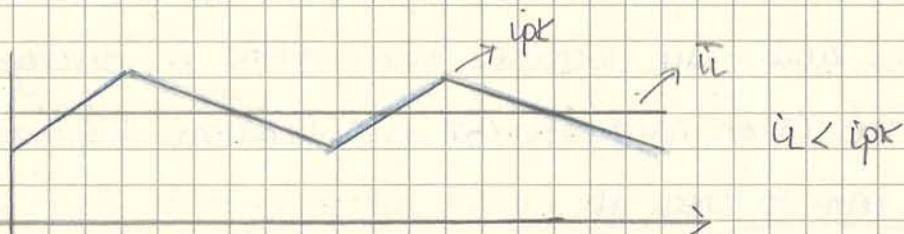

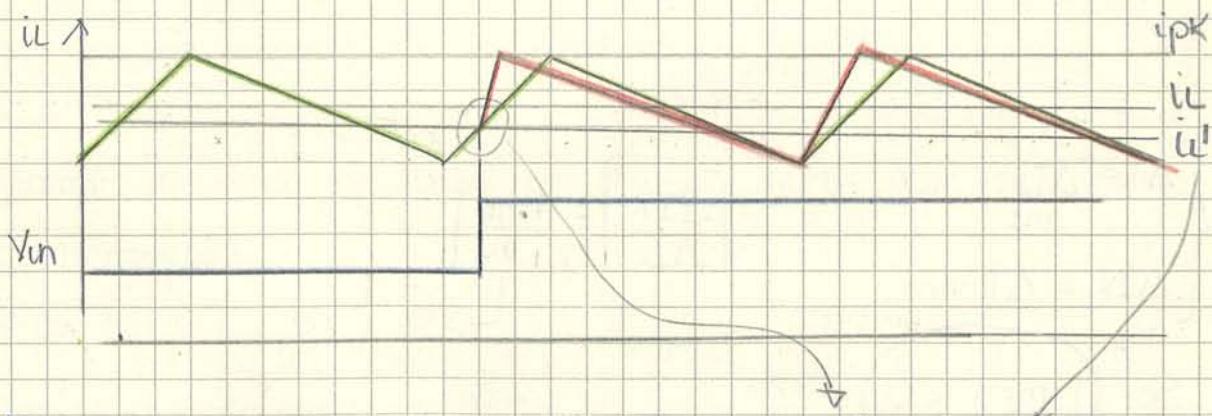For steady state condition is not a big deal because if the current that we provide is <sup>too</sup> small the voltage will be <sup>too</sup> small and the int. voltage loop increase the requested current  $ipk$  value in order to get exactly the output voltage. So this error can be compensated by voltage loop; but let's consider for example :



If  $V_{in}$  increases, I have that D decreases immediately and the average current goes down and so we have an error of average current.

$$m_1 = \frac{\Delta I_{pp}}{T_{on}}$$

$$m_2 = \frac{\Delta I_{pp}}{T_{off}}$$

So :

$$\frac{\Delta I_{pp}}{T_{off}} \cdot \frac{T_{on}}{\Delta I_{pp}} < 1$$

$$\boxed{\frac{T_{on}}{T_{off}} < 1}$$

CONDITION FOR STABILITY

It means that duty cycle must be  $< 50\%$  

If  $D > 0.5$  it happens that the final error is larger than the initial error. (and final error will be larger and larger than initial error ...) Incredibly  $V_o$  stays the same.

For example, instead of having :

$D_1 \ D_2 \ D_1 \ D_2$


we have : (with instability)

$D_1 \ D_2 \ D_3 \ D_4$

$70\% \ 60\% \ 85\% \ 55\%$  (Now the instability is  $\frac{1}{4}$  of fsw)

So if we go more and more we have many cycle!

DACTUAL ↑

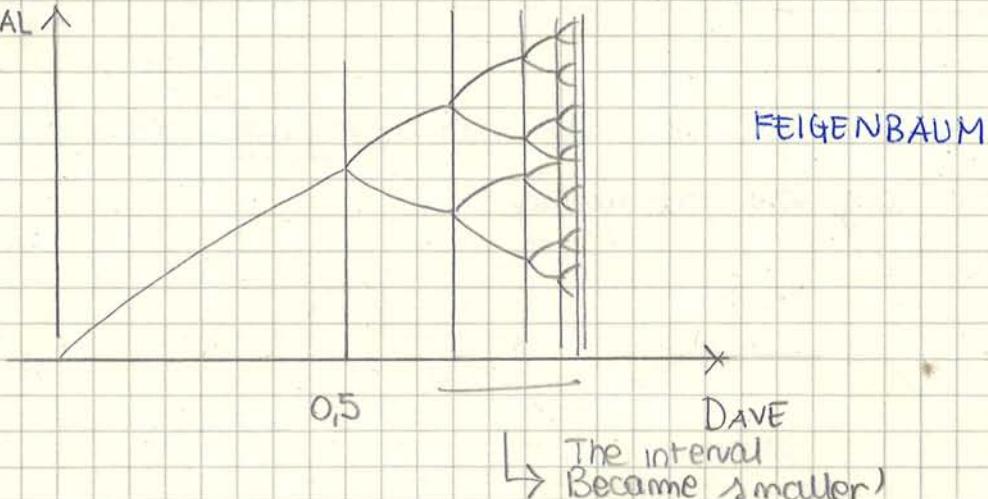


DAVE  
The interval  
became smaller


The same correction for subharmonic stability works also for  $i_L \neq i_{pk}$ .

(Same techniques).


- $i_L \neq i_{pk}$

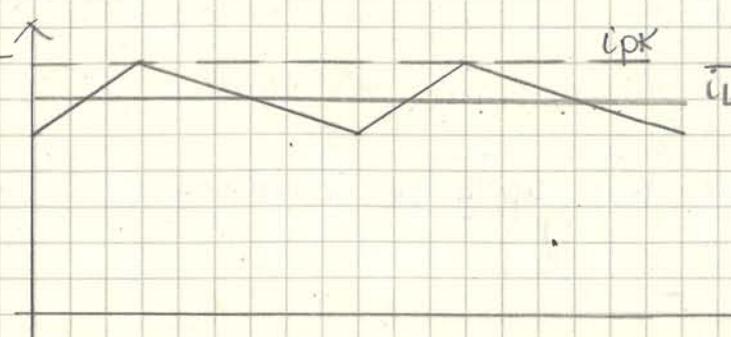


BUCK  
CONV.

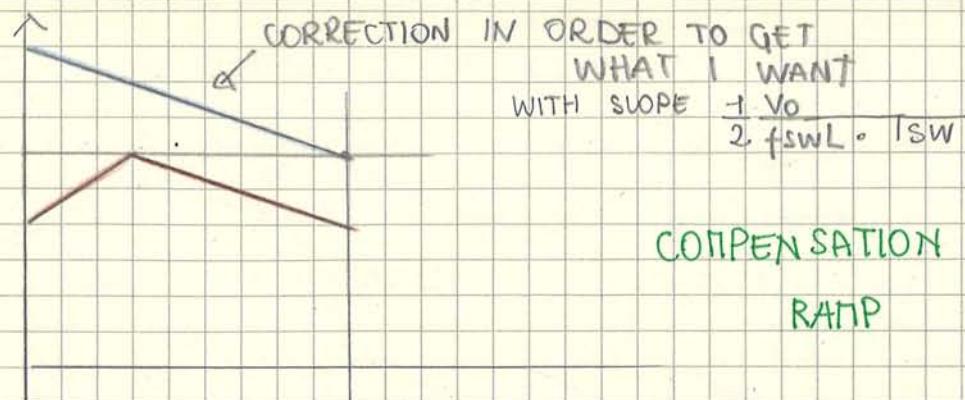

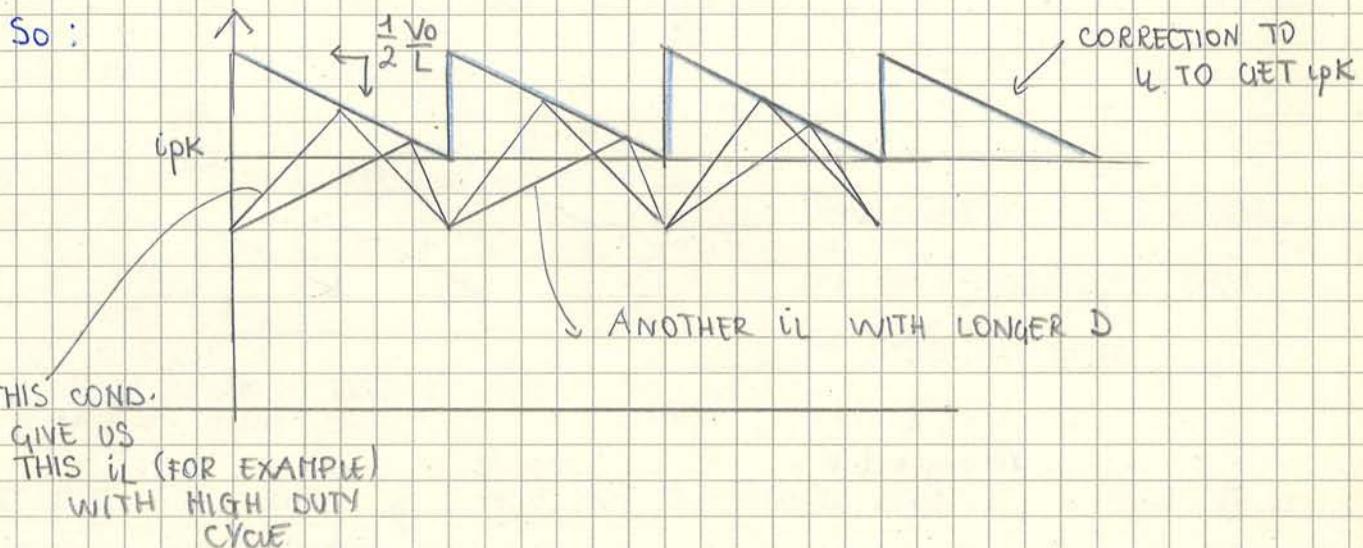SLOPE :  $\frac{1}{2} \frac{V_o}{L f_{sw} T_{sw}} = \frac{1}{2} \frac{V_o}{L}$  (our slope doesn't depend on D and V<sub>in</sub>!)




A circuit that implements this is :

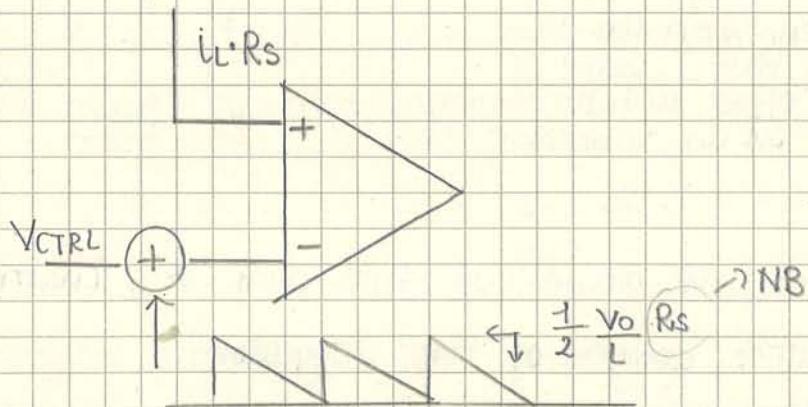

It is never done because this waveform is not easy to generate.


It's better put a compensation ramp on the other side of the comparator. But in this way I have to flip down the ramp :

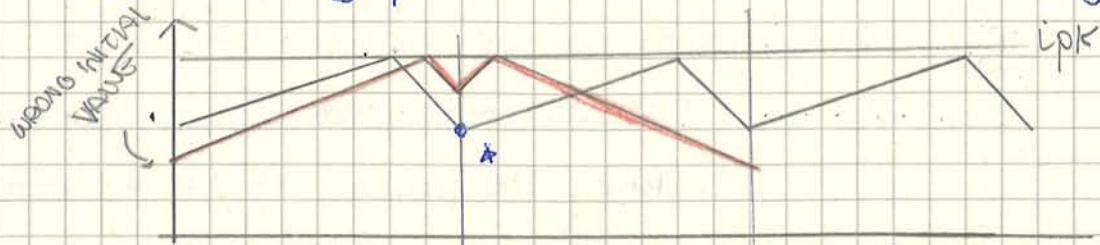We saw that a big problem is the subharmonic instability:



↳ Duty cycle > 50 %

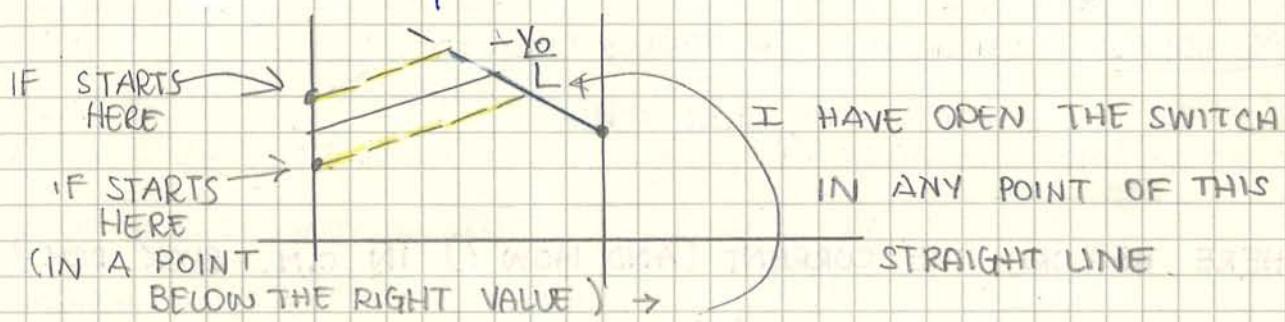
A way to correct this error is the compensation ramp. Compensation ramp for correcting sub-harmonic instability is different than we saw last time. I want that at the end of the cycle the current is here A. For example:



So with the slope  $-\frac{V_o}{L}$  I kill the subharmonic instability. Since  $V_o$  is almost constant the slope is fixed.

# POLES in CM (com). How many poles do we have?

Buck is (with a good approximation)

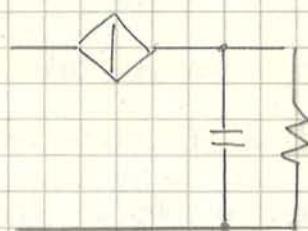

- 1 POLE @  
 $\frac{1}{2\pi RC}$

In the original scheme, if I have a feedback it only moves the pole! (it doesn't add anything). Somebody discovered that this pole moves to high frequency; graphically speaking:

- 1 POLE

- 2 POLES :  $\frac{1}{2\pi RC \omega}$ ; HIGH FREQUENCY ( $\frac{f_{sw}}{\pi}$ )

It can decrease phase margin but no too much; because our  $f_c = \frac{f_{sw}}{5}$


peak current during  $T_{on}$  (like 7)

- 8, NO! Because it's just the average value!
- 7, NO! It's only AC current; I need the total, the actual current.
- 9, I have the inductor current here; it could be a good point but remember; If I connect it to the ground it's a problem!
- 10; same story
- 13, NO we have only AC value.


SO THE GOOD POINTS ARE 2, 3, 4, 5.

THEY SHARE SOME PROPERTIES

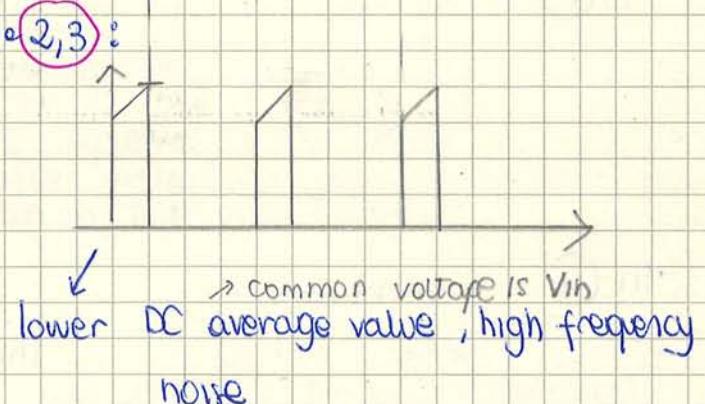- (3,4): In 2 we have  $V_{in}$  that is a DC voltage. The voltage in 3 and 4 is a square wave. So they have a  $V_{noise}$  (up and down 0 to  $V_{in}$  etc...)
- (4,5): they have in common the current. But it is:
- (2,3):  $V_{quiet}$  (DC voltage)



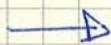The number 4 is not used. So which one do we choose? It depends on the technique that we use to sense the current.



In 2 power dissipation is smaller than 5, because in 5 the current flows all the time! (in 2 only in D).


So 2 is better from pow. dissipation point of view.

But in 2 we have a smaller DC value ( $V_{in} < V_o$ ). So measure when the voltage is higher is better. Inside an IC the resistor is put in 5 and the measure is easier. Quantity that we have to define:


- $R_s = \frac{V_{SENSE\ MAX} (1V)}{I_{LPK}}$  →  $R_s$  ACTUAL must be smaller, otherwise  $I_{LPK}$  decrease.
- $P_D = R_s \cdot I_{RMS}^2$   
↓  
ACTUAL

$R_s$  must be a non-inductive resistor.


What happens if:

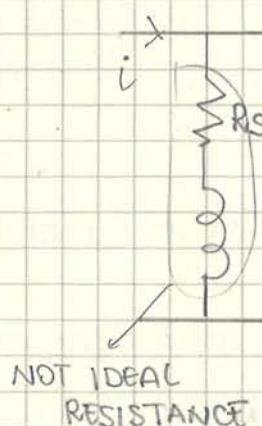


If we send an  $i$  that is:

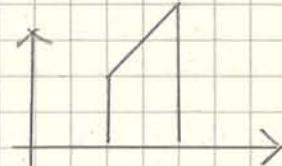

What kind of voltage we have?

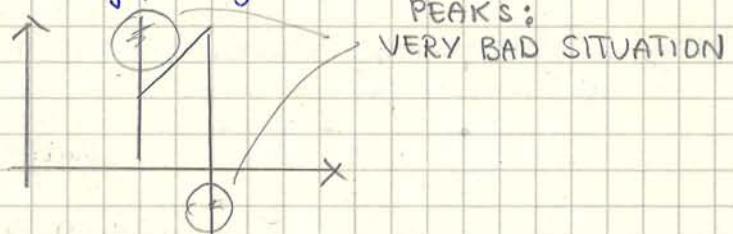

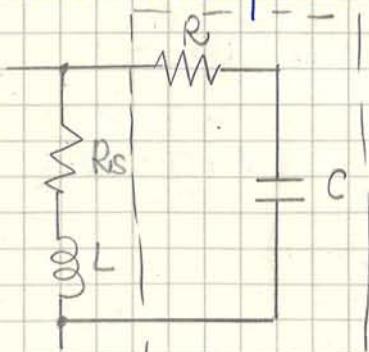We can control these peaks with a low pass filter:



→ this low pass filter remove the peaks. In order to cancel it:


$$\frac{L}{R_s} = RC$$

But in many cases:

$$\left. \begin{array}{l} R = 1 k\Omega \\ C = 470 \text{ pF} \end{array} \right\} \text{FOR CANCEL INDUCTIVE EFFECT OF } R_s$$

AT THE OUTPUT.

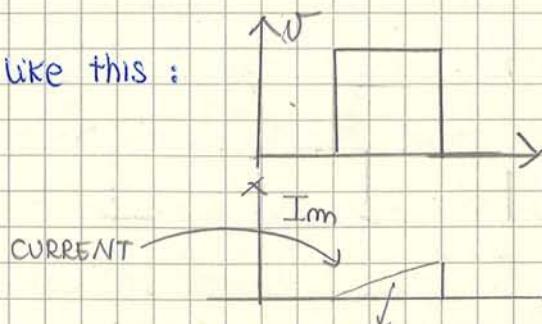But ... if we apply a voltage like this :




SLOW BECAUSE  $L_m$  IS LARGE

And so at the output we obtain more or less the input pulse.

NB: After a certain number of pulses it saturates; but the idea is ok.

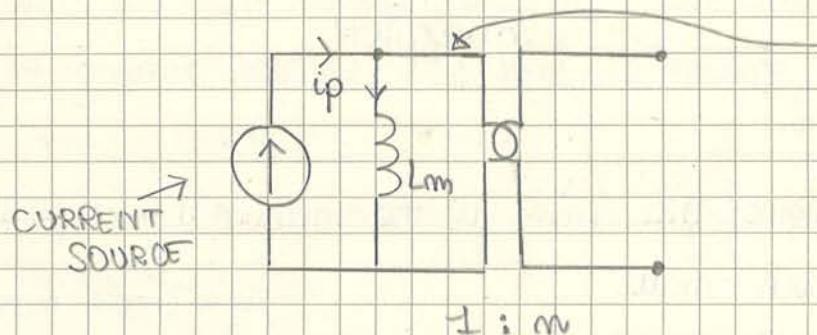But in our case we want to measure a current; so :




IN THIS POINT we have

$$i_1 = 0, \text{ because}$$


$$i_1 = i_2 \cdot m \quad (\text{but } i_2 = 0)$$

And so we have :

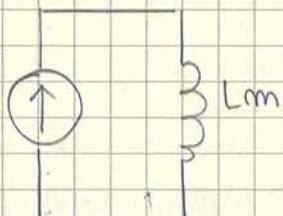

In this way we have a big spike of voltage.

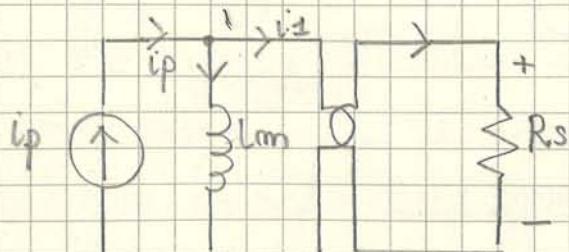for this reason we need to put a load resistance at the secondary:



in order to make a good measurement I want that :

$$\underline{\underline{i_m \ll i_2}}$$

↳ in this way  $L_m$  is not important


And so at the output we have :

$$V_o = i_p \cdot \frac{1}{N} \cdot R_s$$

discharge  $L_m$ .

Bad news:  $i_{im}$  is a small current, and when it goes to the output it generates a very small voltage drop and when it comes back is not enough to discharge  $L_m$ . It means that if we want to discharge  $L_m$  with this voltage we need long time!


So the next pulse must be:

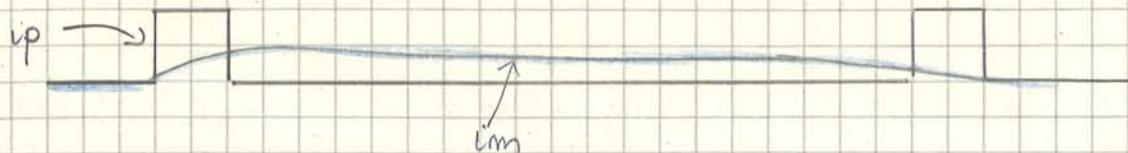

So it is impossible to use. How CAN WE DISCHARGE QUICKLY AN INDUCTOR with an high voltage across it. We should increase  $R_s$ . But it can't be greater because it's here to measure the  $i_p$  current not the  $i_m$ ! OUCH!

So we can put a diode:

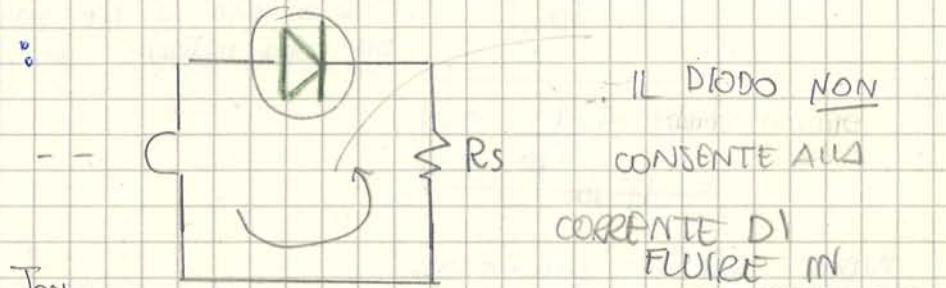DURING  $T_{ON}$  I WANT THAT THE CURRENT FLOWS IN THE RIGHT WAY.



IL DIODO NON

CONSENTE ALLA

CORRENTE DI FLUSSO IN QUESTO NODO

So during the phase  $\checkmark T_{ON}$  :  $V_o = R_s \cdot \frac{i_p}{N}$  (DURING  $T_{ON}$ ); then switch open and the current goes to 0 and current flows to the secondary side but there is the diode; so the inductance is open; and there is a voltage spike (we don't destroy any component)

Is  $V_o$  still the same if I add a diode? It's the same! It's a current!

We have some extra  $i_{im}$ ... but who cares!

So we can have an higher duty cycle.

What are advantages of curr. transformer?

- (+) ISOLATION
- (+)  $R_s$  (SECONDARY) HAS A PD LOWER BY  $N$
- (-) COST

So:

$$P_{R's} = \frac{I_{SW_{RNS}}^2 \cdot R_s}{m} = \frac{P_{Rs}}{m}$$

So the power dissipated by R's is < than Rs.

EX:


$$P_{R's} = \frac{2.5 \text{ W}}{50} = \frac{1}{2} \text{ W OK!}$$

So we have to use current transformer when the power dissipated by Rs is too much. (Otherwise we loose efficiency!) 


We saw that C.M removes one pole from CCM transfer function (see BUCK conv.). What about boost or buck-boost in CCM? We have 2 poles and if we close a loop around inductor, probably inductive poles moves to high frequency as well. But what are problems of these topology used in CCM? RHP zero. And it can't be removed by C.M? Unfortunately no. (Also in V.M.)

What about DCM?

BB DCM (can we use current mode?)

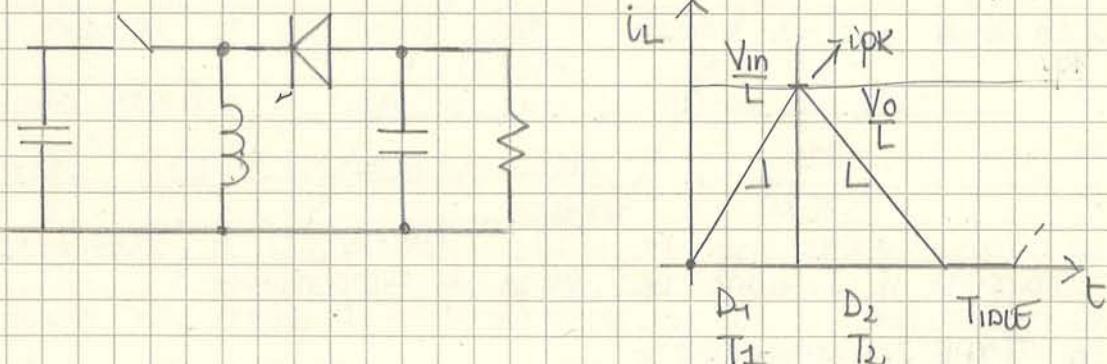

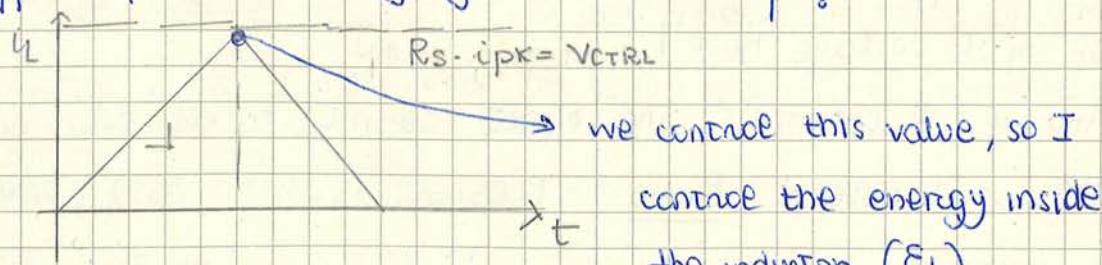What happens if instead duty cycle we control ipk?



$$EL = \frac{1}{2} \cdot L \cdot I_{pk}^2$$

, And so:

$$EL = \frac{1}{2} \cdot L \cdot \left( \frac{V_{CTRL}}{R_s} \right)^2$$

# DERIVED TOPOLOGIES (BASIC TOP. + TRANSFORMER)


- BUCK + TRANSF.  $\Rightarrow$  : there are many topologies
  - FORWARD
  - PUSH PULL
  - HALF BRIDGE
  - FULL BRIDGE
- BOOST + TRANSF.  $\Rightarrow$  Not used very much. (Boost is only used as PFC)
  - CURRENT FED CONVERTERS
- BUCK-BOOST + TRANSF  $\Rightarrow$  FLY BACK conv. (is the most used topology in the world). But it can only work in DCM.

## TRANSFORMER (HF)

Studiare bene per l'esame (teoria)

AAA

- + ISOLATION (very important, don't forget it!)
- + MULTIPLE OUTPUTS
- + NO LIMITATIONS ON  $V_o$  VS  $V_{in}$ . (very important because for example, if we want boost a voltage we can use a buck derived topology!) and  $V_o$  can be larger than  $V_{in}$ .
- + EXTRA DEGREE OF FREEDOM  $\frac{N_p}{N_s}$ 
  - $\rightarrow$  CHOOSE A "CONVENIENT" DC. A good choice is take a DC longer as possible (for some topology 80%, because the switch is cheaper)
  - $\rightarrow$  MOVE STRESSES AROUND : we can decrease the stress of some component ; but I increase it on other part. (we just move them to another place)
- + LIGHT AND SMALL COMPARED TO 50 Hz TRANSFORMER
- COST, WEIGHT, VOLUME, \$
- DIFFICULT TO DESIGN
- PARASITIC ELEMENTS (LOSSES)
  - (PEAK LOSS), (LEAKAGE INDUCTANCES THAT LIMIT fsw)

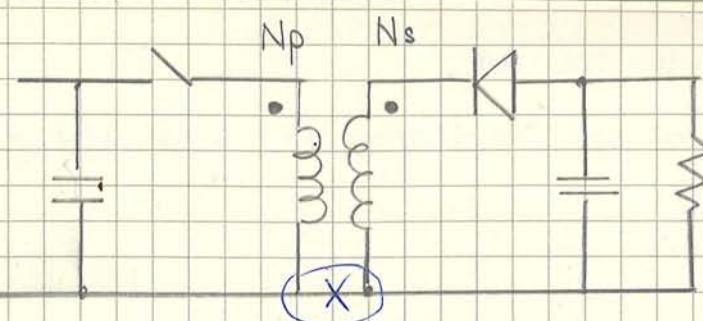


FLY BACK


↳ If I remove this ground they are isolated.

The output voltage has no relationship with the input!

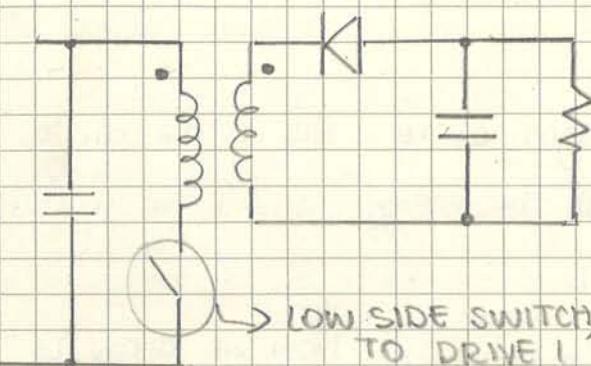We can do some changes: switch and primary L are connected in series and then I can swap them:




It is still a flyback conv.

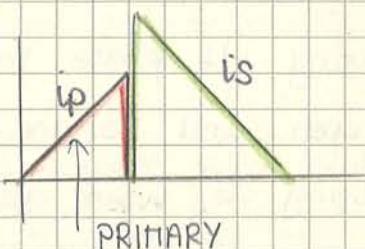

We can control it in voltage mode and current mode. In the last mode we can sense the current with  $R_s$  in series with the switch: with  $V_s$  on  $R_s$ , I don't lose any drive capability.



Can I use  $R_{DS(on)}$  in order to measure the current? We can't use it in discrete case.  $R_{DS}$  changes with temperature!

Last change is:

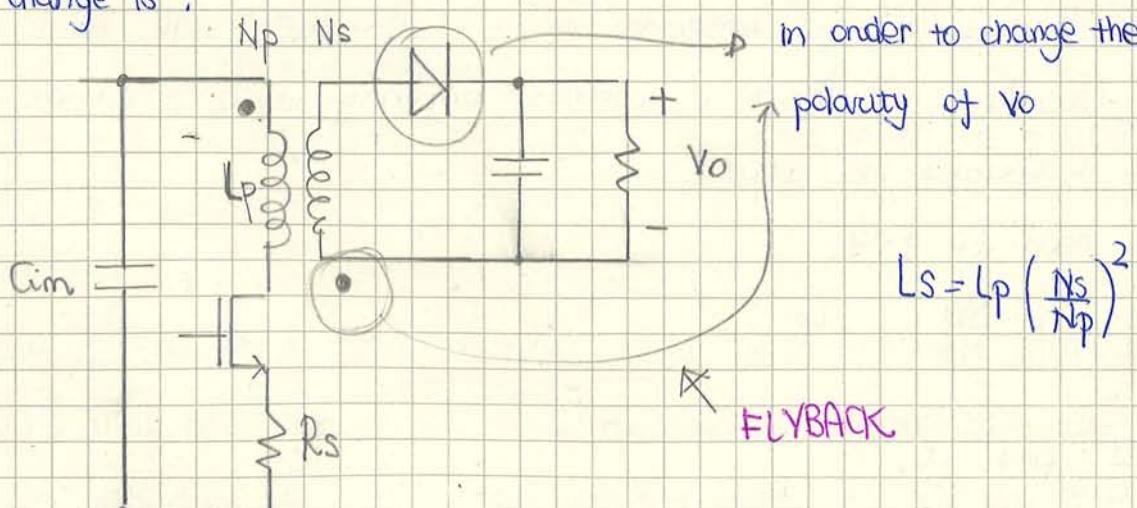


$$L_s = L_p \left( \frac{N_s}{N_p} \right)^2$$

$\frac{N_{S1}}{N_{S2}}$

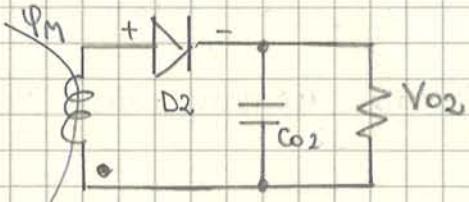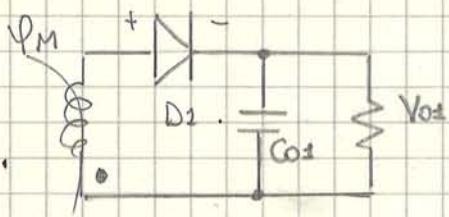

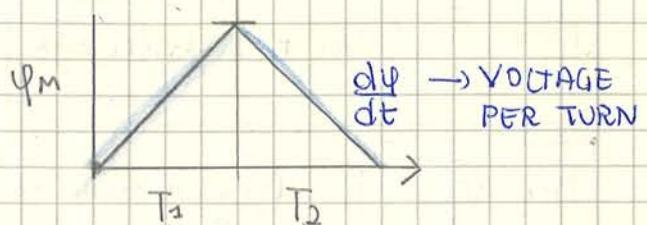Both of them feel the same flux  $\Phi_M$ . It means that when I open the switch the flux starts:



$\frac{d\Phi}{dt}$  is the same for each turn of the winding. If I want that  $V_{01}$  has double voltage respect  $V_{02}$  we can imagine that the first one has double turns respect the second one. We have to consider the voltage drop across the diode; so:

$$\frac{N_{S1}}{N_{S2}} = \frac{V_{01} + V_{D1}}{V_{02} + V_{D2}}$$

$N_{S1}$  and  $N_{S2}$  are integer numbers

We put two different voltage diode because we can have two diff.

output voltage; for example if we have  $V_{01} = 5V$  we can use a Schottky diode ( $\sim 0.5V$ ).

•  $L_p \Rightarrow$

We can choose our duty cycle with the turn ratio.

To find out  $L_p$  we have to do an initial choice: DCM. It means that

$D_1 + D_2 < 1$ . So my initial choice is that  $D_1$  must be  $\approx 40\%$  and  $D_2 \approx 40\%$ .

fsw ( $\approx 300$  kHz).

We have to find the TOTAL OUTPUT POWER and then the TOTAL INPUT POWER. They are the same? In a real world no! we have losses! we can estimate it. And then we can find the ENERGY PER CYCLE and then  $L_p$ .

But  $\epsilon_p$  is equal to  $\frac{Ps}{fsw \cdot m_{MAGN}}$

So we have:

$$\frac{Ps}{fsw \cdot \eta} = \frac{1}{2} L_p [(V_{in\min} - V_{sw} - V_{Rs}) \cdot D_1]^2 / L_p^2 \cdot fsw^2$$

And finding out  $L_p$ :

$$L_p = \frac{[(V_{in\min} - V_{sw} - V_{Rs}) \cdot D_1]^2 \cdot \eta_{MAGN}}{2 fsw \cdot Ps}$$

ONLY IN C.M. !!!

We need the turn ratio  $\frac{Ns}{Np}$ .


In steady state across any winding:  $\bar{V} = 0$

current starts to increase!



if we have it  $\neq 0$ , the

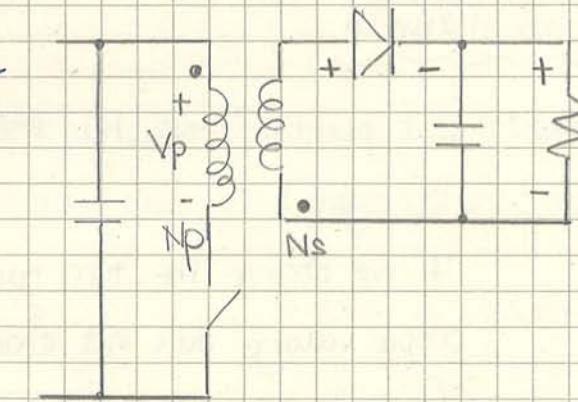In some cases we have to guarantee it. Let's consider:



$V_p$  during  $D_1$ :

$$V_p = V_{in} - V_{sw} - V_{Rs}$$

they are not

constant. They  
depend on current!

But we take the maximum  
for worst case.

$V_p$  during  $D_2$ : (switch open)

is given by the secondary voltage reflected to the primary side.

$$V_p = -(V_o + V_D) \cdot \frac{N_p}{N_s}$$


For designing any magnetic component I need  $\bar{V}_p = 0$  :

$$= D_1 \max (V_{in\min} - V_{sw} - V_{Rs}) - D_2 \max [V_o + V_D] \frac{N_p}{N_s}$$


So finding:

$$\frac{N_s}{N_p} = \frac{D_2 \max (V_o + V_D)}{D_1 \max (V_{in\max} - V_{Rs} - V_{sw})}$$

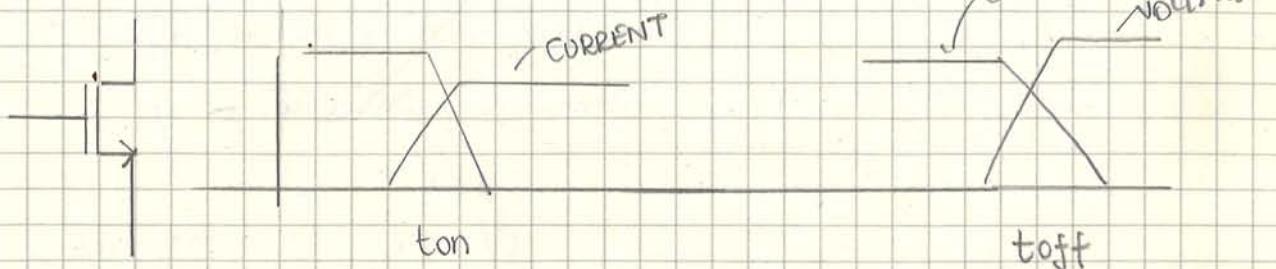Let's see something about speed in MOS transistor.



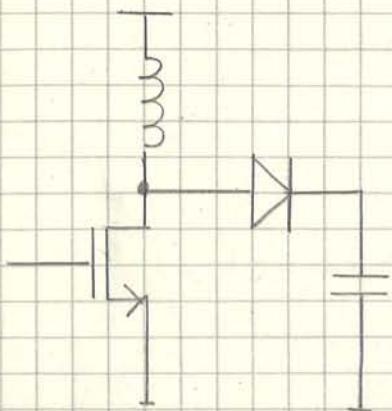
How can we drive the MOS transistor in order to have a short ton and toff?



MOS transistor are device controlled by charge (also bipolar transistor).

It means that we have to inject charge quickly! Fast! and extract it quickly as well. (otherwise toff and ton are too long)

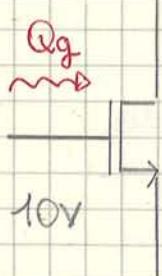A normal MOS transistor needs 10 V for being in full conduction (ohmic region); so we need to inject charge. It depends on the size of silicon




$Q_g$  is on the order ( $10 \text{ nC} \rightarrow 100 \text{ nC}$ )

I want to inject (for example)  $1 \text{ nC}$  in  $30 \text{ ms}$ :

$$\frac{1 \text{ nC}}{30 \text{ ms}} \rightarrow \text{CURRENT} = 30 \text{ mA}$$

Let's suppose:  $30 \text{ nC}$  in  $30 \text{ ns} \rightarrow 1 \text{ A}$  ! ouch!

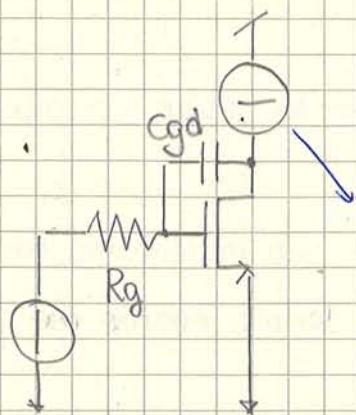NB: The DC current in the gate is zero! So we need a MOS DRIVER able to deliver more than  $1 \text{ A}$  very fast (For few ms it's ok otherwise it burns!). Since the charge comes from power supply we need to provide the storage of charge and send to the MOS transistor.  $\rightarrow$  CAPACITOR (ceramic capacitor). It is a fast capacitor (ceramic capacitor).




Looking for  $\frac{dV_o}{dt}$  ?

An inductance for short time looks like a current source.

Cgd give us a very strong Miller Effect.

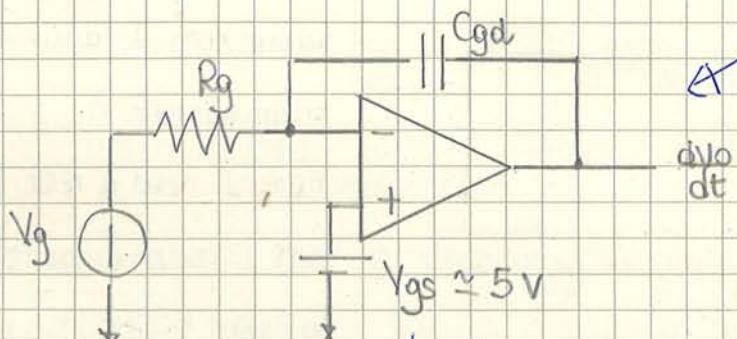But let's go to applied electronics. This is a common source; so we can model our circuit like :



THIS MODEL IS OK  
DURING THE  
SWITCHING TIME  
(because MOS is linear)

↳ (We need to apply a large Vgs in order to have the current that we want.)

Stay in time domain because it's easier.

$$I_g = \frac{V_g - V_{gs}}{R_g} \quad \text{this current goes through capacitor} \quad \frac{dV_c}{dt} = \frac{I_g}{C}$$

And so: 
$$\frac{dV_c}{dt} = \frac{V_g - V_{gs}}{R_g \cdot C_{gd}} \rightarrow I_g$$


The OP-AMP has a dc-gain  $10^4 \div 10^6$ ; but we have only a C.S.  
Can we use it? It's an approximation.

$$V_g \approx 10 \text{ V} \rightarrow 15 \text{ V} \quad V_{gs} = 5 \text{ V}$$

$$C_{gd} \approx 200 \text{ pF} \quad 2\Omega < R_g < 15\Omega$$

Let's see what happens:
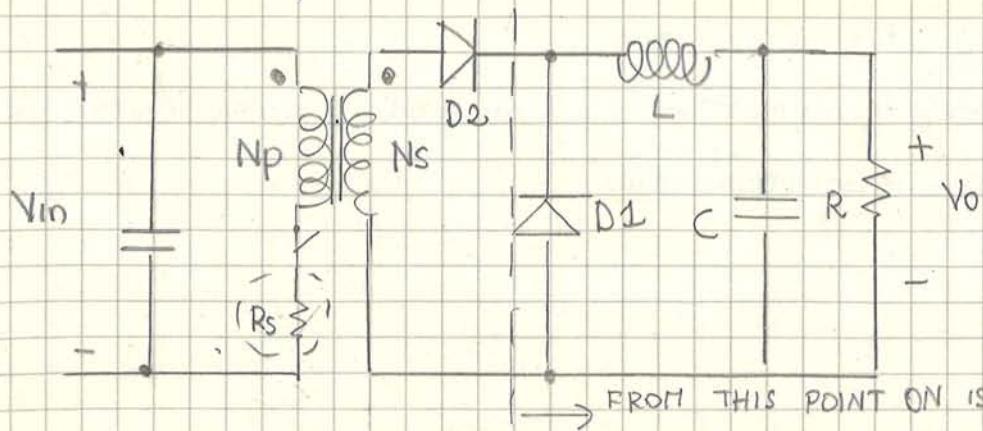
$$\frac{dV_c}{dt} = \frac{0.5 \text{ V}}{10\Omega \cdot 200 \text{ pF}} = \frac{0.5 \text{ A}}{200 \text{ pF}} = 2,5 \frac{\text{GV}}{\text{s}} = 2,5 \frac{\text{V}}{\text{ms}}$$



## FORWARD CONVERTER


We put D2 because we need that during  $T_{off}$  the voltage is reversed and there is no connection.

$$V_o = (V_{in} - V_{sw} - V_{Rs}) \cdot \frac{N_s}{N_p} \cdot D - V_D \quad \text{"V}_{D2} \text{ OR } V_{D1}$$

→ GAIN OF FORWARD CONVERTER

INPUT VOLTAGE OF NEW BUCK CONV.

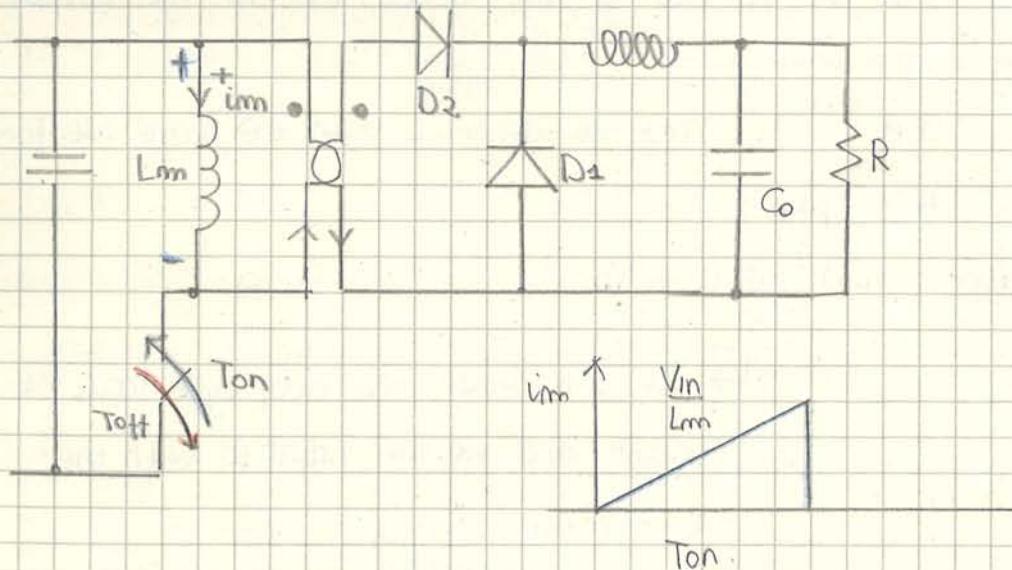The switch generates a lot of electromagnetic noise. We have a transformer (in this case) and  $L_m \rightarrow \infty$ . If we consider it we get :



When the switch is closed ( $T_{on}$ ) we have a current  $i_m$  (not so large) because  $L_m$  is large. During  $T_{off}$  we have a current going down through  $L_m$ ; it can't go on switch and it enters in a "no dot". And it means that in the secondary it wants to enter in a "dot"; and so it wants to go like this (look at schem). Is it possible?

No! There is the diode  $D_2$ ! And we can't remove it.

Looking for a way to discharge it.

Can I put  $V_{in\max}$  and  $D_{min}$ ? Yes. But it's better on the contrary; because  $V_{sw}$  and  $V_{es}$  becomes important when  $V_{in}$  is minimum.

We have to increase  $\frac{N_s}{N_p}$  by 5% (because the transformer is real)

We also need  $\frac{N_t}{N_p}$ . For finding it we must guarantee that the average voltage across  $N_p$  must be zero:

$$\overline{V_p} = V_{in} \cdot D - V_{in} \frac{N_p}{N_t} (1-D) = 0 \Rightarrow \frac{N_p}{N_t} (1-D) = D$$


SWITCH CLOSE      SWITH OPEN      FOR DOT CONVENTION

$$\boxed{\frac{N_p}{N_t} = \frac{D}{1-D}}$$

If  $D_{max} = 0.5$

$$\boxed{\frac{N_p}{N_t}} = \pm 1$$

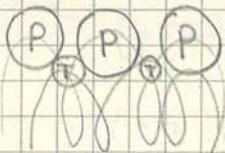The primary winding has a large current; in the  $N_t$  sum the magnetizing current so, the tertiary is very small:



→ we can do these windings together: the par. inductances are very small  $\Delta$

The adv. are isolation,  $V_o$  not related to  $V_{in}$ . But it's expensive! (Respect to flyback; now we have 3 windings). But we can go up in power.

### VOLTAGE STRESSES

•  $D_1$

$$V_{D1} = \frac{V_{in}}{\frac{N_s}{N_p}} \quad (\text{DURING } T_{on})$$

•  $D_2$

$$V_{D2} = \frac{V_{in}}{\frac{N_s}{N_t}} = \frac{V_{in}}{\frac{N_s}{N_p} \cdot \frac{N_p}{N_t}} \quad (\text{DURING } T_{off})$$

During  $T_{off}$   $D_3$  is ON, on the tertiary winding is  $V_{in}$  and so we determine the voltage across  $D_2$ .

•  $D_3$


$$V_{D3} = \frac{V_{in}}{\frac{N_s}{N_p}} - (-V_{in}) \frac{N_t}{N_p} \quad (\text{DURING } T_{on})$$

$V_{in}$  is also applied to the tertiary winding (also on the secondary one) but in opposite way.

Let's set  $D_{MAX} = 0.7$  for our forward converter. What happens?

$$\frac{N_p}{N_t} = \frac{0.7}{0.3} = 2.3 \quad \text{and so the } V_{SW} \text{ becomes larger (3V}_in\text{!!!)}$$

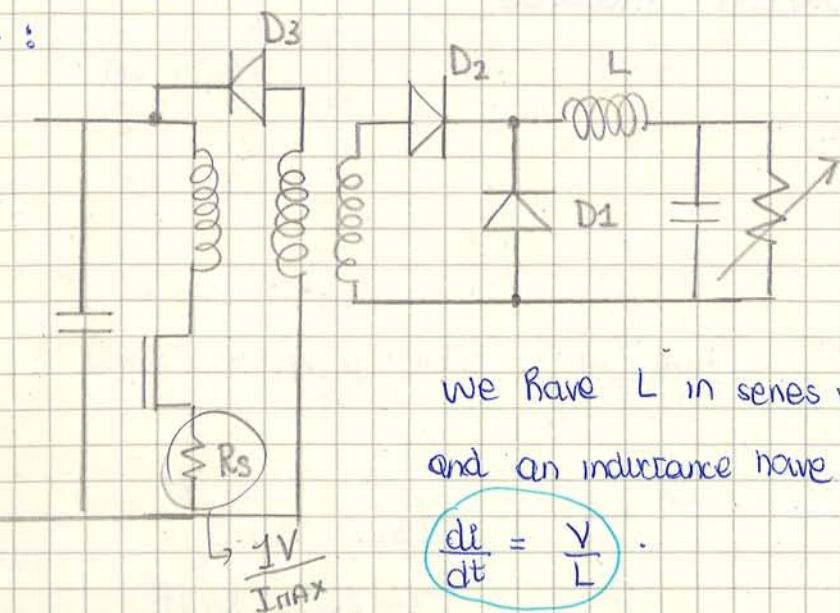
We have to stay quite low than 0.5 because this is a buck derived converter:



We have  $L$  in series with the output; and an inductance now:


$$\frac{di}{dt} = \frac{V}{L}$$

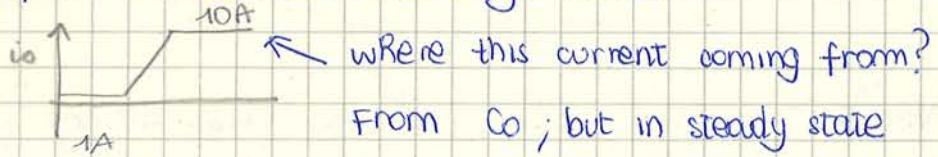Now let's suppose that our load changes from minimum to maximum, the output current goes from a low value to a large value.



From  $C_0$ ; but in steady state this current should come from the inductance.

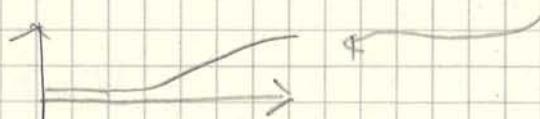Can an inductance change its current suddenly? No way. For doing this we need high voltage and time. If the voltage across  $L$  is not too much high, the current starts to increase in a very very long time.



So where does 10A come from? From capacitor. What does capacitor delivering in current? CHARGES! And the output voltage goes down.

But we have a controller that increases duty cycle in order to keep output voltage constant. So, for this reason we have to stay quite low than the maximum duty cycle. (Because of transient).

comes from the input.

$V_{in} \cdot I_{in}$  is the input power. Since we have to deliver a tot power and the current doesn't change! (MUSTN'T CHANGE).



## CAPACITORS

$C_0$	NO STRESSED	}
$C_{im}$	HEAVY STRESSED	

like a buck converter

$$I_{C_{0,RMS}} = \frac{\Delta I_{LPP}}{\sqrt{12}}$$
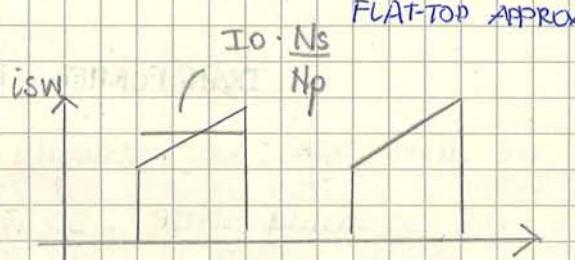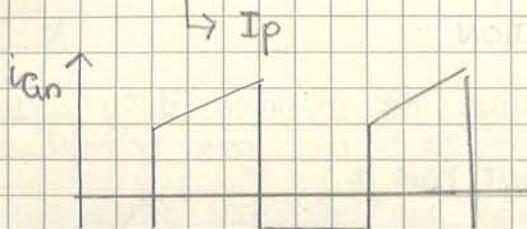
$$I_{C_{im,RMS}} = I_o \cdot \frac{N_s}{N_p} \sqrt{D(1-D)}$$



How much is the stress?

$$\left( \text{If } D \text{ is close to 0.5} = \frac{I_o}{2} \frac{N_s}{N_p} \right)$$

In CM control, with  $R_s$  we have advantages. We protect the switch and, if the transformer for any reason saturates, it opens the switch even if we have done an error in our design.

We have done with stresses, but not with losses.

## LOSSES


$$\begin{aligned} \bullet P_{D1} &= V_{D1} \cdot I_o (1 - D_{min}) \\ &\quad \underbrace{\text{AV. CURRENT}}_{\text{AV. CURRENT}} \end{aligned} \quad \left. \begin{array}{l} \text{of the two diode} \\ \text{TOTAL POWER} \end{array} \right\} \text{is } V_D \cdot I_o$$

$$\bullet P_{D2} = V_{D2} \cdot I_o \cdot D_{MAX}$$

$$\bullet P_{MOS} = P_{\text{conduction}} + P_{\text{switch}} = r_{\text{on,ON}} \cdot I_{SW}^2 \text{ RMS} + f_{SW} \left( V_1 \cdot I_1 t_{on} + V_2 \cdot I_2 t_{off} \right)$$

$\underbrace{\qquad\qquad\qquad}_{P_{\text{COND}}} \quad \underbrace{\qquad\qquad\qquad}_{P_{\text{SWITCH}}}$

We saw that in a forward converter ; a buck converter can handle a power up to 200 W. (especially offline) ; the transformer is not used very well , but only during 40 % of the time ( $T_{on}$ ) because voltage stresses are too high. We need the resonant time in order to reset the magnetization. But there is another way to reset the magnetization inside the core. (without no-wasted time of transformer) ; let's consider this :

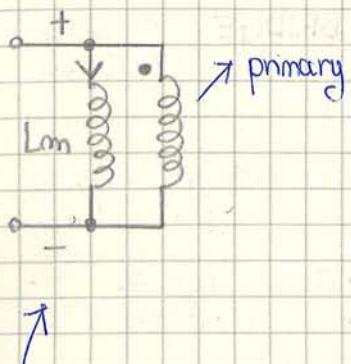

During  $T_{on}$  we apply positive on the dot and then we need a long  $T_{off}$  to reset the magnetize current by the tertiary winding. (old way).

Let's see another way. In order to reset the magn. current (otherwise the transformer saturates) we have to apply a reverse voltage (with opposite polarity). So instead of using a tertiary winding let's suppose to be able to apply to the same winding a polarity that is reverted. (for the same time, for example for 40% of the time).


This reset the core. For example we apply positive voltage for a 40% of the time and then on the secondary we rectify it and then we apply a reverse voltage for 40% of the time and rectify it. In this way we can work with duty cycle that is 80%.

What we need on secondary is a FULL WAVE RECTIFIER.


( In this way we can have an output that is twice the old frequency.)

How can we swap + and - ?

4 switches

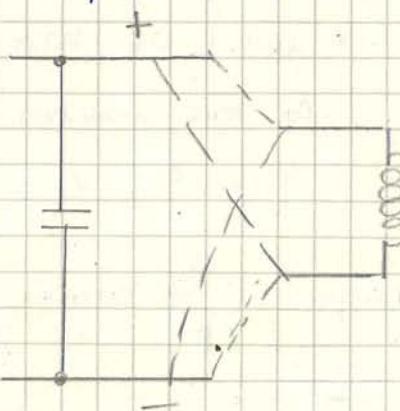

(1)

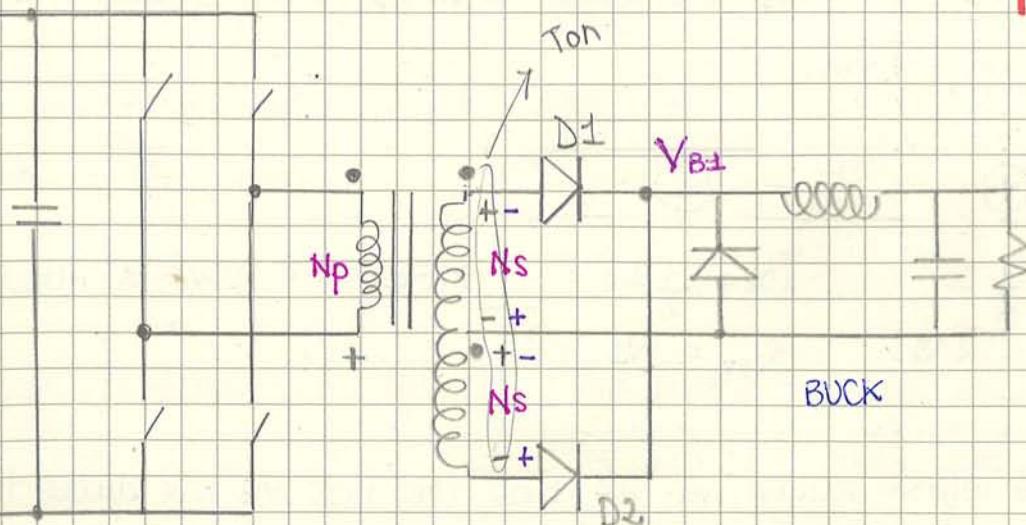

## FULL BRIDGE


On the secondary side, current flowing (comes out from the dot) and D2 is OFF because we have negative polarity of the anode. This happens during the first half wave. During the other half wave we have on the secondary the positive on not-dot and D2 conducts, and the current flows in the opposite way. So, we have a full wave rectification.

NB : the free-wheel diode is not really needed. We see better after.

Ouch ! We have two secondary winding but 2 diodes. If we want only one secondary winding :

(2)

GRÄTZ  
BRIDGE

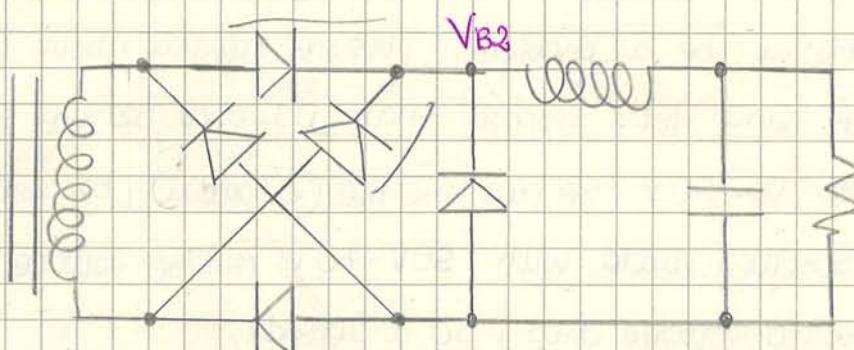

So we have 2 possibilities. Which one is more convenient? It depends on the output voltage. How much voltage do we lose with diodes?

$$V_{B1} = V_s - V_D$$

$$V_{B2} = V_s - 2V_D$$

For low output voltage (< 30V)

is better the first solution.

But it's not the only consideration. We have also to consider

- $D_{SW} = \frac{T_{on,SW}}{T_{SW}} < 0,5$  (otherwise **BOOM!**)

Let's see what happens at the port that is the original buck converter:

- $T_{BUCK} = \frac{T_{SW}}{2}$
- $f_{BUCK} = 2f_{SW}$
- $D_{BUCK} = 2D_{SW}$

Yeah!!! This means that I can obtain (for the buck!) a duty cycle close to 1! And my efficiency ↑.


If our load decreases suddenly we need to apply a large  $V_B$  in order to ramp up quickly the current to the inductor.

We design a buck in CCM. To stay in CCM:

$$L > \frac{R_{max}(1 - D_{min})}{2f_{SW}}$$


$\hookrightarrow$  the buck switching frequency

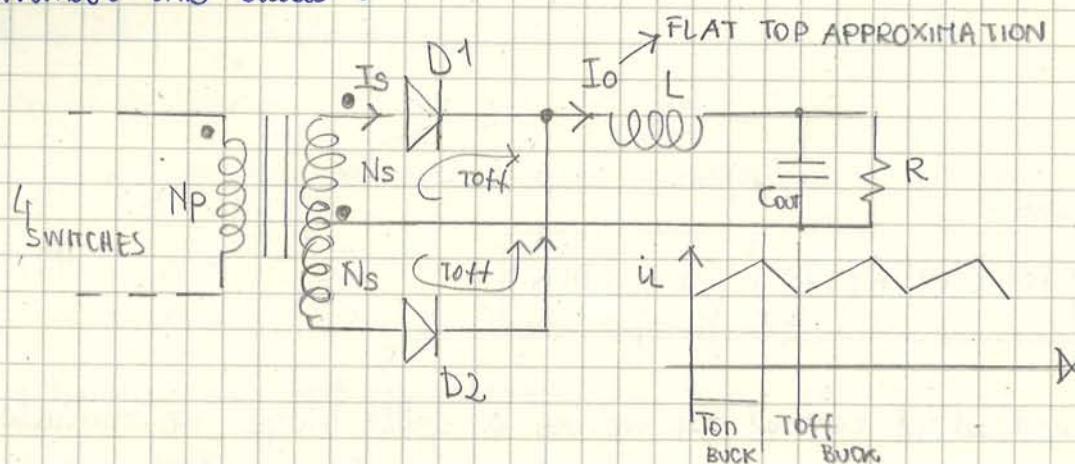Do we really need the freewheel diode? We discuss that our circuit works without this diode:



During  $T_{off}$ , all switches are open, and there is no current flowing in the primary and also there is no current flowing in the secondary winding. But there is a current flowing through  $L$ ; if I don't put the freewheel diode, where this current coming from? One part from  $D_1$  and one part from  $D_2$ . (This current is  $I_o$  basically).

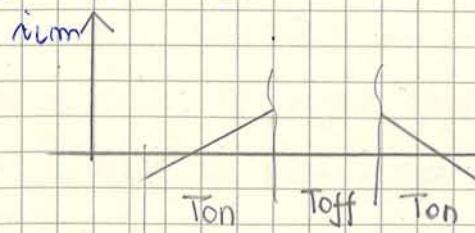$i_{lm}$  goes up during one Ton and goes down during the other Ton.




what happens during Toff?

The 4 switches are open.

Let's suppose that  $i_{lm}$  goes down.

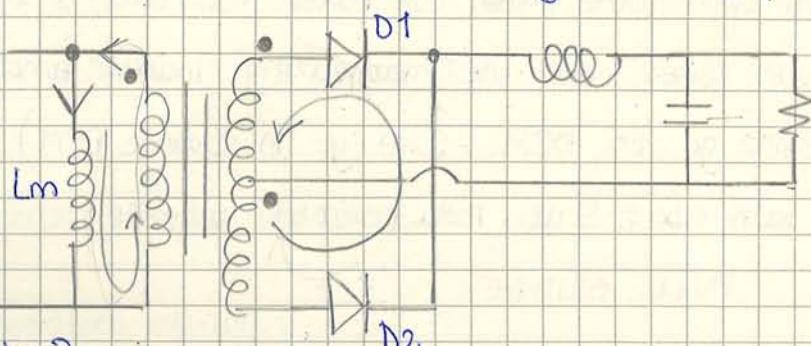During Toff  $i_{lm}$  can't go to the input (switches are open), the current enters in a "no-dot" and on the secondary comes out from the dot:



Is it possible?

No, there is  $D_2$ . This means that  $i_{lm}$  must go up and on the secondary the current goes on the contrary.

Is it possible?

No, there is  $D_1$ .

There is something wrong.

If I can't give a path to the magn. current,  $L_m$  has a very high strong voltage spike.

But! How is it possible? we can't use superposition! It's NONLINEAR  
We saw a moment ago the magn. current the output current that is divided between the two diodes.

So I have to consider the 2 currents together. During Toff:

I have  $I_o$  through  $L$ , and  $i_m$  in  $D_1$  and  $i_m$  in  $D_2$  I also have the  $\frac{I_o}{2}$  and the magn. current. In  $D_1$  :  $\frac{I_o + I_m}{2}$  and  $i_m$

$D_2$  :  $\frac{I_o - I_m}{2}$  and both diode are conducting (They are ON by the output current).

We can put  $R_s$  in ① and ②.

① It has some disadvantages. The common voltage goes from zero to  $V_{in}$ ; there is a lot of switch and it's difficult to measure a voltage that swings up and down. Another dis. is that the voltage across it is bipolar (because the current flows in one sense when 2 part of switches are closed and in the other sense when are closed the other pair).

② When  $s_1$  and  $s_4$  are closed (and  $s_3$  and  $s_2$  are closed) the current always flows to the left. So I put resistor  $R_s$  on ② point.

So if current mode we have to put  $R_s$ .

So the secondary voltage:

$$V_s = (V_{in} - 2V_{sw} - V_{RS}) \cdot \frac{N_s}{N_p}$$

And from this point on we have a buck converter and so for the output voltage:

$$V_o = V_s \cdot D_{BUCK} - \#V_D$$

↳ in C.T. is  $\pm$

So for the last equation we have to find the turn ratio  $\frac{N_s}{N_p}$  with:

- $V_{sw} = 1\%$  or  $2\%$  of  $V_{in}$
- $D_{BUCK}$ : we choose it.

$$\frac{N_s}{N_p} = \frac{V_o + \#V_D}{(V_{in} - \#V_{sw} - V_{RS}) \cdot D_{BUCK}} + 5\% \left( \text{of } \frac{N_s}{N_p} \right)$$

In this formula we put  $D_{BUCK}_{MAX}$  and  $V_{in}_{min}$ .

If  $\frac{N_s}{N_p} \uparrow$ ,  $D_{BUCK}$  must be a little bit smaller.


During Toff There is no driving voltage on the primary side and the current flows like  $\oplus$ . The current is divided between the 2 pairs of diode and this division is not guarantee to 50%.

There is also  $I_{m}$  that comes down. But remember!  $I_{m}$  can't go alone down (between the 2 pairs of diode); in fact we can't use superposition!


$$V_s = V_{in_{MAX}} \cdot \frac{N_s}{N_p}$$

- CT  $V_{D_{MAX}} = 2 \cdot V_{in_{MAX}} \cdot \frac{N_s}{N_p} + V_{SPKES \text{ RINGING}}$  who cares about  $R_s$  and  $V_{SWITCH}$ !
- GB.  $V_{D_{MAX}} = V_{in_{MAX}} \cdot \frac{N_s}{N_p}$

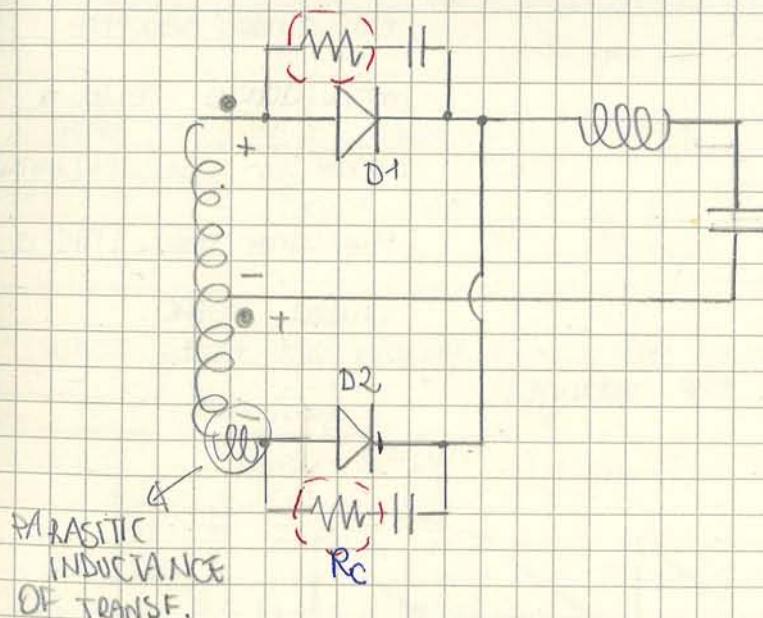We have to add  $V_{RINGING}$  on the central tap because:



If  $V_s$  is:

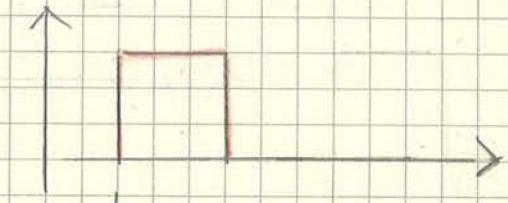

we have a big voltage on the secondary, and  $D_2$  is not conducting and it sees  $V_{sec} + V_{sec}$ . So we have

the parasitic inductance of the secondary; an open diode (that has a capacitor) and so they starts to resonate, ringing. In many cases, to avoid this problem put a resistance  $R_c$  across each diode (snubber). And sometimes it can be put across the secondary winding. It's not very easy to design because we have to estimate the parasitic inductance.

if we close the first pair of switches, suppose that the voltage on the primary winding is positive (  $I_m$  ramps up, because we have positive voltage across the inductance). Then ( during  $T_{off}$  ) the 4 switches are open, and the current stays constant. Then applying a negative voltage on the primary side,  $I_m$  ramps down.

So :

$$I_{sw} = I_o \cdot \frac{N_s}{N_p} \cdot \sqrt{D_{sw}}$$

$$I_{sw \text{ AVE}} = I_o \cdot \frac{N_s}{N_p} \cdot D_{sw}$$

Not important for the MOS, but I find it for checking the input power.

$$\underline{I_{sw \text{ AVE}} = I_{in}}$$


So :

$$I_{in} = I_o \cdot \frac{N_s}{N_p} \cdot 2 D_{sw} \underbrace{\max}_{D_{BUCK \text{ MAX}}}$$

And the input power :

$$\boxed{P_{in} = V_{in \text{ min}} \cdot I_o \cdot \frac{N_s}{N_p} \cdot D_{BUCK \text{ MAX}}} \rightarrow \text{ONLY FOR CHECKING!}$$

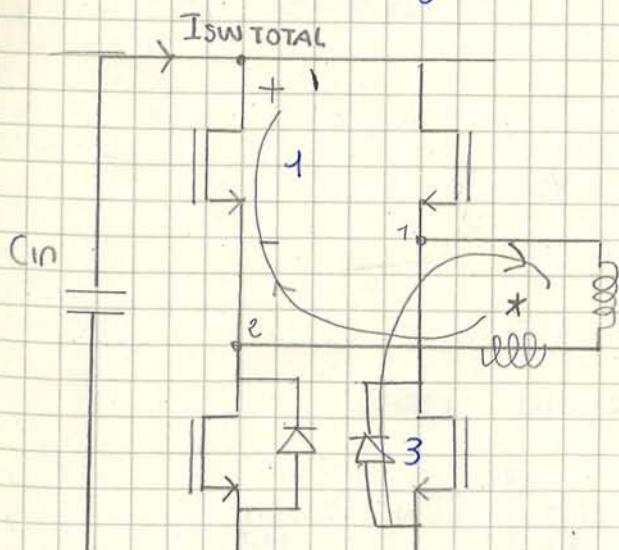what about the voltage across the switches?



$$V_{DS \text{ MAX}} = V_{in} \text{ why?}$$

The node ② can reach maximum (when goes down) is almost  $\emptyset$  (because of body diode).


The spikes that we can have are clamped because we have a leakage inductance.

When we open the switches,

it has some energy and it want to go somewhere. It can't go to the secondary side (because it is no connected) and so

And we have a problem. Why?

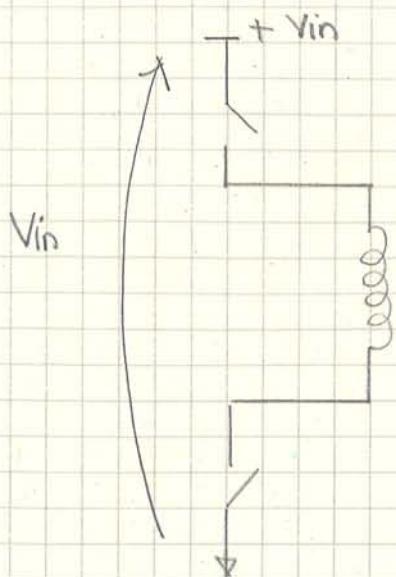Current it's easy to find. The problem is that we have 2 switches in series:



the total voltage Vin is shared between this 2 switches. We can't find it! It depends on the parametric element, symmetry...

BUT we can say that we know the voltage (TOTAL) across the 2 switches is Vin.


What we can say is that the power that we estimate is for one pair:

$$P_{SW} = f_{sw} \cdot \frac{1}{2} (I_1 V_{in\ ton} + I_2 V_{in\ toff})$$

power dissipated by one pair of transistors

## CONTROL (VM OR CM)

### • VM

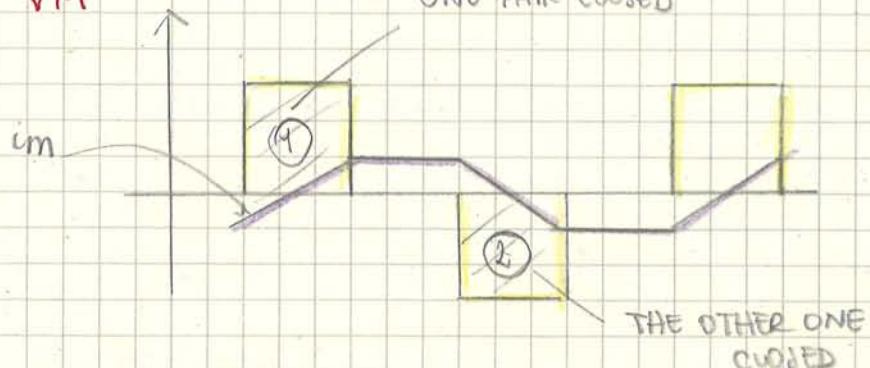


Let's suppose that some accident happens. For example the first pulse is higher than the other one (because for example the 2 switches have a lower a  $r_{DS(on)}$  than the other pair).

Or we can have that the transistors are not symmetrical and the pulse is a little bit longer.

We have many many pulses. It means that the area of pulse

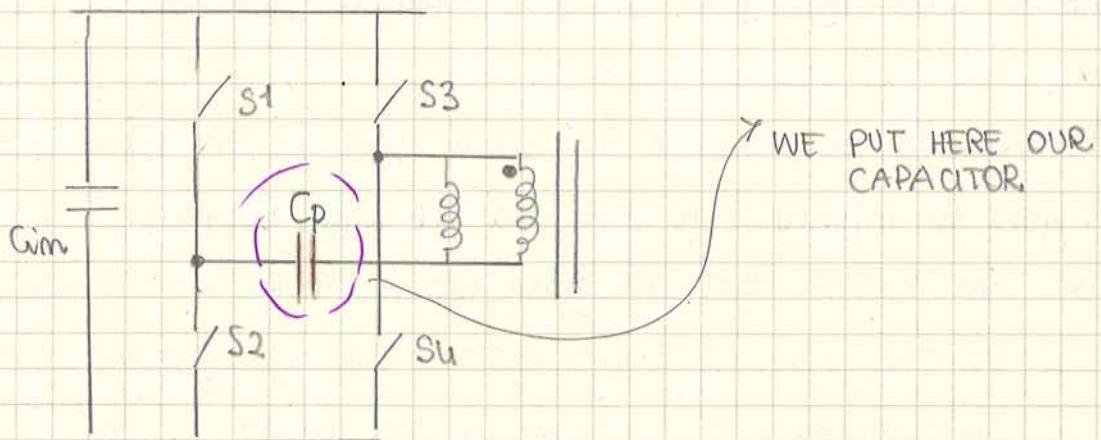(1) is not exactly equal to the area (2) and  $I_{m\ namps}$  up.






- what about  $V_{VY}$ ? The voltage across  $C_p$  (the average) is a few volts; but when we switch on, at beginning of the cycle we can have here a large voltage, and for taking a safe decision let's take  $V_{in}$ .

$$V_{VY} = V_{in}$$

(Because we don't know what happens at start-up)

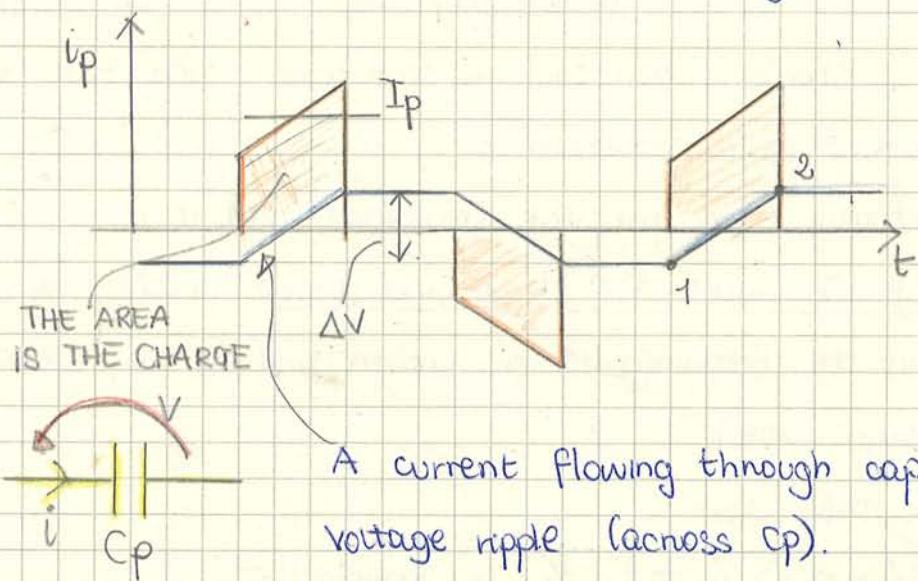$C_p$  is not an elect. capacitor, it is a film capacitor and so we have to evaluate its value. It is evaluated in this way:



A current flowing through capacitor generates voltage ripple (across  $C_p$ ).

$$\Delta Q = C_p \cdot \Delta V$$

$$\Delta V = \frac{\Delta Q}{C_p}$$

$\Delta Q$  is the area:  $\Delta Q = I_p \cdot T_{on}$  (we know everything)

How much is a suitable  $\Delta V$  value over there?

A first idea is to say "I want a very small ripple voltage, so just getting  $C_p$  as larger as possible".


Deriving a practical equation (even if is unuseful):

$$\frac{\Delta Q}{\Delta V} = \frac{I_p \cdot T_{on}}{V_{in} K} = \frac{I_o \cdot \frac{N_s}{N_p} \cdot \frac{D_{MAX}}{f_{SW}}}{V_{in} K} = \frac{I_o \cdot \frac{N_s}{N_p} \frac{D_{BUCK}}{2f_{SW}} \cdot V_{in}}{V_{in} K \cdot V_{in}}$$

$$C_p = \frac{\Delta Q}{\Delta V} = \frac{P_{in}}{2f_{SW} \frac{V_{in}^2}{K}}$$


The order of magnitude of  $C_p$  is  $\mu F$ .

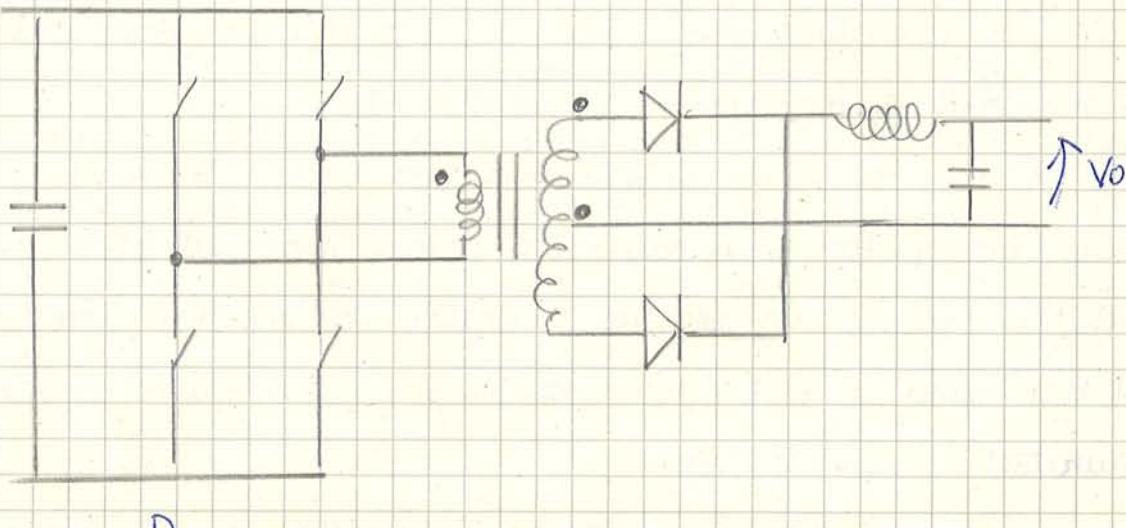What about the transfer function between  $V_o$  and  $D$ ?



$D$

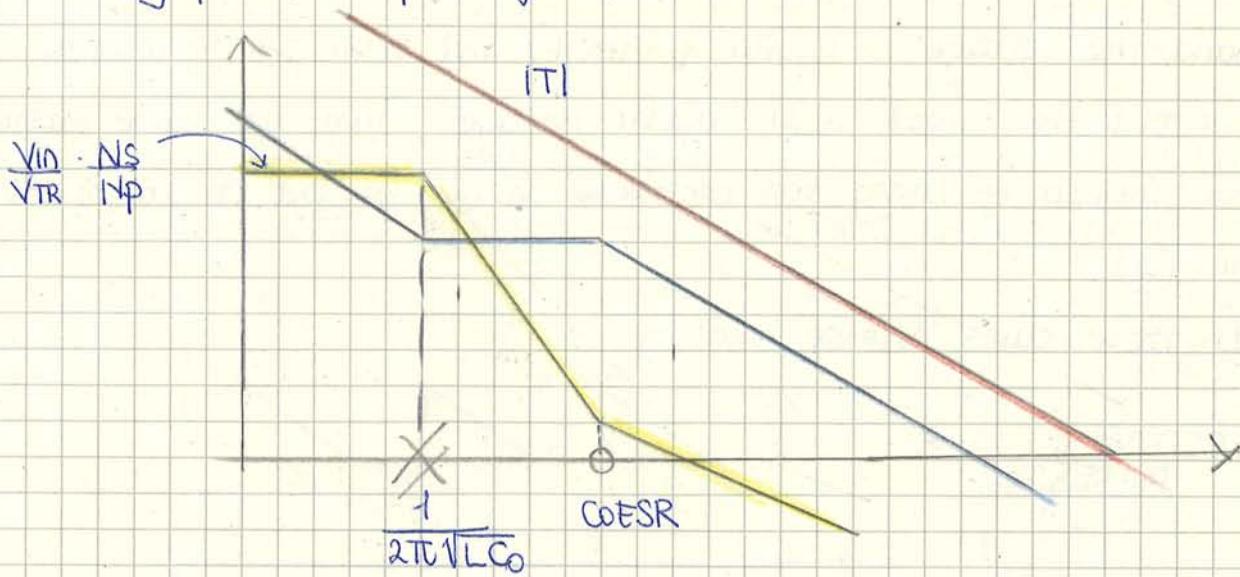
How many poles? 2 pole (fixed) and one zero



And we know how to compensate it.

Let's go in current mode.

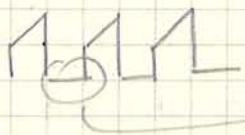Can we use a transformer over here? No, there is a DC! No! Yes we can because :



we have this period of time when we discharge a transformer, and so it is OK.


What is our goal? It's to measure over  $R_s \pm V$ .

How much is the  $R_s$  value?

$$V_{RS} = \pm V \cdot I_{P_{MAX}} = R_s \cdot I_o \cdot \frac{N_s}{N_p}$$

+ RIPPLE (because we want consider very max value)

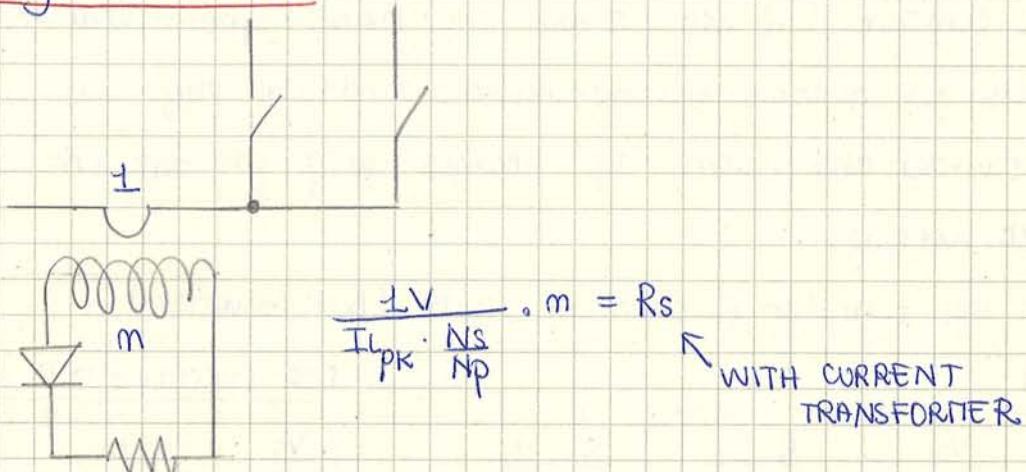
And what if we put a current transformer? It could happen! when we have a large current value.



So, it is a good idea to use full bridge in current mode? Yes! Because

with  $R_s$  we protect the circuit from saturation, and we save  $\Phi$ .

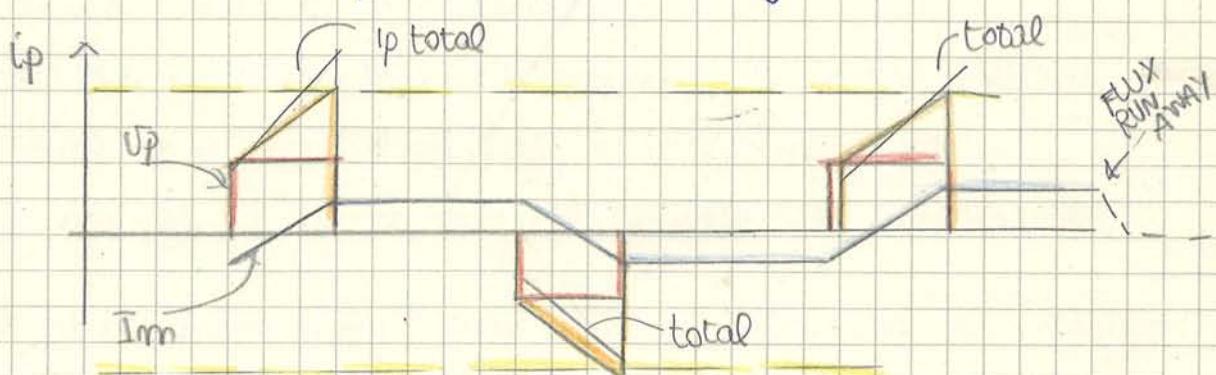WHY DON'T WE NEED  $C_p$  IN CM? It's easy.




If  $V_p$  is not regular we can have flux runaway. For example if  $V_p$  is larger, smaller, higher.

Some remarks: this is a high voltage configuration. In addition, the switches "share" the stresses because the input current divides into the 2 branches. → Typical configuration for high power configuration.

## HOUSE KEEPING (OF POWER SUPPLY)

It's valid for any topology. (isolated).

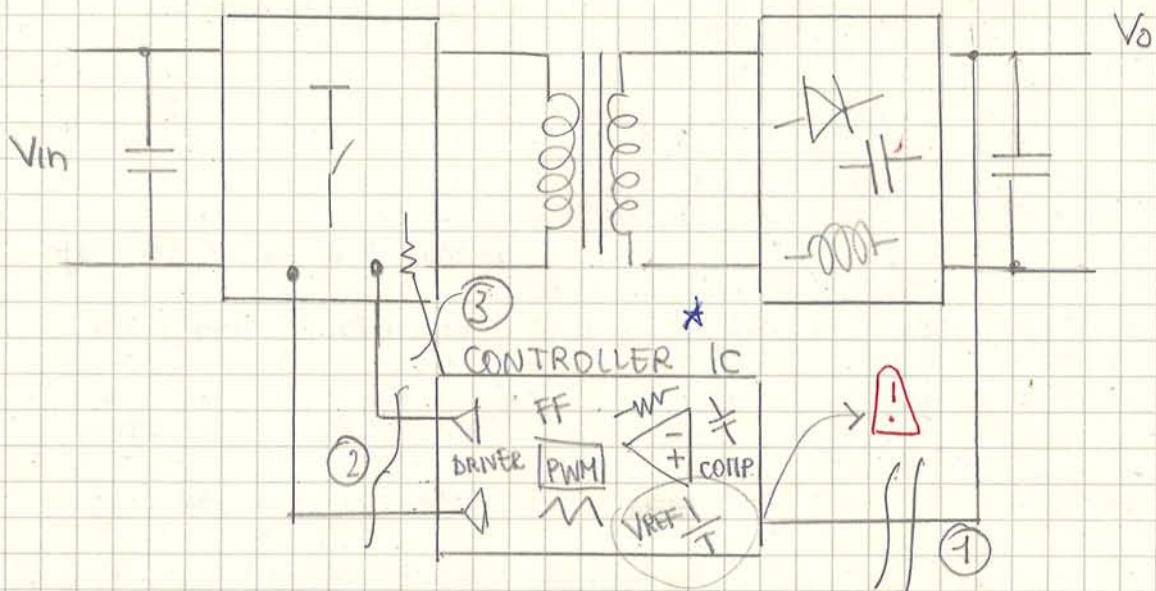

What about isolation? If we put  $V_{REF}$  linked to the output the system is no longer isolated, so we need to place an isolation somewhere.

→ point where we can put isolation.


We can put isolation in ②; we can use driver transformer and in ③ we can have current transformer that give us isolation. These two solutions changes the name of controller.

If we use ① we say that the controller is on the **PRIMARY SIDE**. Because it is connected directly to the primary side.

If in ② and ③ it is on the **SECONDARY SIDE CONTROLLER**.

And what about power supply? How can we supply the IC controller?

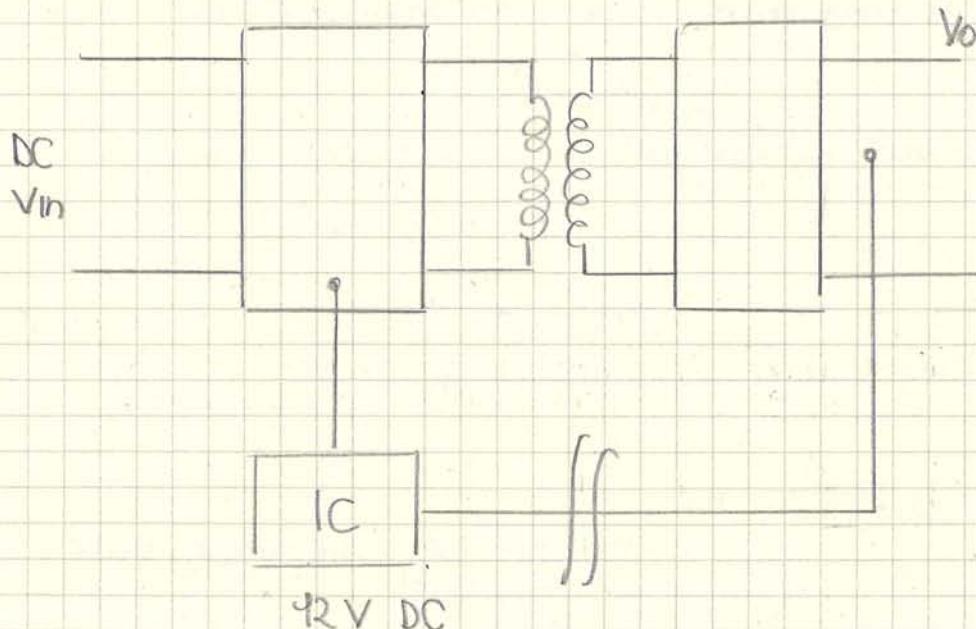
We put another power supply with another controller that needs power supply ☺. We can put another transformer here ✎, but




If we have  $V_{in} = 15 \text{ V DC}$  we connect directly  $V_{in}$  to our IC and it's ok.

If  $V_{in} = 24 \text{ V}, 48 \text{ V}$  we can still use a linear regulator because IC doesn't take too much power. ( $\sim 100 \text{ mW}$ ). And if  $V_{in} = 300 \text{ V}?$  we can't use a resistor to going down in voltage because, for example if  $I = 50 \text{ mA}$ ,  $P = 300 \text{ V} \cdot 50 \text{ mA} = 15 \text{ W}$ ! No, we don't want to waste this power just to supply the IC!

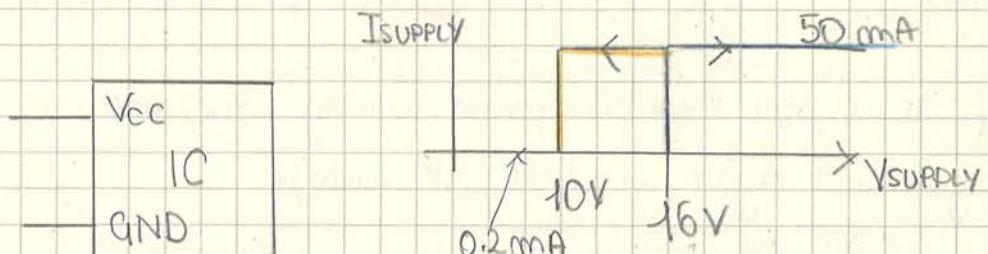ICs have a specific feature that is called **LOW START UP CURRENT**.



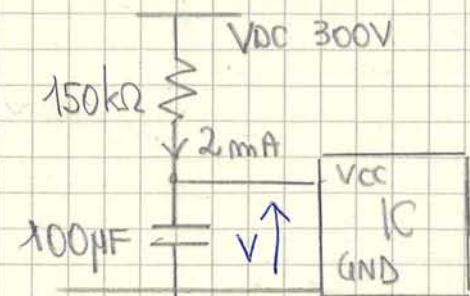When the input voltage reaches a given threshold (for example 16V), OK, it's time to work. If the voltage comes back it maya up to another threshold (10V) and then it drops. With these ICs we can do:



$$2 \text{ mA} \cdot 300 \text{ V} = 0.6 \text{ W} \text{ (Better!)}$$


C starts to charge slowly and it would charge to 300V; but when  $V = 16 \text{ V}$ , IC wakes up and it

Do we need a compensation ramp? We need it if  $D > 50\%$ . Yes! Because we have D<sub>BUCK</sub>.

So we have to move the compensation ramp (that is in L) on the primary side.  $\frac{V_0}{2L} \left( \frac{A}{\mu s} \right)$

Let's see the adv. and disadv. of using current transformer or only  $R_s$ .

The current through  $R_s$  is:

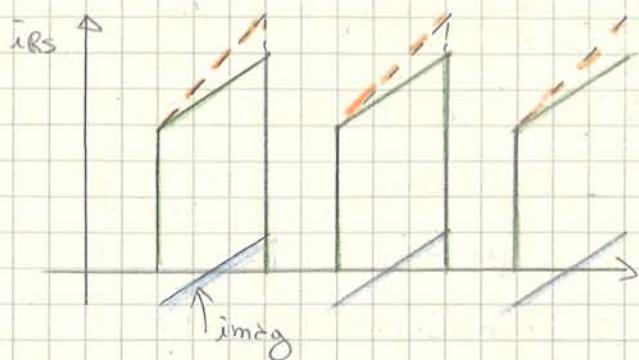


i<sub>Rs</sub> is the standard input waveform for a Buck converter. We have a very high D because we are measuring the current over there.

We have to remember that what we have on the primary side is not only the secondary current moved on the primary side, but there is also the magnetizing current in top of it. This current has the effect of having a steeper i<sub>Rs</sub>.

We have to put a compensation ramp, but the magnetizing current is already helpful!

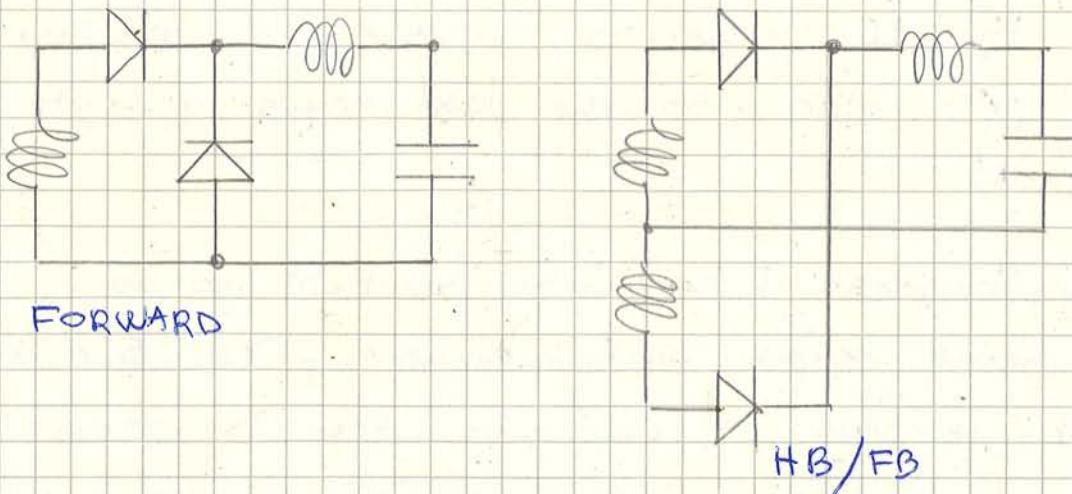Let's consider the multiple outputs solution for Buck derived converters.




What if the first output passes from CCM to DCM?

The controller keep the output voltage constant reducing the

▷ so the voltage in the second output goes down!

So the solution is this one:

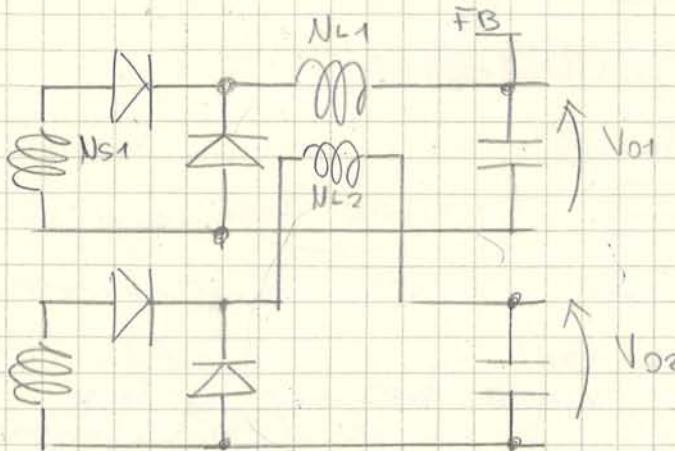

$$\frac{N_{L1}}{N_{L2}} = \frac{V_{01}}{V_{02}} = \frac{N_{S1}}{N_{S2}}$$


A very huge advantage of this solution is that we have only one magnetic core

We still take the feedback from the first output but this time if the load in ② changes the change goes immediately in ① and so the controller can do something! So the dynamic behaviour is better.

We still have the problem CCM → DCM because

For example if ② goes in DCM current tries to go backward, but there are the two diodes.

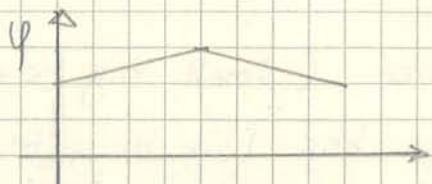In this case is not so bad as before because the flux in the coupled inductors is unique and this flux  $\Phi = L \cdot I$  is translated into a current ripple.



It is therefore called Ripple-steering

Flux goes up and down → current ripple

but we can steer the ripple on the output we want so ① never goes to DCM. ② has problem to

go in DCM because the ripple is small (unless the current is very small).  $\Phi = 0 \rightarrow$  System DCM

In many cases in multiple outputs Buck-derived converters, we can find one big transformer with all the outputs windings and small ring cores in series with the secondaries in order to make the ripple steering.

## HALF BRIDGE

Why we moved from forward converter to full bridge?

We want to reset the magnetic core without wasting time. We can force the input voltage to be reversed so at the same time we reset the magnetic core and we use the transformer to transfer power! We have to remember that if the reset isn't very precise we have the flux runaway.


(So we have to put a capacitor in series).

The full bridge has a very big disadvantage:

We have 4 switches. This is the reason why for low power the full-bridge is a waste of money (we have 2 switches in series with  $V_{IN}$ ).

There are other ideas to solve this...

For example:

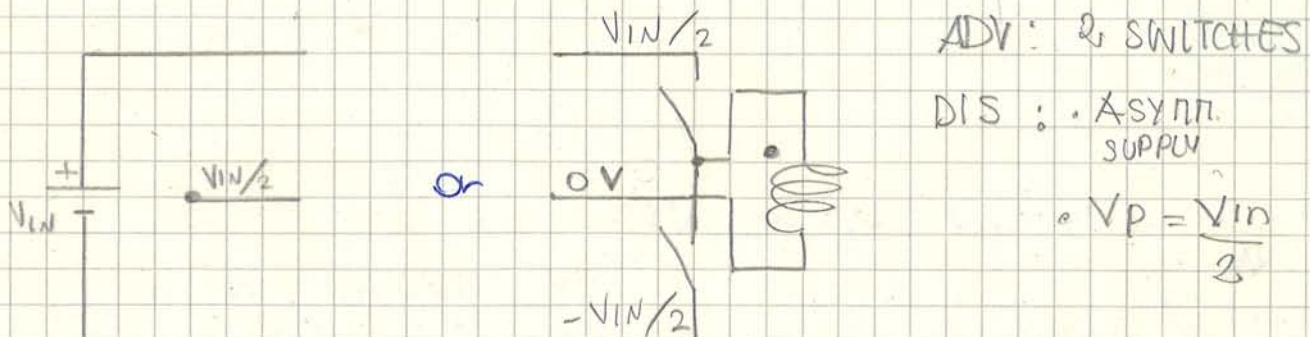

If we have  $V_{IN}/2$ , 0 and  $-V_{IN}/2$  and we want to supply the primary with an AC we can use two switches!

\* If  $V_p$  it's a little bit longer we have an extra current so the voltage increases. (ACROSS C)


So  $D_{S1} > D_{S2}$   $V_C$  won't be at  $V_{IN}/2$  but  
little bit

a little bit higher because the two capacitors absorb the unbalance

Half bridge has the advantage of having only two switches but the primary voltage is only  $V_{IN}/2$  and we need the two capacitors.

long time ago maybe two caps costed less than two switches

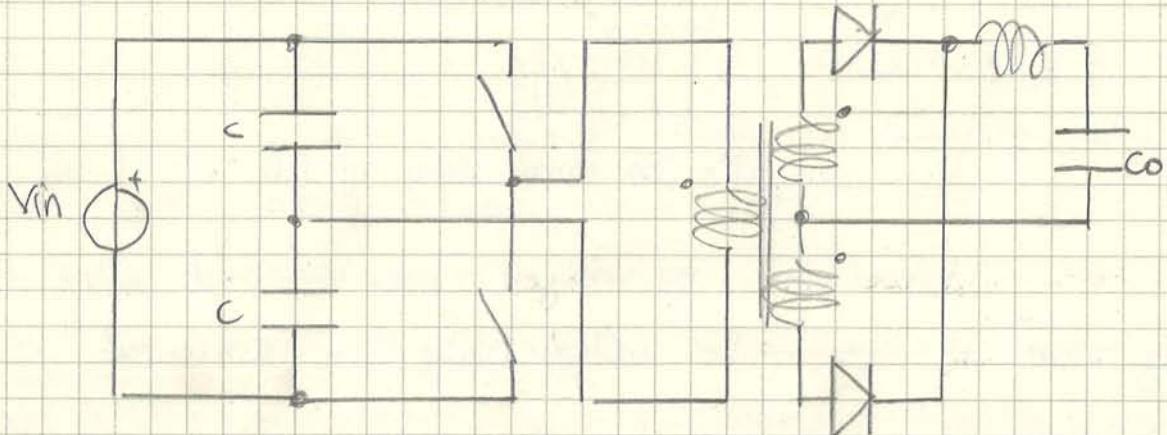Obviously having  $\Delta V_p = V_{IN}/2$  requires a change in the turn ratio to get the same output voltage.  
It will also modify the current ratio.



I'm looking for  $\frac{V_D}{V_{IN}}$  to design the transformer.  
We have a Buck so:

$$\frac{V_D}{V_{IN}} = D \cdot V_{sec} - V_D = D \cdot V_p \cdot \frac{N_S}{N_P} - V_D = D \cdot \left( \frac{V_{IN}}{2} - V_{sw} \right) \frac{N_S}{N_P} - V_D$$

always a drop on a switch

$$\text{So the } \left| I_{IN} \right|_{HB} = 2 \left| I_{IN} \right|_{FB}$$


because we have to deliver the same power with  $V_{IN}/2$   
so less voltage  $\rightarrow$  double current.

Let's remove one possible error from this design:

Do we control it voltage mode or current mode?

Current mode is absolutely forbidden because we have a capacitor in series with  $V_{IN}$  so we can't put  $R_s$ .  
It is voltage mode only.

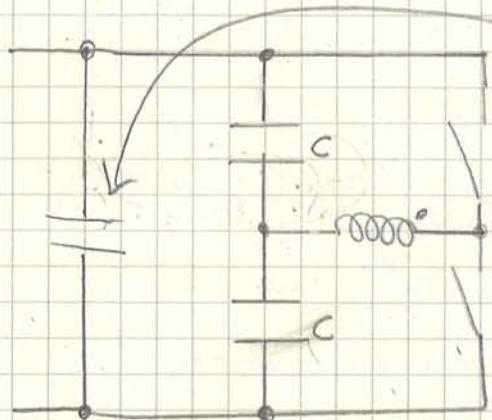Actually it can be done but it's very complicated since requires an extra winding. Let's see now input capacitor:



Have we to put it?

The capacitance seen by

the input winding is  $C_p = 2C$   
because  $C$  &  $C$  are in parallel for the high frequency coming out from the winding

How we design these two caps?

Exactly as we did it for the full bridge.

The two caps make  $V_{IN}/2$  but are also used to absorb the unbalances without saturates the primary winding.

$$C_p = \frac{\Delta \varphi}{\Delta V} = \frac{\tan \varphi}{10\% V_{IN}/2} \quad \left( V_p = \frac{V_{IN}}{2} \right)$$

$$\left( \Delta V_{IN} \approx 5\% \div 15\% \right) \text{ (primary)}$$

Comparing:

$$\left| C_p \right|_{HB} = 4 \left| C_p \right|_{FB}$$


because

$$\begin{cases} \left| I_p \right|_{HB} = 2 \left| I_p \right|_{FB} \\ \Delta V \mid_{HB} = \frac{1}{2} \Delta V \mid_{FB} \end{cases}$$

We have a DC in series with a cap

What's the effect?

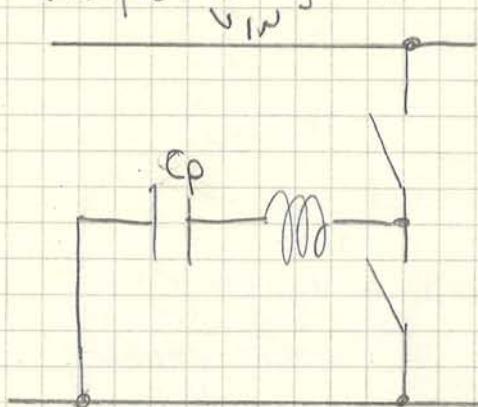When we have a cap connected to a fixed voltage point, we can move that point to any other fixed point in the circuit without changing nothing, for example to ground:





It seems that I can make this circuit and save one cap, but if I make it and I start the circuit... KA BOOM!

Wait a moment. I derived this circuit using two exact rules. Why it doesn't work?

There is something that seems to be right! But it isn't! →  $E_Q$

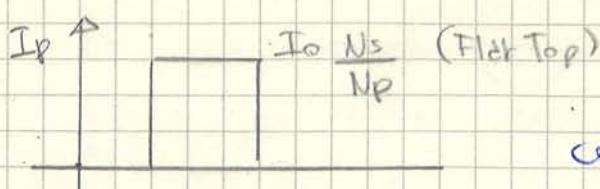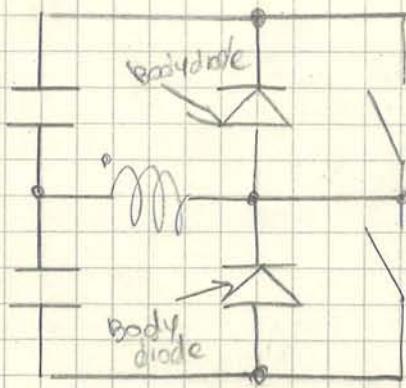Let's go back to our circuit and in particular on the switches shesses



$$V_{DS\text{ MAX}} = V_{IN}$$

line in a full bridge

It tells me that this topology is for high voltage!

But for not so high current because of the current shesses.

(ALL CURRENT GOES ALL IN ONE BRANCH)

In a full bridge the DC current is shared between the two legs. In an HB we have only one leg! And all DC current comes over here.

## Push - PULL topology

Before looking to the last topology let's make a comparison

MAXIMUM VOLTAGE STRESS

- Full Bridge

$SW : I \cdot V$

- Half Bridge


$SW : 2I \cdot V$

- Push Pull

$SW : I \cdot 2V$  ← medium power low  $V_{IN}$


- Forward

$SW : 2I \cdot 2V$

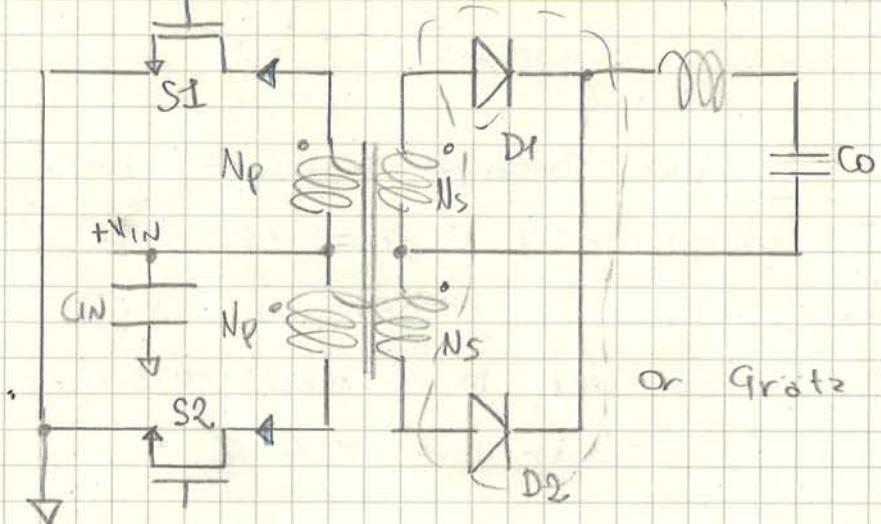

PUSH PULL

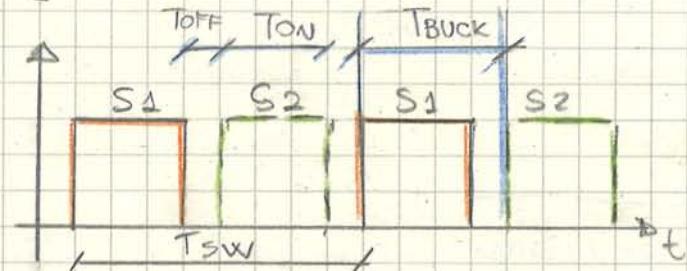As usual we drive the switches in a non overlapping way




When we close  $S_2$  we apply  $V_{IN}$  old non-dot.

So we have the positive on non-dot on the secondary and vice versa. (With  $S_2$  ON, magnetic flux starts to decrease because  $S_2$  ON,  $D_2$  OFF)

What about the input capacitor? What it seen as current?

It experiences both the current in  $S_1$  and  $S_2$ . It

works at the same frequency as Buck.

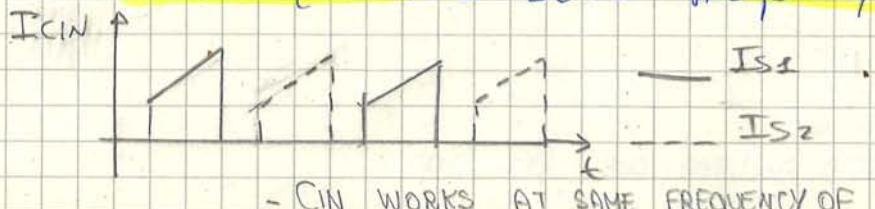

TWICE FREQUENCY OF  
 $S_1$  AND  $S_2$ .


As usual the magnetizing current increase the slope but this is useless for the stresses

$$I_{SW} = I_o \frac{N_S}{N_P} \rightarrow D_{SW} \approx \text{BJTs and estimate } P_{IN}$$

$$I_{SW_{RMS}} \approx I_o \frac{N_S}{N_P} \sqrt{D_{SW}} \leftarrow \text{we can choose the wire gauge of our transformer}$$

We can check our calculations:

$$P_{IN} = V_{IN} \cdot I_{SW}$$

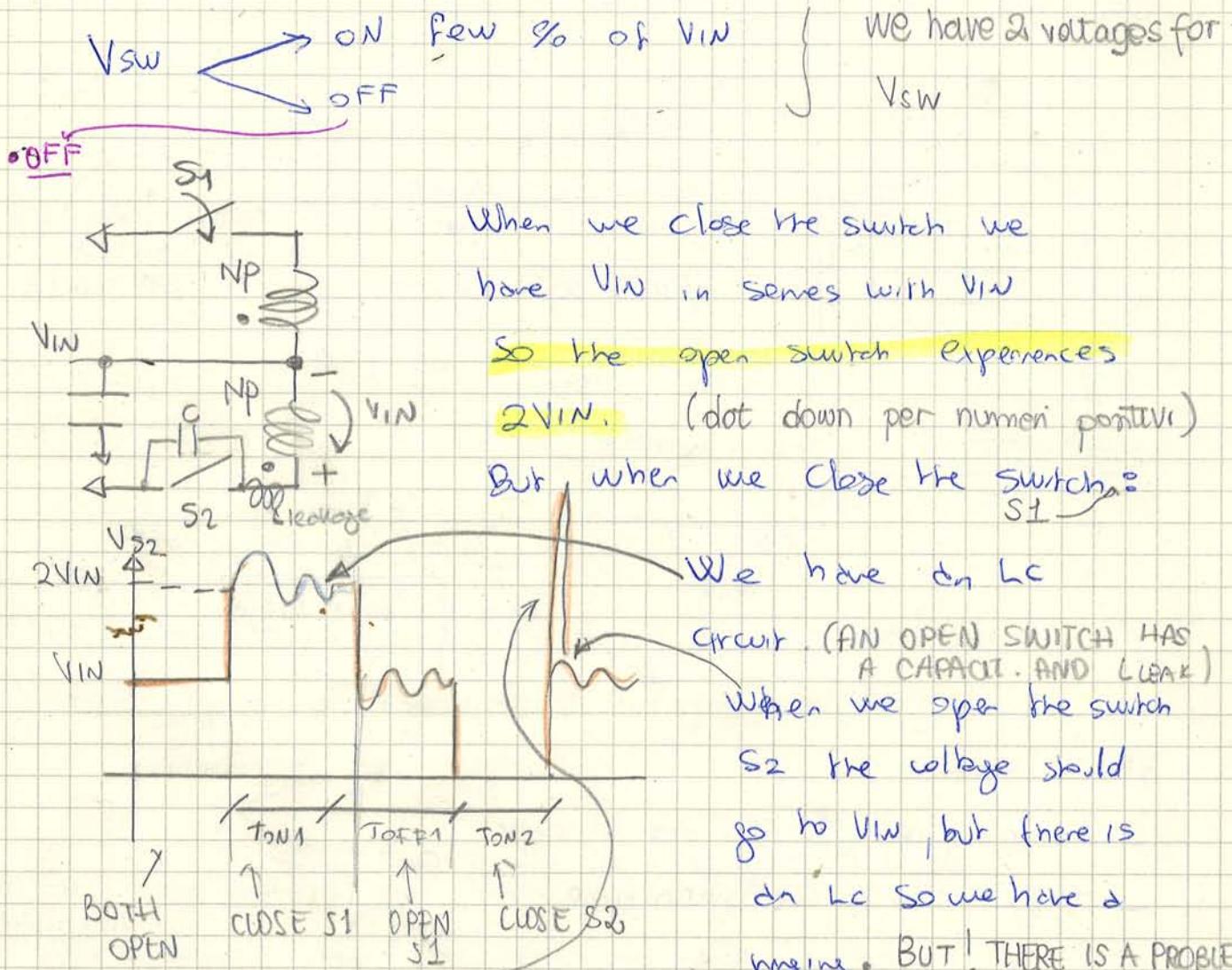

Low voltage + Medium power  $\rightarrow$  lot of current that flows in the leakage inductor

Since there is a lot of current in the leakage inductor when we stop the flow the inductor get mad!

There isn't a recycle path. so we have to put a transistor or a zener. The spike is  $\approx 6V_{IN}$